

## Homework 3 (Due date: 10/19)

## HW3.1: (20 points)

Fig. 3.1 shows a fully differential amplifier and its transfer curves. Assume  $V_{in1}$  and  $V_{in2}$  are differential signals, for  $I_{D1}=I_{D2}=I_{SS}/2$ ,  $V_{GS1} = V_{GS2} = V_{TH}+200\text{mV}$ .  $\Delta V_{in1}$  is a specified voltage means  $M1$  or  $M2$  is turned off. Please identify  $\Delta V_{in1}$  and describe  $G_m = f(\Delta V_{in})$ . Note: *channel length modulation* and *body effect* are ignored.

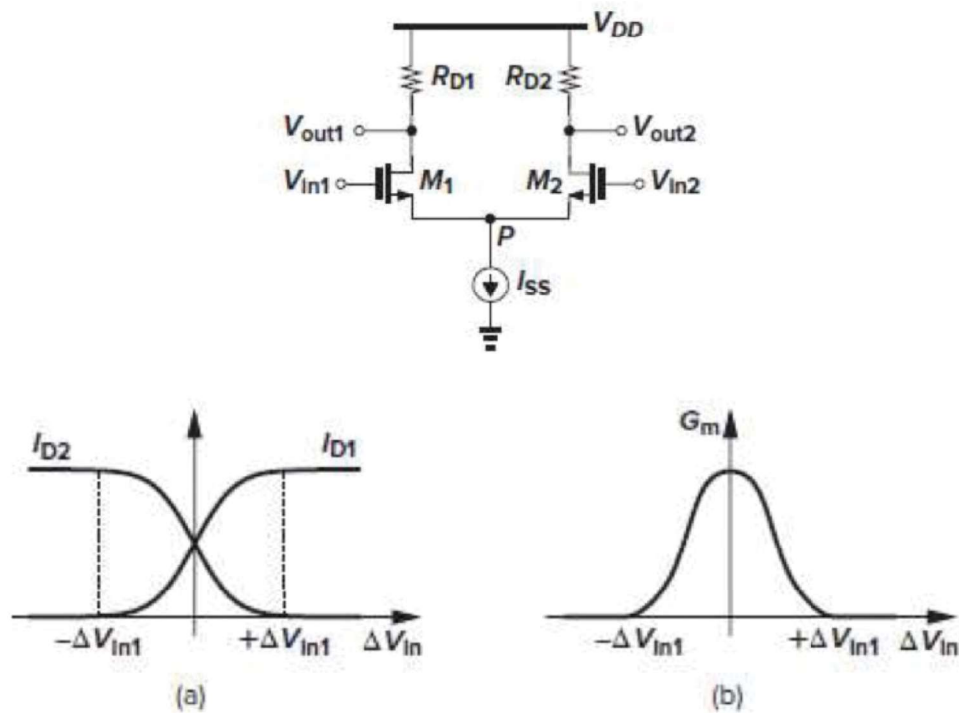


Fig. 3.1

$$\textcircled{1} V_{in1} - V_{in2} \approx V_{gs1} - V_{gs2}$$

$$(V_{gs} - V_{th})^2 = \frac{I_D}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}}$$

$$V_{gs} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{th} \Rightarrow V_{gs1} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} + V_{th}$$

$$\cancel{\frac{1}{2} I_{D1} - I_{D2}}$$

$$\Rightarrow V_{in1} - V_{in2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}}$$

$$(V_{in1} - V_{in2})^2 = \frac{2(I_{D1} + I_{D2})}{\mu_n C_{ox} \frac{W}{L}} - 2 \sqrt{\frac{4I_{D1}I_{D2}}{(\mu_n C_{ox} \frac{W}{L})^2}} \quad \times I_{D1} + I_{D2} = I_{SS}$$

$$= \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{SS} - 2\sqrt{I_{D1}I_{D2}})$$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - I_{SS} = -2\sqrt{I_{D1}I_{D2}} \quad \left\{ \begin{array}{l} V_{in1} = V_{gs1} - V_{th} \\ V_{in2} = V_{gs2} - V_{th} \end{array} \right.$$

$$\xrightarrow{\text{2边平方}} \frac{1}{4} (\mu_n C_{ox} \frac{W}{L})^2 (V_{in1} - V_{in2})^4 + I_{SS}^2 - \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 \cdot I_{SS} = 4I_{D1}I_{D2}$$

$$\times 4I_{D1}I_{D2} = (I_{D1} + I_{D2})^2 - (I_{D1} - I_{D2})^2 = I_{SS}^2 - (I_{D1} - I_{D2})^2$$

$$\Rightarrow \frac{1}{4} (\mu_n C_{ox} \frac{W}{L})^2 (V_{in1} - V_{in2})^4 + \cancel{I_{SS}^2} - \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 \cdot I_{SS} = \cancel{I_{SS}^2} - (I_{D1} - I_{D2})^2$$

$$\Rightarrow (I_{D1} - I_{D2})^2 = -\frac{1}{4} (\mu_n C_{ox} \frac{W}{L})^2 (V_{in1} - V_{in2})^4 + \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 \cdot I_{SS}$$

$$= -\frac{1}{4} (\mu_n C_{ox} \frac{W}{L})^2 (V_{in1} - V_{in2})^4 + \frac{4}{4} I_{SS} \cdot \frac{(\mu_n C_{ox} \frac{W}{L})^2}{\mu_n C_{ox} \frac{W}{L}} \cdot (V_{in1} - V_{in2})^2$$

$$= -\frac{1}{4} (\mu_n C_{ox} \frac{W}{L})^2 (V_{in1} - V_{in2})^4 + \frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} \cdot \frac{1}{4} (\mu_n C_{ox} \frac{W}{L})^2 (V_{in1} - V_{in2})^2$$

$$= \frac{1}{4} (\mu_n C_{ox} \frac{W}{L})^2 (V_{in1} - V_{in2})^2 \left[ \frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2 \right]$$

$$(I_{D1} - I_{D2}) = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

$$= \sqrt{\frac{1}{4} (\mu_n C_{ox} \frac{W}{L})^2 \cdot \frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} \cdot (V_{in1} - V_{in2})^2} \cdot \sqrt{1 - \frac{\mu_n C_{ox} \frac{W}{L}}{4I_{SS}} (V_{in1} - V_{in2})^2}$$

$$= \sqrt{\mu_n C_{ox} \frac{W}{L} \cdot I_{SS}} \cdot (V_{in1} - V_{in2}) \cdot \sqrt{1 - \frac{\mu_n C_{ox} \frac{W}{L}}{4I_{SS}} (V_{in1} - V_{in2})^2}$$

$$\Rightarrow \Delta I_D = \sqrt{\mu_n C_{ox} \frac{W}{L} \cdot I_{SS}} \cdot \Delta V_{in} \cdot \sqrt{1 - \frac{\mu_n C_{ox} \frac{W}{L}}{4I_{SS}} \cdot \Delta V_{in}^2}$$

$$g_m = \frac{\partial I_D}{\partial V_m} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot \frac{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - 2\Delta V_m^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - \Delta V_m^2}} \quad *$$

$$\textcircled{2} \Delta V_{in1} = ?$$

$$\text{M2 off, } I_{D1} = I_{SS}, \quad V_{in1} = V_{GS} - V_{th} = \Delta V_{in1}$$

$$I_{SS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot \Delta V_{in1}^2$$

$$\Rightarrow \Delta V_{in1} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \quad *$$

### HW3.2: (30 points)

Assuming that all the transistors in the circuits of Figs. 3.2 are saturated and  $\lambda \neq 0$ , calculate the small-signal differential voltage gain. Please specify their positive and negative input and output nodes.



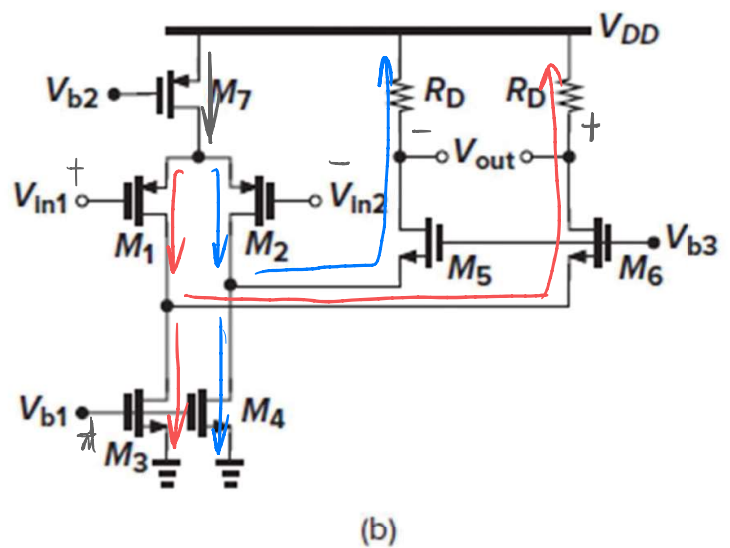
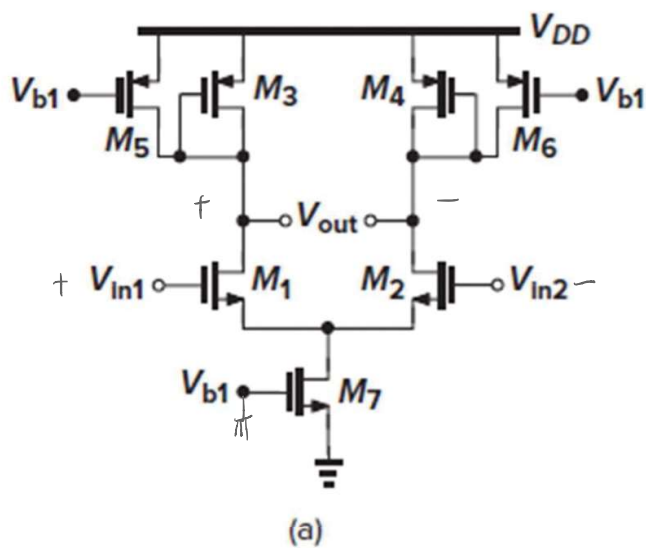


Fig. 3.2

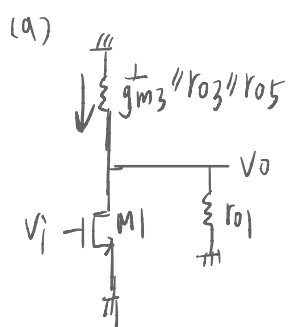
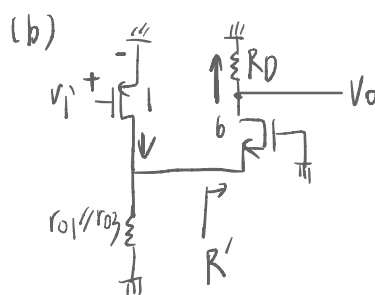
$$A_V = -g_{m1} \cdot (r_{o1} \parallel g_{m3}^{-1} \parallel r_{o3} \parallel r_{o5}) \quad *$$



$$R' = \frac{r_{o6} + R_D}{1 + g_{m6} r_{o6}}$$

$$V_o = -V_i \cdot g_{m1} \cdot \frac{r_{o1} \parallel r_{o3}}{r_{o1} \parallel r_{o3} + R'} \cdot R_D$$

$$A_V = \frac{-g_{m1} r_{o3} R_D}{r_{o3} + R'} \quad *, \quad R' = \frac{r_{o6} + R_D}{1 + g_{m6} r_{o6}}$$

## Homework 3 (Due date: 10/19)

**Table 2.1** Level 1 SPICE models for NMOS and PMOS devices.

NMOS Model			
LEVEL = 1	VTO = 0.7	<i>body effect</i> <u>GAMMA = 0.45</u>	<i>2φ<sub>f</sub></i> <u>PHI = 0.9</u>
NSUB = 9e+14	LD = 0.08e-6	UO = 350	<i>channel length</i> <u>LAMBDA = 0.1</u>
TOX = 9e-9	PB = 0.9	CJ = 0.56e-3	CJSW = 0.35e-11
MJ = 0.45	MJSW = 0.2	CGDO = 0.4e-9	JS = 1.0e-8
PMOS Model			
LEVEL = 1	VTO = -0.8	GAMMA = 0.4	PHI = 0.8
NSUB = 5e+14	LD = 0.09e-6	UO = 100	LAMBDA = 0.2
TOX = 9e-9	PB = 0.9	CJ = 0.94e-3	CJSW = 0.32e-11
MJ = 0.5	MJSW = 0.3	CGDO = 0.3e-9	JS = 0.5e-8

VDD=3.3V; VSS=0V

- What are the maximum and minimum allowable input common-mode levels if the differential swing at the input and output are small? (10 points)
- For  $V_{in,CM} = 1.2V$ , calculate the small-signal differential voltage gain. (10 points)
- Suppose  $M_1$  and  $M_2$  have a threshold voltage mismatch of  $1mV$ . What is the CMRR? (10 points)

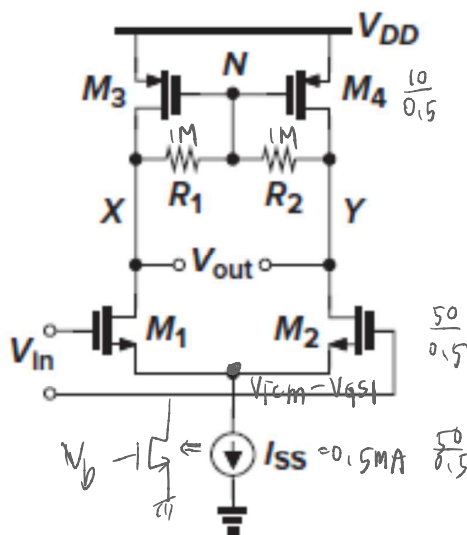


Fig. 3.3

$$(a) \quad \textcircled{1} \quad V_b - (V_{icm} - V_{gs1}) \leq V_{thN} \Rightarrow V_{icm} \geq V_b + V_{gs1} - V_{thN}$$

$$I_{SS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot (V_b - V_{thN})^2$$

$$0,25m = \frac{1}{2} \times 350 \cdot \frac{3,9 \times 8,85 \times 10^{-14}}{9 \times 10^{-9}} \cdot \frac{50}{0,5} \cdot (V_b - 0,7)^2$$

$$10^{-3} = 1,34 \times 10^{-2} \times (V_b - 0,7)^2$$

$$(V_b - 0,7)^2 = \frac{10^{-3}}{1,34 \times 10^{-2}} \Rightarrow V_b = 0,97$$

•  $M_1, M_2$  body effect:

$$V_t = V_{to} + V \left( \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right), \quad V_{SB} = V_{ov, I_{SS}} = V_b - V_{th} = 0,97 - 0,7 = 0,27$$

$$= 0,7 + 0,45 \left( \sqrt{0,7 + 0,27} - \sqrt{0,7} \right) = 0,76$$

$$0,25m = \frac{1}{2} \times 350 \cdot \frac{3,9 \times 8,85 \times 10^{-14}}{9 \times 10^{-9}} \times \frac{50}{0,5} \times (V_{gs1} - 0,76)^2 \Rightarrow V_{gs1} = 0,953$$

$$\Rightarrow V_{icm} \geq 0,97 + 0,953 - 0,7 = 1,22$$

$$\textcircled{2} \quad V_{icm} - (V_{DD} - V_{SD3}) \leq V_{th1} \Rightarrow V_{icm} \leq V_{th1} + V_{DD} - \textcircled{V_{SD3}} \rightarrow V_{SQ3}$$

$$0,25m = \frac{1}{2} \times 100 \times \frac{3,9 \times 8,85 \times 10^{-14}}{9 \times 10^{-9}} \times \frac{10}{0,5} \times (V_{SQ3} - 0,8)^2 \Rightarrow V_{SQ3} = 1,6$$

$$\Rightarrow V_{icm} \leq 0,76 + 3,3 - 1,6 = 2,46$$

$$\Rightarrow 1,22 \leq V_{icm} \leq 2,46$$

$$(b) \quad V_o = V_{icm} \cdot g_{m1} \cdot (R_1 \parallel r_{o1} \parallel r_{o3}) \cdot (-1)$$

$\frac{W}{L}$  channel length modulation:

$$r_{o1} = \frac{1}{\lambda_n I_D} = \frac{1}{0,1 \times 0,25m} = 40k, \quad r_{o2} = \frac{1}{\lambda_p I_D} = \frac{1}{0,2 \times 0,25m} = 20k$$

$$g_{m1} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} \cdot I_{D1}}$$

$$= \sqrt{2 \times 350 \times \frac{3,9 \times 8,85 \times 10^{-14}}{9 \times 10^{-9}} \times \frac{50}{0,5} \times 0,25m} = 2,59m$$


$$A_v = -2,59m \cdot (1M \parallel 20k \parallel 40k)$$

$$= -2,59m \times 13,1k$$

$$= -34$$

$$1M \parallel 13,3k$$

$$1000k \parallel 13,3k$$

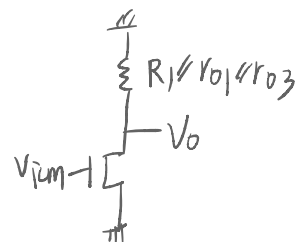

$$(c) CMRR = \frac{A_{DM}}{A_{CM-DM}}, \quad V_{th1} + 1m = V_{th2}, \quad g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}), \quad g_{m1} \neq g_{m2}$$

①  $A_{CM-DM}$

$$(g_{m1} + g_{m2}) \cdot (V_{icm} - V_p) R_{SS} = V_p$$

$$V_p = \frac{(g_{m1} + g_{m2}) R_{SS}}{1 + (g_{m1} + g_{m2}) R_{SS}} \cdot V_{icm}$$

$$V_x = -g_{m1} \cdot (V_{icm} - V_p) R_D = -g_{m1} \cdot R_D \cdot \frac{1}{1 + (g_{m1} + g_{m2}) R_{SS}} V_{icm}$$

$$V_y = -g_{m2} \cdot (V_{icm} - V_p) R_D = -g_{m2} \cdot R_D \cdot \frac{1}{1 + (g_{m1} + g_{m2}) R_{SS}} V_{icm}$$


$$\Rightarrow V_x - V_y = -(g_{m1} - g_{m2}) \cdot R_D \cdot \frac{1}{1 + (g_{m1} + g_{m2}) R_{SS}} \cdot V_{icm}$$

$$\Rightarrow A_{CM-DM} = \frac{-\Delta g_m R_D}{1 + (g_{m1} + g_{m2}) R_{SS}}$$

②  $A_{DM}$

$$A_{DM} = \frac{R_D}{2} \cdot \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{1 + (g_{m1} + g_{m2}) R_{SS}}$$

Fig. 4.17

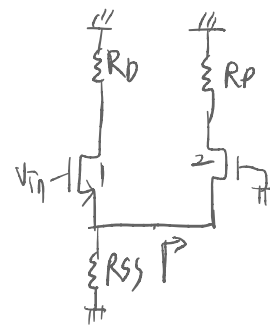

$$\textcircled{3} CMRR = \frac{A_{DM}}{A_{CM-DM}}$$

$$= \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{2\Delta g_m} \approx \frac{g_m}{\Delta g_m} (1 + 2g_m R_{SS})$$

$$g_m = \frac{g_{m1} + g_{m2}}{2} = \frac{\mu_n C_{ox} \frac{W}{L} [V_{GS} - V_{th1} + V_{GS} - V_{th2}]}{2} = \frac{\mu_n C_{ox} \frac{W}{L} [2V_{GS} - (V_{th1} + V_{th2})]}{2}$$

$$\textcircled{a} \begin{cases} V_{GS} = 0.953 \\ V_{th} = 0.176 \end{cases}$$

$$\Rightarrow g_m = 350 \times \frac{3.9 \times 81.85 \times 10^{-14}}{9 \times 10^{-9}} \times \frac{50}{0.5} \times \left[ (2 \times 0.953 - (2 \times 0.176 + 10^{-3})) \right] \times \frac{1}{2}$$

$$= 5.16m \times \frac{1}{2} = 2.58m$$

$$\Delta g_m = g_{m1} - g_{m2} = \mu_n C_{ox} \frac{W}{L} [V_{GS} - V_{th1} - V_{GS} + V_{th2}] = \mu_n C_{ox} \frac{W}{L} \left( \frac{V_{th2} - V_{th1}}{\Delta V_{th}} \right)$$

$$= 350 \times \frac{3.9 \times 81.85 \times 10^{-14}}{9 \times 10^{-9}} \times \frac{50}{0.5} \times 10^{-3} = 13.4 \mu$$

$$R_{SS} = \frac{1}{\lambda I_{SS}} = \frac{1}{0.1 \times 0.5m} = 20k$$

$$\Rightarrow CMRR = \frac{2.58 \times 10^{-3}}{13.4 \times 10^{-6}} \times (1 + 2 \times 2.58m \times 20k) = 20062$$

$$\Rightarrow 20 \log 20062 = 86 \text{ dB}$$

# Introduction to Analog Integrated Circuits (111), DECE, NTUST

## Homework 3 (Due date: 10/19)

### HW3.4: (20 points)

Consider the circuit shown in Fig. 3.4.  $V_{DD}=3.3V$  and  $V_{SS}=0$ .

- Sketch  $V_{out}$  as  $V_{in1}$  and  $V_{in2}$  vary differentially from zero to  $V_{DD}$ .
- If  $\lambda = 0$ , obtain an expression for the voltage gain. What is the voltage gain if  $W_{3,4} = 0.8W_{5,6}$ ?


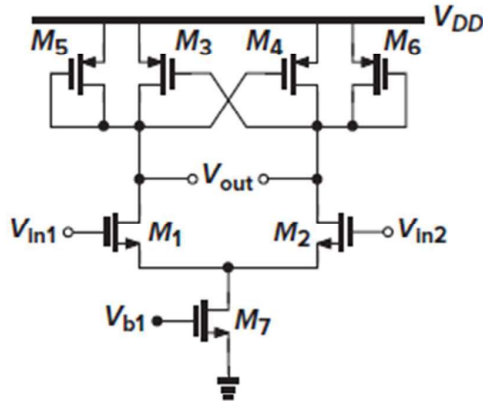


Fig. 3.4

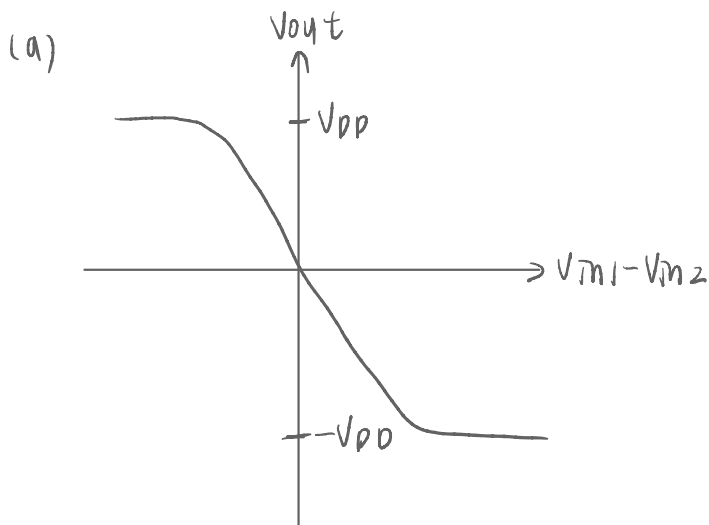

- ①  $V_{in1} = V_{DD}, V_{in2} = 0$   
 $\rightarrow V_{out1} = 0, V_{out2} = V_{DD}$
- ②  $V_{in1} = 0, V_{in2} = V_{DD}$   
 $\rightarrow V_{out1} = V_{DD}, V_{out2} = 0$
- ③  $V_{in1} = V_{in2}$   
 $\rightarrow V_{out} = 0$

(b)

$$I_X = -V_3 g_{m3} \cdot (-1) = -V_4 g_{m4}$$


$$I_X = V_3 g_{m3} = -V_4 g_{m4}$$

$$V_3 = -V_4$$


$$\text{又 } V_3 + V_X = V_4$$

$$V_X = V_4 - V_3 = 2V_4$$
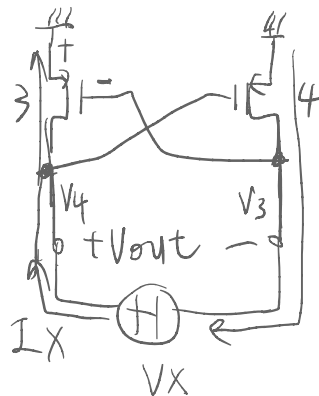
$$\frac{V_X}{I_X} = \frac{2V_4}{-V_4 g_{m4}} = \frac{-2}{g_{m4}}$$



$$W_{3,4} = 0,8 W_{5,6} \quad | \quad g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) \Rightarrow g_{m3} = 0,8 g_{m5}$$

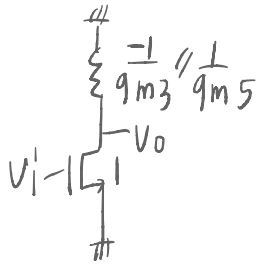

$$\begin{aligned} A_v &= -g_{m1} \left( \frac{1}{g_{m3}} \parallel \frac{1}{g_{m5}} \right) \\ &= -g_{m1} \left( \frac{1}{0,8 g_{m5}} \parallel \frac{1}{g_{m5}} \right) \\ &= \frac{-g_{m1}}{0,2 g_{m5}} \quad \# \end{aligned}$$

$$\frac{\frac{-1}{0,8 g_{m5}^2}}{\frac{-1}{0,8 g_{m5}} + \frac{0,8}{g_{m5}}}$$

$$\frac{\frac{1}{g_{m5}}}{+0,2} = \frac{1}{0,2 g_{m5}}$$