

### Homework 1

**Due 5:00PM Tuesday, October 11, 2022**

1. (10 pts) Please find  $V_1$  in the circuit in Fig. 1.

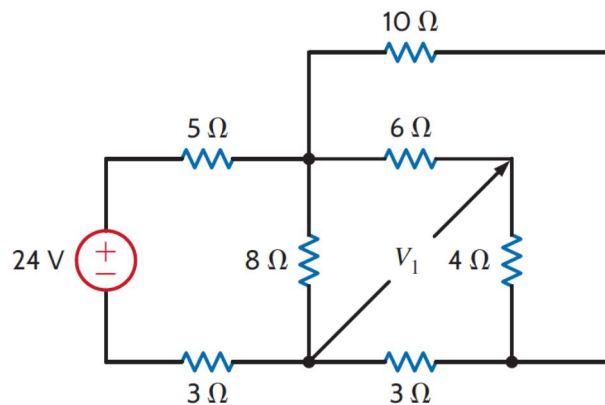


Fig. 1

2. (10 pts) Please find the power supplied by the 36-V source in the circuit in Fig. 2.

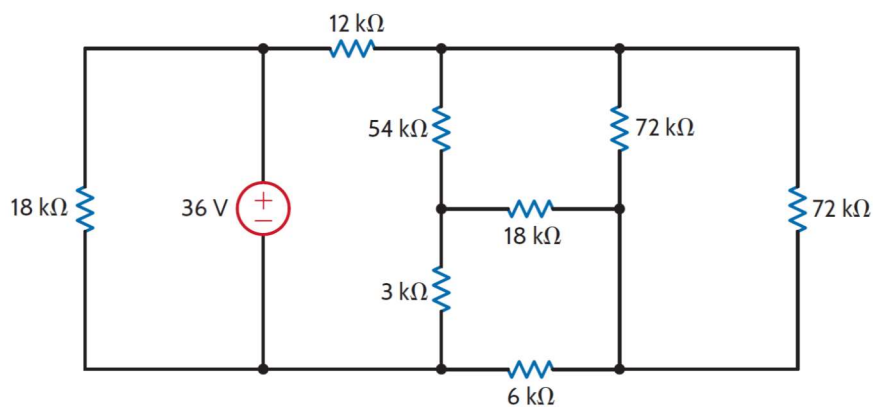


Fig. 2

3. (10 pts) Please find  $V_o$  in the circuit in Fig. 3 using nodal analysis.

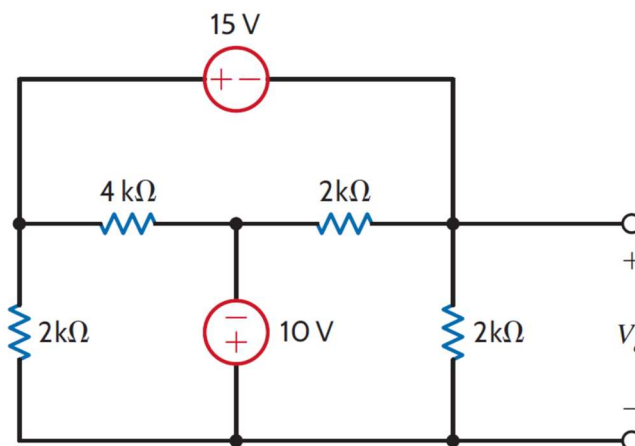


Fig. 3

4. (10 pts) Please find  $V_o$  in the circuit in Fig. 4 using nodal analysis.

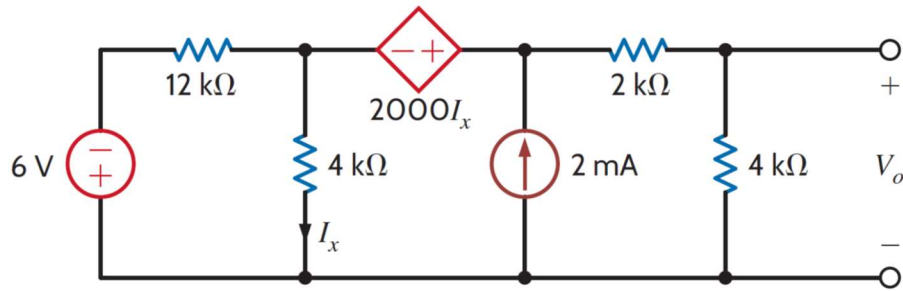


Fig. 4

5. (10 pts) Please find  $V_o$  in the circuit in Fig. 5 using nodal analysis.

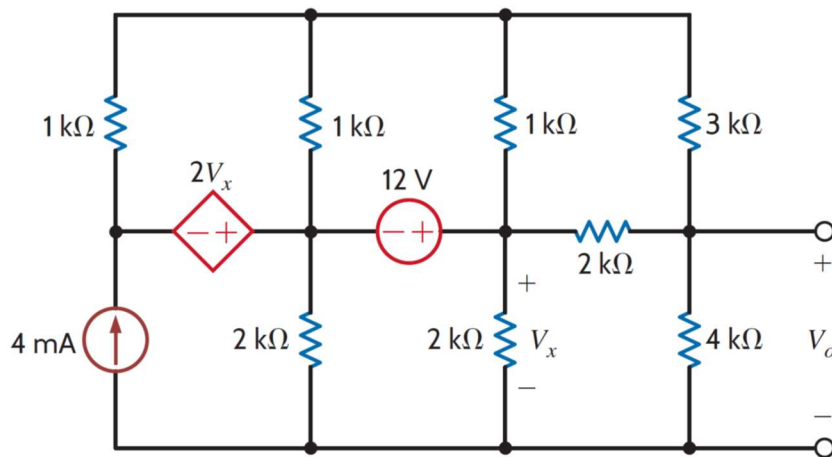


Fig. 5

6. (10 pts) Please find  $V_o$  in the circuit in Fig. 6 using mesh analysis.

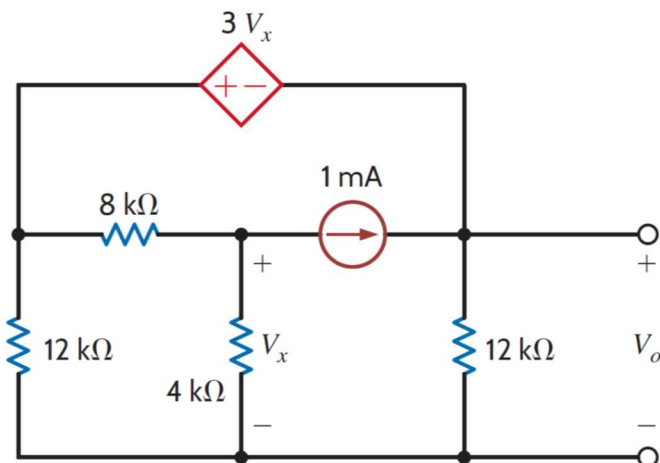


Fig. 6

7. (10 pts) Please find  $I_o$  in the circuit in Fig. 7 using loop analysis.

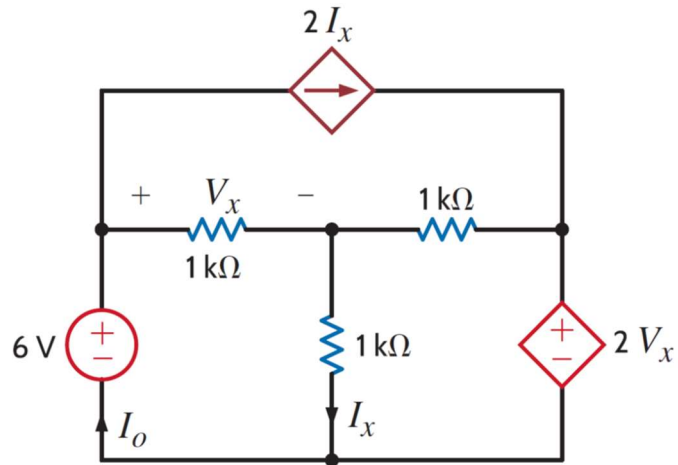


Fig. 7

8. (10 pts) Please find  $I_o$  in the circuit in Fig. 8 using Thévenin's theorem.

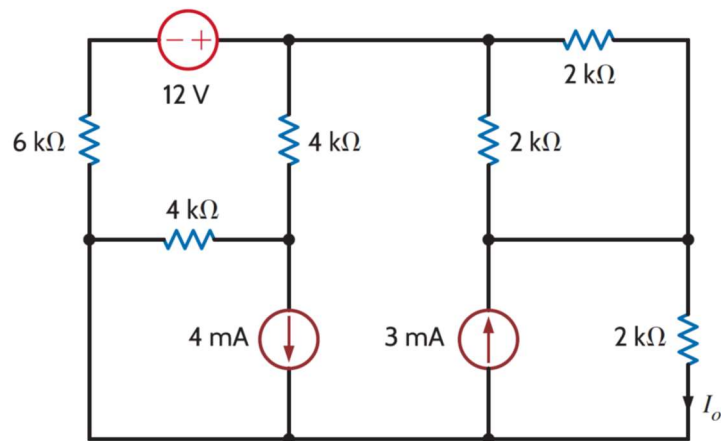


Fig. 8

9. (10 pts) Please find  $V_o$  in the circuit in Fig. 9 using Thévenin's theorem.

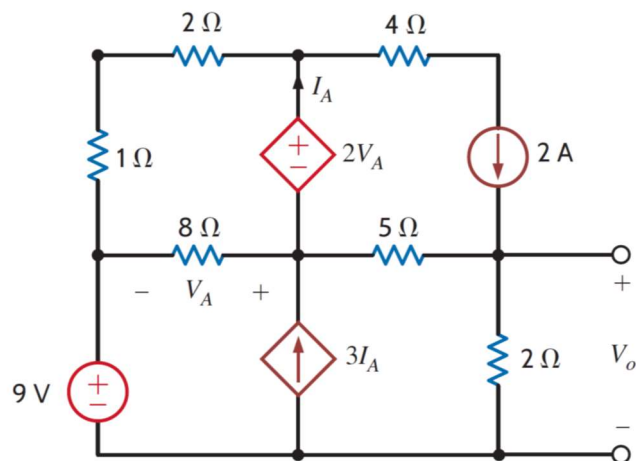


Fig. 9

10. (10 pts) Please find  $I_o$  in the circuit in Fig. 10 using Norton's theorem.

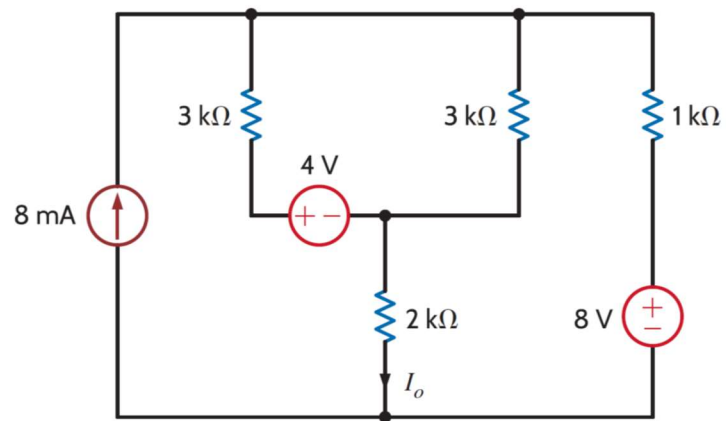


Fig. 10