

Homework 4 (Due date: 10/25)

HW4.1: (20 points)

Using a long-channel model, **prove** that, in strong inversion, the transistor M_R behaves like a resistor ($R_{on,R}$) with its resistance,

$$R_{on,R} = \frac{(W/L)_C}{(W/L)_R} \frac{1}{g_{m,C}}$$

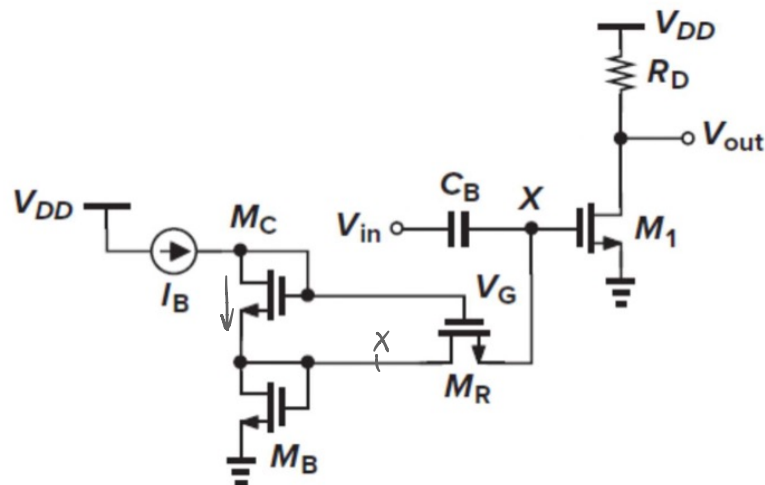


Fig. 4.1

$$R_{on,R} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_R (V_G - V_X - V_{th})}$$

$$I_B = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_C (V_G - V_X - V_{th})^2$$

$$V_G - V_X - V_{th} = \sqrt{\frac{2I_B}{\mu_n C_{ox} \left(\frac{W}{L}\right)_C}} = \sqrt{\frac{2\mu_n C_{ox} \left(\frac{W}{L}\right)_C I_B}{(\mu_n C_{ox} \left(\frac{W}{L}\right)_C)^2}} = \frac{g_{m,C}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_C}$$

$$\Rightarrow R_{on,R} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_R \frac{g_{m,C}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_C}}$$

$$= \frac{\left(\frac{W}{L}\right)_C}{\left(\frac{W}{L}\right)_R} \cdot \frac{1}{g_{m,C}}$$

HW4.2: (30 points)

The circuit of Fig. 4.2 is designed with $(W/L)_{1,2} = 8/2$, $(W/L)_{3,0} = 8/2$, and $I_{REF} = 100 \mu A$.

Assume $\mu_n C_{ox} = 800 \mu A/V^2$, $V_{DD} = 3V$ and $\gamma = 0$. $V_{TH} = 0.7V$

(a) Determine V_X and the acceptable range of V_b .

(b) Estimate the deviation of I_{out} from $100 \mu A$ if the drain voltage of M_3 is higher than V_X by 1 V, if $\lambda = 0.1 V^{-1}$.

(c) How to design V_b to have a minimum drain voltage of M_3 ?

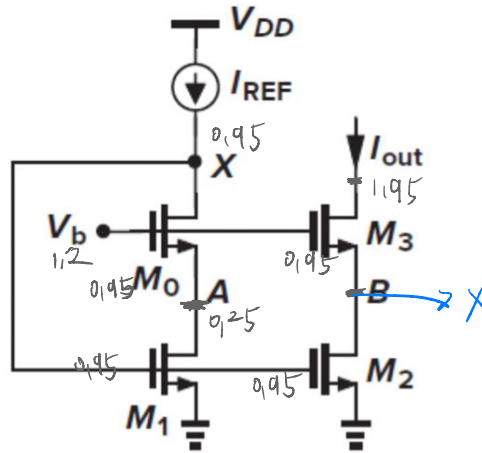


Fig. 4.2

(a) M_0 sat: $V_b - V_{th0} \leq V_X$

M_1 sat: $V_{gs1} - V_{th1} \leq V_b - V_{gs0} \Rightarrow V_{gs0} + V_{gs1} - V_{th1} \leq V_b \leq V_X + V_{th0}$

$$I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_X - V_{th})^2$$

$$100 = \frac{1}{2} \times 800 \times \frac{8}{2} (V_X - 0.7)^2 \Rightarrow V_X = 0.95 = V_{gs1} \quad \#$$

$$100 = \frac{1}{2} \times 800 \times \frac{8}{2} (V_{gs0} - 0.7)^2 \Rightarrow V_{gs0} = 0.95$$

$$\Rightarrow 0.95 + 0.95 - 0.7 \leq V_b \leq 0.95 + 0.7$$

$$\Rightarrow 1.2 \leq V_b \leq 1.65 \quad \#$$

$$(b) \quad V_{ov1} = 0.25 = V_{ov0}, \quad V_{b,min} = 1.2, \quad V_A = 0.25, \quad V_{DS0} = 0.7, \quad V_{D3} = 1.7$$

1 个 λ 在 $M2$ 的 drain 有 ΔV , 且 $I_{D2} = I_{D3}$

$$I_{D2} = (V_{ov1})^2 [1 + \lambda(V_{DS1} + \Delta V)]$$

$$I_{D3} = (V_{ov0} - \Delta V)^2 [1 + \lambda(V_{DS3} - \Delta V)] \Rightarrow I_{D2} = I_{D3}$$

$$(0.25)^2 [1 + 0.1(0.25 + \Delta V)] = (0.25 - \Delta V)^2 [1 + 0.1(1.7 - \Delta V)]$$

$$0.0625 [1 + 0.025 + 0.1\Delta V] = (0.0625 - 0.5\Delta V + \Delta V^2) [1 + 0.17 - 0.1\Delta V]$$

$$0.0640625 + 6.25m\Delta V = 0.073125 - 6.25m\Delta V - 0.585\Delta V + 0.05\Delta V^2 + 1.17\Delta V^2 - 0.1\Delta V^3$$

$$\Rightarrow 0.1\Delta V^3 - 1.22\Delta V^2 + 0.5975\Delta V - 9.0625m = 0$$

$$\Delta V = 11.68, 0.49, \underline{0.015}$$

$$\Rightarrow I_{out} = [1 + \lambda(0.25 + 0.015)]$$

$$I_{ref} = [1 + \lambda(0.25)]$$

$$\Rightarrow I_{out} = \frac{[1 + \lambda \cdot 0.265]}{1 + \lambda \cdot 0.25} \times 100\mu A = \underline{100.146\mu A}$$

$$(c) \quad V_{D3(min)} = V_{ov2} + V_{ov3}$$

$$\Rightarrow V_b = V_{ov2} + V_{ov3} + V_{th3} = 0.25 + 0.25 + 0.7 = \underline{1.2}$$

Homework 4 (Due date: 10/25)

HW4.3 (30 points)

In the circuit shown in Fig. 4.3, a source follower using a wide transistor and a small bias current is inserted in series with the gate of M_3 so as to bias M_2 at the edge of saturation.

Assuming M_0 – M_3 are identical and $\lambda \neq 0$, estimate the mismatch between I_{out} and I_{REF} if (a) $\gamma = 0$, (b) $\gamma \neq 0$.

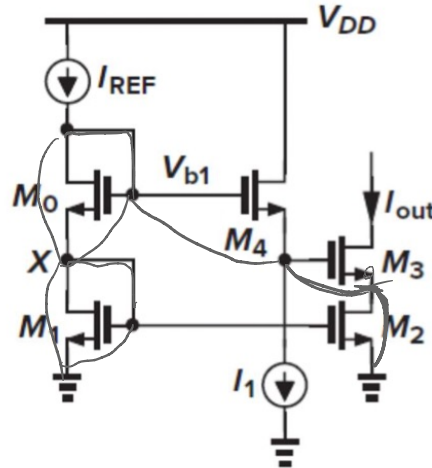


Fig. 4.3

$$(a) I_{ref} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs1} - V_{th})^2 (1 + \lambda V_{ds1}) \quad , \quad V_{ds1} = V_{gs1}$$

$$I_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs1} - V_{th})^2 (1 + \lambda V_{ds2}) \quad , \quad V_{ds2} = V_{gs1} + V_{gs0} - V_{gs4} - V_{gs3} \approx V_{gs1} - V_{gs4}$$

$$\rightarrow \frac{I_{out}}{I_{ref}} = \frac{1 + \lambda (V_{gs1} - V_{gs4})}{1 + \lambda V_{gs1}}$$

$$\begin{cases} I_{ref} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs1} - V_{th})^2 \Rightarrow V_{gs1} = \sqrt{\frac{2 I_{ref}}{\mu_n C_{ox}} \cdot \frac{L}{W}} + V_{th} \\ I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs4} - V_{th})^2 \Rightarrow V_{gs4} = \sqrt{\frac{2 I_1}{\mu_n C_{ox}} \cdot \frac{L}{W}} + V_{th} \end{cases}$$


$$(b) V_{th} = V_{th0} + \gamma \left[\sqrt{|2\phi_f - V_{bs}|} - \sqrt{2\phi_f} \right]$$

$$\begin{cases} V_{gs1} = \sqrt{\frac{2 I_{ref}}{\mu_n C_{ox}} \cdot \frac{L}{W}} + V_{th0} \\ V_{gs0} = \sqrt{\frac{2 I_{ref}}{\mu_n C_{ox}} \cdot \frac{L}{W}} + V_{th0} + \gamma \left[\sqrt{|2\phi_f + V_{gs1}|} - \sqrt{2\phi_f} \right] \\ V_{gs3} = \sqrt{\frac{2 I_{ref}}{\mu_n C_{ox}} \cdot \frac{L}{W}} + V_{th0} + \gamma \left[\sqrt{|2\phi_f + V_{ds2}|} - \sqrt{2\phi_f} \right] \\ V_{gs4} = \sqrt{\frac{2 I_1}{\mu_n C_{ox}} \cdot \frac{L}{W}} + V_{th0} + \gamma \left[\sqrt{|2\phi_f + V_{gs3} + V_{ds2}|} - \sqrt{2\phi_f} \right] \end{cases}$$

$$\rightarrow \frac{I_{out}}{I_{ref}} = \frac{1 + \lambda (V_{gs1} + V_{gs0} - V_{gs4} - V_{gs3})}{1 + \lambda V_{gs1}}$$

~~X~~

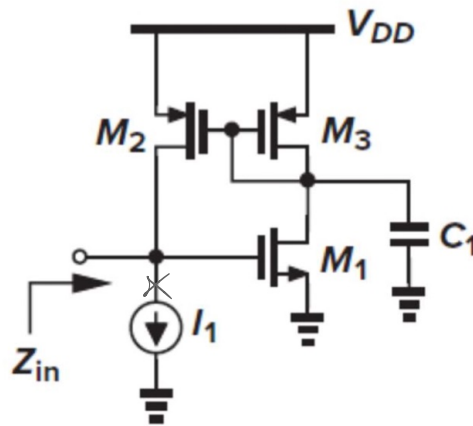The circuit shown in Fig. 4.4 exhibits a *negative input inductance*. Calculate the input impedance of the circuit and identify the inductive component.



$$V_1 = V_1' \cdot g_{m1} \cdot \left(g_{m3}^{-1} \parallel \frac{1}{sC_1} \right) = V_1' \cdot g_{m1} \cdot \frac{-1}{g_{m3} + sC_1}$$

$$Z_{in} = \frac{\cancel{V_1}}{g_{m2} \cdot \cancel{V_1} + g_{m1} \cdot \frac{-1}{g_{m3} + sC_1}}$$

$$Z_m = \frac{g_{m3} + sC_1}{-g_{m1}g_{m2}}$$