

考試規則：

- Close book。
- 可以使用計算機，但不能用手機或其他電子產品。請關閉手機。
- 考試時間: 13:20~15:20
- 沒有過程不給分
-

表 2.1 NMOS 和 PMOS 元件的第一層 SPICE 模型。

| | | | |
|--------------|--------------|---------------|-----------------|
| NMOS 模型 | | | |
| LEVEL = 1 | VTO = 0.7 | GAMMA = 0.45 | PHI = 0.9 |
| NSUB = 9e+14 | LD = 0.08e−6 | UO = 350 | LAMBDA = 0.1 |
| TOX = 9e−9 | PB = 0.9 | CJ = 0.56e−3 | CJSW = 0.35e−11 |
| MJ = 0.45 | MJSW = 0.2 | CGDO = 0.4e−9 | JS = 1.0e−8 |
| PMOS 模型 | | | |
| LEVEL = 1 | VTO = −0.8 | GAMMA = 0.4 | PHI = 0.8 |
| NSUB = 5e+14 | LD = 0.09e−6 | UO = 100 | LAMBDA = 0.2 |
| TOX = 9e−9 | PB = 0.9 | CJ = 0.94e−3 | CJSW = 0.32e−11 |
| MJ = 0.5 | MJSW = 0.3 | CGDO = 0.3e−9 | JS = 0.5e−8 |

- V_{DD} =3V for all questions if not mentioned.
- $\epsilon_0 = 8.85 \times 10^{-14}$ F/cm ; $\epsilon_{SiO2} = 3.9 \times \epsilon_0$; $\epsilon_{Si} = 11.7 \times \epsilon_0$

=====

Q1: (10%)

Calculate the voltage gain ($A_v = V_{out}/V_{in}$) of the circuit shown in Fig. 1.

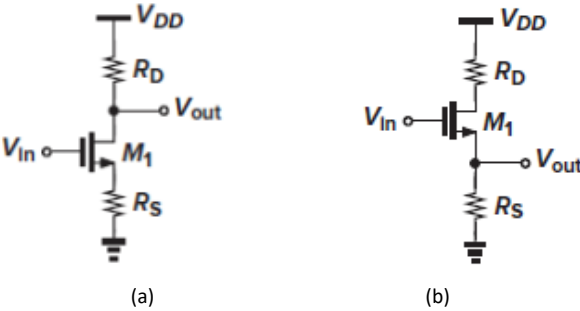


Fig. 1

Q2: (10%)

Assume the M3's drain node is the output (V_{out}) of the circuit shown in Fig. 2. Please show the minimum voltage of V_{out} using transistor parameters. The body effect is ignored. Hint: $M_i \sim (V_{THi}, V_{ovi}, g_{mi}, r_{oi})$

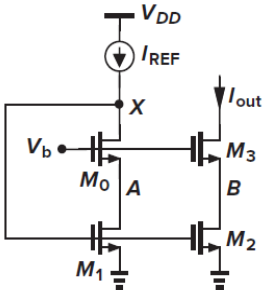


Fig. 2

Q3: (10%)

If ignore all other parasitic capacitors of MOSFETs, please calculate the equivalent input impedance of the circuits in Fig. 3. $\lambda \neq 0$ for (a) and (b).

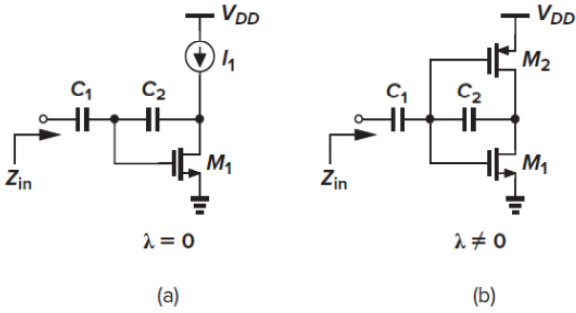


Fig. 3

Q4: (10%)

Calculate the input-referred thermal noise voltage and current of the circuit in Fig. 4. Assume that $\lambda=\gamma=0$.

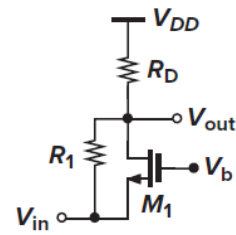


Fig. 4

Q5: (10%)

Calculate the close-loop input and output resistance ($R_{in,CL}$ and $R_{out,CL}$) using small-signal parameters.

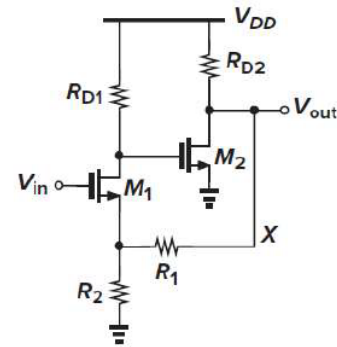


Fig. 5

Q6: (10%)

Assuming that $\lambda = \gamma = 0$, calculate the input-referred thermal noise voltage of the circuit in Fig. 6. Assume that $g_{m3,4} = 3/4 * g_{m5,6}$.

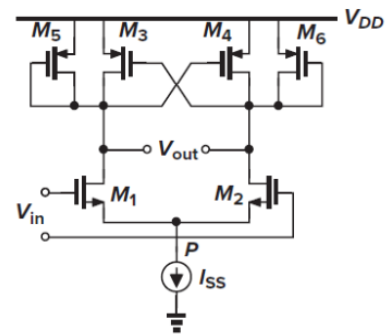


Fig. 6

Q7: (20%)

Suppose the amplifier of the circuit shown in Fig.7 has an open-loop transfer function $A_0/(1+s/\omega_0)$ and an output resistance R_0 . Calculate the output resistance ($R_{o,CL}$) and the voltage gain ($A_{v,CL}$) of the closed-loop circuit.

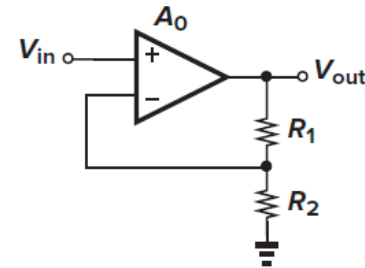


Fig. 7

Q8: (20%)

Consider the transimpedance amplifier shown in Fig. 8, where $R_D = 1 \text{ k}\Omega$, $R_F = 10 \text{ k}\Omega$, $g_{m1} = g_{m2} = 1/(100\Omega)$, and $C_A = C_X = C_Y = 100 \text{ fF}$. Neglecting all other capacitances and assuming that $\lambda = \gamma = 0$, compute the phase margin of the circuit. (Hint: break the loop at node X .)

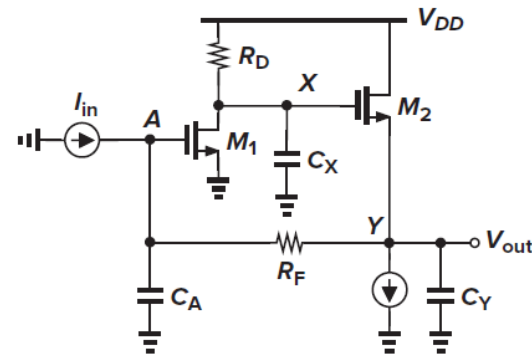


Fig. 8

Q1: (10%)

Calculate the voltage gain ($A_v = V_{out}/V_{in}$) of the circuit shown in Fig. 1.

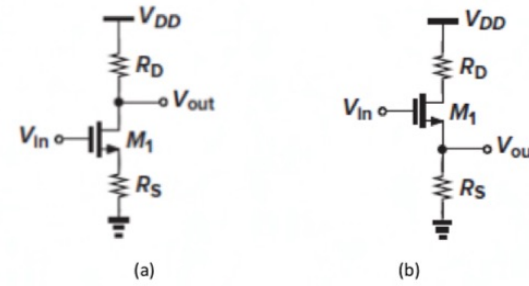



Fig. 1

考慮 body effect

$$G_m = g_m + g_{mb}$$

(a)
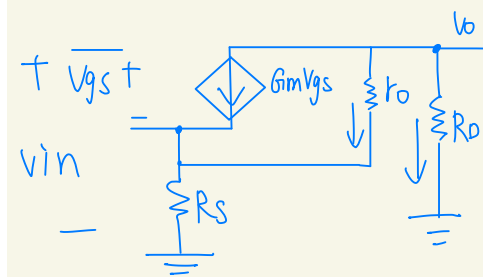
$$\frac{V_{out}}{V_{in}} = \frac{-g_m R_D \cdot r_o}{(1 + G_m r_o) R_S + r_o + R_D} \quad \#$$



$$\frac{V_o + V_{gs}}{r_o} + G_m V_{gs} + \frac{V_o}{R_D} = 0$$

$$V_o \left(\frac{1}{r_o} + \frac{1}{R_D} \right) = -V_{gs} \left(\frac{1}{r_o} + G_m \right)$$

$$V_{gs} = \frac{-(r_o + R_D) \cdot V_o}{(1 + G_m r_o) R_D} \quad \dots \quad (1)$$

$$V_{in} = -V_o \left(\frac{r_o + R_D}{1 + G_m r_o} + \frac{R_S}{R_D} \right)$$

$$\frac{V_o}{V_{in}} = \frac{-(1 + G_m r_o) R_D}{r_o + R_D + (1 + G_m r_o) R_S}$$

$$V_{in} = V_{gs} + \frac{-V_o}{R_D} \times R_S \quad \dots \quad (2)$$

(b)

$$\frac{g_m r_o R_S}{(G_m r_o R_S) + r_o + R_D + R_S} \quad \# \quad \text{OR} \quad \frac{g_m}{g_m + \frac{1}{R_S} + \frac{R_D}{r_o R_S} + \frac{1}{r_o}}$$

Q2: (10%)

Assume the M3's drain node is the output (Vout) of the circuit shown in Fig. 2. Please show the minimum voltage of Vout using transistor parameters. **The body effect is ignored.** Hint: $M_1 \sim (V_{TH1}, V_{ov1}, g_{m1}, r_{o1})$

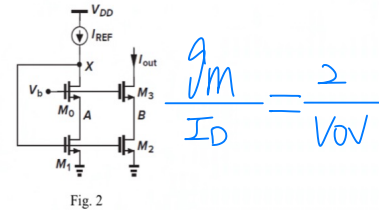


Fig. 2

Q2:

$$V_{out} = V_{ov2} + V_{ov3} \quad I_{out} = I_{D3} = I_{D2} \quad V_{GS2} = V_{GS1} = V_X$$

$$V_{ov2} = \sqrt{\frac{2I_{out}}{\mu_n C_{ox} \frac{W}{L_2}}} \quad V_{ov3} = \sqrt{\frac{2I_{out}}{\mu_n C_{ox} \frac{W}{L_3}}} \quad V_X - V_{TH1} = V_{ov1}$$

$$V_{ov2} = V_{GS2} - V_{TH2} = \underbrace{V_X}_{\Rightarrow \sqrt{\frac{2I_{ref}}{\mu_n C_{ox} \frac{W}{L_1}}}} - V_{TH2}$$

$$V_{ov3} = V_{GS3} - V_{TH3} = (V_b - V_{ov2}) - V_{TH3} \#$$

Q3:

(a)

先別看C1, 後續再加

$$V_X = \frac{I_X}{SC_2} + (I_X - g_m V_X) r_o$$

$$\Rightarrow V_X (1 + g_m r_o) = I_X \left(\frac{1 + SC_2 r_o}{SC_2} \right)$$

$$\frac{V_X}{I_X} = \frac{1 + SC_2 r_o}{(1 + g_m r_o) SC_2}$$

$$\bar{Z}_{in} = \frac{1}{SC_1} + \frac{1 + SC_2 r_o}{(1 + g_m r_o) SC_2} \#$$

$$\text{OR } \frac{1}{SC_1} + \frac{\frac{1}{SC_2} + r_o}{1 + g_m r_o} \#$$

(b)

$$V_{GS1} = V_{GS2} = V_{GS} = V_X$$

$$I_X = (V_{GS} - V_o) \cdot SC_2 \dots \textcircled{1}$$

$$I_X = \frac{V_o}{r_{o1} // r_{o2}} + (g_{m1} + g_{m2}) V_{GS}$$

設 $r_{o1} // r_{o2} = R_o$ $g_{m1} + g_{m2} = g_m$

$$V_o = I_X r_o - g_m r_o V_{GS} \text{ 代 } \textcircled{1} \quad V_{GS} - I_X r_o + g_m r_o V_{GS} = \frac{I_X}{SC_2}$$

$$V_{GS} (1 + g_m r_o) = I_X \left(r_o + \frac{1}{SC_2} \right) \quad \frac{V_X}{I_X} = \frac{r_o + \frac{1}{SC_2}}{1 + g_m r_o}$$

$$\text{再 } \bar{Z}_{in} = \frac{1}{SC_1} + \frac{r_o + \frac{1}{SC_2}}{1 + g_m r_o}$$

↳ 可省略

$$\frac{1}{SC_1} + \frac{r_{o1} // r_{o2} + \frac{1}{SC_2}}{1 + (g_{m1} + g_{m2}) (r_{o1} // r_{o2})} \#$$

Q3: (10%)

If ignore all other parasitic capacitors of MOSFETs, please calculate the equivalent input impedance of the circuits in Fig. 3. $\lambda \neq 0$ for (a) and (b).

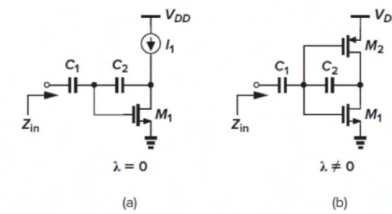


Fig. 3

Q4: (10%)

Calculate the input-referred thermal noise voltage and current of the circuit in Fig. 4. Assume that $\lambda = \gamma = 0$.


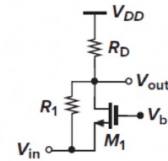


Fig. 4

$$\overline{V_{n^2, out}} = \left(4kT r_{gm} + \frac{4kT}{R_D} + \frac{4kT}{R_1} \right) (R_1 \parallel R_D)^2 \quad A_V = \left(\frac{1}{R_1} + g_m \right) (R_D \parallel R_1)$$
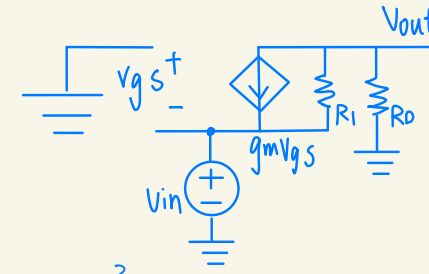
$$\overline{V_{n^2, in}} = \frac{\overline{V_{n^2, out}}}{A_V^2} = \frac{4kT \left(\frac{1}{R_D} + \frac{1}{R_1} + r_{gm} \right)}{\left(\frac{1}{R_1} + g_m \right)^2} \quad \# \quad \overline{I_{n^2, in}} = \frac{4kT}{R_D} \quad \#$$



Q5: (10%)

Calculate the close-loop input and output resistance ($R_{in, CL}$ and $R_{out, CL}$) using small-signal parameters.

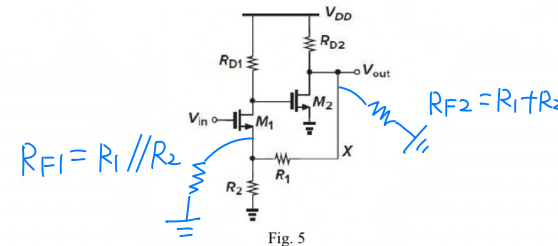


Fig. 5

$$R_{in, OL} = \infty$$

$$R_{O, OL} = R_{D2} \parallel R_{F2} \parallel r_{o2}$$

$$V_F = V_X \cdot g_{m1} R_{D1}; \quad V_X = -g_{m2} V_t \cdot \frac{R_{D2} \cdot (R_2 \parallel \frac{R_{D1} + r_{o1}}{1 + g_{m1} r_{o1}})}{R_{D2} + [R_1 + R_2 \parallel \frac{R_{D1} + r_{o1}}{1 + g_{m1} r_{o1}}]}$$

$$\frac{V_F}{V_t} = \frac{V_F}{V_X} \times \frac{V_X}{V_t} = g_{m1} R_{D1} \times -g_{m2} \cdot \frac{R_{D2} \cdot (R_2 \parallel \frac{R_{D1} + r_{o1}}{1 + g_{m1} r_{o1}})}{R_{D2} + [R_1 + R_2 \parallel \frac{R_{D1} + r_{o1}}{1 + g_{m1} r_{o1}}]}$$

$$= -g_{m1} g_{m2} R_{D1} R_{D2} (R_2 \parallel \frac{R_{D1} + r_{o1}}{1 + g_{m1} r_{o1}}) \div [R_{D2} + R_1 + R_2 \parallel \frac{R_{D1} + r_{o1}}{1 + g_{m1} r_{o1}}] = -AB$$

$$R_{in, CL} = \infty \times (1 + AB) = \infty \quad \#$$

$$R_{out, CL} = \frac{R_{D2} \parallel R_{F2}}{1 + AB} \quad \#$$

Q6: (10%)

Assuming that $\lambda = \gamma = 0$, calculate the input-referred thermal noise voltage of the circuit in Fig. 6. Assume that $g_{m3,4} = 3/4 g_{m5,6}$.

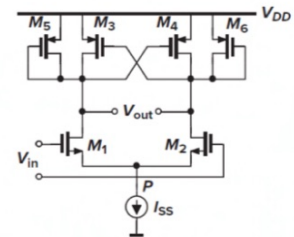


Fig. 6

$\times 2$

ANS6 =

$$A_v = g_{m1,2} / (g_{m5,6} - g_{m3,4})$$

$$= 4 g_{m1,2} / g_{m5,6}$$

$$\overline{I_{n,o}^2} = 4kT \nu (g_{m3} + g_{m5} + g_{m1})$$

$$\overline{V_{n,in}^2} = 4kT \nu (g_{m3} + g_{m5} + g_{m1}) / g_{m1}^2$$

$$= \overline{I_{n,o}^2} / g_{m1}^2$$

Q7: (20%)

Suppose the amplifier of the circuit shown in Fig. 7 has an open-loop transfer function $A_0/(1+s/\omega_0)$ and an output resistance R_0 . Calculate the output resistance ($R_{o,CL}$) and the voltage gain ($A_{v,CL}$) of the closed-loop circuit.

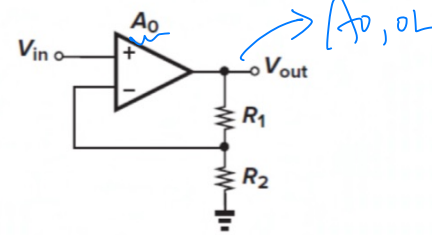


Fig. 7

ANS? (V-V Feedback)

$$R_{o,OL} = R_0 \parallel (R_1 + R_2), \quad A_{o,OL} = A'_0 = g_m(R_0 \parallel (R_1 + R_2))$$

$$1 + \beta A_{o,OL} = 1 + \frac{R_2}{R_1 + R_2} \cdot A'_0$$

$$R_{o,CL} = \frac{R_{o,OL}}{1 + \beta A_{o,OL}} = \frac{R_0 \parallel (R_1 + R_2)}{1 + \frac{R_2}{R_1 + R_2} \cdot g_m(R_0 \parallel (R_1 + R_2))} \approx \frac{R_0}{\frac{R_2}{R_1 + R_2} g_m R_0} = \frac{1}{\beta g_m}$$

$$A_{v,CL} = \frac{A'_0}{1 + \beta A'_0} = \frac{g_m(R_0 \parallel (R_1 + R_2))}{1 + \frac{R_2}{R_1 + R_2} g_m(R_0 \parallel (R_1 + R_2))} \approx g_m R_{o,CL}$$

Q8: (20%)

Consider the transimpedance amplifier shown in Fig. 8, where $R_D = 1 \text{ k}\Omega$, $R_F = 10 \text{ k}\Omega$, $g_{m1} = g_{m2} = 1/(100\Omega)$, and $C_A = C_X = C_Y = 100 \text{ fF}$. Neglecting all other capacitances and assuming that $\lambda = \gamma = 0$, compute the phase margin of the circuit. (Hint: break the loop at node X .)

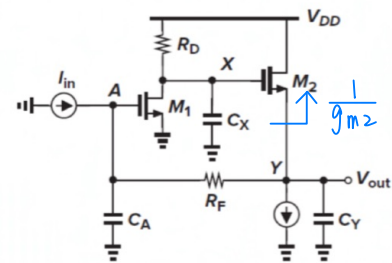


Fig. 8

ANS 8 = $V-V$ Feedback

To break the loop after node X

We have three poles at nodes Y, A, X , ~~resulting three poles~~ labeled as ω_Y, ω_A , and ω_X

$$\omega_Y \cong 1/(1/g_{m2} \parallel R_F) C_Y$$

$$\omega_A \cong 1/(R_F C_A)$$

$$\omega_X \cong 1/(R_D C_X)$$

$\therefore R_F > R_D > 1/g_{m2}$, $C_X = C_Y = C_A$

$\Rightarrow \omega_A < \omega_X < \omega_Y$ $\left[\omega_A = \frac{1}{10} \omega_X = \frac{1}{100} \omega_Y \right]$

$$\beta A_0 \cong (R_F \cdot g_{m1} R_D) / R_F = g_{m1} R_D = 10$$

$$H(s) = \frac{\beta A_0}{(1+s/\omega_A)(1+s/\omega_X)(1+s/\omega_Y)}$$

$\omega_u = 10 \omega_A \approx \omega_X$

$\Rightarrow PM \cong 45^\circ$

\downarrow real is $\sim 40^\circ$
(by $\omega_Y = 10 \omega_X$)