

台灣科技大學一百零八學年度下學期期中考

科目名稱：電路學(二) 開課系所：電子系 ET2104301 地點：國際大樓 IB306

考試時間：109 年 4 月 23 日 下午 13:20 至 15:10 (雙面試題，可使用工程計算機)

1. (20%) Please find the current I_o in Fig. 1.

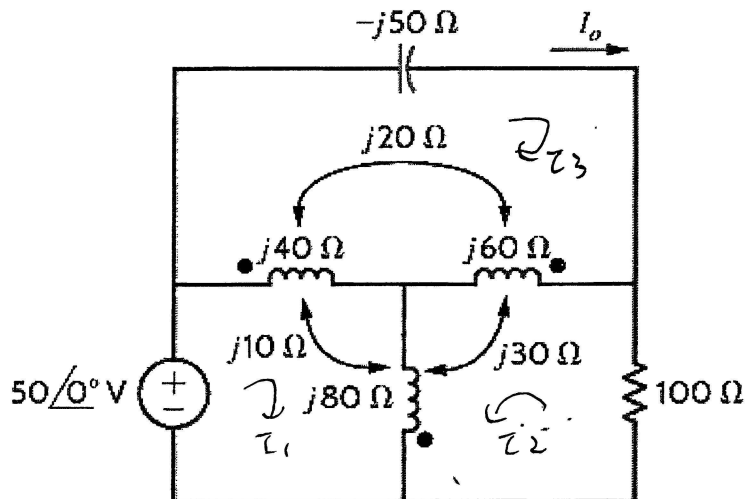


Fig. 1.

2. (20%) A balanced Y-connected load and a balanced Δ -connected load are supplied by a three-phase 480-Vrms 50Hz generator. The branch impedances of the Y and Δ loads are $15\angle 20^\circ \Omega$ and $25\angle -40^\circ \Omega$, respectively.

(a) Please determine the active and reactive powers drawn by Y and Δ -connected loads. (10%)

(b) Please determine the phasor voltage and phasor current for any one branch of each three-phase load, and substitute into the power equation for balanced three-phase loads. Given that the phase angle for Y system V_{AN} is 30° (and the phase angle for Δ system V_{AB} is 0°). (10%)

$V_{AN} V_{BN} V_{CN} I_{AN} I_{BN} I_{CN} \rightarrow$ 逐相代換

$\sin(\omega t + \theta) \rightarrow$ 逐相代換 $V_{BL} \neq V_{CN}$

3. (15%) Find I_o in the circuit in Fig. 3.

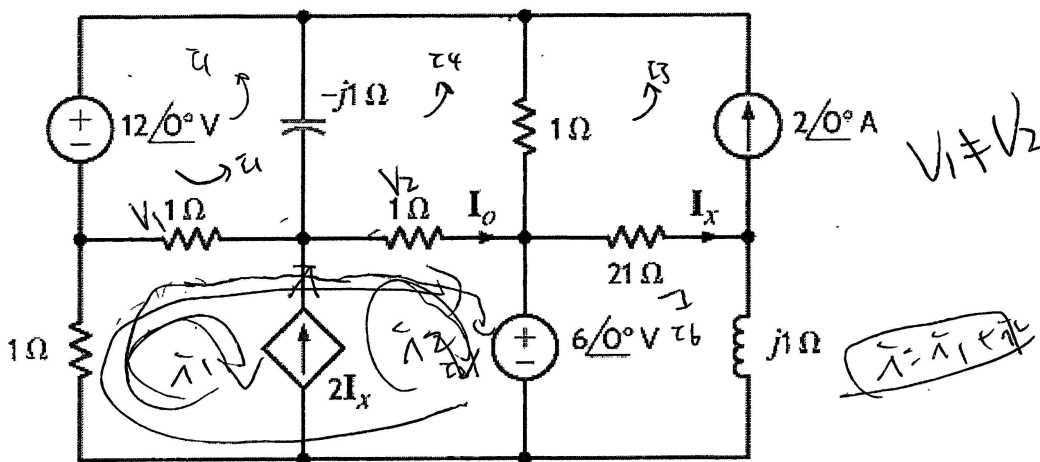


Fig. 3.

$3\lambda \times 6 \rightarrow$

$2\lambda + \lambda = 6$

4. (10%) A balanced three-phase source supplies powers to three loads: $\bar{S} = VI^*$
 Load 1: 36kW at 0.8 pf leading Load 2: 10kVA at 1.0 pf
 Load 3: unknown

If the line voltage at the load is $208V_{rms}$, the magnitude of the total complex power is 60 kVA, and the combined power factor at the load is 0.84 lagging.

Please find the unknown load, and its power factor (Please specify whether it is leading or lagging). Z

5. (20%) Please find the V_o in Fig. 5.

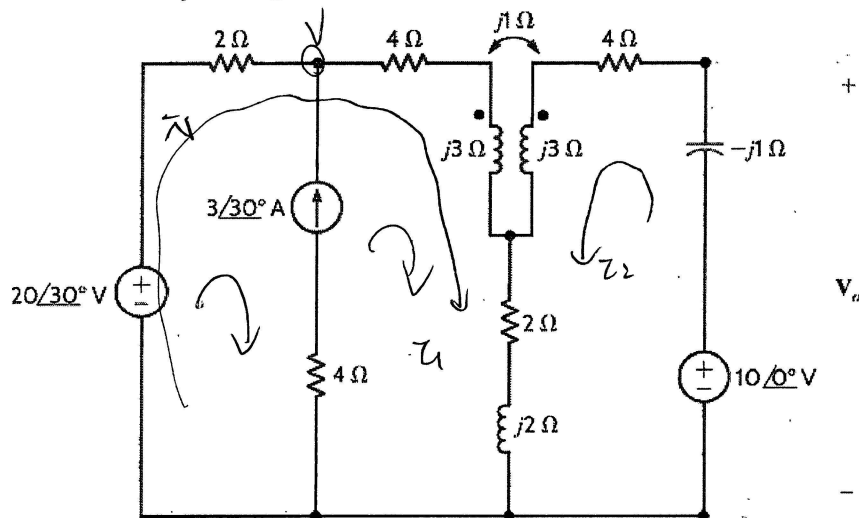


Fig. 5.

6. (15%) If Z_L has unity ^{pf=1} power factor feature, please find Z_L for maximum power transfer and the maximum power that can be transferred to the load Z_L in Fig. 6.

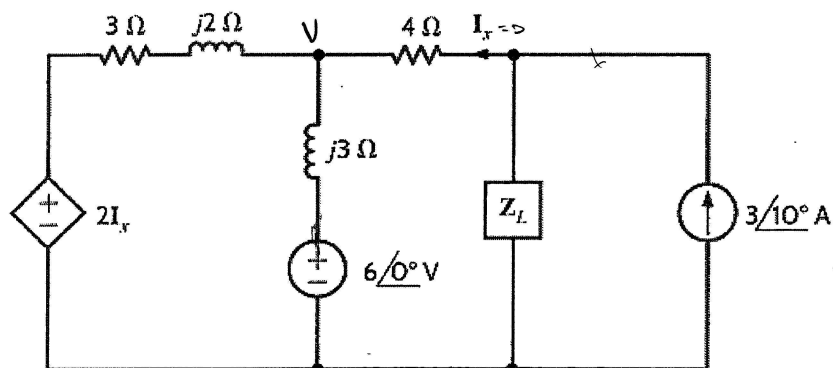


Fig. 6.