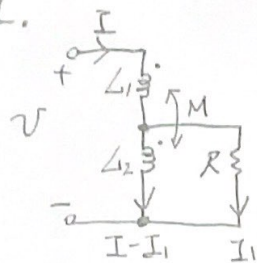


1.



$\because M$ is maximum, $M = \sqrt{L_1 L_2}$


$\therefore k_{max} = 1 \Rightarrow M = \sqrt{L_1 L_2}$

$$V = sL_1 I + s\sqrt{L_1 L_2} (I - I_1) + sL_2 (I - I_1) + s\sqrt{L_1 L_2} I$$

$$sL_2 (I - I_1) + s\sqrt{L_1 L_2} I = R I_1$$

$$\Rightarrow \begin{cases} V = (sL_1 + 2s\sqrt{L_1 L_2} + sL_2) I - (s\sqrt{L_1 L_2} + sL_2) I_1 & \text{--- ①} \\ (s\sqrt{L_1 L_2} + sL_2) I = (R + sL_2) I_1 & \text{--- ②} \end{cases}$$
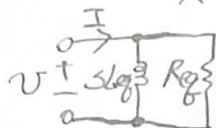
$$\text{②} \rightarrow I_1 = \frac{sL_2 + s\sqrt{L_1 L_2}}{R + sL_2} \text{ --- ③ 代入 ① 整理 } \rightarrow V = \frac{SR(L_1 + L_2 + 2\sqrt{L_1 L_2})}{sL_2 + R} \text{ --- ④}$$



$$V = \frac{sL_1 Req}{sL_1 + Req} \text{ --- ⑤}$$


$\therefore \text{④} = \text{⑤}$

$$\Rightarrow sL_1 Req + Req^2 = sL_2 + R$$

$$\Rightarrow sL_1 Req = s(L_1 + L_2 + 2\sqrt{L_1 L_2}) R$$

$$\Rightarrow L_1 = 0 \text{ (H)} \quad \therefore \begin{cases} Req = R \text{ (}\Omega\text{)} \\ L_{eq} = L_2 \text{ (H)} \end{cases}$$

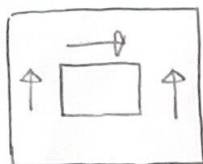
2. (a) \rightarrow Induction magnetic field direction




$$\Rightarrow L_{ae} = (L_{ab} + 1 - 1) + (L_{dc} + 1 - 2) + (L_{fe} - 2 - 1)$$

$$= 1 + 1 - 1 + 3 + 1 - 2 + 4 - 2 - 1$$


$$= 4 \text{ (H)} \quad \#$$

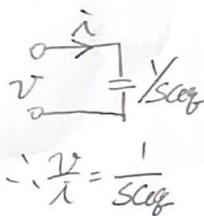
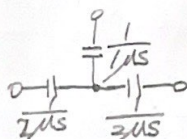
$$\therefore \frac{V}{i} = \frac{1}{sC_{eq}}$$



Δ to Δ

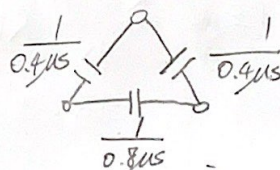

$$V = \frac{\tilde{V}_1}{0.2us} + \frac{i}{0.5us} \text{ --- ①}$$

$$\frac{\tilde{V}_1}{0.2us} = \frac{i}{2us} + \frac{i - \tilde{V}_1}{0.4us} \text{ --- ②}$$

$$\text{②} \rightarrow \tilde{V}_1 = \frac{2}{5} i \text{ --- ③ 代入 ①}$$


$$\rightarrow \frac{V}{i} = \frac{1}{0.25us} \quad \therefore C_{eq} = 0.25 \mu\text{(F)} \quad \#$$

(b) \therefore Parallel & critically system

$$\alpha^2 - \omega_0^2 = 0$$

$$\therefore \alpha = \frac{1}{2R_{ab}C_{eq}}, \quad \omega_0 = \frac{1}{\sqrt{L_{ae}C_{eq}}}$$
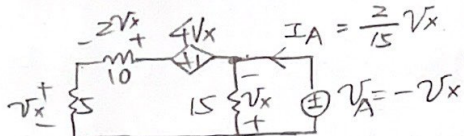
$$\rightarrow R_{ab} = \pm \sqrt{\frac{L_{ae}}{4C_{eq}}} = \pm 2000 \text{ (取正)}$$



$$\therefore R_A = \frac{V_A}{I_A} = -7.5 \text{ (}\Omega\text{)}$$

$$R_{ab} = 2000 = R_x + (-7.5) \quad \therefore R_x = 2007.5 \text{ (}\Omega\text{)} \quad \#$$


$$(c) \omega_0 = \frac{1}{\sqrt{L_{ac} C_{eq}}} = 10^3 \text{ (rad/s)} \quad \# \quad Q = \omega_0 R_{ab} C_{eq} = 0.5 \text{ (單位)} \quad \#$$

$$BW = 2\alpha = 2000 \text{ (rad/s)} \quad \#$$

$$\text{zero} = s = 0 \text{ (rad/s)}$$

$$\text{pole} = s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -1000 \pm 0 \quad \rightarrow$$

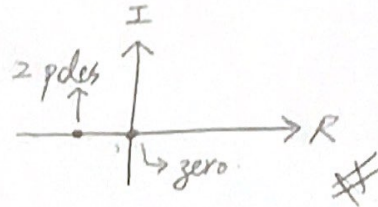
$$= -1000 \text{ or } -1000 \text{ (rad/s)}$$




$$\omega_H = \alpha + \sqrt{\alpha^2 + \omega_0^2} = 1000 + 1000\sqrt{2} = 2414.214 \text{ (rad/s)} \quad \#$$

$$\omega_L = -\alpha + \sqrt{\alpha^2 + \omega_0^2} = -1000 + 1000\sqrt{2} = 414.214 \text{ (rad/s)} \quad \#$$

3. (a)

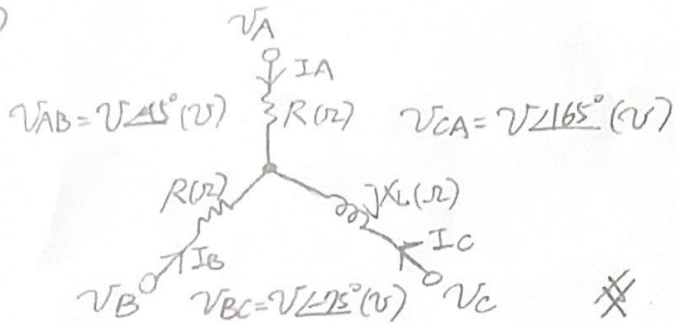

(b).

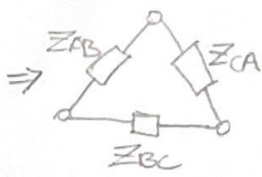

$$\because R = |jX_L| \therefore X_L = R$$

$$\rightarrow R \cdot R + R \cdot jR + R \cdot jR = R^2(1+j^2)$$

$$\rightarrow Z_{AB} = \frac{R^2(1-j^2)}{jR} = R(2-j)(\Omega), Z_{BC} = Z_{CA} = \frac{R^2(1+j^2)}{R} = R(1+j^2)(\Omega)$$

$$\begin{cases} I_{AB} = \frac{V\angle 45^\circ}{R(2-j)} \text{ (A)} \\ I_{BC} = \frac{V\angle -75^\circ}{R(1+j^2)} \text{ (A)} \\ I_{CA} = \frac{V\angle 165^\circ}{R(1+j^2)} \text{ (A)} \end{cases} \rightarrow$$

$$I_A = I_{AB} - I_{CA} = 0.231 \frac{V}{R} \angle -3.435^\circ \text{ (A)}$$

$$I_B = I_{BC} - I_{AB} = 0.864 \frac{V}{R} \angle -123.435^\circ \text{ (A)}$$

$$I_C = I_{CA} - I_{BC} = 0.775 \frac{V}{R} \angle 21.565^\circ \text{ (A)}$$

$$S = \frac{1}{2} (|I_A|^2 R + |I_B|^2 R + |I_C|^2 jR) = \frac{V^2}{R} (0.4 + j0.3) \text{ (VA)}$$

$$\therefore I_N = I_A + I_B + I_C = I_{AB} - I_{CA} + I_{BC} - I_{AB} + I_{CA} - I_{BC} = 0 \text{ (A)} \quad \#$$

\therefore The neutral current is zero $\#$.

$$(c) S = V^2(0.4 + j0.3)$$

$$\Rightarrow P_{\text{old}} = 0.8 \text{ lagging}$$

$$\therefore Q_{\text{new}} = \pm 0.4 V^2 \tan[\cos^{-1}(0.98)]$$


$$= \pm 0.081 V^2 \text{ (VAR)}$$

$$\therefore Q_{\text{new}} = |Q_{\text{new}} - Q_{\text{old}}| = |\pm 0.081 V^2 - 0.3 V^2| = 0.381 V^2 \text{ or } 0.219 V^2 \text{ (VAR)} \quad \#$$

Advantage: Improve voltage, Reduce line loss, Increase the life of equipment, Reduce electricity bills... etc $\#$

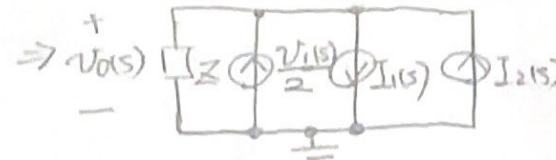4. $\Rightarrow V_0(s) = \left[\frac{V_1(s)}{2} - I_1(s) + I_2(s) \right] \cdot Z$

$Z = 2 // 2 // \frac{1}{s} = \frac{1}{s+1}$



令 $V_1(s) = \sin[3(t - \frac{\pi}{6})]u(t - 6\pi)$

$\mathcal{L}\{V_1(s)\} = e^{-6\pi s} \mathcal{L}\{\sin[3(t + 6\pi - \frac{\pi}{6})]\} = e^{-6\pi s} \mathcal{L}\{\sin(3t - \frac{\pi}{2})\} = -e^{-6\pi s} \frac{s}{s^2 + 9}$

$\therefore V_1(t) = V_1(4t) \therefore \mathcal{L}\{V_1(t)\} = -\frac{1}{4} e^{-\frac{3}{4}\pi s} \frac{\frac{s}{4}}{(\frac{s}{4})^2 + 9} = -e^{-\frac{3}{4}\pi s} \frac{s}{s^2 + 144}$

$\mathcal{L}\{I_1(s)\} = \int_s^\infty \frac{4}{s_1^2 + 4^2} ds_1 = \theta \Big|_{\tan^{-1}(\frac{s}{4})}^{\frac{\pi}{2}} = \frac{\pi}{2} - \tan^{-1}(\frac{s}{4})$ (令 $s_1 = 4 \tan \theta$ 用三角代换)

$\mathcal{L}\{I_2(t)\} = e^{-10s} \mathcal{L}\{\frac{t}{4} \sin(2t)u(t)\} = -\frac{e^{-10s}}{4} \cdot \frac{d}{ds} \left(\frac{2}{s^2 + 4} \right) = \frac{se^{-10s}}{(s^2 + 4)^2}$

$\therefore V_0(s) = \frac{-se^{-\frac{3}{4}\pi s}}{2(s+1)(s^2 + 144)} - \frac{\frac{\pi}{2} - \tan^{-1}(\frac{s}{4})}{s+1} + \frac{se^{-10s}}{(s+1)(s^2 + 4)^2} = A(s) - B(s) + C(s)$

$A(s) = e^{-\frac{3}{4}\pi s} \left(\frac{-\frac{1}{2}90}{s+1} + \frac{-1}{290} \cdot \frac{s+12 \cdot 12}{s^2 + 144} \right)$

$\therefore \mathcal{L}^{-1}\{A(s)\} = \left\{ \frac{-e^{-\frac{3}{4}\pi}}{290} e^{-t} - \frac{1}{290} \left\{ \cos[12(t - \frac{3}{2}\pi)] + 12 \sin[12(t - \frac{3}{2}\pi)] \right\} \right\} u(t - \frac{3}{2}\pi)$

$\mathcal{L}^{-1}\{B(s)\} = e^{-t} \int_0^t \mathcal{L}^{-1}\left\{ \frac{\pi}{2} - \tan^{-1}(\frac{s-1}{4}) \right\} dt = e^{-t} \int_0^t \frac{1}{t} \mathcal{L}^{-1}\left\{ \frac{d}{ds} \left[\tan^{-1}(\frac{s-1}{4}) - \frac{\pi}{2} \right] \right\} dt$

$= e^{-t} \int_0^t \frac{1}{t} \mathcal{L}^{-1}\left\{ \frac{4}{(s-1)^2 + 16} \right\} dt = e^{-t} \int_0^t \frac{e^{\tau} \sin(4\tau)}{\tau} u(\tau) dt$

$\mathcal{L}^{-1}\{C(s)\} = \mathcal{L}^{-1}\left\{ e^{-10s} \left[\frac{-1/5}{s+1} + \frac{(s-1)/5}{s^2 + 4} + \frac{s/5}{(s^2 + 4)^2} + \frac{4/5}{(s^2 + 4)^2} \right] \right\}$

$= \left\{ \frac{-e^{-10}}{25} e^{-t} + \frac{1}{25} \left\{ \cos[2(t-10)] - \frac{1}{2} \sin[2(t-10)] \right\} + \frac{t-10}{20} \sin[2(t-10)] + \frac{1}{20} \sin[2(t-10)] \right. \\ \left. - \frac{t-10}{40} \cos[2(t-10)] \right\} u(t-10)$

$\therefore V_0(t) = \mathcal{L}^{-1}\{V_0(s)\} = \mathcal{L}^{-1}\{A(s)\} - \mathcal{L}^{-1}\{B(s)\} + \mathcal{L}^{-1}\{C(s)\}$


$= \left\{ \frac{-e^{-\frac{3}{4}\pi}}{290} e^{-t} - \frac{1}{290} \left\{ \cos[12(t - \frac{3}{2}\pi)] + 12 \sin[12(t - \frac{3}{2}\pi)] \right\} \right\} u(t - \frac{3}{2}\pi)$

$- e^{-t} \int_0^t \frac{e^{\tau} \sin(4\tau)}{\tau} u(\tau) dt + \left\{ \frac{-e^{-10}}{25} e^{-t} + \frac{1}{25} \left\{ \cos[2(t-10)] - \frac{1}{2} \sin[2(t-10)] \right\} \right. \\ \left. + \frac{t-10}{20} \sin[2(t-10)] + \frac{1}{20} \sin[2(t-10)] - \frac{t-10}{40} \cos[2(t-10)] \right\} u(t-10) \quad (v) \quad \#$


$$G(j\omega) = G(s) = \frac{-4(1 + \frac{j\omega}{100}) \left[1 + \frac{j\omega}{12.5} + \left(\frac{j\omega}{5} \right)^2 \right]}{(j\omega)^2 (1 + \frac{j\omega}{25}) \left[1 + \frac{j\omega}{50} + \left(\frac{j\omega}{10} \right)^2 \right]}$$

$$\Rightarrow \zeta_1 \cdot \frac{1}{5} = \frac{1}{12.5}, \zeta_1 = 0.2$$
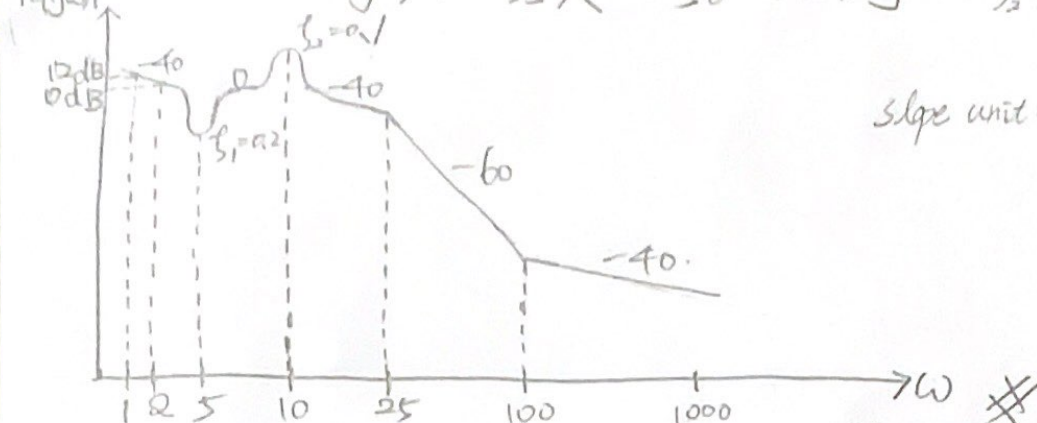
$$\Rightarrow \zeta_2 \cdot \frac{1}{10} = \frac{1}{50}, \zeta_2 = 0.1$$



slope unit: dB/decade

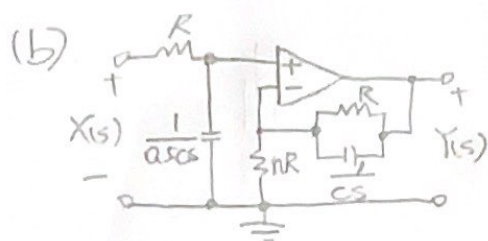

$$V_- = V_+ = X(s) \cdot \frac{1/sRC}{R + 1/sRC} = X(s) \frac{1}{1 + sRC}$$

$$\frac{V_- - 0}{nR} = \frac{Y(s) - V_-}{R + 1/sC} \Rightarrow Y(s) = V_- \cdot \frac{s + \frac{1}{nRC}}{s + \frac{1}{RC}}$$

$$\Rightarrow \frac{Y(s)}{X(s)} = \frac{1 \cdot (1/sRC) \left[s + \frac{1}{(n+1)RC} \right]}{\left(s + \frac{1}{RC} \right) \left(s + \frac{1}{sRC} \right)}$$

- If $n=1$, this is a 1st order lowpass filter.
- If $n \neq 1$ & $n > 0$, this is a 2nd order lowpass filter. *

$$(c) \frac{Y(j\omega)}{X(j\omega)} \Big|_{\omega=0} = 21 = \frac{n+1}{n} \Rightarrow \text{choose } n=0.05 *$$

$$\frac{Y(j\omega)}{X(j\omega)} \Big|_{\omega=50 \cdot 2\pi} = \frac{21}{\sqrt{2}} \angle 45^\circ, \therefore \frac{1}{RC} < \frac{1}{sRC} \text{ \& \> } \frac{1}{RC} < \frac{1}{(n+1)RC}$$

$\frac{1}{RC}$ is first corner frequency \Rightarrow choose $\begin{cases} R = 20 \text{ k}(\Omega) \\ C = 160 \text{ n}(F) \end{cases} *$

$$(d) X(s) = \int_0^\infty t^2 \delta(t-2) e^{-st} dt = t^2 e^{-st} \Big|_{t=2} = 4e^{-2s}$$

$$G(s) = e^{-2s} \mathcal{L}\{u(t+1) + 1\} = e^{-2s} \mathcal{L}\{u(t-(-2))\} = \frac{se^{-s}}{s} \left(\because (-2) < 0, \text{ \& \> } u(t) \text{ - 様} \right)$$

$$\left(\because \mathcal{L}\{u(t+2)\} = \mathcal{L}\{u(t)\} = \frac{1}{s} \right)$$


$$R \cdot C = 1 \text{ m} \cdot 10 \text{ k} = 10, n=1$$

$$\therefore Z(s) = 4e^{-2s} \cdot \frac{1}{s} \cdot \frac{1}{s+0.1} \cdot \frac{se^{-s}}{s} = \frac{4e^{-3s}}{s(s+0.1)}$$

$$= 4e^{-3s} \cdot \left(\frac{10}{s} + \frac{-10}{s+0.1} \right)$$

$$\therefore Z(t) = \mathcal{L}^{-1}\{Z(s)\} = 40 [1 - e^{0.1(t-3)}] u(t-3) \text{ (V)}$$

$$\therefore Z(3) = 0 \text{ (V)} *$$

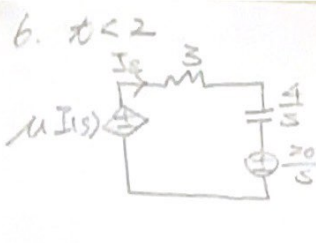

$$\mu I(s) = I(s) \left(3 + \frac{4}{s} \right) + \frac{20}{s}$$

$$I(s) \left(\mu - 3 - \frac{4}{s} \right) = \frac{20}{s}$$


$$\Rightarrow I(s) = \frac{20}{(\mu-3)s-4} = \frac{20}{\mu-3} \cdot \frac{1}{s - \frac{4}{\mu-3}}$$

The stable circuit means that the pole position must be on the left of the complex plane.

$$\therefore \frac{4}{\mu-3} < 0$$

$$\Rightarrow \mu-3 < 0 \Rightarrow \mu < 3$$

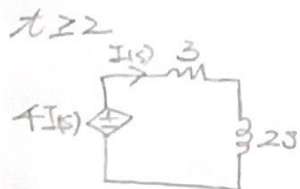$\therefore \mu < 3$ makes the circuit stable for $\kappa < 2$.




$$4I(s) = I(s) \cdot (3 + 2s)$$

$$\Rightarrow I(s) \cdot (1 - 2s) = 0$$


$$\Rightarrow I(s) = 0$$

$$\therefore V_2(s) = 0 \cdot 2s = 0$$
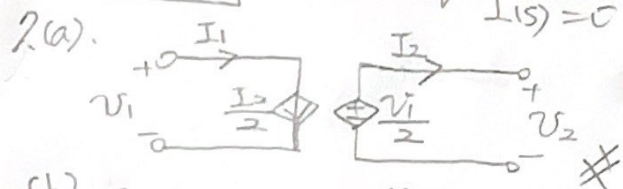
$$\Rightarrow V_2(t) = \mathcal{L}^{-1}\{V_2(s)\} = 0 (V)$$




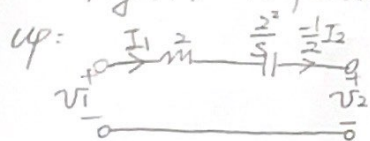(b) Fig. 6(a) is parallel of up and down.



$$\begin{cases} I_1 = \frac{v_1}{2 + \frac{4}{s}} - \frac{2v_2}{2 + \frac{4}{s}} \\ I_2 = \frac{-2v_1}{2 + \frac{4}{s}} + \frac{4v_2}{2 + \frac{4}{s}} \end{cases}$$
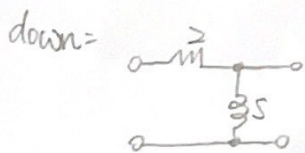
$$\therefore Y_{up} = \begin{bmatrix} \frac{1}{2 + \frac{4}{s}} & \frac{-2}{2 + \frac{4}{s}} \\ \frac{-2}{2 + \frac{4}{s}} & \frac{4}{2 + \frac{4}{s}} \end{bmatrix} (s)$$




$$\therefore Y_{down} = \begin{bmatrix} \frac{1}{2} & \frac{-1}{2} \\ \frac{-1}{2} & \frac{1}{2 + \frac{1}{s}} \end{bmatrix} (s)$$

$$Y|_{\omega=2} = (Y_{up} + Y_{down})|_{\omega=2} = \begin{bmatrix} \frac{3+j}{4} & \frac{-2-j}{2} \\ \frac{-2-j}{2} & \frac{3+j}{2} \end{bmatrix} (s)$$

Parameter Conversion:
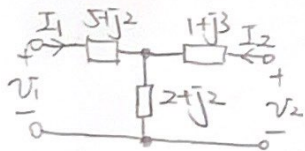
$$Y \text{ to } Z \Rightarrow Z_Y = \begin{bmatrix} \frac{Y_{22}}{\Delta} & \frac{-Y_{12}}{\Delta} \\ \frac{-Y_{21}}{\Delta} & \frac{Y_{11}}{\Delta} \end{bmatrix} = \begin{bmatrix} 2+j4 & 1+j3 \\ 1+j3 & 1+j2 \end{bmatrix} (\Omega)$$




$$\begin{cases} v_1 = I_1(1+j4) + I_2(2+j2) \\ v_2 = I_1(2+j2) + I_2(3+j5) \end{cases}$$

$$\Rightarrow Z_1 = \begin{bmatrix} 7+j4 & 2+j2 \\ 2+j2 & 3+j5 \end{bmatrix} (\Omega)$$

$\therefore Z_1$ & Z_Y is in series.
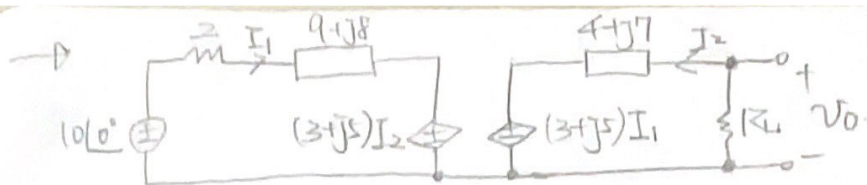
$$\therefore Z_{total} = Z_1 + Z_Y = \begin{bmatrix} 9+j8 & 3+j5 \\ 3+j5 & 4+j7 \end{bmatrix} (\Omega)$$



求 V_{oc} \downarrow

$$\begin{cases} 10\angle 0^\circ = (11+j8)I_1 + (3+j5)I_2 \\ I_2 = 0 \text{ 代入上式} \end{cases}$$

$$\Rightarrow I_1 = 0.735\angle 36.027^\circ \text{ (A)}$$

$$\therefore V_{oc} = (3+j5)I_1 = 4.287\angle 28.009^\circ \text{ (V)}$$

求 I_{sc} \downarrow

$$\begin{cases} 10 = (11+j8)I_1 + (3+j5)I_2 \\ (3+j5)I_1 + (4+j7)I_2 = 0 \end{cases}$$

$$\Rightarrow I_2 = \frac{\Delta I_2}{\Delta} = 0.737\angle 151.935^\circ \text{ (A)}$$

$$\therefore I_{sc} = -I_2 = 0.737\angle -28.065^\circ \text{ (A)}$$

$$\therefore Z_{th} = \frac{V_{oc}}{I_{sc}} = 5.819\angle 51.074^\circ \text{ (}\Omega\text{)} \quad \rightarrow R_L = |Z_{th}| \text{ 时 } \rightarrow P_{max}$$

$$\therefore P_{max} = \frac{1}{2} \cdot \left| \frac{V_{oc}}{Z_{th} + R_L} \right|^2 \times R_L = 0.485 \text{ (W)}$$

8. $s = j\omega$

$$\begin{aligned} \therefore F(j\omega) = F(s) &= \frac{1}{s(1 - e^{\frac{\pi}{2}s})} + \frac{se^{\frac{\pi}{2}s} - 1}{(s^2 + 1)(1 - e^{\frac{\pi}{2}s})} \\ &= \frac{e^{-\frac{\pi}{2}s}}{s} \cdot \frac{1}{1 - e^{\frac{\pi}{2}s}} + \frac{se^{\frac{\pi}{2}s} - 1}{s^2 + 1} \cdot \frac{1}{1 - e^{\frac{\pi}{2}s}} \\ &= \left(\frac{e^{-\frac{\pi}{2}s}}{s} + \frac{se^{\frac{\pi}{2}s} - 1}{s^2 + 1} \right) (1 + e^{\frac{\pi}{2}s} + e^{\frac{\pi}{4}s} + e^{\frac{\pi}{6}s} + \dots) \end{aligned}$$

$$\therefore \mathcal{L}^{-1}\{F(s)\} = f(t) = \left[t u(t - \frac{\pi}{2}) \right] + \left[\sin t u(t - \frac{\pi}{2}) - \sin t u(t) \right], 0 \leq t \leq \frac{\pi}{2}, f(t) = f(t + \frac{\pi}{2})$$

