

台灣科技大學一百零七學年度上學期期末考

科目名稱：電路學(一) 開課系所：電子系 ET2103301 地點：國際大樓 IB501

考試時間：108 年 1 月 3 日 下午 13:20 至 15:10 (可使用工程計算機)

1. (10%) Please find V_o in Fig. 1.

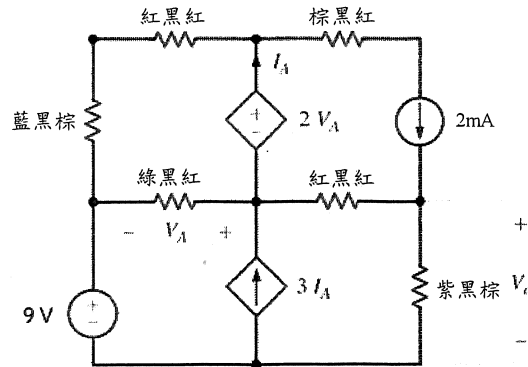


Fig. 1.

2. (10%) Please answer the following questions in Fig. 2.
- What is the characteristic equation? (2%)
 - What is the resonant frequency ω_n ? (2%)
 - What is the type of damping exhibited by the circuit? (3%)
 - Please compute $v_o(t)$ for $t > 0$ (3%)

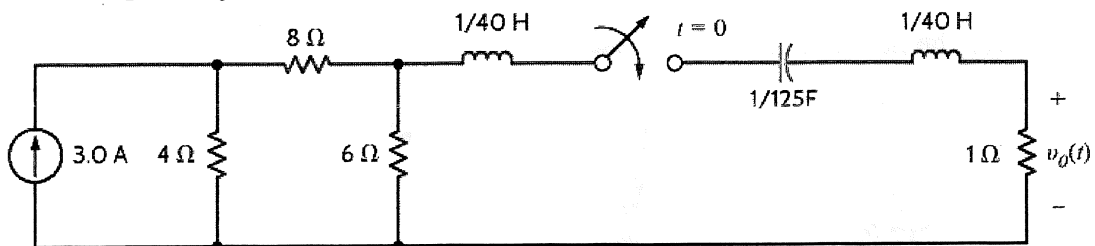


Fig. 2.

3. (15%) If Z_L has unity power factor feature, please find Z_L for maximum power transfer and the maximum power that can be transferred to the load Z_L in Fig. 3.

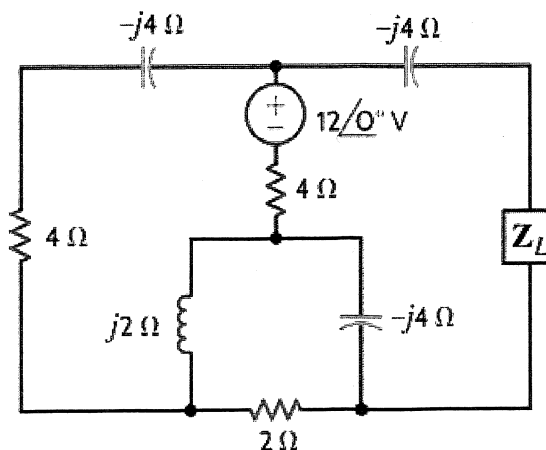


Fig. 3.

4. (10%) In Fig. 4, a load is modeled by an impedance of $4 + j4$. Please determine the value of capacitance that must be connected in parallel with the load to correct the power factor of the combined load and capacitor to 0.97 lagging at $f = 50\text{Hz}$.

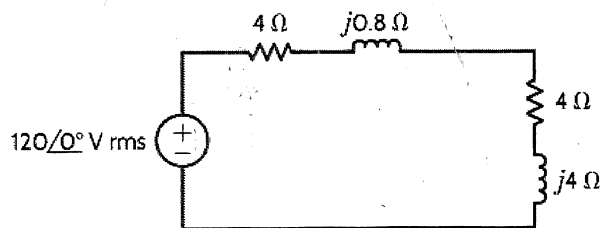


Fig. 4

5. (15%) The circuit in Fig. 5 is operated at steady state before the switch open. Please determine the inductor current $i(t)$ for $t > 0$.

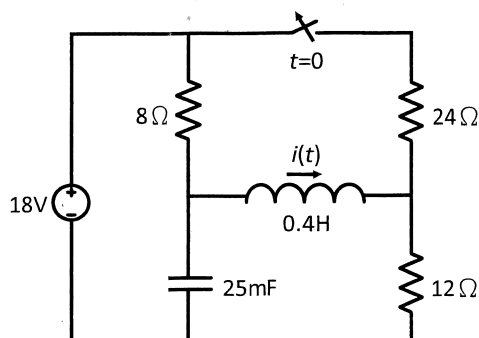


Fig. 5.

6. (20%) Given the network in Fig. 6. Please compute (a) the input source voltage and (b) the input power factor.

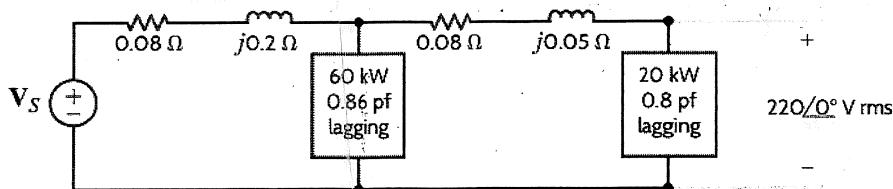


Fig. 6.

7. (20%) There are two input voltage in Fig. 7 including $v_1(t) = 50 \cos(20t - 75^\circ)\text{V}$ and $v_2(t) = 35 \cos(20t + 110^\circ)\text{V}$. If the node voltage can be obtained as $v(t) = 21.25 \cos(20t - 168.8^\circ)\text{V}$ at steady state, please determine the values of R and L .

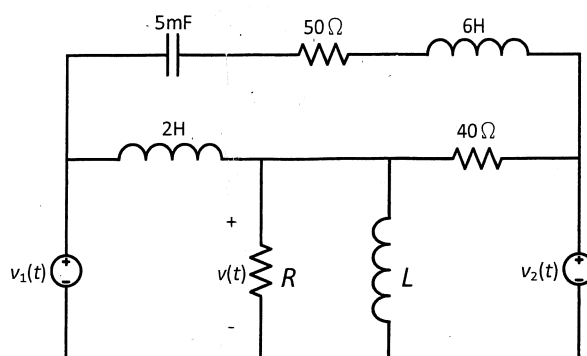


Fig. 7.