

# Introduction to Analog Integrated Circuit Design

Fall 2023


## Frequency Response

Yung-Hui Chung

MSIC Lab  
DECE, NTUST


Mixed-Signal  
IC Laboratory   
NTUST

# Frequency Response

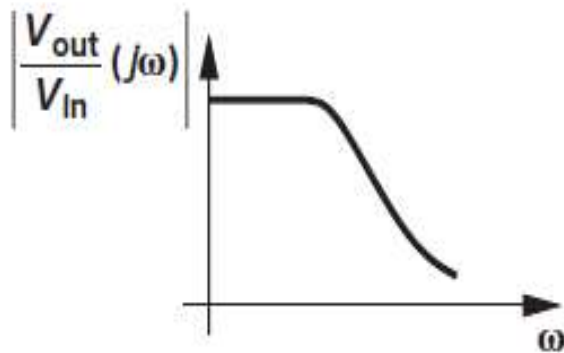


(a)

Low-Pass Filter

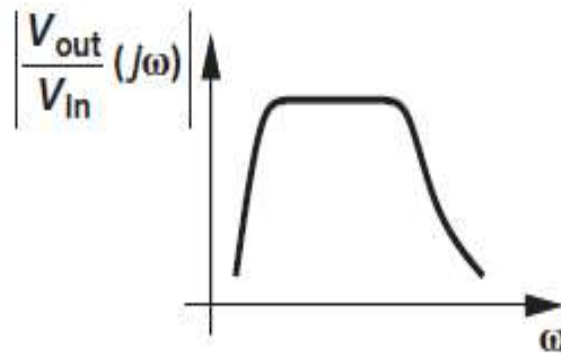

(b)

Band-Pass Filter

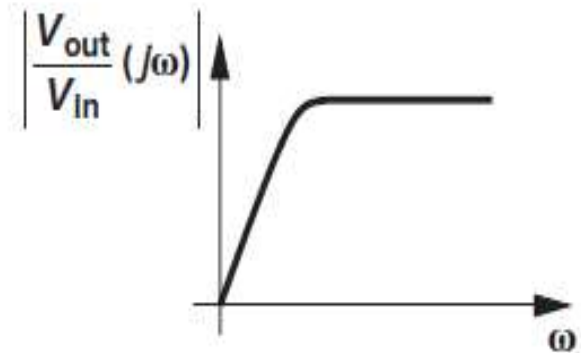

(c)


High-Pass Filter

For MOSFETs, **parasitic capacitors** are existed between two nodes to construct poles or zeros


- Poles: decreased magnitude if higher frequency
- Zeros: increased magnitude if higher frequency
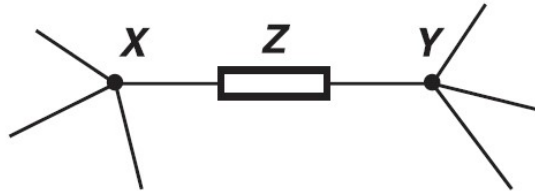
# Miller Effect

如果圖(a)之電路可以被轉換成圖(b)之電路，則  $Z_1 = Z/(1 - A_v)$  且  $Z_2 = Z/(1 - A_v^{-1})$ ，其中  $A_v = V_Y/V_X$ 。



(a)

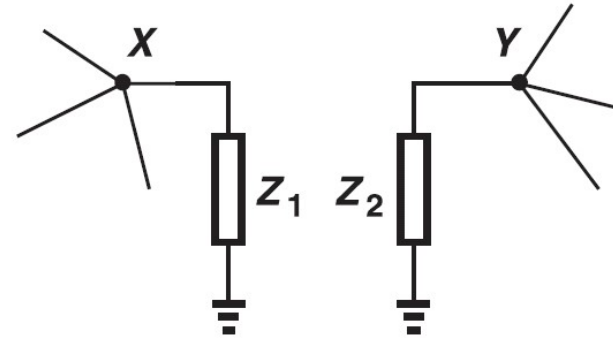


(b)

證明：從  $X$  流經  $Z$  至  $Y$  之電流為  $(V_X - V_Y)/Z$ ，若這兩個電路要相等時，此電流必須與流經  $Z_1$  之電流相同。因此

$$\frac{V_X - V_Y}{Z} = \frac{V_X}{Z_1} \Rightarrow Z_1 = \frac{Z}{1 - \frac{V_Y}{V_X}} = \frac{Z}{1 - A_v}$$

$$\frac{V_Y - V_X}{Z} = \frac{V_Y}{Z_2} \Rightarrow Z_2 = \frac{Z}{1 - \frac{V_X}{V_Y}} = \frac{Z}{1 - A_v^{-1}}$$

# Miller Effect (Supplement)

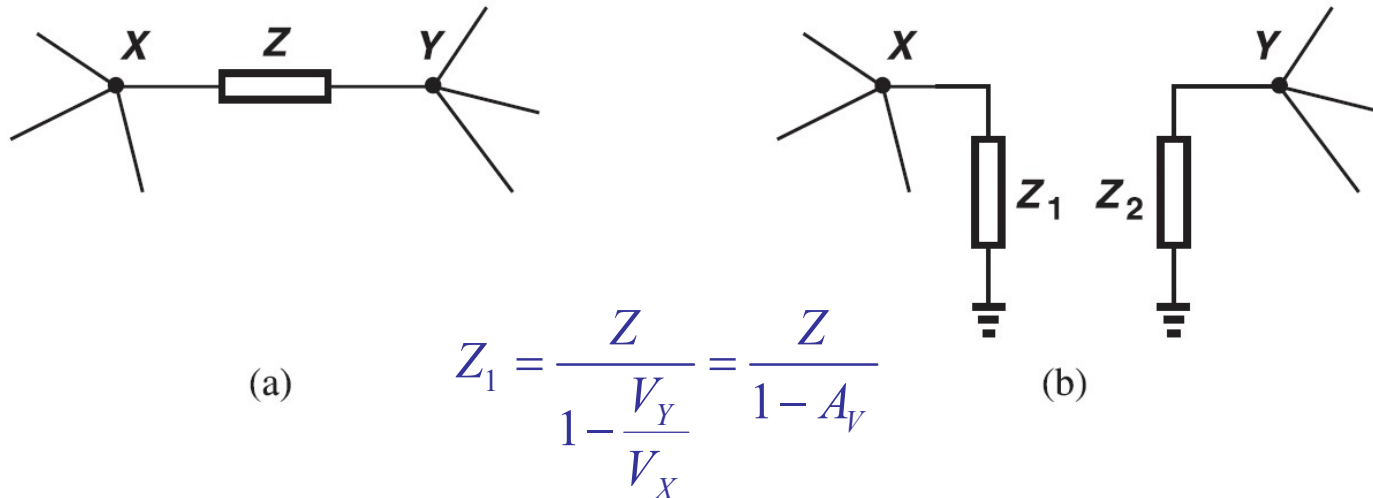

For capacitor in Miller path,  $Z = 1/sC$

$$Z_1 = 1/sC(1-A_v) \Rightarrow Z_1 = 1/s(C*(1-A_v))$$



Since  $A_v < 0$ ,  $Z_1 = 1/sC_m \Rightarrow C_m = C*(1-A_v)$ , Cap is scaled up

For resistor in Miller path,  $Z = R$ ,


$$Z_1 = R/(1-A_v)$$

Since  $A_v < 0$ ,  $Z_1 = R_m$ ,  $R_m = R/(1-A_v)$ , Res is scaled down

## 不適用米勒定律的例子

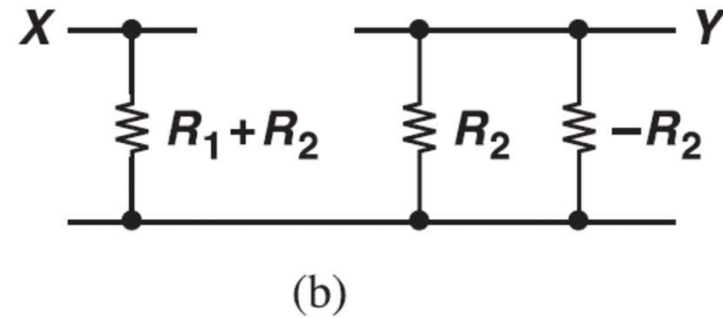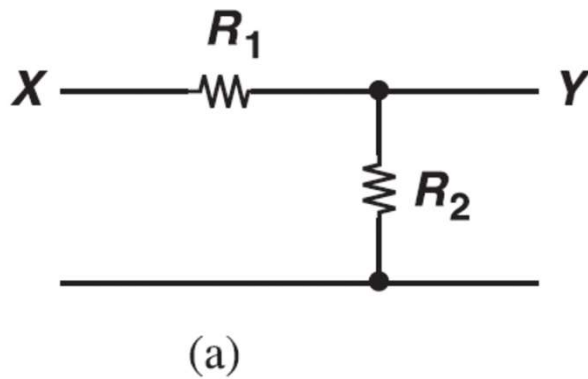


## 典型有效地應用米勒定律的例子

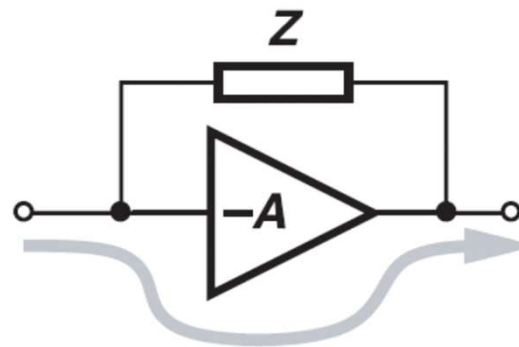

主要信號路徑
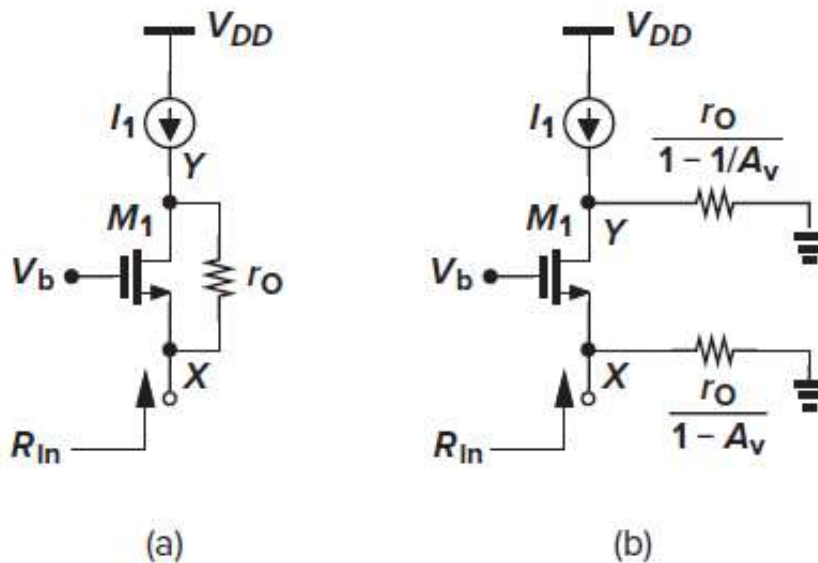
# Miller Effect

- 使用米勒效應去簡化電路將會遺漏轉移函數的零點 (zeros)。
- 如果應用在求得輸入 - 輸出轉移函數時，**米勒定律不可同時用來計算輸出阻抗** (page 179, textbook)。
- 圖(b)之電路輸入阻抗為




$$A_v = 1 + (g_m + g_{mb})r_O$$

$$\begin{aligned} R_{in} &= \frac{r_O}{1 - [1 + (g_m + g_{mb})r_O]} \parallel \frac{1}{g_m + g_{mb}} \\ &= \frac{-1}{g_m + g_{mb}} \parallel \frac{1}{g_m + g_{mb}} \\ &= \infty \end{aligned}$$
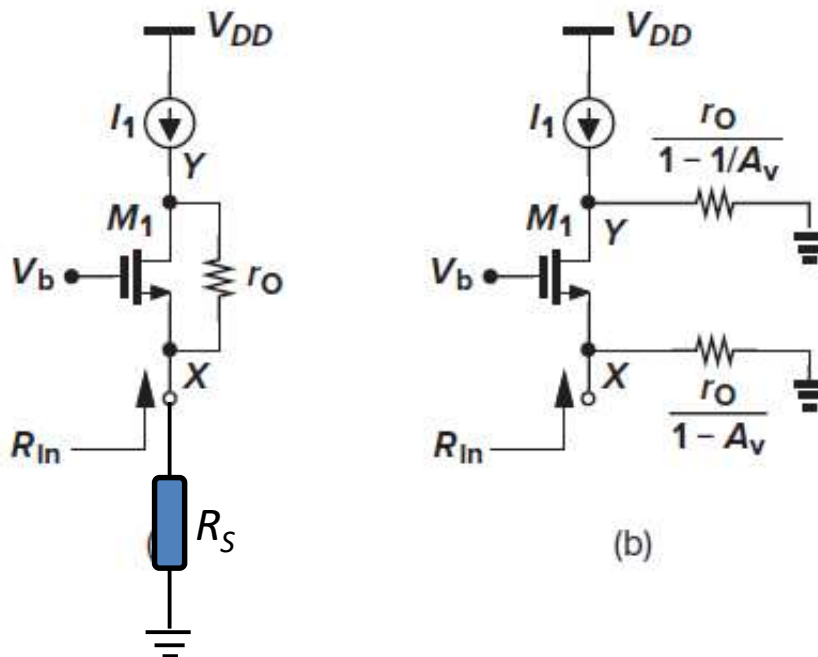
# Miller Effect

- 使用米勒效應去簡化電路將會遺漏轉移函數的零點 (zeros)。
- 如果應用在求得輸入 - 輸出轉移函數時，**米勒定律不可同時用來計算輸出阻抗** (page 179, textbook)。
- 圖(b)之電路輸出阻抗為



Applying Miller effect,

$$\begin{aligned}
 R_{out} &= \frac{r_O}{1 - 1/A_v} \\
 &= \frac{r_O}{1 - [1 + (g_m + g_{mb})r_O]^{-1}} \\
 &= \frac{1}{\cancel{g_m + g_{mb}}} + r_O
 \end{aligned}$$


But, in real,

$$R_{out} = r_{o1} + R_S + g_{m1}r_{o1}R_S$$

# Association of Poles with Nodes



Mixed-Signal  
IC Laboratory

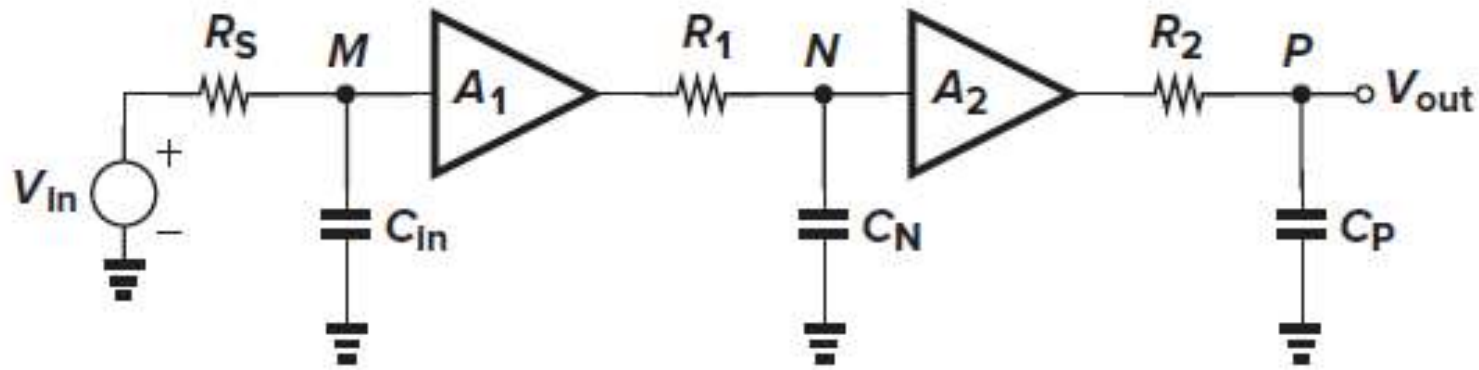


整體轉移函數 
$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + sR_S C_{in}} \cdot \frac{A_2}{1 + sR_1 C_N} \cdot \frac{1}{1 + sR_2 C_P}$$

This configuration is easy to analyze!!

But, does it worth?



# Association of Poles with Nodes

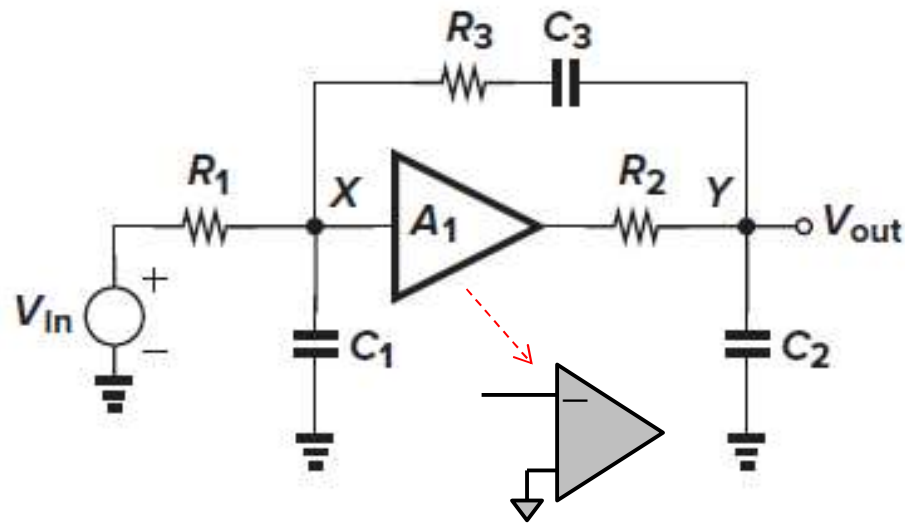

$$V_X = -\frac{V_a}{A_1}$$


$$\frac{V_X - V_{in}}{R_1} + sC_1 V_X + \frac{V_X - V_{out}}{Z_3} = 0$$

$$\frac{V_X - V_{out}}{Z_3} + sC_2 V_{out} + \frac{V_{out} - V_a}{R_2} = 0$$


=> To get its transfer function (T.F.) =>  $V_{out}/V_{in}$

# Review of MOSFET


## Parasitic capacitors

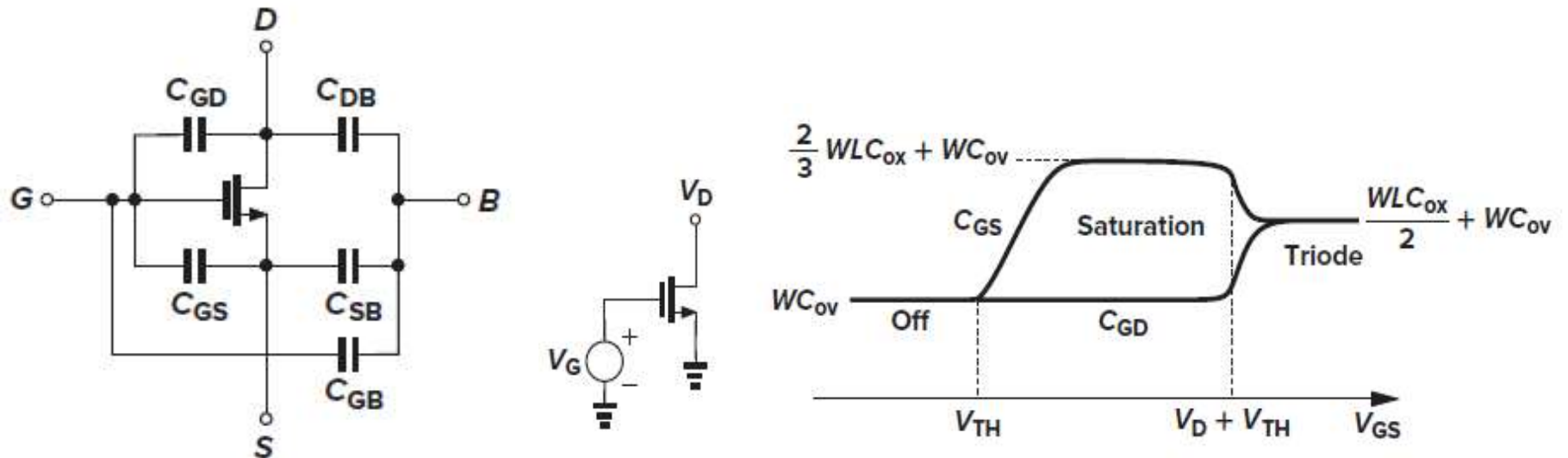

## Small-signal model (w/ cap)

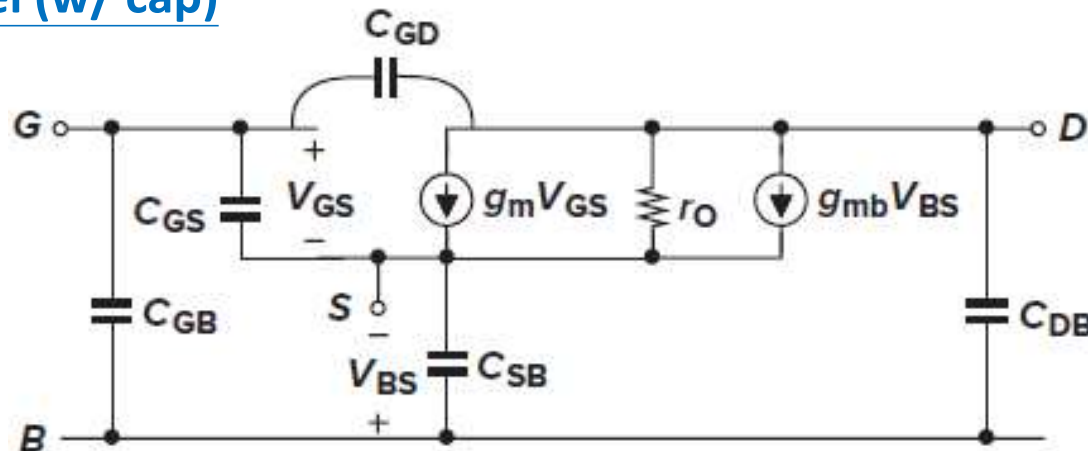

# Common-Source Stage (C-S)

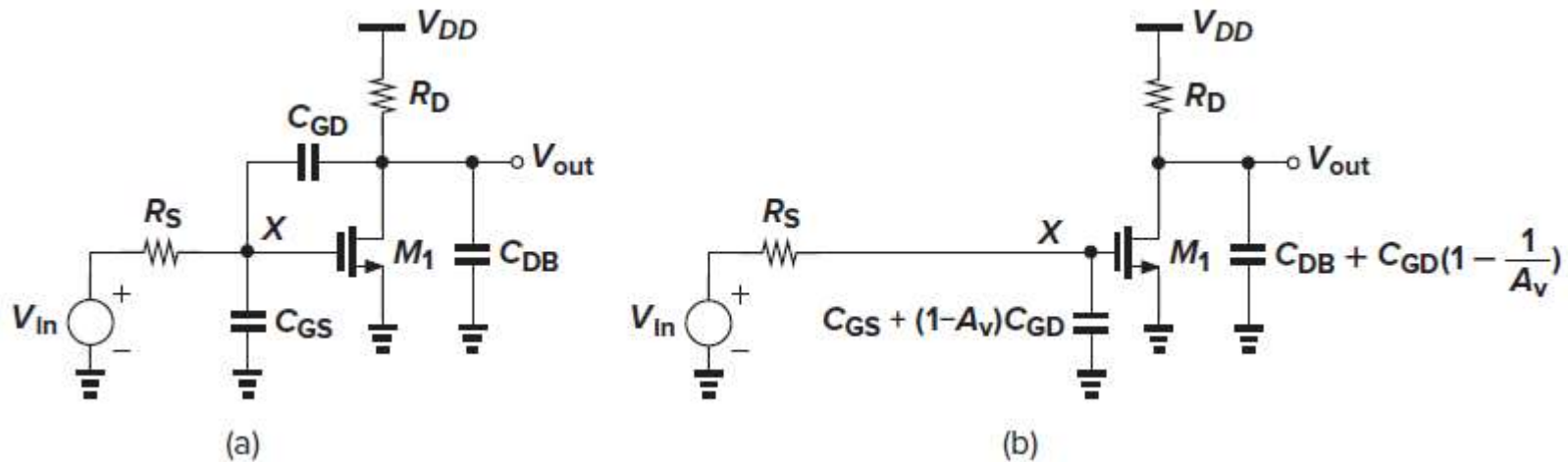


輸入節點：  $C_{GS} + (1 - A_v)C_{GD}$ ，其中  $A_v = -g_m R_D$

$$\omega_{in} = \frac{1}{R_S [C_{GS} + (1 + g_m R_D) C_{GD}]}$$

輸出節點(?)：  $C_{DB} + (1 - A_v^{-1})C_{GD} \sim C_{DB} + C_{GD}$

$$\omega_{out} = \frac{1}{R_D (C_{DB} + C_{GD})}$$

# T. F. of C-S Stage

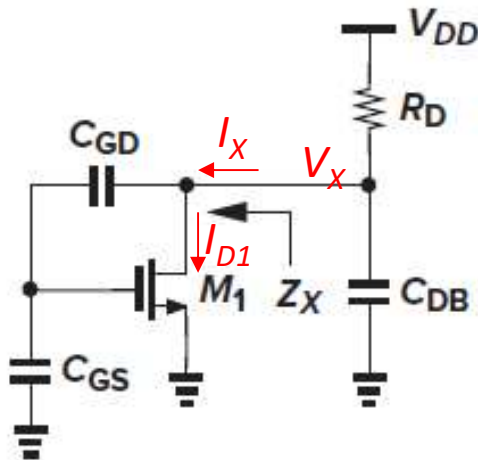

$$V_X = \left( I_X - g_m \frac{C_{GD}}{C_{GS} + C_{GD}} V_X \right) \cdot \frac{1}{sC_{eq}}$$

$I_{D1}$

$$C_{eq} = C_{GD}C_{GS}/(C_{GD} + C_{GS})$$

$$\Rightarrow Z_X = \frac{1}{C_{eq}s} \parallel \left( \frac{C_{GD} + C_{GS}}{C_{GD}} \cdot \frac{1}{g_{m1}} \right)$$

$R_X$

$$\Rightarrow \omega_{out} = \frac{1}{\left[ R_D \parallel \left( \frac{C_{GD} + C_{GS}}{C_{GD}} \cdot \frac{1}{g_{m1}} \right) \right] (C_{eq} + C_{DB})}$$

Thus is different from one shown on the last page


=> Miller effect cannot be applied at the output node

Transfer Function (T. F., ignored zero here)

$$\frac{V_{out}}{V_{in}}(s) = \frac{-g_m R_D}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)}$$

Two poles

# Direct Analysis of T. F.

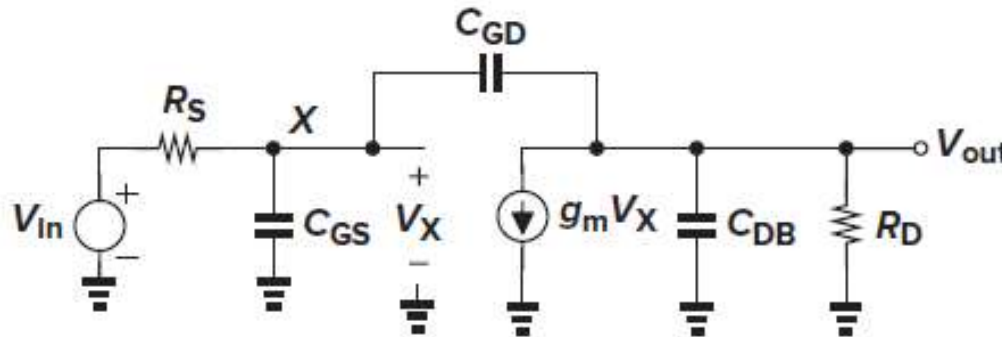

Two poles  
One zero

KCL at node X 
$$\frac{V_X - V_{in}}{R_S} + V_X C_{GS} s + (V_X - V_{out}) C_{GD} s = 0$$

KCL at node Vout 
$$(V_{out} - V_X) C_{GD} s + g_m V_X + V_{out} \left( \frac{1}{R_D} + C_{DB} s \right) = 0$$

$$V_X = - \frac{V_{out} \left( C_{GD} s + \frac{1}{R_D} + C_{DB} s \right)}{g_m - C_{GD} s}$$

$$-V_{out} \frac{[R_S^{-1} + (C_{GS} + C_{GD})s][R_D^{-1} + (C_{GD} + C_{DB})s]}{g_m - C_{GD} s} - V_{out} C_{GD} s = \frac{V_{in}}{R_S}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{GD} s - g_m) R_D}{R_S R_D \xi s^2 + [R_S (1 + g_m R_D) C_{GD} + R_S C_{GS} + R_D (C_{GD} + C_{DB})] s + 1}$$

where  $\xi = C_{GS} C_{GD} + C_{GS} C_{DB} + C_{GD} C_{DB}$

A complex T. F., but...

$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{GD}s - g_m)R_D}{R_S R_D s^2 + [R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$

分子  $\Rightarrow -g_m R_D (1 - s C_{GD} / g_m)$

分母:

If  $R_D(C_{GD} + C_{DB})$  is much smaller,




$$\omega_{p1} = 1/[R_S(C_{GS} + C_{GD}(1 + g_m R_D))]$$

$$\Rightarrow \omega_{p2} = \dots$$

$$\begin{aligned} & \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \\ &= 1 + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + \frac{s^2}{\omega_{p1}\omega_{p2}} \\ & \text{(If } \omega_{p1} \ll \omega_{p2}) \\ & \sim 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1}\omega_{p2}} \end{aligned}$$
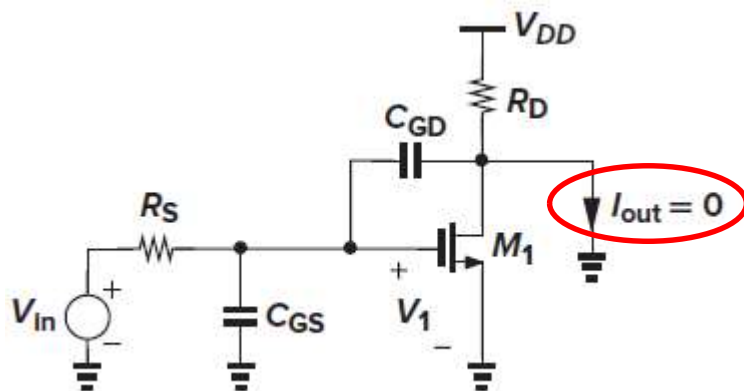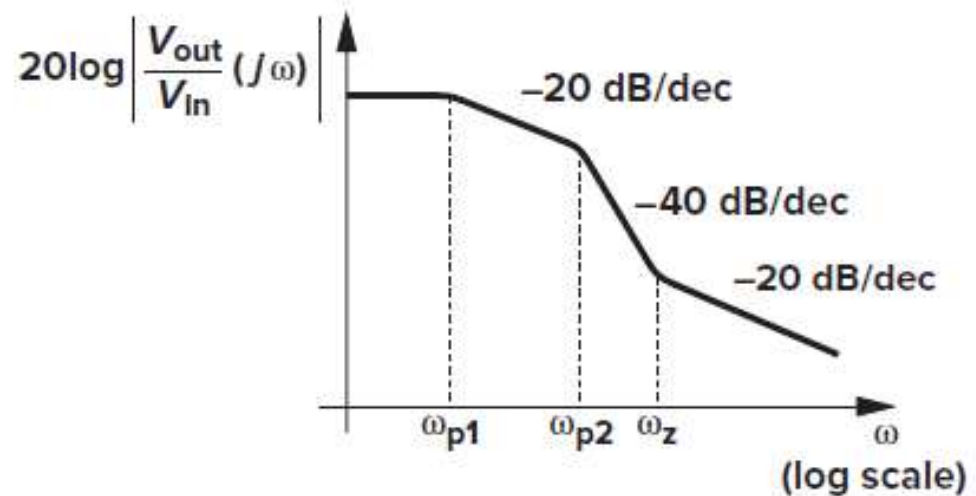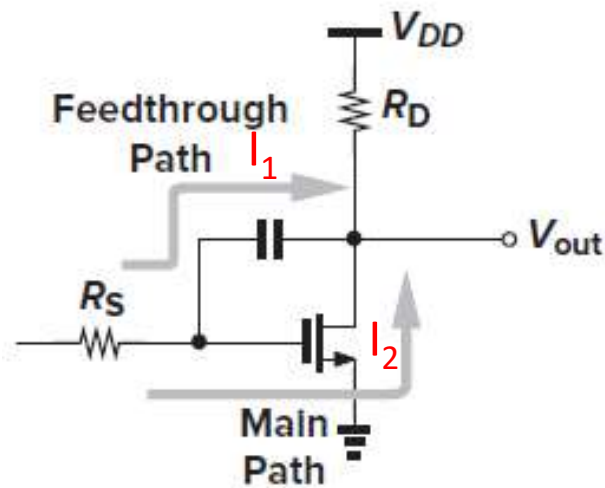
# Zero of C-S Stage

How to determine a zero? **By definition**




$$I_{out} = I_1 + I_2 = 0$$

By definition,

$$sC_{GD}V_1 - g_mV_1 = 0$$

...

# Zin of C-S Stage

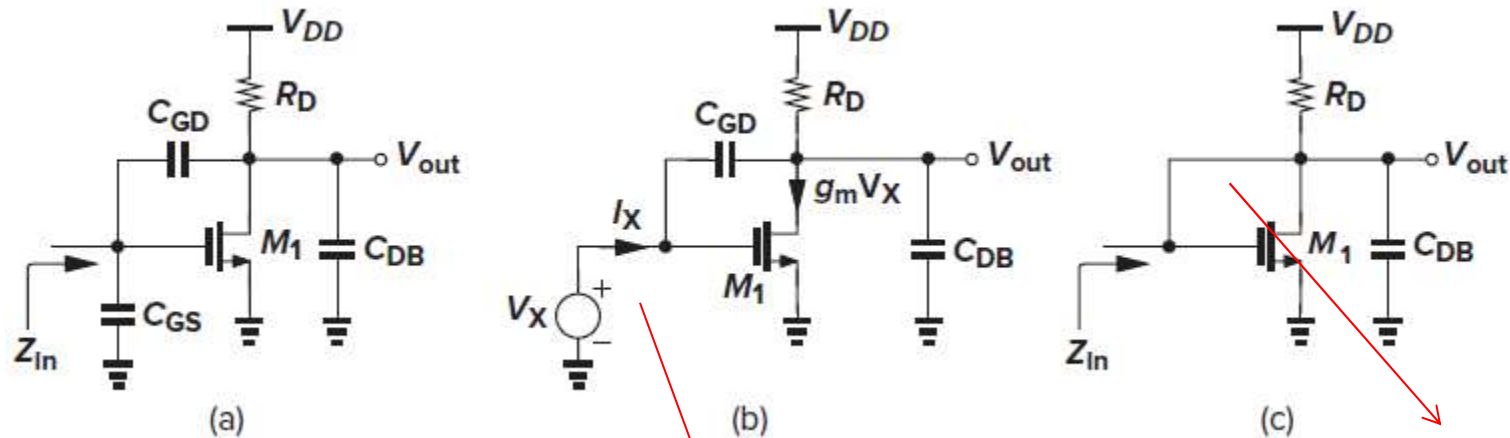

If large  $C_{GD}$  or  
at high-freq

## Miller Effect

$$Z_{in} = \frac{1}{[C_{GS} + (1 + g_m R_D)C_{GD}]s}$$

A simplified watch, but be careful  
the assumption is true

## Compact Analysis (at low-freq.)


$$(I_X - g_m V_X) \frac{R_D}{1 + R_D C_{DB} s} + \frac{I_X}{C_{GD} s} = V_X$$

$$Z_X = \frac{V_X}{I_X} = \frac{1 + \cancel{R_D(C_{GD} + C_{DB})s}}{C_{GD}s(1 + g_m R_D + \cancel{R_D C_{DB}s})}$$

$$Z_{in} = 1/sC_{GS} // Z_X$$



# Source Follower

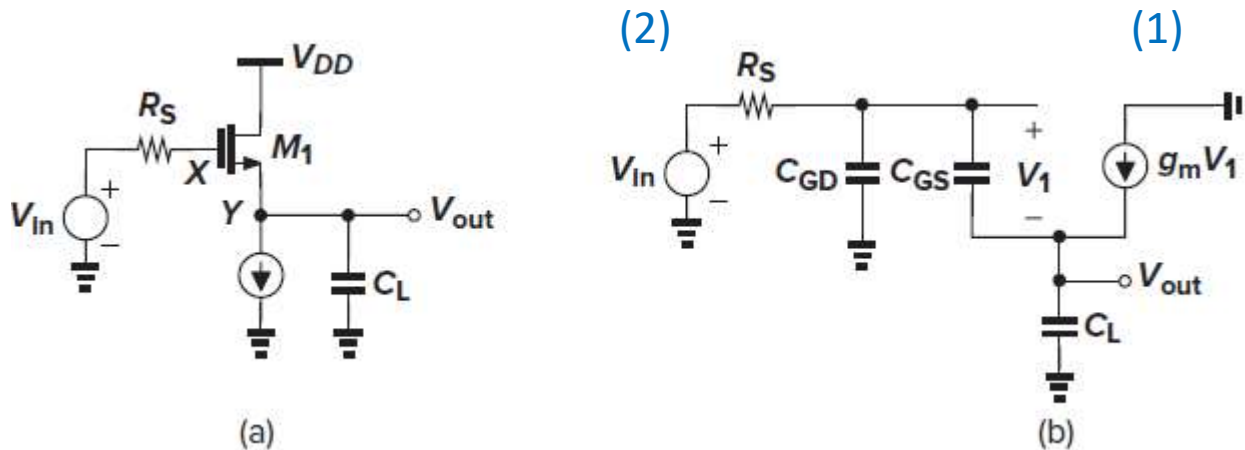

$$\begin{aligned} & \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \\ &= 1 + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + \frac{s^2}{\omega_{p1}\omega_{p2}} \\ & \text{(If } \omega_{p1} \ll \omega_{p2}) \\ & \sim 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1}\omega_{p2}} \end{aligned}$$

$$(1) V_1 C_{GS} s + g_m V_1 = V_{out} C_L s$$

$$\Rightarrow V_1 = \frac{C_L s}{g_m + C_{GS} s} V_{out}$$

$$(2) V_{in} = R_S [V_1 C_{GS} s + (V_1 + V_{out}) C_{GD} s] + V_1 + V_{out}$$

$$\begin{aligned} \omega_{p1} &\approx \frac{g_m}{g_m R_S C_{GD} + C_L + C_{GS}} \\ &= \frac{1}{R_S C_{GD} + \frac{C_L + C_{GS}}{g_m}} \end{aligned}$$


If  $\omega_{p1} \ll \omega_{p2}$

$$\frac{V_{out}}{V_{in}}(s) = \frac{g_m + C_{GS} s}{R_S (C_{GS} C_L + C_{GS} C_{GD} + C_{GD} C_L) s^2 + (g_m R_S C_{GD} + C_L + C_{GS}) s + g_m}$$

=> What do you get from this equation?
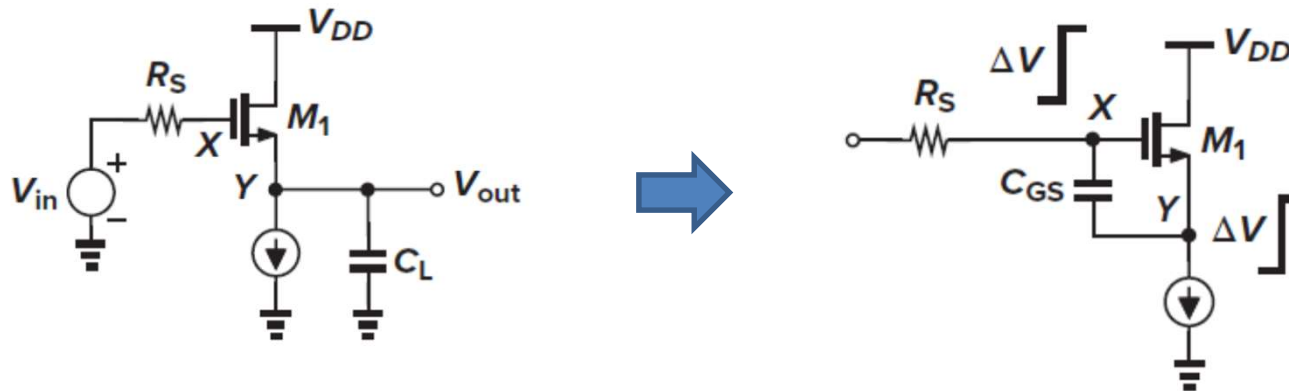
# Example 6.11

Examine the source follower transfer function if  $C_L = 0$ .




$$\frac{V_{out}}{V_{in}}(s) = \frac{g_m + C_{GS}s}{R_S(C_{GS}C_L + C_{GS}C_{GD} + C_{GD}C_L)s^2 + (g_m R_S C_{GD} + C_L + C_{GS})s + g_m}$$



$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{g_m + C_{GS}s}{R_S C_{GS} C_{GD} s^2 + (g_m R_S C_{GD} + C_{GS})s + g_m} \\ &= \frac{g_m + C_{GS}s}{(1 + R_S C_{GD}s)(g_m + C_{GS}s)} \\ &= \frac{1}{1 + R_S C_{GD}s} \end{aligned}$$

# Zin of Source Follower

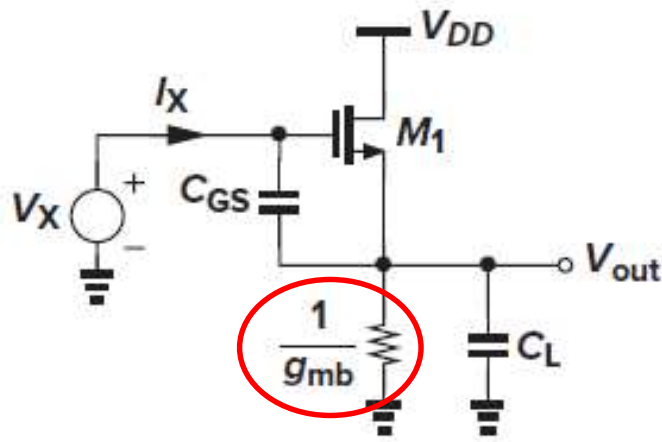

$$V_X = \frac{I_X}{C_{GSS}} + \left( I_X + \frac{g_m I_X}{C_{GSS}} \right) \left( \frac{1}{g_{mb}} \parallel \frac{1}{C_L s} \right)$$


$$Z_{in} = \frac{1}{C_{GSS}} + \left( 1 + \frac{g_m}{C_{GSS}} \right) \frac{1}{g_{mb} + C_L s}$$

$$Z_{in} = \frac{1}{s C_{GS}} \left( 1 + \frac{g_m + s C_{GS}}{g_{mb} + s C_L} \right)$$

low frequencies,  $g_{mb} \gg |C_L s|$  and  $Z_{in} \approx \frac{1}{C_{GSS}} \left( 1 + \frac{g_m}{g_{mb}} \right) + \frac{1}{g_{mb}}$

At high frequencies,  $g_{mb} \ll |C_L s|$  and  $Z_{in} \approx \frac{1}{C_{GSS}} + \frac{1}{C_L s} + \frac{g_m}{C_{GS} C_L s^2}$

# Negative Resistance

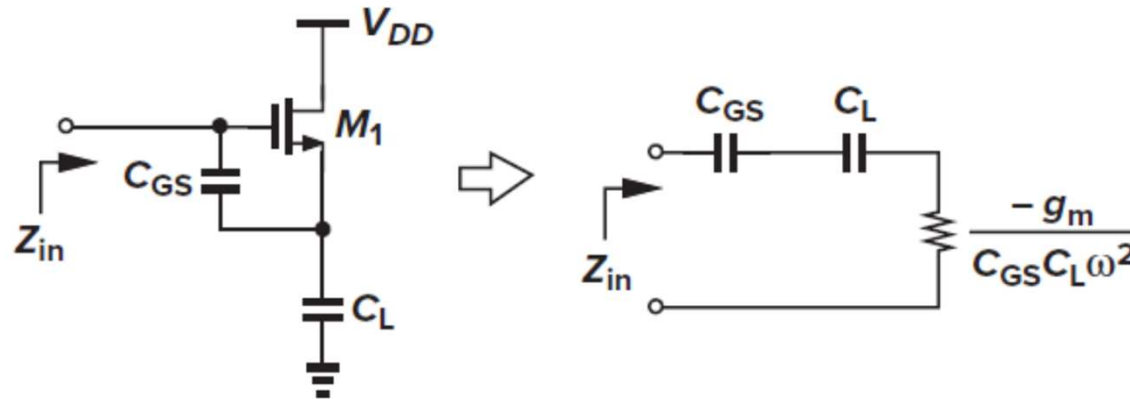




$$Z_{in} \approx \frac{1}{C_{GS}s} + \frac{1}{C_Ls} + \frac{g_m}{C_{GS}C_Ls^2}$$

$C_L$  and  $C_{GS}$  are  
series-connected

$$s = j\omega$$

$$\frac{-g_m}{C_{GS}C_L\omega^2}$$

# Zout of Source Follower

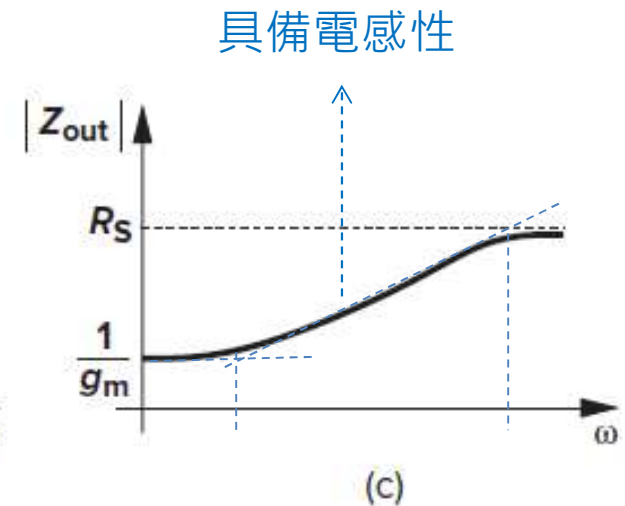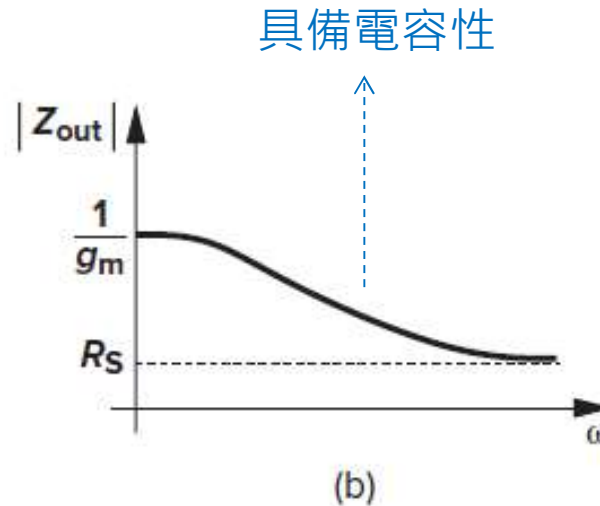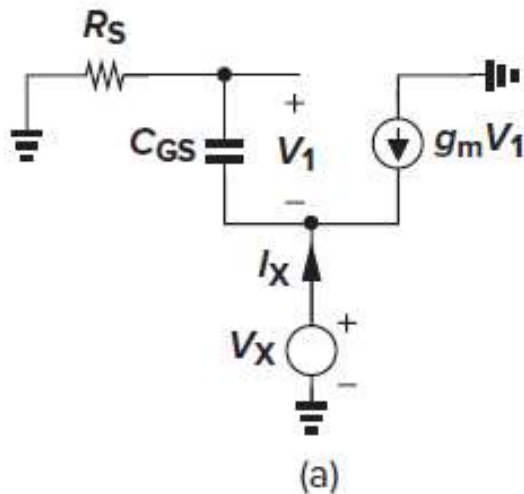

Q: Which one is right? It depends!!

- $Z_{out}(\text{DC}) = 1/g_m$
- $Z_{out}(\text{HF}) = R_S$


$$\begin{aligned}
 Z_{out} &= \frac{V_X}{I_X} \\
 &= \frac{R_S C_{GS} s + 1}{g_m + C_{GS} s}
 \end{aligned}$$



Pole is  $g_m/C_{GS}$

Zero is  $1/R_S C_{GS}$

# Zout of Source Follower

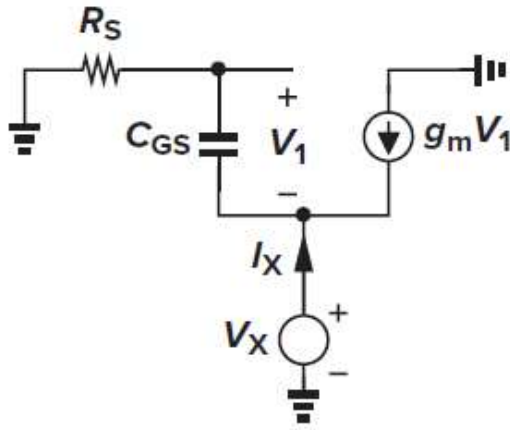


$$Z_{out} = \frac{V_X}{I_X} = \frac{R_S C_{GS} s + 1}{g_m + C_{GS} s}$$



$$Z_{out} - \frac{1}{g_m} = \frac{s C_{GS} \left( R_S - \frac{1}{g_m} \right)}{g_m + C_{GS} s}$$

$$\frac{1}{Z_{out} - \frac{1}{g_m}} = \frac{1}{R_S - \frac{1}{g_m}} + \frac{1}{s \frac{C_{GS}}{g_m} \left( R_S - \frac{1}{g_m} \right)}$$

電感性之分析

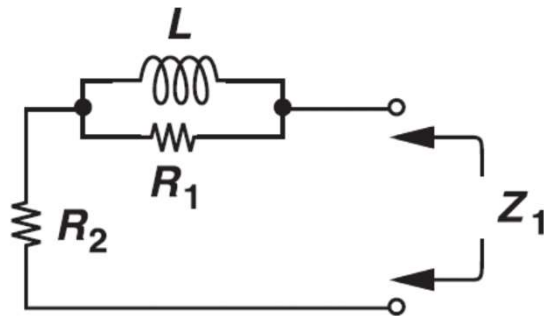

$$Z_{out} = Z_1 = sL // R_1 + R_2$$

$$R_2 = 1/g_m$$


$$R_1 = R_S - 1/g_m$$



$$L = \frac{C_{GS}}{g_m} \left( R_S - \frac{1}{g_m} \right)$$
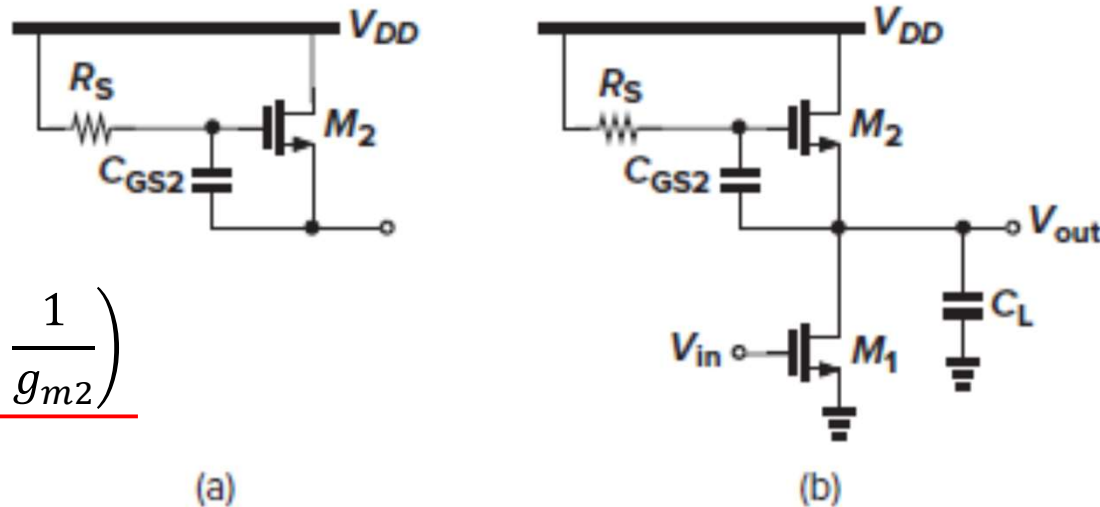
# Example 6.14

Can we construct a (two-terminal) inductor from a source follower?



$$L = \frac{C_{GS2}}{g_{m2}} \left( R_S - \frac{1}{g_{m2}} \right)$$

$$R_1 = R_S - \frac{1}{g_{m2}}$$

$$R_2 = \frac{1}{g_{m2}}$$

Yes, we can. Called an “active inductor,” such a structure is shown in Fig. 6.30(a), providing an inductance of  $(C_{GS2}/g_{m2})(R_S - 1/g_{m2})$ . But the inductor is not ideal because it also incurs a parallel resistance equal to  $R_1 = R_S = 1/g_{m2}$  and a series resistance equal to  $1/g_{m2}$ . Figure 6.30(b) depicts an application of active inductors: the inductance can partially cancel the load capacitance,  $C_L$ , at high frequencies, thus extending the bandwidth. However, the voltage headroom consumed by  $M_2$  ( $= V_{GS2}$ ) limits the gain. Also,  $C_{GD2}$ , which has been neglected in our analysis, limits the bandwidth enhancement.


# Common-Gate Stage

$$C_D = C_L + C_{GD} + C_{DB}$$

$$C_S = C_{GS} + C_{SB}$$

C-G stage, 
$$Z_{in} \approx \frac{Z_L + r_o}{1 + (g_m + g_{mb})r_o}$$
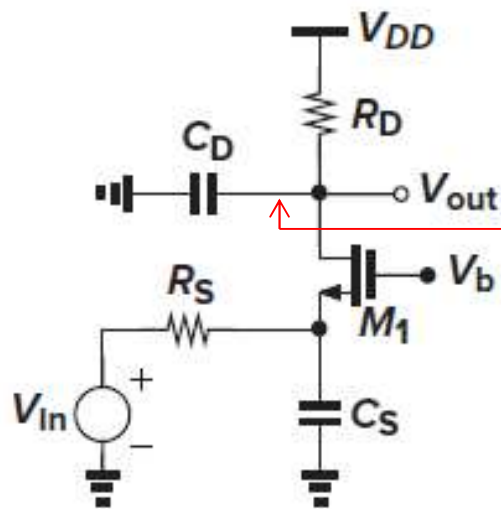
$$Z_{in} \approx \frac{Z_L}{(g_m + g_{mb})r_o} + \frac{1}{g_m + g_{mb}}$$



$$Z_L = R_D \parallel [1/(C_D s)]$$



the input and output nodes are “isolated” if channel-length modulation is neglected.

$$\frac{V_{out}}{V_{in}}(s) = \frac{(g_m + g_{mb})R_D}{1 + (g_m + g_{mb})R_S} \frac{1}{\left(1 + \frac{C_S}{g_m + g_{mb} + R_S^{-1}}s\right) \underline{(1 + R_D C_D s)}}$$


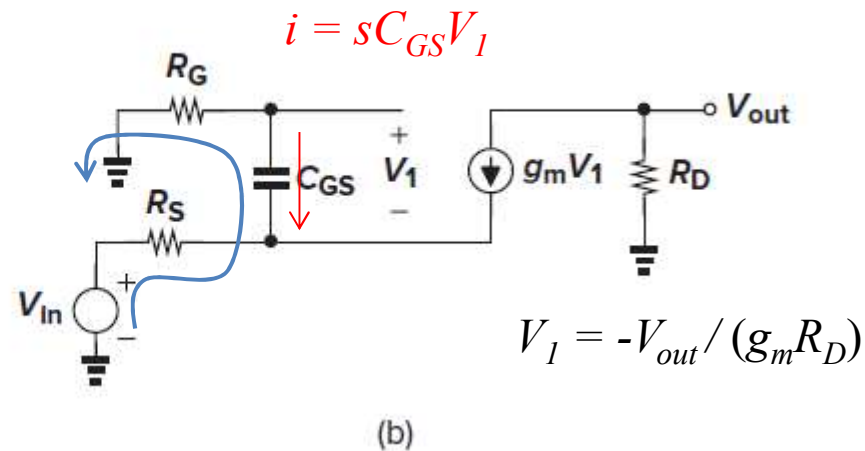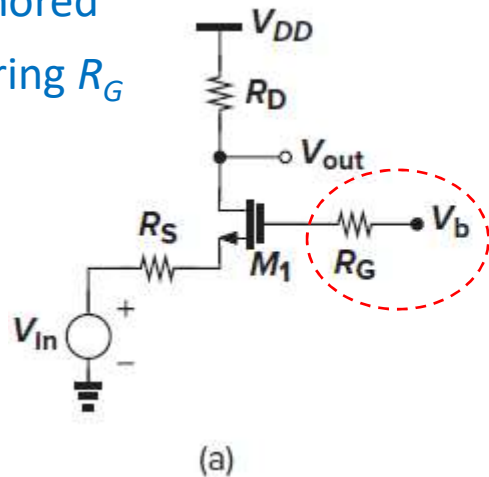
# T.-F. of Common-Gate ( $C_{GS}$ only)

- $g_{mb}$  is ignored
- Considering  $R_G$



$$V_{in} - (C_{GS} + g_m) \frac{V_{out}}{g_m R_D} R_S - \frac{V_{out}}{g_m R_D} - C_{GS} s \frac{V_{out}}{g_m R_D} R_G = 0$$


It follows that

$$\frac{V_{out}}{V_{in}} = \frac{g_m R_D}{(R_G + R_S) C_{GS} s + 1 + g_m R_S}$$

yielding a pole at

$$\omega_p = \frac{1 + g_m R_S}{(R_G + R_S) C_{GS}} \quad (\text{a higher frequency})$$

# Q: Why mention $R_G$ ?

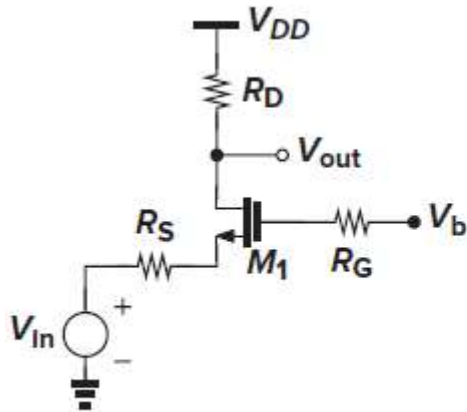


$C_{GS}$  only

$$\frac{V_{out}}{V_{in}} = \frac{g_m R_D}{(R_G + R_S)C_{GS}s + 1 + g_m R_S}$$

$$\omega_p = \frac{1 + g_m R_S}{(R_G + R_S)C_{GS}}$$

$R_G$  directly adds to  $R_S$  in this case, lowering the pole magnitude

# Cascode Stage

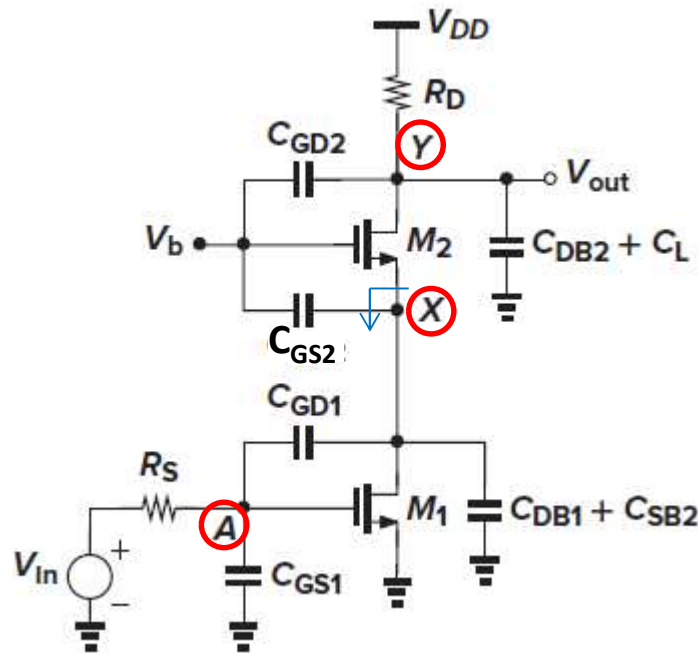

$$\omega_{p,A} = \frac{1}{R_S \left[ C_{GS1} + \left( 1 + \frac{g_{m1}}{g_{m2} + g_{mb2}} \right) C_{GD1} \right]}$$

$$\omega_{p,X} = \frac{g_{m2} + g_{mb2}}{2C_{GD1} + C_{DB1} + C_{SB2} + C_{GS2}} \rightarrow C_X$$

$$\omega_{p,Y} = \frac{1}{R_D(C_{DB2} + \underline{C_L} + C_{GD2})}$$

Why "cascode" ?


⇒  $\omega_{p,A}$  is higher

⇒ What is the dominant pole?

$$Z_{out} = (1 + g_{m2}r_{O2})Z_X + r_{O2}$$

$$Z_X = r_{O1} || (\underline{C_X s})^{-1}$$

# Example 6.16

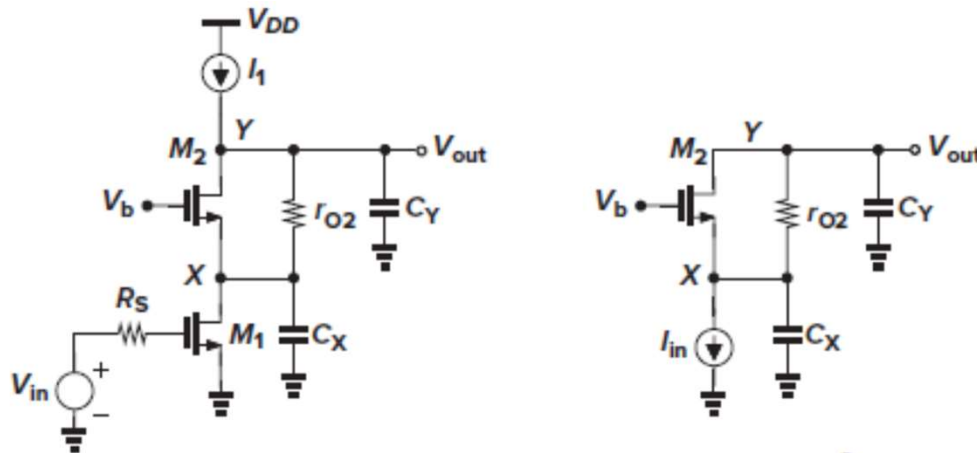

$$-r_{O2} \left[ (V_{out}C_Ys + I_{in}) \frac{g_{m2}}{C_Xs} + V_{out}C_Ys \right] - (V_{out}C_Ys + I_{in}) \frac{1}{C_Xs} = V_{out}$$

That is

$$\frac{V_{out}}{I_{in}} = -\frac{g_{m2}r_{O2} + 1}{C_Xs} \cdot \frac{1}{1 + (1 + g_{m2}r_{O2}) \frac{C_Y}{C_X} + C_Yr_{O2}s}$$


which, for  $g_{m2}r_{O2} \gg 1$  and  $g_{m2}r_{O2}C_Y/C_X \gg 1$  (i.e.,  $C_Y > C_X$ ), reduces to

$$\frac{V_{out}}{I_{in}} \approx -\frac{g_{m2}}{C_Xs} \frac{1}{\frac{C_Y}{C_X}g_{m2} + C_Ys}$$

and hence

$$\frac{V_{out}}{V_{in}} = -\frac{g_{m1}g_{m2}}{C_YC_Xs} \frac{1}{g_{m2}/C_X + s}$$

# Differential Pair: CMRR

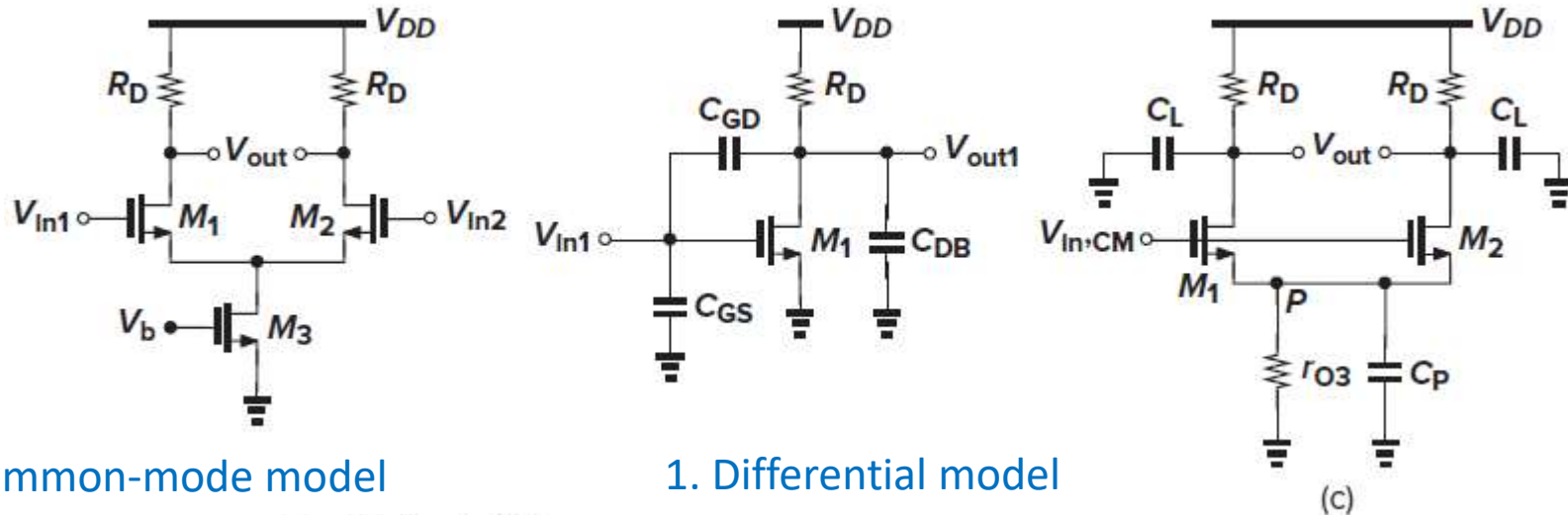

## 2. Common-mode model

$$A_{v,CM} = - \frac{\Delta g_m \left[ R_D \parallel \left( \frac{1}{C_{LS}} \right) \right]}{(g_{m1} + g_{m2}) \left[ r_{O3} \parallel \left( \frac{1}{C_{PS}} \right) \right] + 1}$$


## 1. Differential model

$$A_{DM} = -g_m (R_D \parallel Z_L)$$

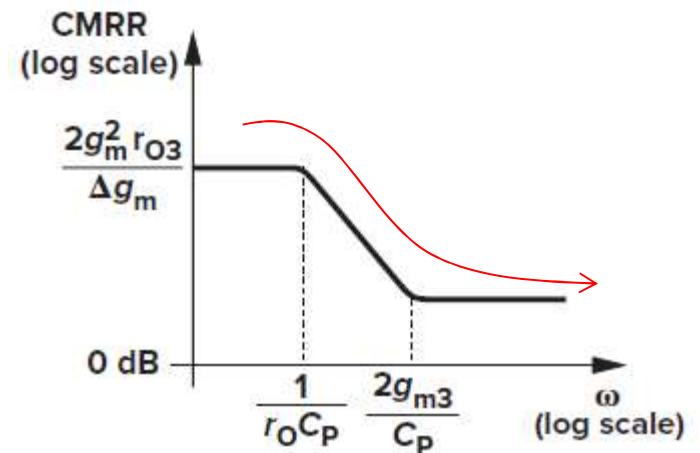
## 3. CMRR calculation:

$$\begin{aligned} \text{CMRR} &\approx \frac{g_m}{\Delta g_m} \left[ 1 + 2g_m \left( r_{O3} \parallel \frac{1}{C_{PS}} \right) \right] \\ &\approx \frac{g_m}{\Delta g_m} \frac{r_{O3} C_{PS} + 1 + 2g_m r_{O3}}{r_{O3} C_{PS} + 1} \end{aligned}$$

$$\text{where } g_m = (g_{m1} + g_{m2})/2$$





# Differential Pair: PSRR

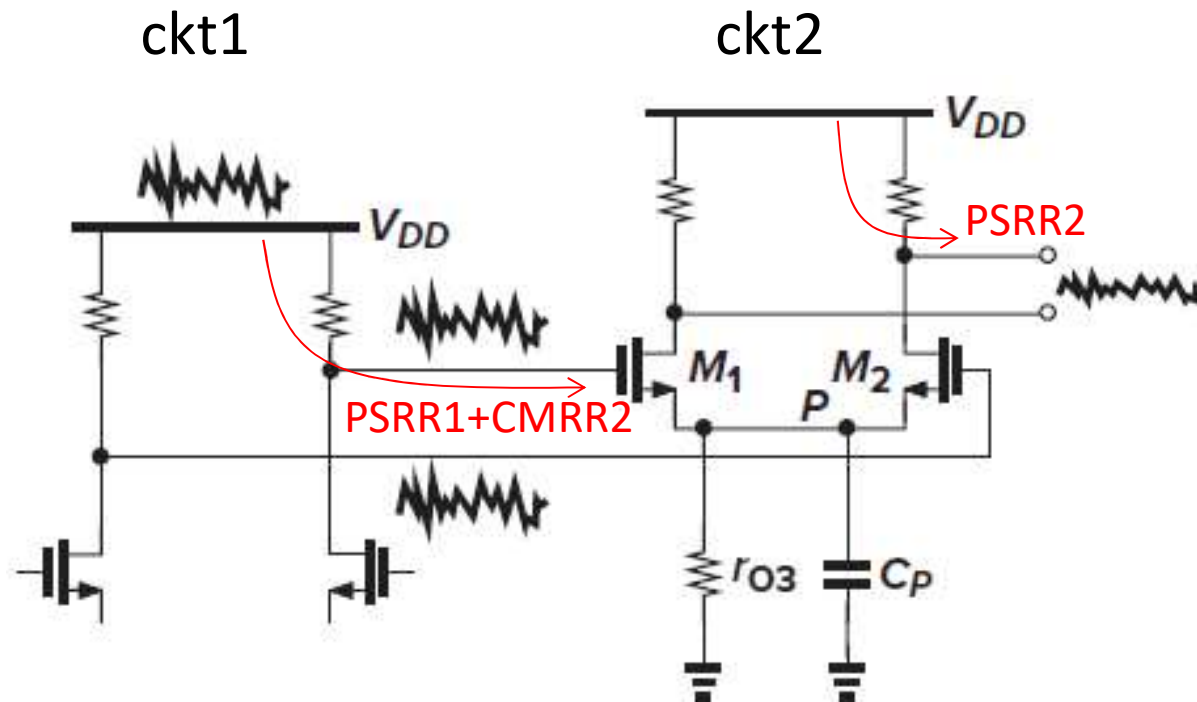

Two kinds of supply errors for ckt1 and ckt2

- (1) **PSRR1 + CMRR2** (Supply noise to input common-mode ( $V_{i,CM}$ ); then  $V_{i,CM}$  affects diff. output by  $A_{CM-DM}$ )
- (2) **PSRR2** (Supply noise directly affects the diff. output)

# Differential Pair with high-Z loads

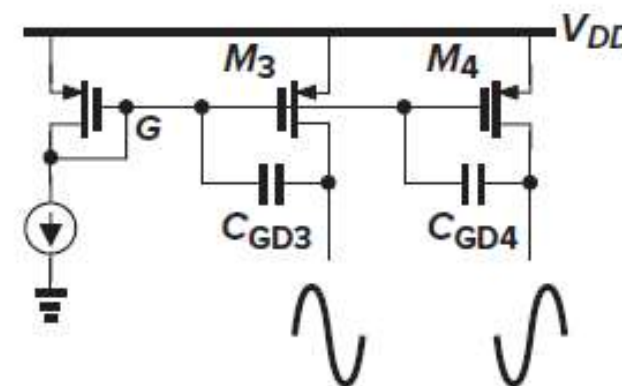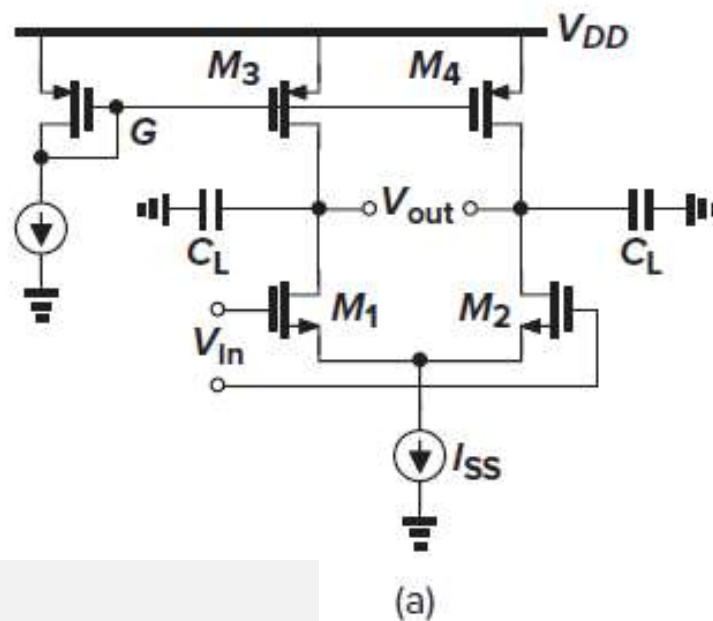


To find all poles and zeros, check the signal path

Hint:

This fully-differential amplifier has something to be concerned, the output common-mode voltage ( $V_{ocm}$ )



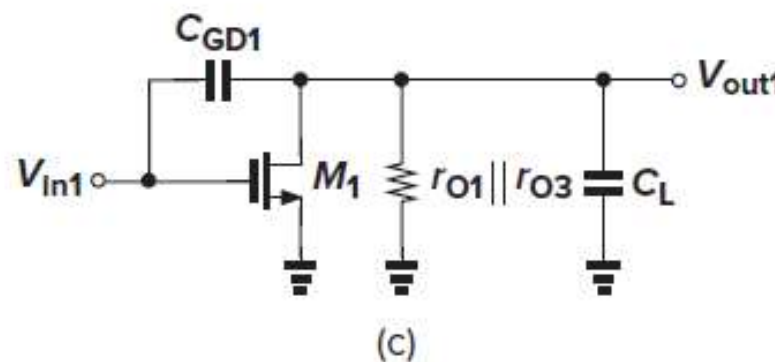
In fact, we need a CMFB (common-mode feedback) loop to maintain this (we discuss this in later lectures)!!



A simple **single-pole** circuit



# Differential Pair with active loads

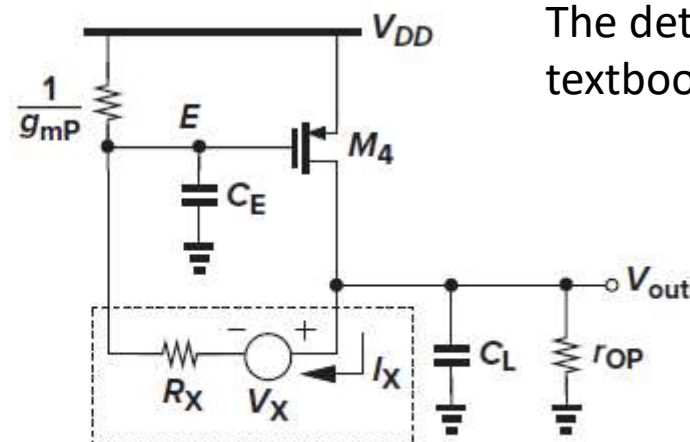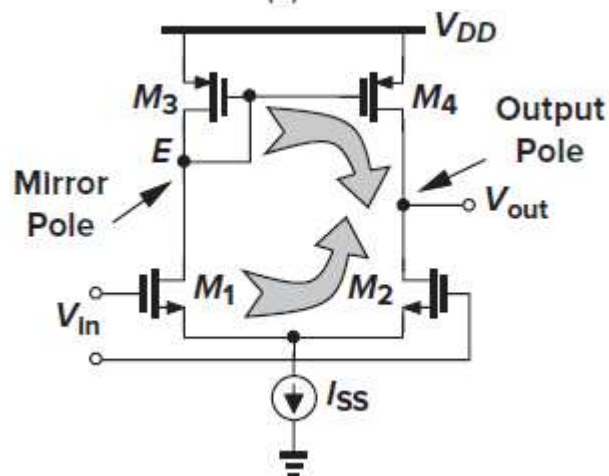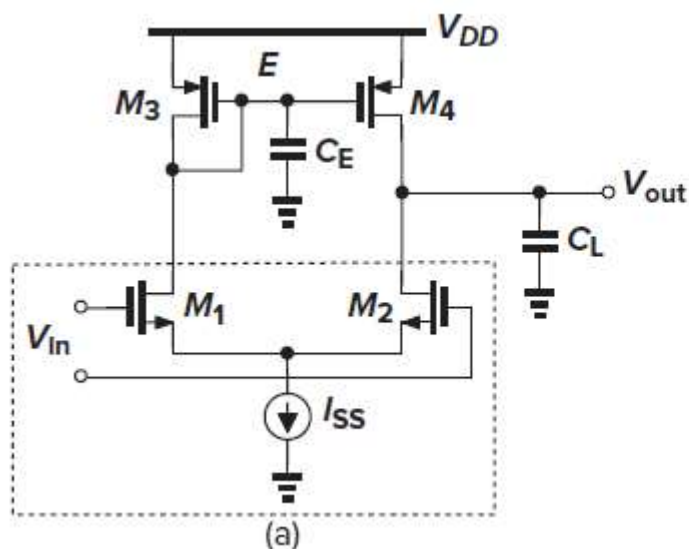

The detail is in the textbook, page 202

$$V_X = g_{mN} r_{ON} V_{in} \quad R_X = 2r_{ON}$$

we have assumed that  $1/g_{mP} \ll r_{OP}$

$$I_X = -g_{mN} V_{in} / 2$$


$$V_E = (V_{out} - V_X) \frac{1}{\frac{C_E s + g_{mP}}{1} + R_X}$$

$$V_{out} = (-g_{mp} V_E - I_X)(r_{op} || 1/sC_L) = \dots$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{mN} r_{ON} (2g_{mP} + C_E s) r_{OP}}{2r_{OP} r_{ON} C_E C_L s^2 + [(2r_{ON} + r_{OP}) C_E + r_{OP} (1 + 2g_{mP} r_{ON}) C_L] s + 2g_{mP} (r_{ON} + r_{OP})}$$



# Differential Pair with active loads

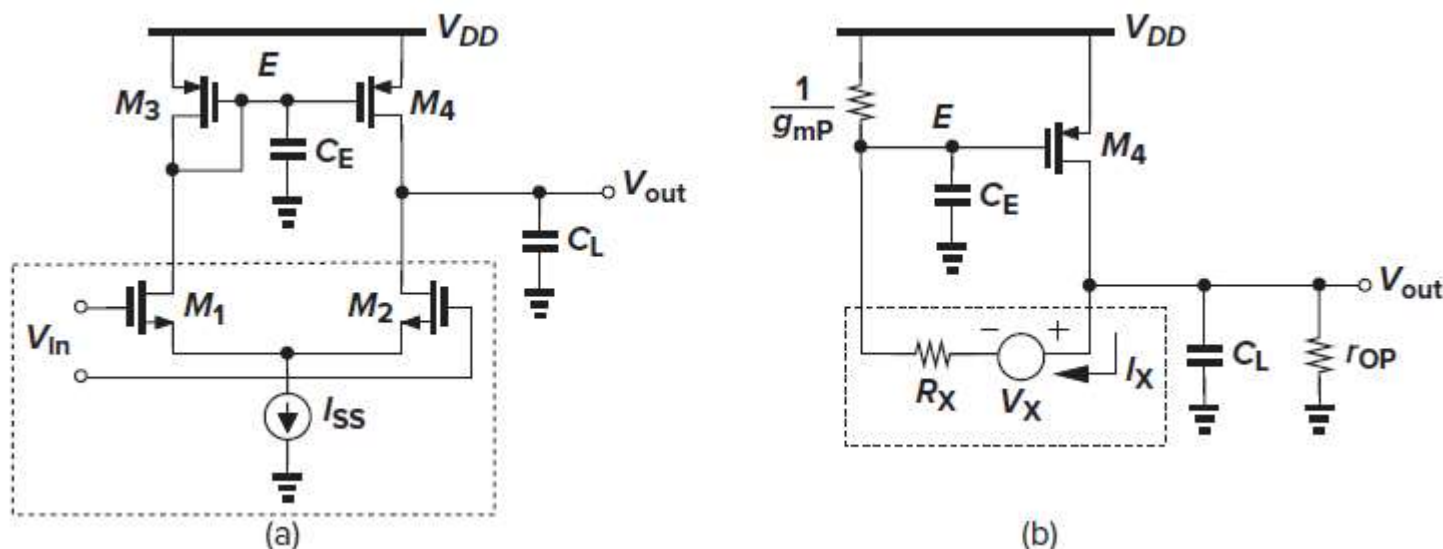



$$\frac{V_{out}}{V_{in}} = \frac{g_{mN}r_{ON}(2g_{mP} + C_E s)r_{OP}}{2r_{OP}r_{ON}C_EC_Ls^2 + [(2r_{ON} + r_{OP})C_E + r_{OP}(1 + 2g_{mP}r_{ON})C_L]s + 2g_{mP}(r_{ON} + r_{OP})}$$

$$\frac{V_{out}}{V_{in}} = \frac{2g_{mP}g_{mN}r_{OP}r_{ON}}{2g_{mP}(r_{OP} + r_{ON})} \frac{1 + s/(2g_{mP}/C_E)}{1 + as + bs^2}$$

$$\frac{V_{out}}{V_{in}} = g_{mN}(r_{OP}||r_{ON}) \frac{1 + s/\omega_z}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

$$\begin{aligned} & \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \\ &= 1 + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + \frac{s^2}{\omega_{p1}\omega_{p2}} \\ & \text{(If } \omega_{p1} \ll \omega_{p2}) \\ & \sim 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1}\omega_{p2}} \end{aligned}$$

# Differential Pair with active loads

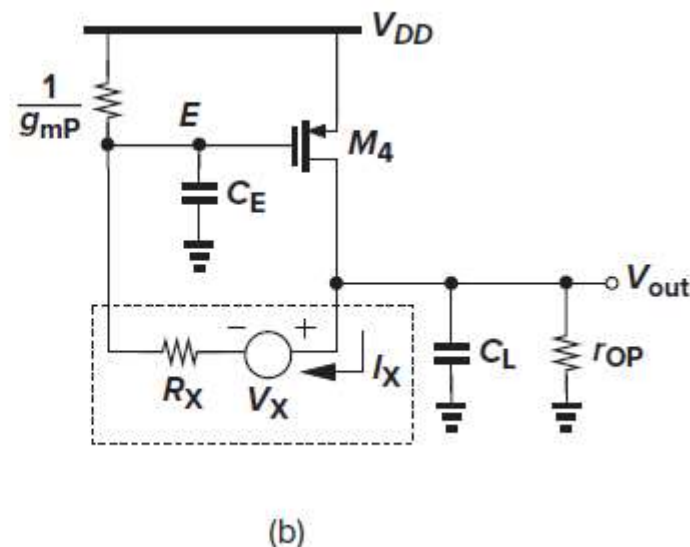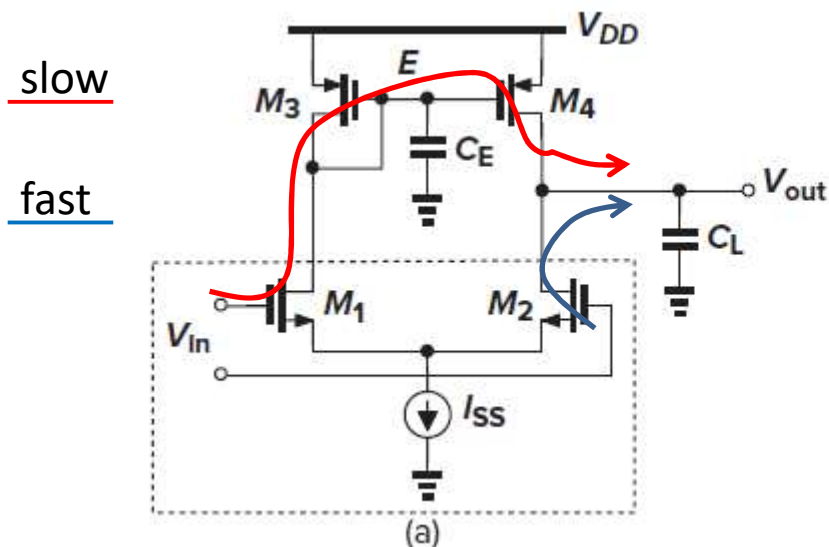

Another circuit analysis method:

$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + s/\omega_{p1}} \left( \frac{1}{1 + s/\omega_{p2}} + 1 \right)$$

$$= \frac{A_0(2 + s/\omega_{p2})}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

$$A_0 = \frac{g_{mN}(r_{OP} \parallel r_{ON})}{2}$$



$$\omega_{p1} \approx \frac{2g_{mP}(r_{ON} + r_{OP})}{(2r_{ON} + r_{OP})C_E + r_{OP}(1 + 2g_{mP}r_{ON})C_L}$$

$$\approx \frac{1}{(r_{ON} \parallel r_{OP})C_L}$$

$$\omega_{p2} \approx \frac{g_{mP}}{C_E} \quad \omega_z = \frac{2g_{mp}}{C_E} = 2\omega_{p2}$$

# Gain-Bandwidth Trade-Offs

## One-Pole Circuits

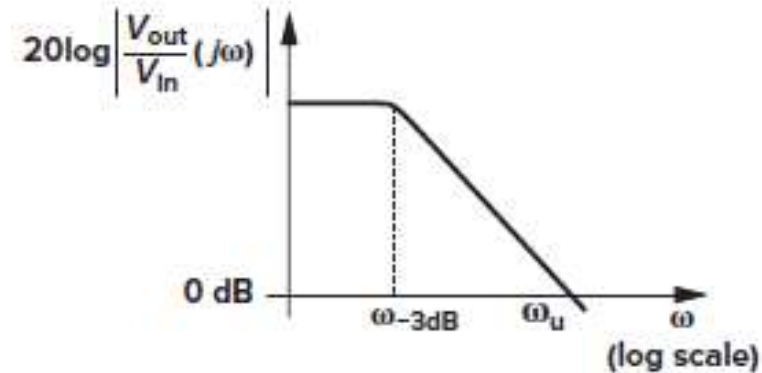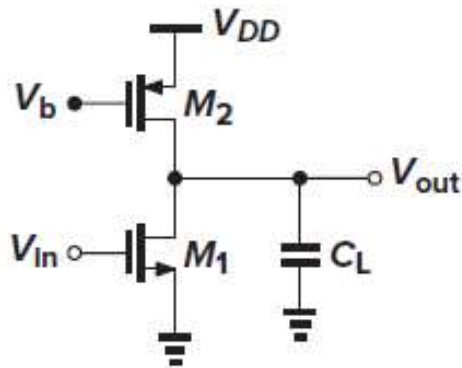


$$\begin{aligned} \text{GBW} &= A_0 \omega_p \\ &= g_{m1} (r_{O1} \parallel r_{O2}) \frac{1}{2\pi (r_{O1} \parallel r_{O2}) C_L} \\ &= \frac{g_{m1}}{2\pi C_L} \end{aligned}$$

$$\frac{A_0}{\sqrt{1 + \left(\frac{\omega_u}{\omega_p}\right)^2}} = 1$$

$$\begin{aligned} \text{if } A_0^2 \gg 1 \quad \omega_u &= \sqrt{A_0^2 - 1} \omega_p \\ &\approx A_0 \omega_p \end{aligned}$$

# Gain-Bandwidth Trade-Offs


## Multi-Pole Circuits

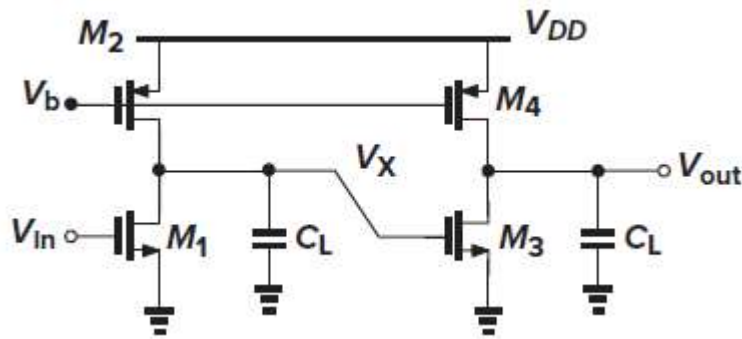

$$\frac{V_{out}}{V_{in}} = \frac{A_0^2}{\left(1 + \frac{s}{\omega_p}\right)^2}$$

$$\frac{A_0^2}{1 + \frac{\omega_{-3dB}^2}{\omega_p^2}} = \frac{A_0^2}{\sqrt{2}}$$
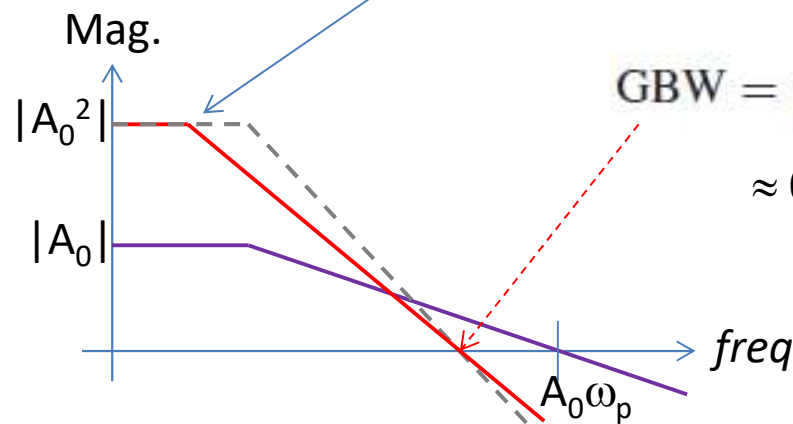
$$\omega_{-3dB} = \sqrt{\sqrt{2} - 1} \omega_p \approx 0.64 \omega_p$$



$$GBW = \sqrt{\sqrt{2} - 1} A_0 \omega_p \approx 0.64 A_0 \omega_p$$

$N$  single pole circuits series-connected,  $\omega_{-3dB} = \sqrt{\sqrt[N]{2} - 1} \omega_p$