

考試時間：107 年 11 月 08 日 下午 13:20 至 15:10 (雙面試題，不可使用工程計算機)

1. (25%) Consider an OP-AMP circuit in Fig. 1. (a) Please determine the relation between the output voltage and the input voltages. (10%) (b) If $1V \leq V_1 \leq 2V$ and $2V \leq V_2 \leq 3V$, please determine the range of V_o . (5%) (c) Whether this circuit will produce the full range of V_o given that the dc supplies are $\pm 10V$. If the answer is no, what is the practical output range of V_o . (10%)

- (a)
 $8V_1 - 4V_2$
(b)
 $-4V \leq V_o \leq 8V$
(c)
 $-2V \leq V_o \leq 2V$

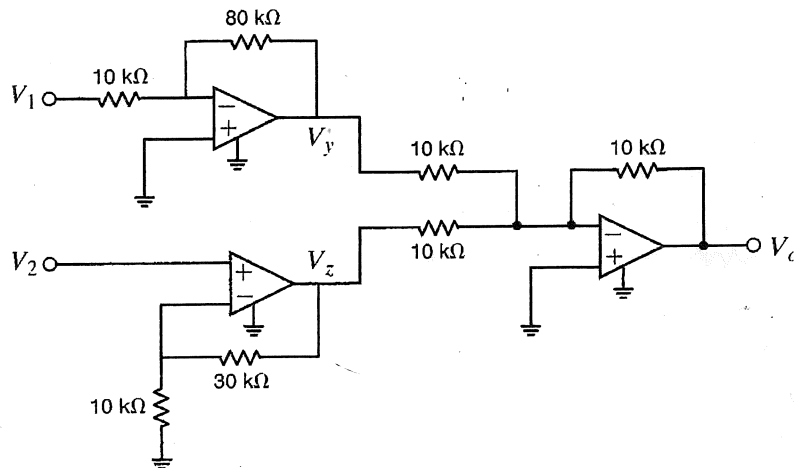


Fig. 1.

2. (15%) Please find R_L for maximum power transfer and the maximum power transferred to this load in the following circuit.

9075w

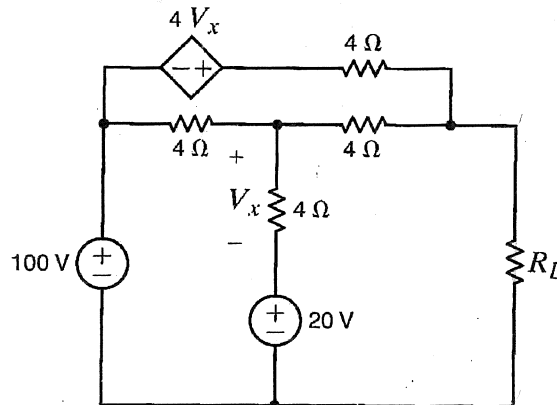


Fig. 2.

3. (15%) Please calculate I_o in Fig. 3.

-48mA

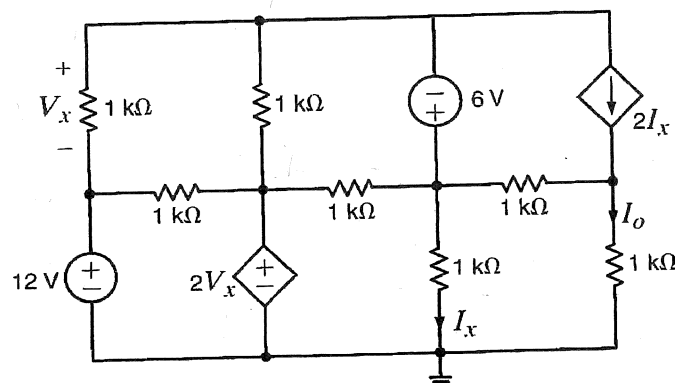


Fig. 3.

4. (15%) Please calculate V_o in Fig. 4 by using Norton's theorem.

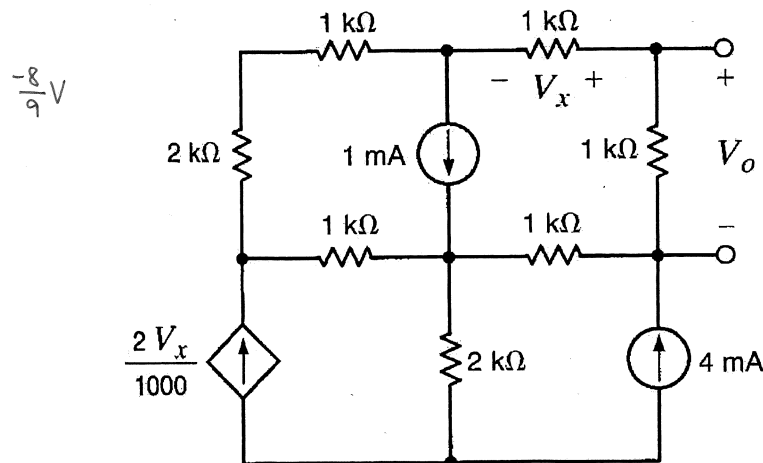


Fig. 4.

5. (15%) Please find the total energy stored in the circuit as shown in Fig. 5.

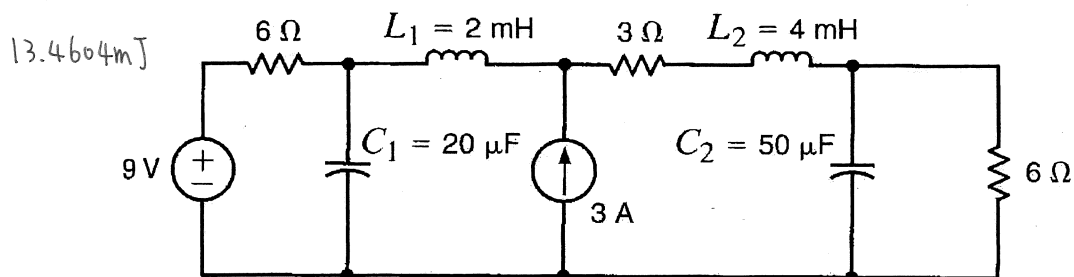


Fig. 5.

6. (15%) Please derive the expression of the output voltage v_o in Fig. 6. (a) What is the output voltage expressed by the input sources v_{s1} and v_{s2} ? (10%) (b) If the sources are given as $v_{s1} = 80 \cos 377t$ and $v_{s2} = 40 \cos 377t$, what is the value of the output voltage? (5%)

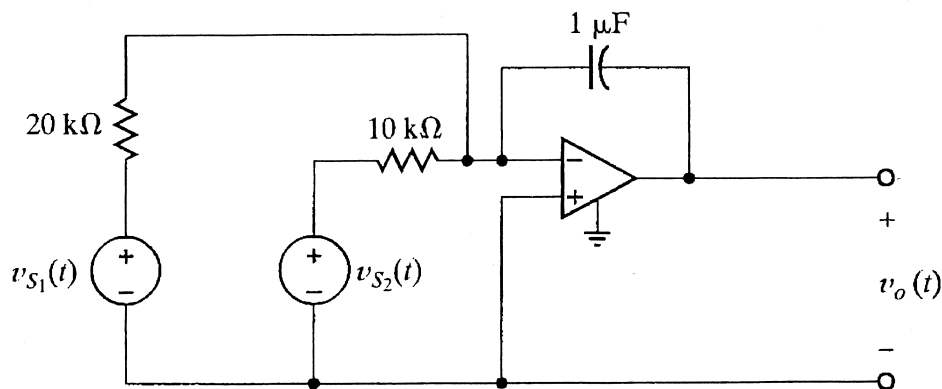


Fig. 6.

(a)

$$V_o = -50 \int (V_{s1} + 2V_{s2}) dt$$

(b)

$$V_o = -21.2 \sin 377t \text{ V}$$