

台灣科技大學一百零七學年度下學期平時考 (二)

科目名稱：電路學(二) 開課系所：電子系 ET2104301 地點：國際大樓 IB308

考試時間：108 年 6 月 6 日 下午 13:20 至 15:10 (不可使用工程計算機)

1. (5%) Please find the inverse Laplace transform of the following function:

$$F(s) = e^{-3s} \frac{(95s + 100)}{s(s^2 + 2s + 2)}$$

2. (5%) Please find the Laplace transform of the following function:

$$f(t) = [2e^{-t} \cos 2t + 5e^{-t} \sin 2t]q(t)$$

3. (25%) A second-order circuit in Fig. 1 is assumed to be in a steady-state condition prior to switch at  $t = 0$ . Please use the Laplace transforms to calculate the voltage  $v_o(t)$  for  $t > 0$ .

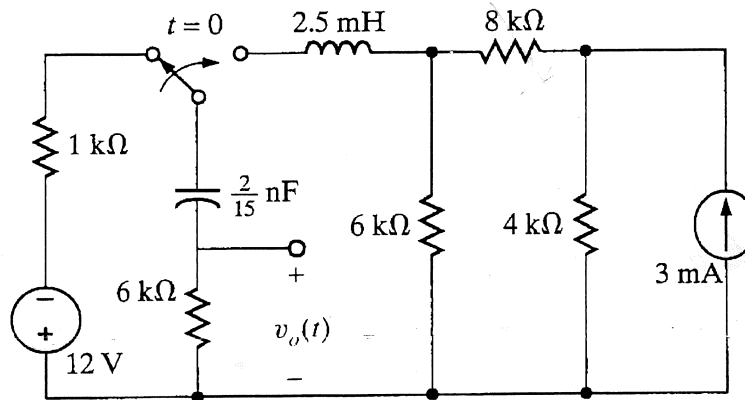


Fig. 1.

4. (15%) The switch shown in Fig. 2 moves from position 1 to position 2 at  $t = 0$ . Please use the Laplace transforms to find  $v_o(t)$  for  $t > 0$ .

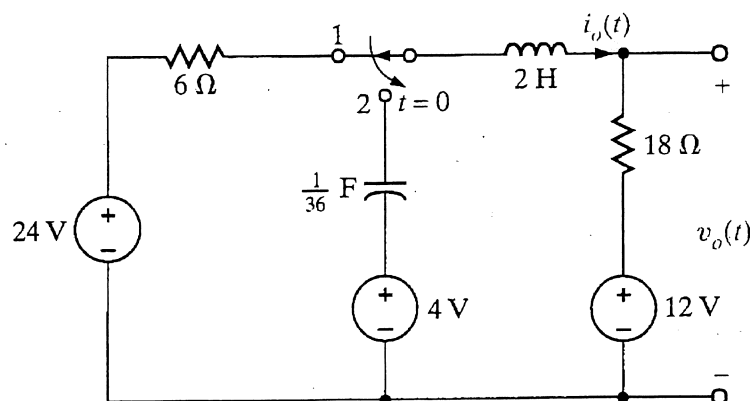


Fig. 2.

5. (25%) A second-order circuit in Fig. 3 is assumed to be in a steady-state condition prior to switch at  $t = 0$ . Please use Laplace transforms to the voltage  $v_o(t)$  for  $t > 0$ .

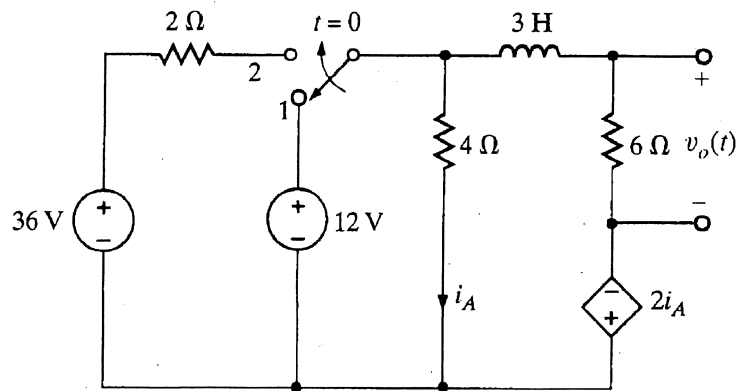


Fig. 3

6. (10%) The magnitude characteristic of a band-elimination filter is depicted in Fig. 4. Please determine the transfer function of  $H(j\omega)$ .

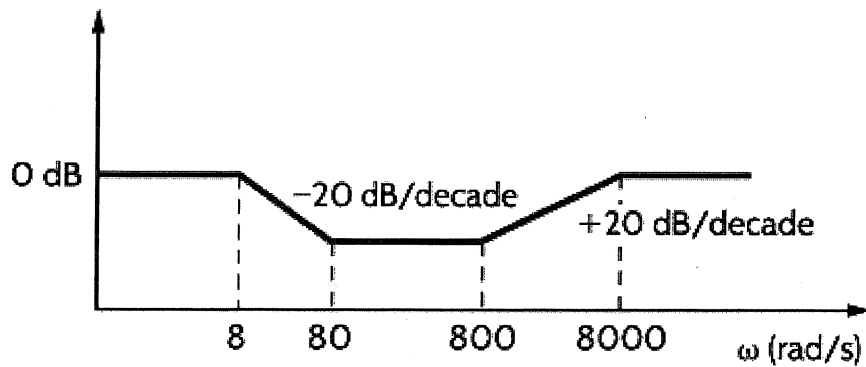


Fig. 4

7. (15%) Please sketch the magnitude characteristic of the Bode plot, labeling all critical slopes and points for the following function:

$$G(j\omega) = \frac{0.1(2j\omega + 1)}{j\omega(0.1j\omega + 1)(0.01j\omega + 1)}$$