

# Introduction to Analog Integrated Circuit Design

Fall 2022


Feedback

Yung-Hui Chung

MSIC Lab **DECE, NTUST** 




#### **Outline**

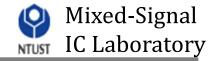

- Benefits of Feedback Systems
- Feedback Topologies
- Difficulties of Feedback Analysis
- Two-Port Network Models
- Loop Gain Calculation


# A Feedback System

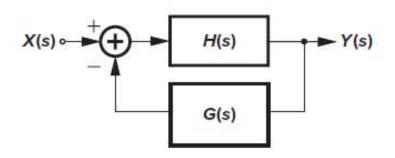

$$Y(s) = H(s)[X(s) - G(s)Y(s)]$$


$$\frac{Y(s)}{X(s)} = \frac{H(s)}{1 + G(s)H(s)}$$

#### Feedforward error amplifier

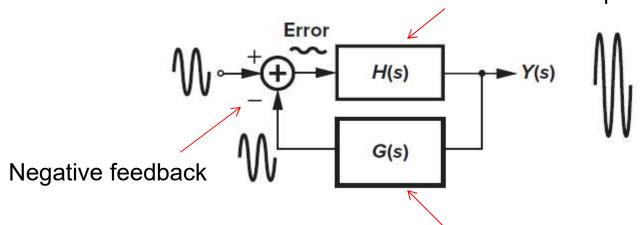


Output sensor (on the feedback path)

## Properties of Feedback Circuits

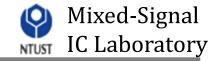

- Gain Desensitization
  - Using feedback to stabilize the gain accuracy
- Terminal Impedance Modification
  - Using feedback to approach ideal impedance
- Bandwidth Modification
  - Using feedback to extend the -3dB bandwidth
- Nonlinearity Reduction
  - Using feedback to improve the output nonlinearity

### Gain Desensitization

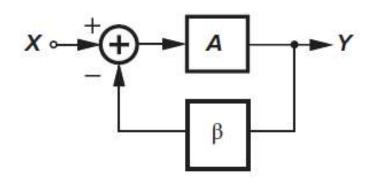


$$\frac{Y}{X} = \frac{A}{1 + \beta A}$$

$$\approx \frac{1}{\beta} \left( 1 - \frac{1}{\beta A} \right) \text{ if } \beta A >> 1$$

Cap. Ratio or Resistor ratio


High-gain opamp


#### Loop Gain

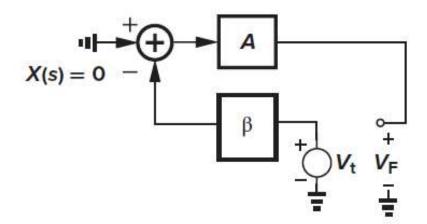


$$V_F/V_t = -\beta A$$

### Gain Desensitization

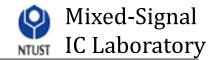


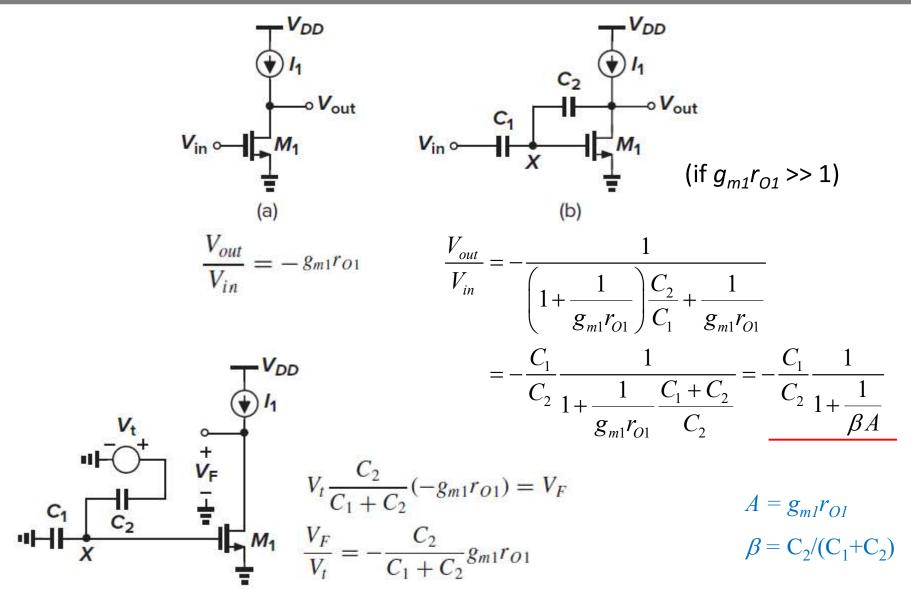


# Terminal Impedance Modification

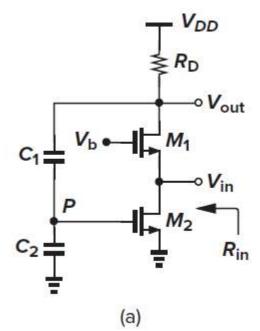
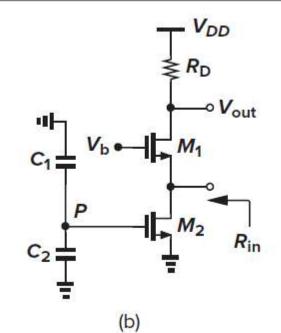
$$R_{in,open} = \frac{1}{g_{m1} + g_{mb1}}$$



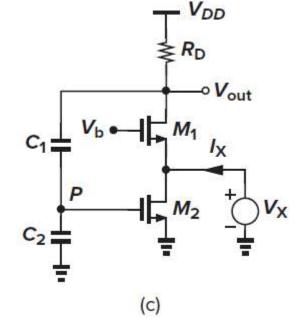

$$R_{in,closed} = V_X/I_X$$


$$= \frac{1}{g_{m1} + g_{mb1}} \frac{1}{1 + g_{m2}R_D \frac{C_1}{C_1 + C_2}}$$

$$Z_{in,open} o rac{Z_{in,open}}{1 + \beta A}$$

(The detail is on p.278, textbook)


L7-7


# Terminal Impedance Modification

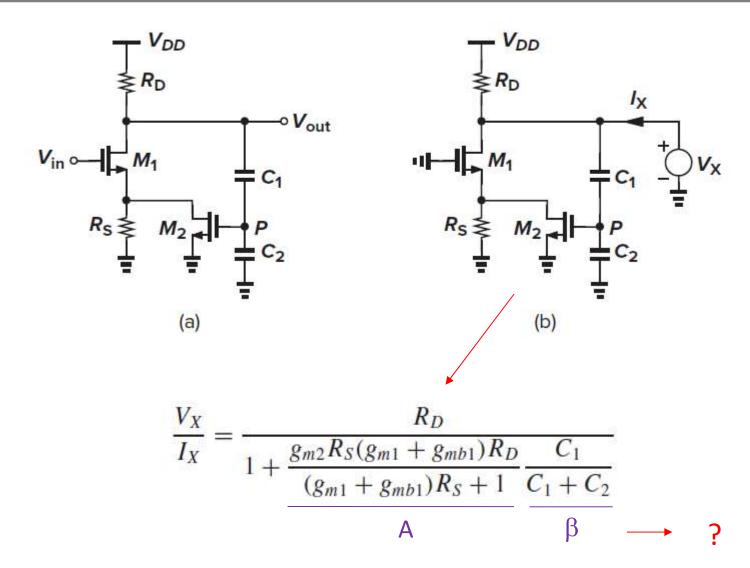

### **Bandwidth Modification**



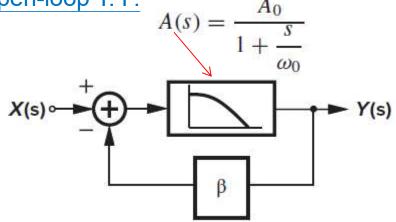

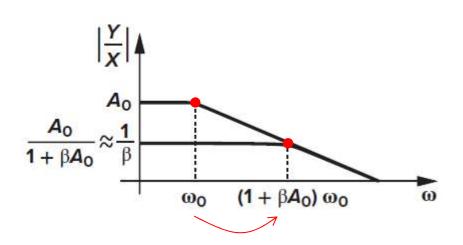

#### Closed-loop T. F.


$$\frac{Y}{X}(s) = \frac{\frac{A_0}{1 + \frac{s}{\omega_0}}}{1 + \beta \frac{A_0}{1 + \frac{s}{\omega_0}}} = \frac{A_0}{1 + \beta A_0 + \frac{s}{\omega_0}}$$

$$= \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{(1 + \beta A_0)\omega_0}}$$


Q: For the closed-loop T. F.,

- What is the DC gain?
- What is the -3dB bandwidth?

# Nonlinearity Reduction

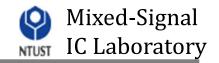

#### **Open-loop**

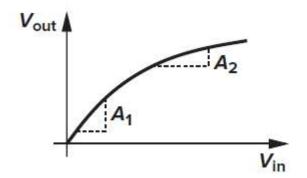


$$r_{open} = \frac{A_2}{A_1}$$

$$r_{open} = 1 - \frac{\Delta A}{A_1}$$

For ICs,  $A \approx k (g_m r_O)^N$ 

#### **Close-loop**

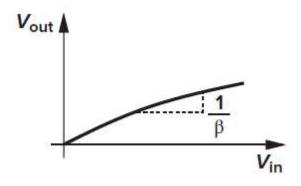

$$r_{closed} = \frac{\frac{A_2}{1 + \beta A_2}}{\frac{A_1}{1 + \beta A_1}}$$
$$= \frac{1 + \frac{1}{\beta A_1}}{1 + \frac{1}{\beta A_2}}$$

$$Err_{CL} = Err_{OL} / (1+\beta A)$$

#### r: gain ratio


$$r_{closed} \approx 1 - \frac{\frac{1}{\beta A_2} - \frac{1}{\beta A_1}}{1 + \frac{1}{\beta A_2}}$$
$$\approx 1 - \frac{A_1 - A_2}{1 + \beta A_2} \frac{1}{A_1}$$

Err

# Properties of Feedback Circuits: Recal Laboratory

- Gain Desensitization
  - Using feedback to stabilize the gain accuracy
- Terminal Impedance Modification
  - Using feedback to approach ideal impedance
- Bandwidth Modification
  - Using feedback to extend the -3dB bandwidth
- Nonlinearity Reduction
  - Using feedback to improve the output nonlinearity

# Types of Amplifiers

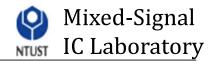



Voltage Amp.








Current Amp.

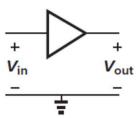


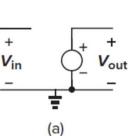


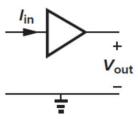


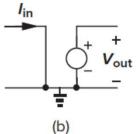

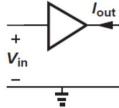

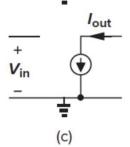

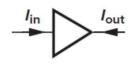

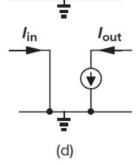

Zout


**V**out


#### 輸入阻抗的連接:


- •電壓輸入是並聯
- •電流輸入是串聯


#### 輸出等效電路:

- •電壓是戴維寧
- •電流是諾頓

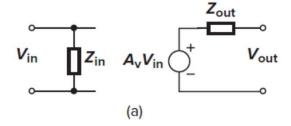

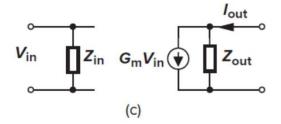

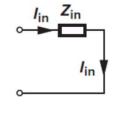

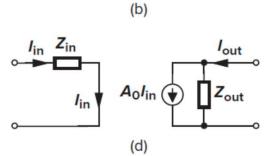

Rolin

# Types of Amplifiers





Voltage Amp.


Transimpedance Amp.


Transconductance Amp.


Current Amp.

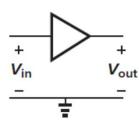


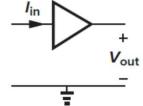


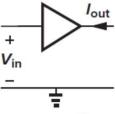


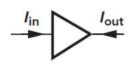

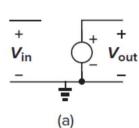


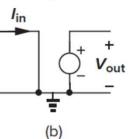


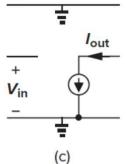


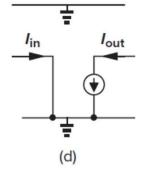


#### Four circuit examples

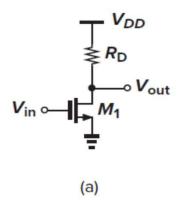


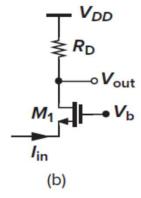


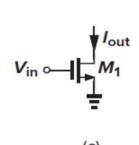

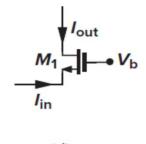


# Types of Amplifiers

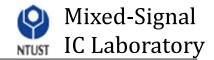

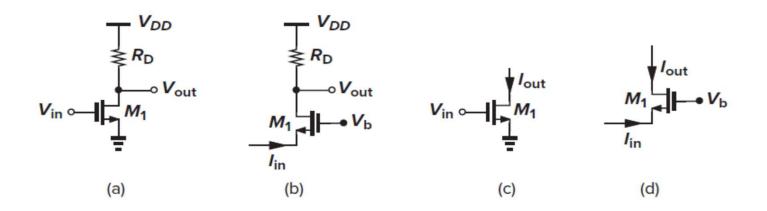


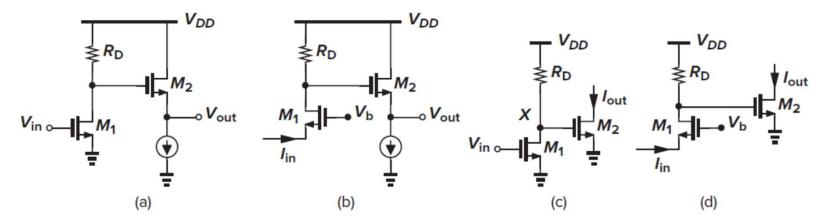Four improved circuit examples: key issue is the output terminal




#### Sense and Return Mechanisms

#### Sensing

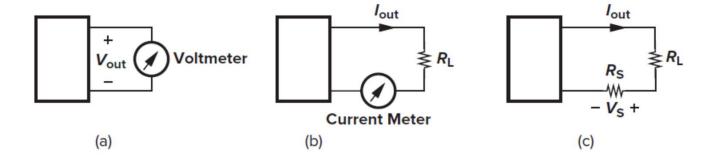



#### Addition

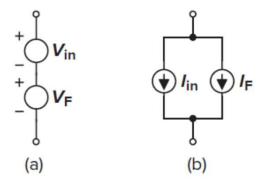


- In general, sensing and return circuits will change the original circuitry!!
- It's hard not to change, but we may reduce the effect reasonably!!

### Practical Sensing/Feedback Circuits

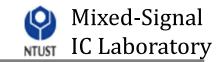


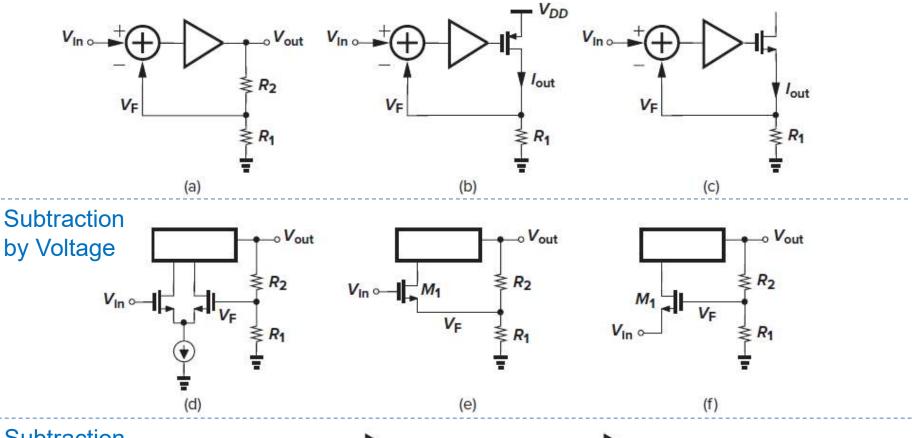

Subtraction by Current

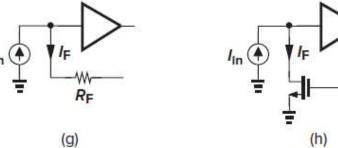

## Feedback Topologies

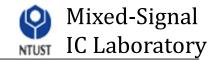


(Output – Input)

Voltage-Voltage Feedback


Current-Voltage Feedbag

Voltage-Current Feedbace

Current-Current Feedback

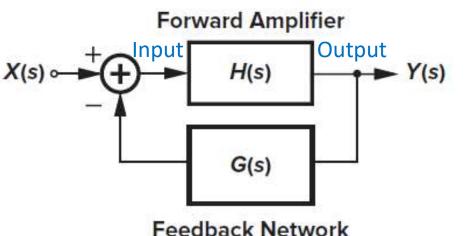

# Voltage-Voltage Feedback

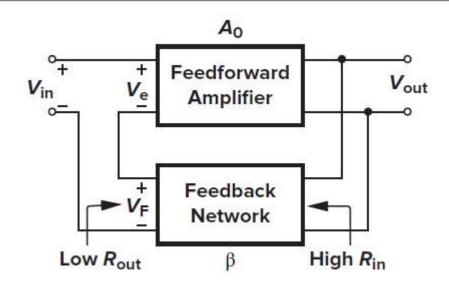


$$V_F = \beta V_{out}$$

$$V_e = V_{in} - V_F$$


$$V_{out} = A_0(V_{in} - \beta V_{out})$$


$$A_{CL} = \frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \beta A_0}$$

#### Example

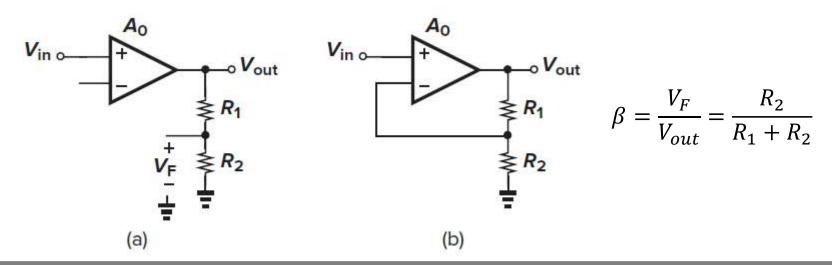

# Output Resistance Modification

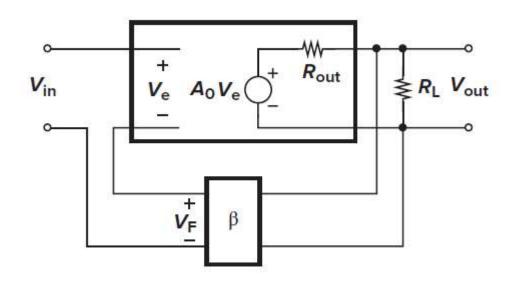

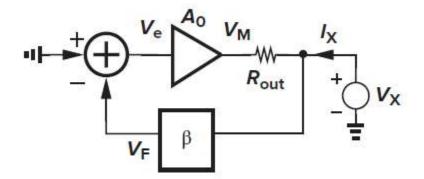

$$V_F = \beta V_X$$

$$V_e = 0 - V_F = -\beta V_X$$


$$V_M = A_0 V_e = -\beta A_0 V_X$$


$$I_X = \frac{V_X - V_M}{R_{out}}$$

$$R_{out,CL} = \frac{V_X}{I_X} = \frac{R_{out}}{1 + \beta A_0}$$

# Input Resistance Modification



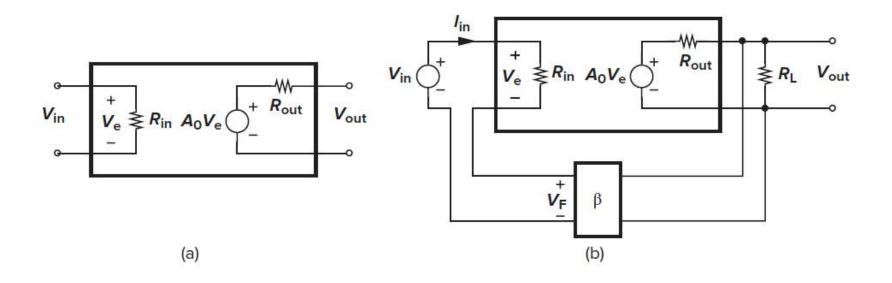


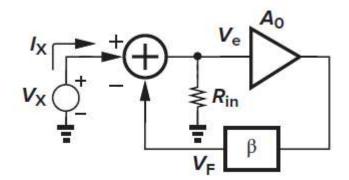

$$V_F = \beta A_0 V_e$$
 and  $V_e = I_X R_{in}$   
 $V_e = V_X - V_F = V_X - \beta A_0 I_X R_{in}$   
 $I_X R_{in} = V_X - \beta A_0 I_X R_{in}$   
 $R_{in,CL} = \frac{V_X}{I_X} = R_{in}(1 + \beta A_0)$ 

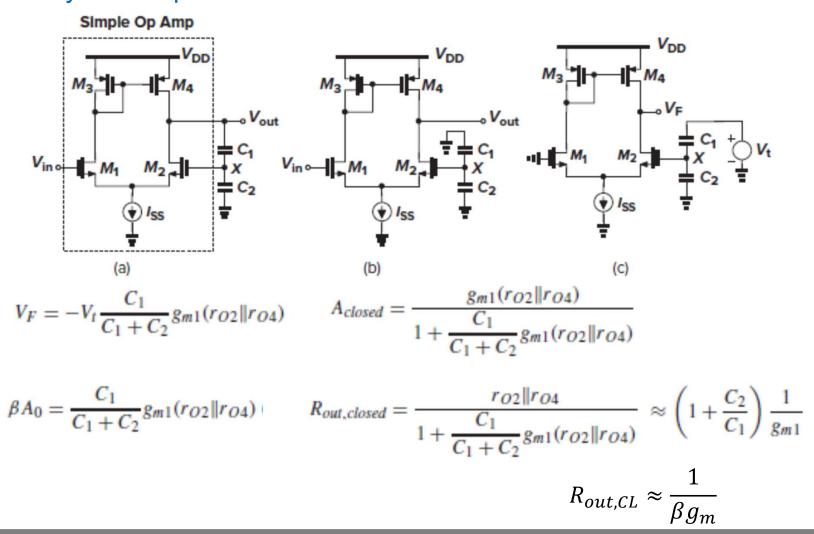
## Example 8.4

Calculate the closed-loop gain and output resistance of the amplifier at relatively low frequencies.


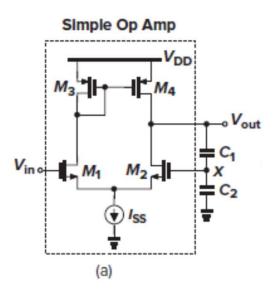
# Example 8.4 (at high frequencies) Mixed-Signal IC Laboratory

Calculate the closed-loop gain and output resistance of the amplifier at high frequencies.




# Example 8.6

In textbook, Figure 8.29(a) shows a common-gate topology placed in a voltage-voltage feedback configuration. Note that the summation of the feedback voltage and the input voltage is accomplished by applying the former to the gate and the latter to the source (Vgs = Vg - Vs).

 Calculate the input resistance at low frequencies if channel-length modulation is negligible
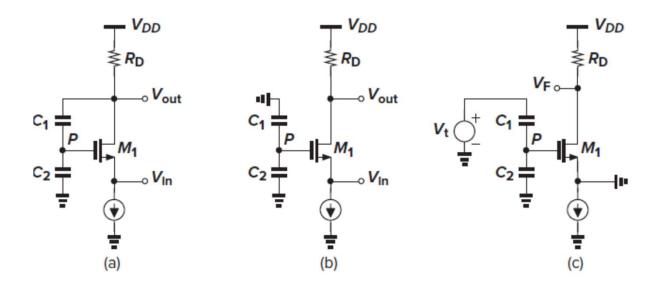
#### [Solution]

As shown in Fig.(b), breaking the loop at output feedback path




# Example 8.6


$$R_{in} = \frac{1}{g_{m1} + g_{mb1}}$$
$$R_{in,CL} = R_{in}(1 + \beta A_0)$$


$$\beta A_0 = -\frac{V_F}{V_t} = -\frac{C_1}{C_1 + C_2} (-g_{m1}R_D)$$

$$\beta A_0 = \frac{C_1}{C_1 + C_2} g_{m1}R_D$$
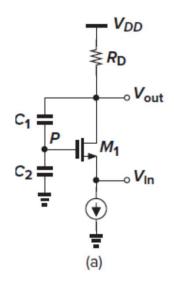
$$R_{in,CL} = \frac{1}{g_{m1} + g_{mb1}} \left( 1 + \frac{C_1}{C_1 + C_2} g_{m1}R_D \right)$$




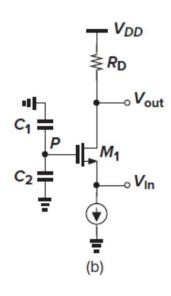

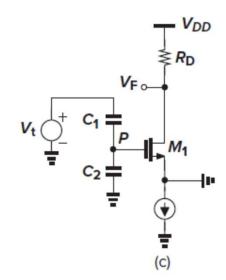

# Current-Voltage Feedback



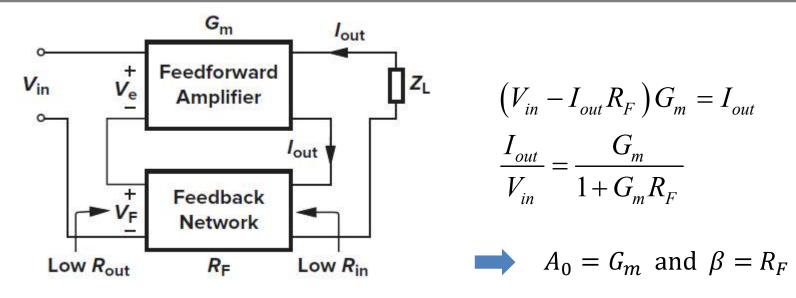


#### Feedforward Amplifier:

- Input is Voltage
- Output is Current

# Current-Voltage Feedback




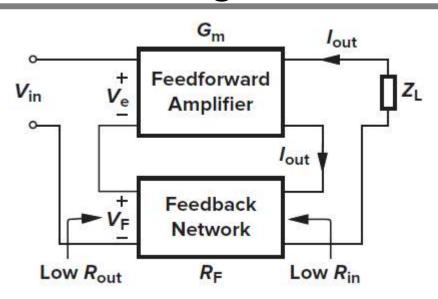

$$(V_{in} - I_{out}R_F)G_m = I_{out}$$

$$\frac{I_{out}}{V_{in}} = \frac{G_m}{1 + G_mR_F}$$


#### Calculation of loop gain

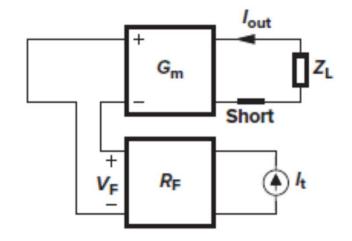

$$\begin{split} V_F &= R_F I_t \\ I_{out} &= G_m (0 - R_F I_t) \\ \text{Loop gain} &= -\frac{I_{out}}{I_t} = G_m R_F \end{split}$$


Closed-loop gain: 
$$\frac{I_{out}}{V_{in}} = \frac{G_m}{1 + G_m R_F}$$

# **Output Resistance Modification**

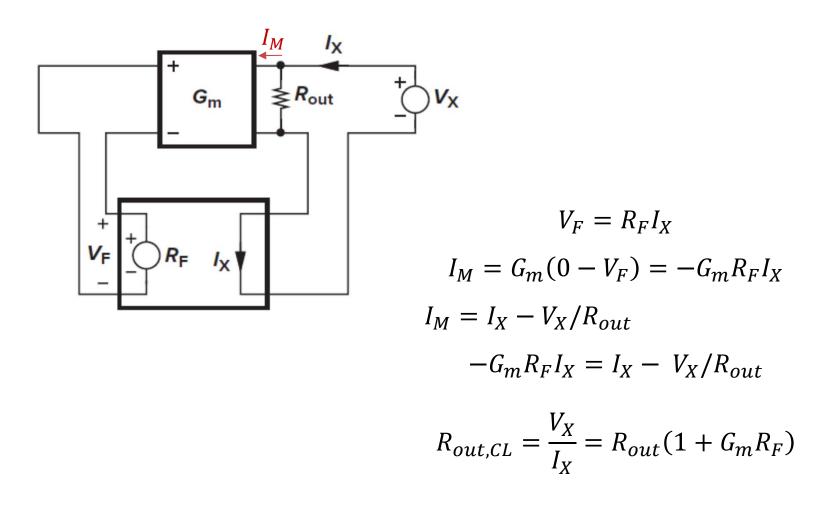

# Input Resistance Modification



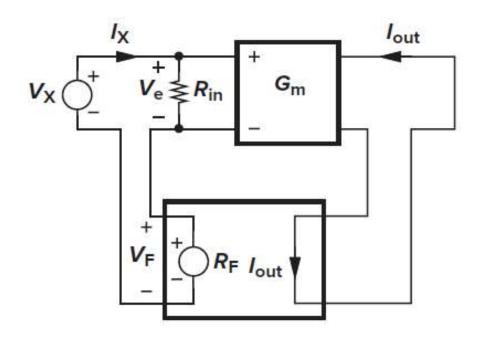


$$V_F = R_F I_{out} = R_F G_m V_e$$


$$V_e = V_X - V_F = V_X - R_F G_m V_e$$

$$V_e = V_X / (1 + G_m R_F) = I_X R_{in}$$

$$R_{in,CL} = \frac{V_X}{I_X} = R_{in} (1 + G_m R_F)$$

# Example 8.7

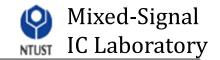


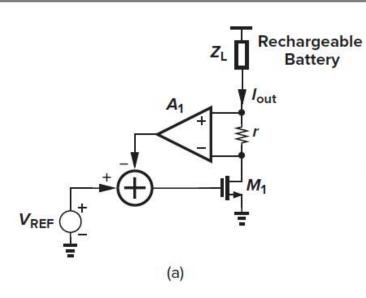

$$(V_{REF} - A_1 I_{out} r) \cdot g_{m1} = I_{out}$$

$$g_{m1} V_{REF} = (1 + A_1 g_{m1} r) I_{out}$$
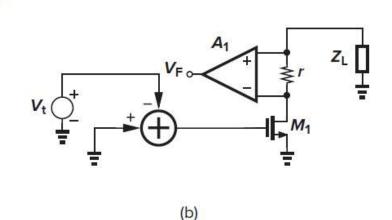
$$\frac{I_{out}}{V_{REF}} = \frac{g_{m1}}{1 + A_1 g_{m1} r}$$



$$V_F = A_1 I_{M1} r$$

$$I_{M1} = g_{m1} (0 - V_t) = -g_{m1} V_t$$


$$V_F = -A_1 g_{m1} r V_t$$

$$Loop \ gain = -\frac{V_F}{V_t} = A_1 g_{m1} r$$

$$R_{out,CL} = (r_o + r)(1 + A_1 g_{m1} r)$$

# Voltage-Current Feedback



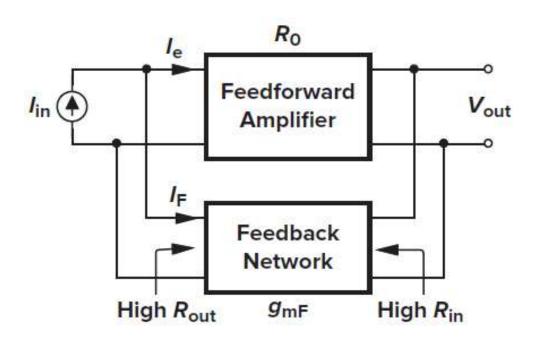


$$\begin{split} V_{out} &= I_e R_O \\ I_e &= I_{in} - I_F = I_{in} - g_{mF} V_{out} \\ V_{out} &= R_O \big( I_{in} - g_{mF} V_{out} \big) \end{split}$$

#### Feedforward Amplifier:

- Input is Current
- Output is Voltage


$$\frac{V_{out}}{I_{in}} = \frac{R_0}{1 + g_{mF}R_0}$$

# **Output Impedance Modification**

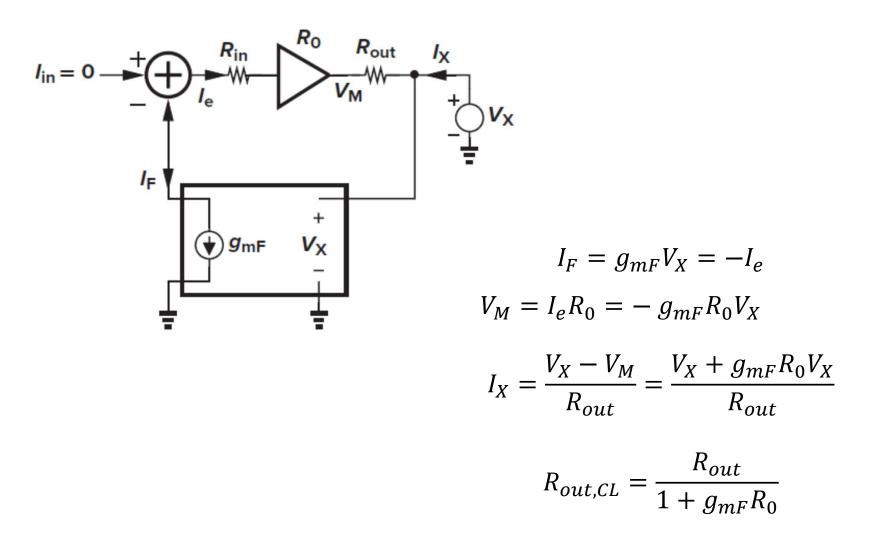

# Input Impedance Modification



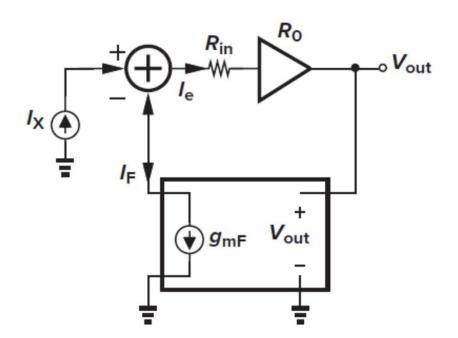

$$I_{e} = \frac{V_{X}}{R_{in}}$$

$$I_{F} = I_{X} - I_{e} = I_{X} - \frac{V_{X}}{R_{in}}$$

$$I_{F} = g_{mF}R_{0}I_{e} = g_{mF}R_{0}\frac{V_{X}}{R_{in}}$$


$$I_{X} - \frac{V_{X}}{R_{in}} = g_{mF}R_{0}\frac{V_{X}}{R_{in}}$$

$$I_{X} = \frac{V_{X} + g_{mF}R_{0}V_{X}}{R_{in}}$$


$$R_{in,CL} = \frac{R_{in}}{1 + g_{mF}R_{0}}$$
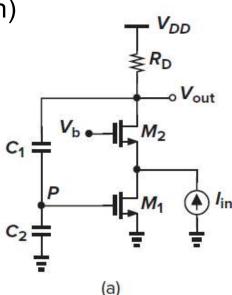
# Example 8.8

Calculate the transimpedance,  $V_{out}/I_{in}$ , of the circuit shown in Fig. 8.36(a) at relatively low frequencies. Assume that  $\lambda = 0$ . (The bias network of  $M_1$  is not shown)


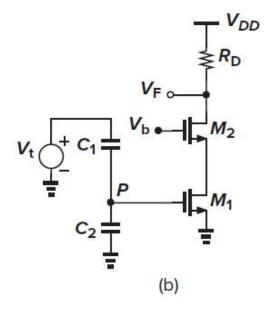
$$R_{0,CL} = \frac{V_{out}}{I_{in}} = \frac{R_D}{1 + \frac{C_1}{C_1 + C_2} g_{m1} R_D}$$





$$-\left(V_t \frac{C_1}{C_1 + C_2} g_{m1} R_D\right) = V_F$$

$$\beta A_0 = -\frac{V_F}{V_t} = \frac{C_1}{C_1 + C_2} g_{m1} R_D$$
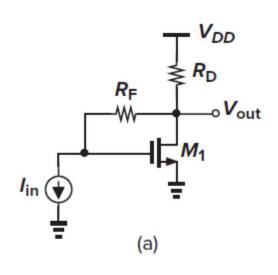
# Example 8.10

Calculate the input and output impedances, assume that  $R_F >> R_D$ .



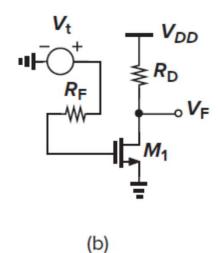

$$-(V_t g_{m1} R_D) = V_F = \beta A = -\frac{V_F}{V_t} = g_m R_D$$


$$R_{in,CL} = \frac{R_F}{1 + g_m R_D}$$


$$R_{out,CL} = \frac{R_D}{1 + g_m R_D}$$

$$R_{out,CL} = \frac{1}{g_m} || R_D$$

$$R_{out,CL} = \frac{1}{g_m} || R_L$$

# Optical Fiber Example

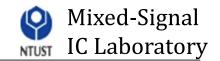

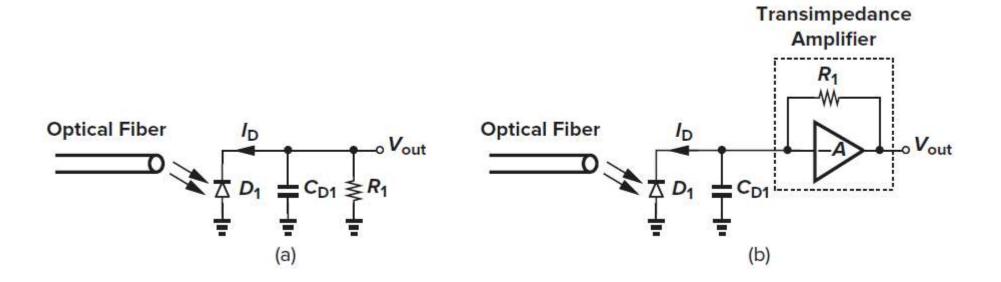


Bandwidth issue??

We need to get a small  $R_1$  but keep a large amplitude of  $V_{out}$ 

$$R_{in} = \frac{R_1}{1+A}$$

### **Current-Current Feedback**

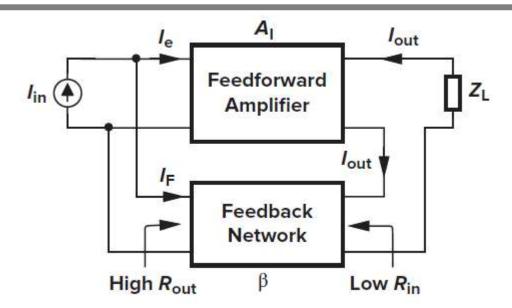


$$\frac{I_{out}}{I_{in}} = \frac{A_I}{1 + \beta A_I}$$

#### Feedforward Amplifier:


- Input is Current
- Output is Current

### **Current-Current Feedback**

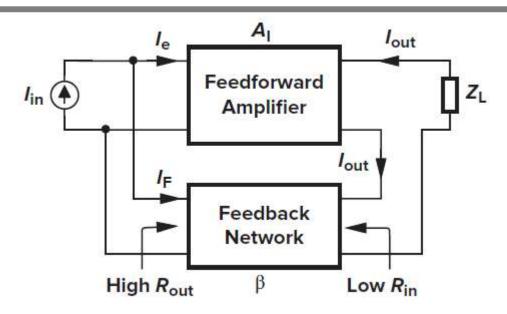

$$\frac{I_{out}}{I_{in}} = \frac{A_I}{1 + \beta A_I}$$


#### Example

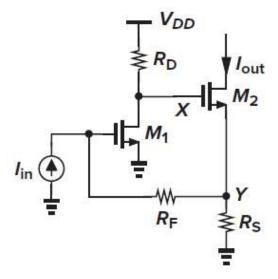


$$R_{in,CL} = ?$$


$$R_{in,CL} = ?$$
 $R_{out,CL} = ?$ 

### Effect of Feedback on Noise

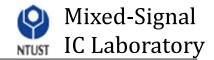

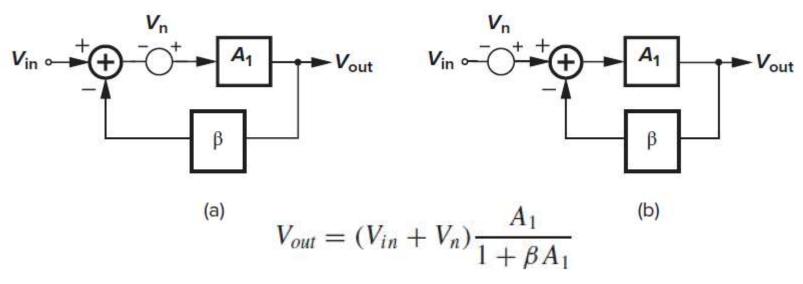Feedback does not improve the noise performance of circuits?



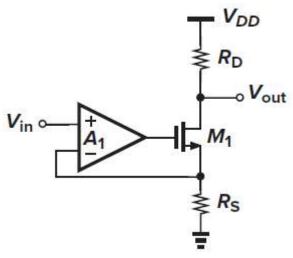


$$\left|V_{n,in,open}\right| = \frac{\left|V_{n,RD}\right|}{A_1 R_D} \left[\frac{1}{g_m} + R_S\right]$$

if the feedback network is noiseless

$$\left|V_{n,in,closed}\right| = \frac{\left|V_{n,RD}\right|}{A_1 R_D} \left[\frac{1}{g_m} + (1+A_1)R_S\right]$$

### Feedback Analysis Difficulties

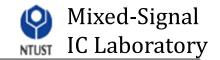


- 1. Breaking the loop with loading effect
- 2. Circuits cannot be clearly decomposed
- 3. Circuits cannot be mapped into four topologies
- 4. Bilateral Circuits
- 5. Multiple Feedback Circuits

Loading	Ambiguous	Noncanonical	Nonunilateral	Multiple Feedback
	Decomposition	Topologies	Loop	Mechanisms
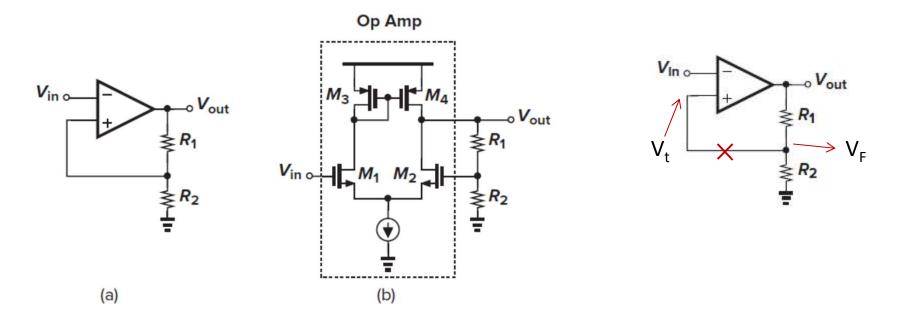
### Breaking the loop with loading effect





The feedback branch consisting of  $R_1$  and  $R_2$  may draw a significant signal current from the op amp, reducing its *open-loop* gain

So, what is the real feedforward output resistance?

=> The answer is  $Ro, amp \mid\mid (R_1+R_2)$ 

### Breaking the loop with loading effect

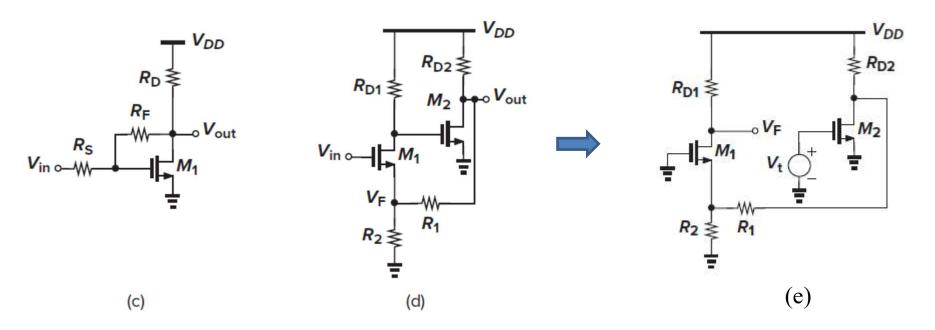


Fig.(c) shows the open-loop gain of the forward CS stage falls if  $R_F$  is not very large. ( $R_F$  must be as large as possible!!)


The "output" loading results from the nonideal input impedance of the feedback network.

Fig.(d) has similar condition for  $R_1$  and  $R_2$ 


Loop broken as "Fig.(e)" is good for loading effect. But, what is *Ro*?
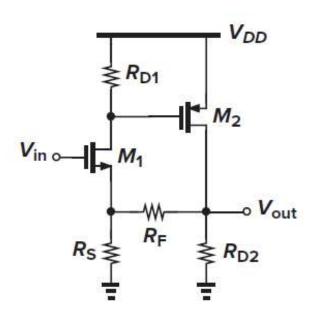
#### Circuits cannot be clearly decomposed






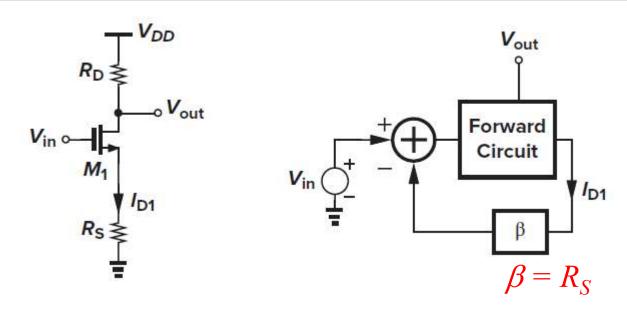- Is  $R_{D2}$  a feedback element? The answer can be yes or no!!
- How about  $R_S$  and  $R_F$ ?
- Actually, these three resistors are both in a feedforward circuit.
  - ⇒Voltage-Voltage topology



- $R_S$  is used as both feedforward and feedback elements
- This is a "Current-Voltage" topology

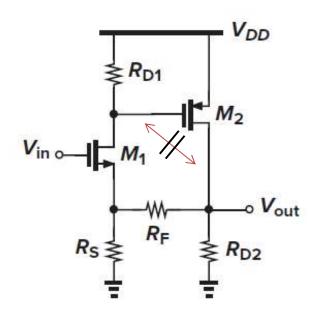
### Bilateral circuits in the feedback path



- It is a bilateral circuit
- For example, the signal leaks from the drain of M2 to its gate through  $C_{GD2}$  at high frequencies

### Multiple Feedback Circuits



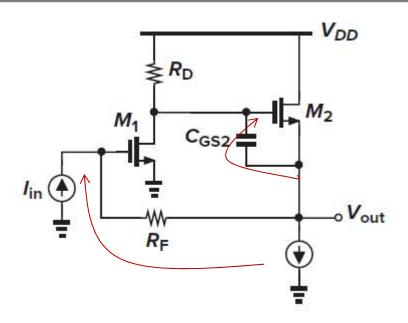


Q: How to analyze this circuit?


⇒Two feedback loops

⇒Then, ...


### Multiple Feedback Circuits



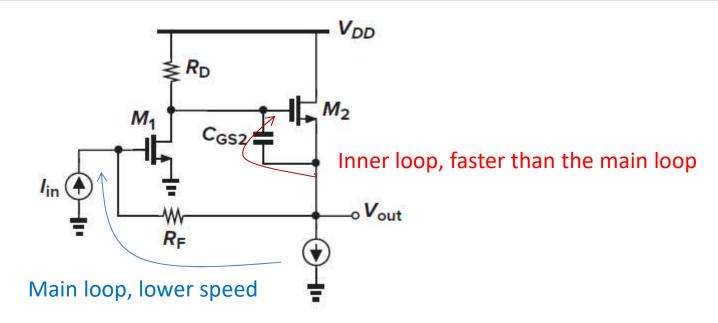

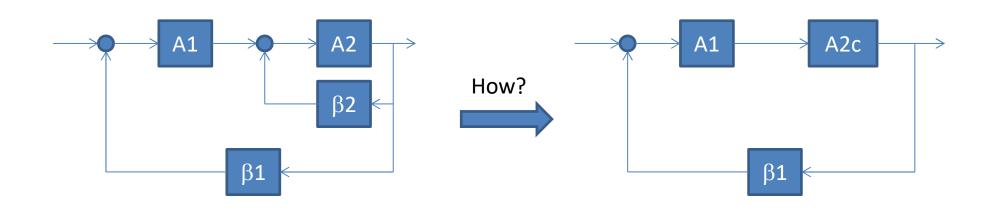
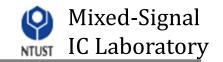
### Feedback Analysis Difficulties: Recall



- 1. Breaking the loop with loading effect
- Circuits cannot be clearly decomposed
- 3. Circuits cannot be mapped into four topologies
- 4. Bilateral Circuits
- 5. Multiple Feedback Circuits

Loading	Ambiguous	Noncanonical	Nonunilateral	Multiple Feedback
	Decomposition	Topologies	Loop	Mechanisms


# Analysis Methods of Feedback Circuits Mixed-Signal IC Laboratory


Two-Port Method	Bode's Method	Middlebrook's Method
<ul> <li>Computes open-loop and closed-loop quantities and the loop gain.</li> <li>Includes loading effects.</li> </ul>	<ul> <li>Computes closed-loop quantities without breaking the loop.</li> <li>Applies to any topology.</li> </ul>	Computes closed-loop quantities without breaking the loop.      Applies to any topology.
Neglects feedforward through feedback network.	Provides loop gain only if one feedback mechanism is present.	Provides loop gain only if local and global loops are distinguishable.
<ul> <li>Can be applied recursively to multiple feedback mechanisms.</li> <li>Does not apply to noncanonical topologies.</li> </ul>		Reveals effect of reverse loop gain in nonunilateral loops.

Not mentioned in this lecture

### **Two-Port Network Models**



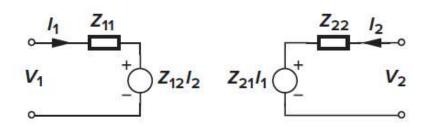


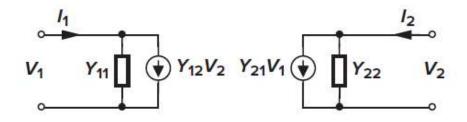


(a) 
$$V_1 = Z_{11}I_1 + Z_{12}I_2$$
 
$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

(b)
$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

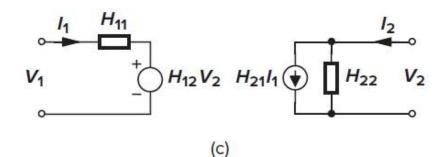


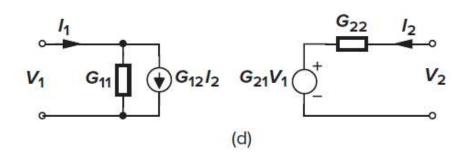

$$V_1 = H_{11}I_1 + H_{12}V_2$$
$$I_2 = H_{21}I_1 + H_{22}V_2$$


$$I_1 = G_{11}V_1 + G_{12}I_2$$
$$V_2 = G_{21}V_1 + G_{22}I_2$$

### Voltage-Voltage Feedback

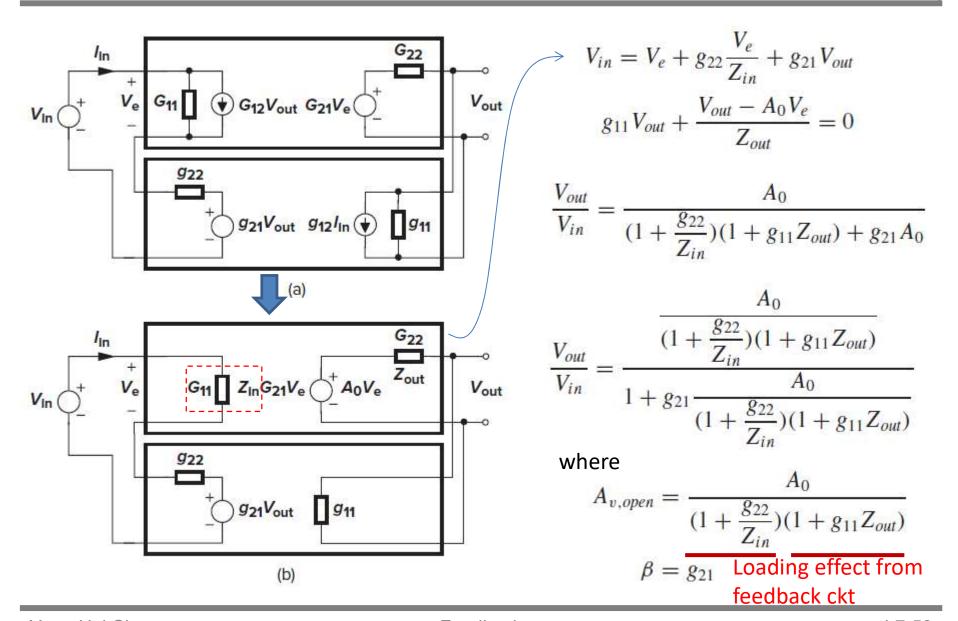

### Voltage-Voltage Feedback



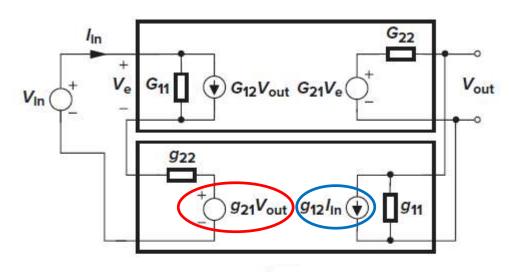


$$\frac{V_{out}}{V_{in}} = \frac{\frac{A_0}{(1 + \frac{g_{22}}{Z_{in}})(1 + g_{11}Z_{out})}}{1 + g_{21}\frac{A_0}{(1 + \frac{g_{22}}{Z_{in}})(1 + g_{11}Z_{out})}}$$

where

$$A_{v,open} = \frac{A_0}{(1 + \frac{g_{22}}{Z_{in}})(1 + g_{11}Z_{out})}$$
$$\beta = g_{21}$$


FF: Feedforward amplifier

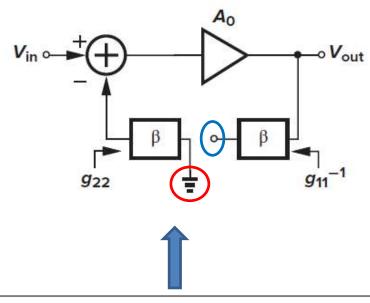

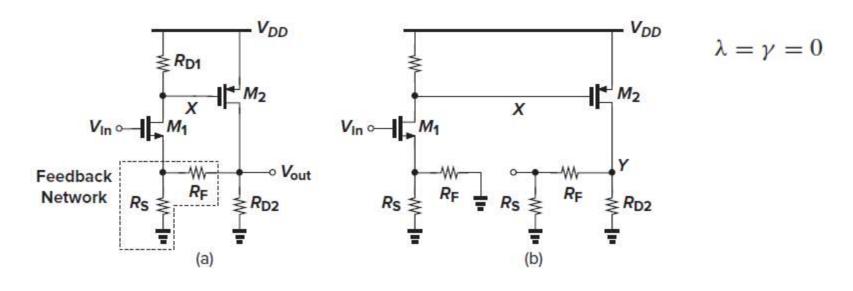- (1) Find out feedback (FB) network, and get " $\beta$ "
- (2) Find "A<sub>0,OL</sub>" firstly w/ loading effect

Step-1: For FF's input, Vout=0 (connection is short)


Step-2: For FF's output, lin=0 (connection is open)




$$g_{21} = R_S/(R_F + R_S) \qquad A_{v,open} = \frac{V_Y}{V_{in}} = \frac{-R_{D1}}{R_F \|R_S + 1/g_{m1}} \{-g_{m2}[R_{D2}\|(R_F + R_S)]\}$$

$$A_{v,closed} = A_{v,open}/(1 + g_{21}A_{v,open})$$

### Current-Voltage Feedback

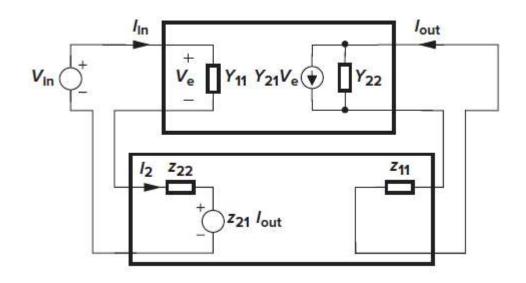
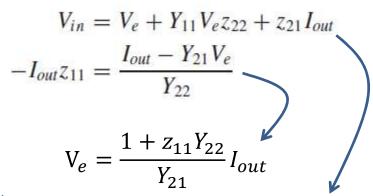
$$\frac{I_{out}}{V_{in}} = \frac{\frac{Y_{21}}{(1 + z_{22}Y_{11})(1 + z_{11}Y_{22})}}{\frac{Y_{21}}{(1 + z_{22}Y_{11})(1 + z_{11}Y_{22})}}$$






$$V_{in} = V_e(1 + z_{22}Y_{11}) + z_{21}I_{out}$$

where

$$G_{m,open} = \frac{Y_{21}}{(1 + z_{22}Y_{11})(1 + z_{11}Y_{22})}$$
$$\beta = z_{21}$$

### Current-Voltage Feedback

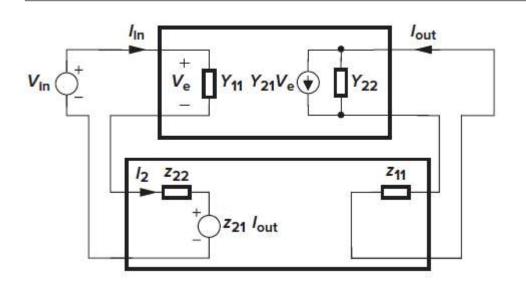


$$\frac{I_{out}}{V_{in}} = \frac{\frac{Y_{21}}{(1 + z_{22}Y_{11})(1 + z_{11}Y_{22})}}{\frac{Y_{21}}{(1 + z_{22}Y_{11})(1 + z_{11}Y_{22})}}$$


#### where


$$G_{m,open} = \frac{Y_{21}}{(1 + z_{22}Y_{11})(1 + z_{11}Y_{22})}$$
$$\beta = z_{21}$$

#### Breaking the loop

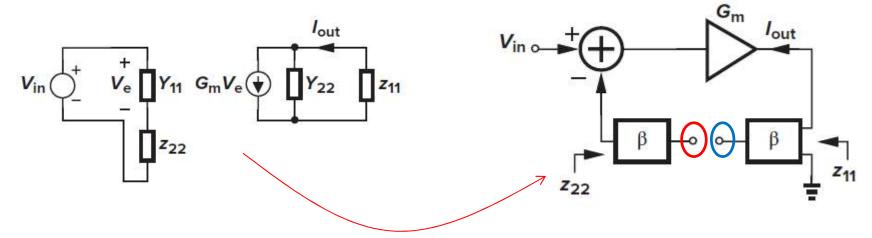


### Example 8.14

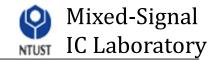

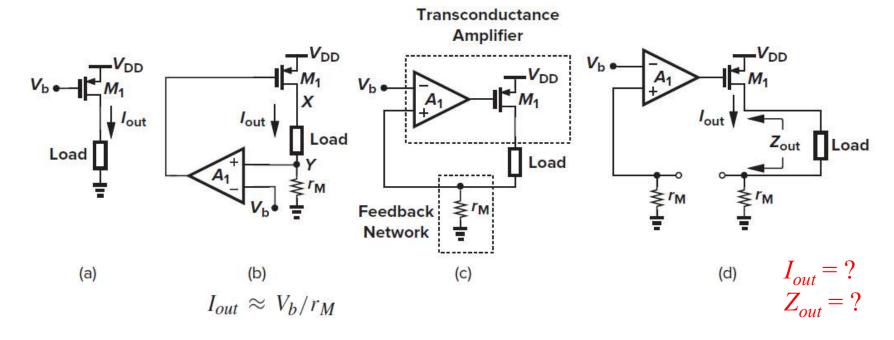

$$G_{m,open} = \frac{I_{out}}{V_b}$$
  $I_{out} = \frac{A_1 g_m}{1 + A_1 g_m r_M} V_b$    
 $\approx A_1 g_m$   $r_O + r_M \longrightarrow Z_{out} = (1 + A_1 g_m r_M)(r_O + r_M)$ 

### Voltage-Current Feedback

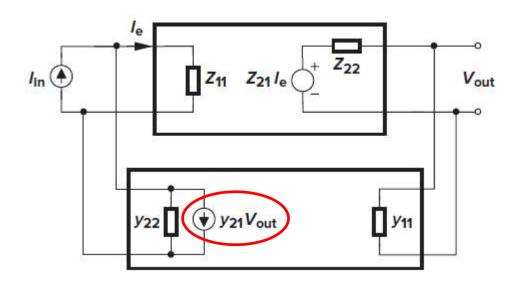


$$I_{in} = I_e + I_e Z_{11} y_{22} + y_{21} V_{out}$$
$$y_{11} V_{out} + \frac{V_{out} - Z_{21} I_e}{Z_{22}} = 0$$


$$\frac{V_{out}}{I_{in}} = \frac{\frac{Z_{21}}{(1 + y_{22}Z_{11})(1 + y_{11}Z_{22})}}{\frac{Z_{21}}{(1 + y_{22}Z_{11})(1 + y_{11}Z_{22})}}$$


where
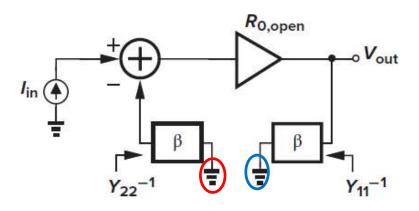
$$R_{0,open} = \frac{Z_{21}}{(1 + y_{22}Z_{11})(1 + y_{11}Z_{22})}$$
$$\beta = y_{21}$$



### Example 8.15

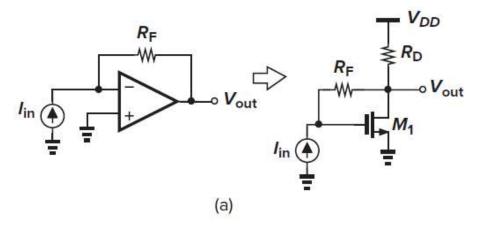

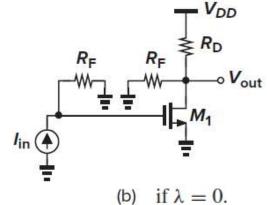

$$R_{0,open} = -R_F g_m(R_F||R_D)$$


$$\beta = \frac{1}{R_F}$$

$$\frac{V_{out}}{I_{in}} = \frac{-R_F g_m(R_F||R_D)}{1 + g_m(R_F||R_D)}$$

$$R_{in} = \frac{R_F}{1 + g_m(R_F||R_D)}$$

$$R_{out} = \frac{R_F||R_D}{1 + g_m(R_F||R_D)}$$

### **Current-Current Feedback**

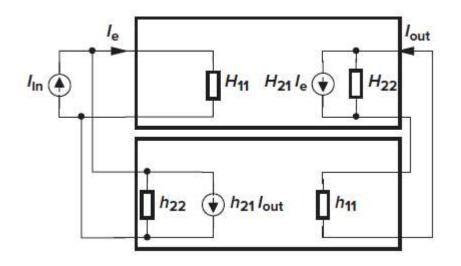



$$I_{in} = I_e H_{11} h_{22} + h_{21} I_{out} + I_e$$
$$I_{out} = -I_{out} h_{11} H_{22} + H_{21} I_e$$

$$\frac{I_{out}}{I_{in}} = \frac{\frac{H_{21}}{(1 + h_{22}H_{11})(1 + h_{11}H_{22})}}{1 + h_{21}\frac{H_{21}}{(1 + h_{22}H_{11})(1 + h_{11}H_{22})}}$$

where
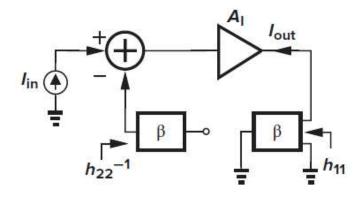
$$A_{I,open} = \frac{H_{21}}{(1 + h_{22}H_{11})(1 + h_{11}H_{22})}$$
$$\beta = h_{21}$$



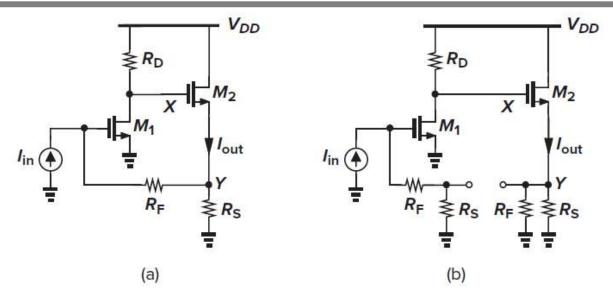


#### Solution


In this circuit,  $R_S$  and  $R_F$  sense the output current and return a fraction thereof to the input. Breaking the loop according to Fig. 8.65, we arrive at the circuit in Fig. 8.66(b), where we have


$$A_{I,open} = -(R_F + R_S)g_{m1}R_D \frac{1}{R_S ||R_F + 1/g_{m2}}$$
(8.106)


The loop gain is given by  $h_{21}A_{I,open}$ , where, from (8.62),  $h_{21} = I_2/I_1$  with  $V_2 = 0$ . For the feedback network consisting of  $R_S$  and  $R_F$ , we have  $h_{21} = -R_S/(R_S + R_F)$ . The closed-loop gain equals  $A_{I,open}/(1 + h_{21}A_{I,open})$ .


## Summary of Loading Effects

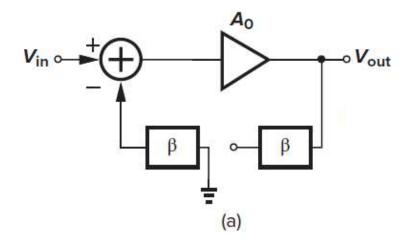


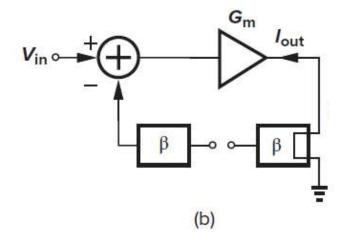


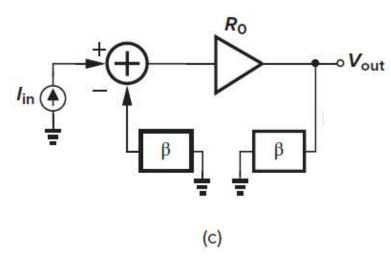


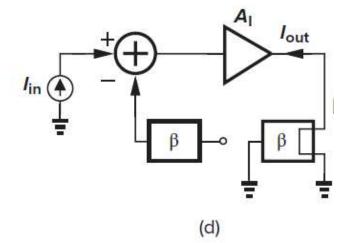

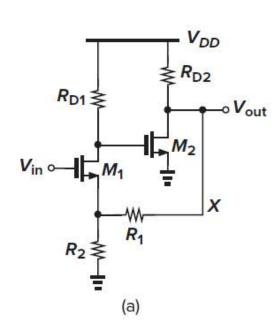

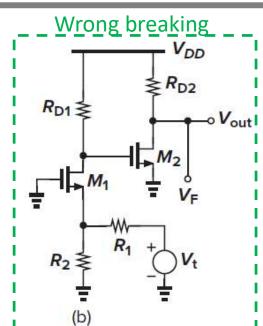


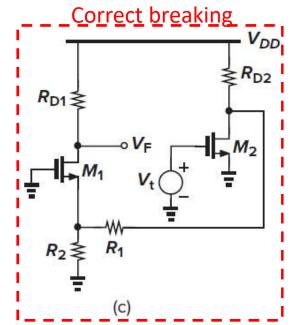


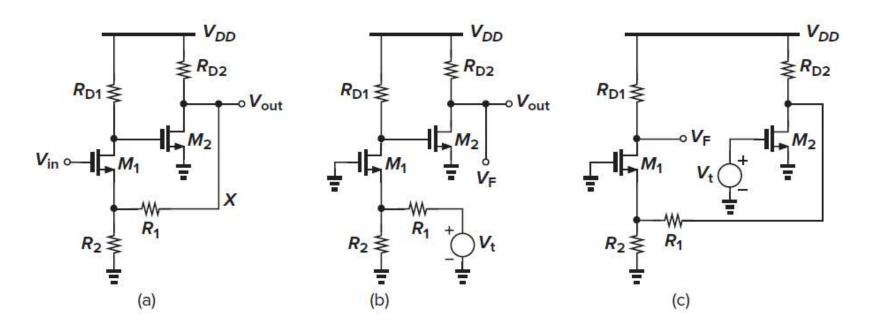

Q: Is it always possible to break the loop at the gate of a MOSFET?

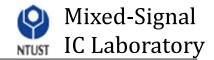- $\Rightarrow$  **Yes, indeed** (at least at low frequencies).
- ⇒ For the feedback to be negative, the signal must be sensed by at least one gate in the loop because only the common-source topology inverts signals.



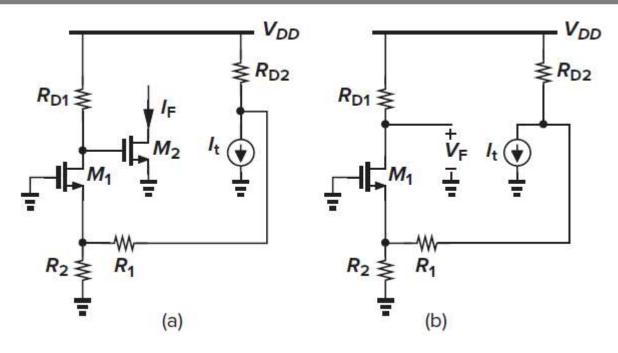



Under what condition can we apply a test current?

The reader can prove that  $I_F/I_t$  in this case is the same as  $V_F/V_t$  in Fig. 8.85(c) on the last page


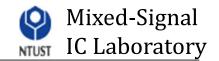
# I want to skip this part because it is not intuitive!!




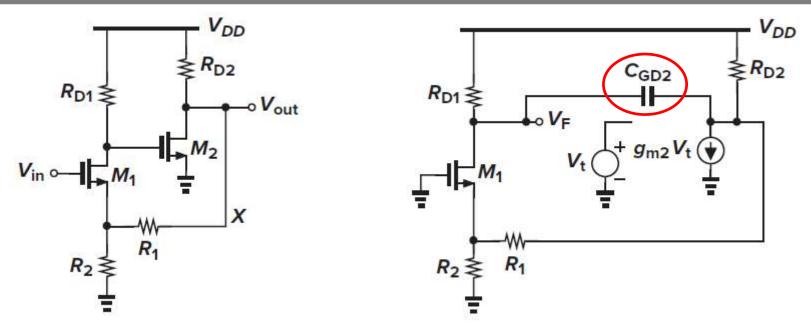

As shown in Fig. 8.88, even though we provide the gate-source voltage by the independent source,  $V_t$ ,  $C_{GD2}$  still creates "local" feedback from the drain of  $M_2$  to its gate, raising the question of whether the loop gain should be obtained by nulling all feedback mechanisms.

Can you give a trial?



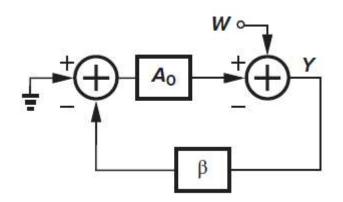

$$Y/W = 1/(1 + \beta A_0)$$

$$\text{Loop Gain} = \left(\frac{Y}{W}\right)^{-1} - 1$$

#### Example

#### Which one is right?

