

Introduction to Analog Integrated Circuit Design

Fall 2023


Differential Amplifiers

Yung-Hui Chung


MSIC Lab
DECE, NTUST

Mixed-Signal
IC Laboratory  NTUST

類比設計八邊形

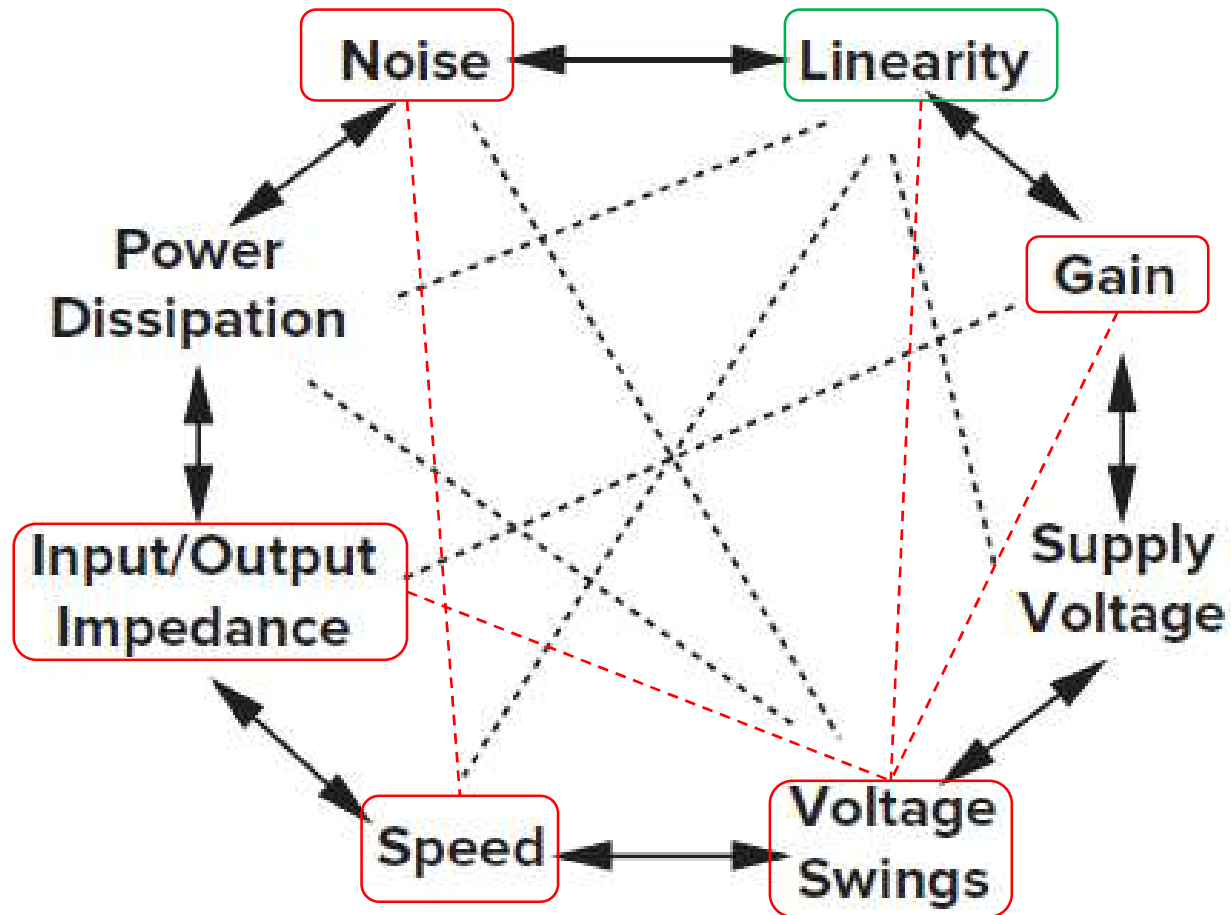

放大器之輸入－輸出特性

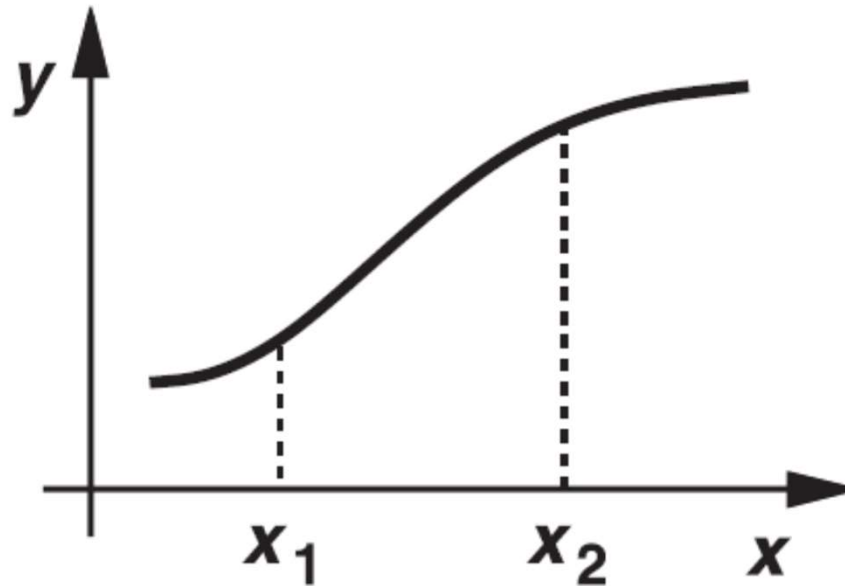

一個放大器之輸入－輸出特性通常為一非線性函數

$$y(t) \approx \alpha_0 + \alpha_1 x(t) + \alpha_2 x^2(t) + \cdots + \alpha_n x^n(t) \quad x_1 \leq x \leq x_2$$

x 的範圍夠小時 $y(t) \approx \alpha_0 + \alpha_1 x(t)$

Chapter 4

Differential Amplifiers

Differential output, $y = y_p - y_n$

Differential input, $x = x_p - x_n$


$$y_p = a_0 + a_1(x) + a_2(x)^2 + a_3(x)^3 + a_4(x)^4 + a_5(x)^5 + \text{H.O.T.}$$

$$y_n = a_0 + a_1(-x) + a_2(-x)^2 + a_3(-x)^3 + a_4(-x)^4 + a_5(-x)^5 + \text{H.O.T.}$$


$$y = y_p - y_n = 2a_1x + 2a_3x^3 + 2a_5x^5 + \text{H.O.T. (odd terms)}$$

H.O.T. = High Order Terms


Single-Ended or Differential

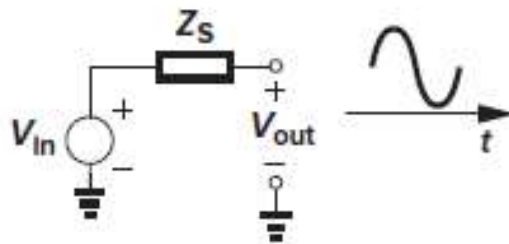


(a)

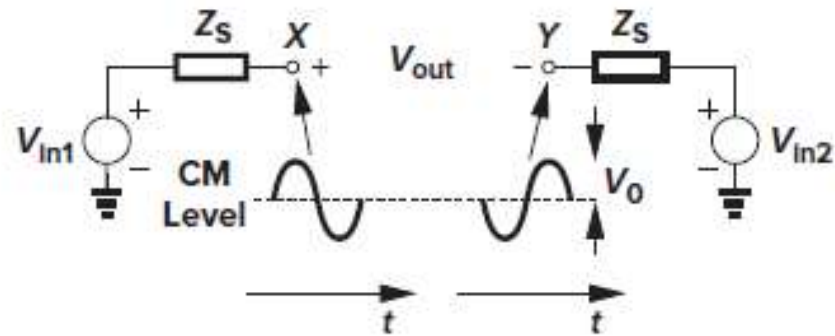

(b)

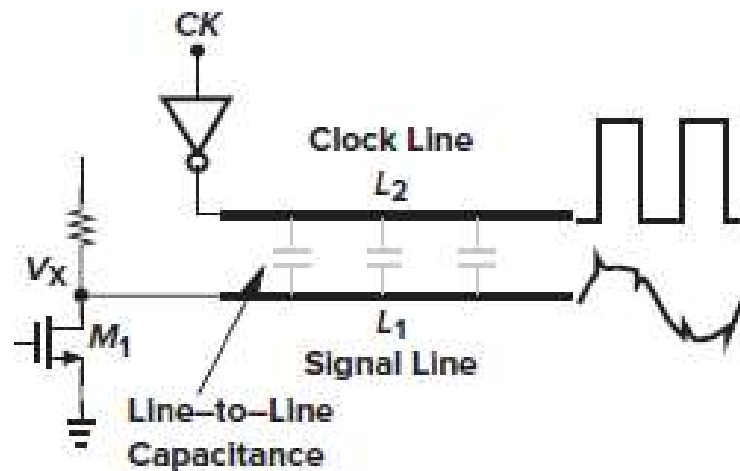


(a)

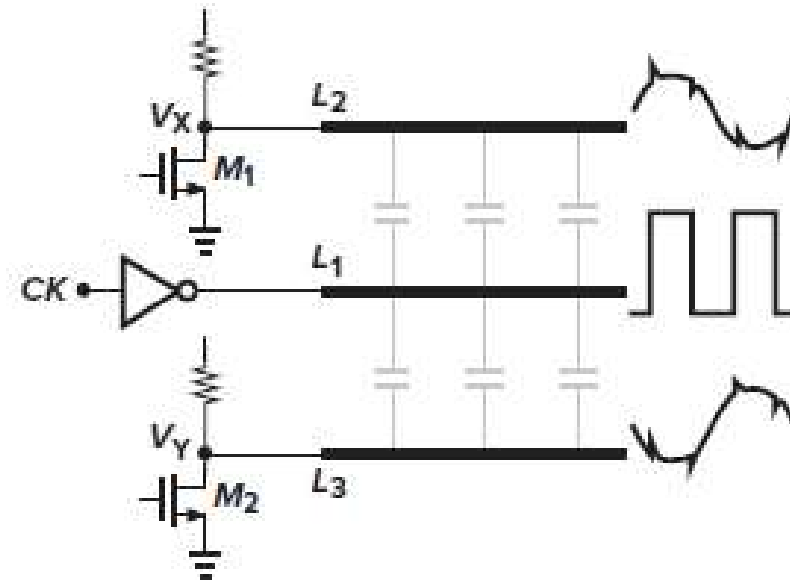


(b)

Effect of Coupling Noise

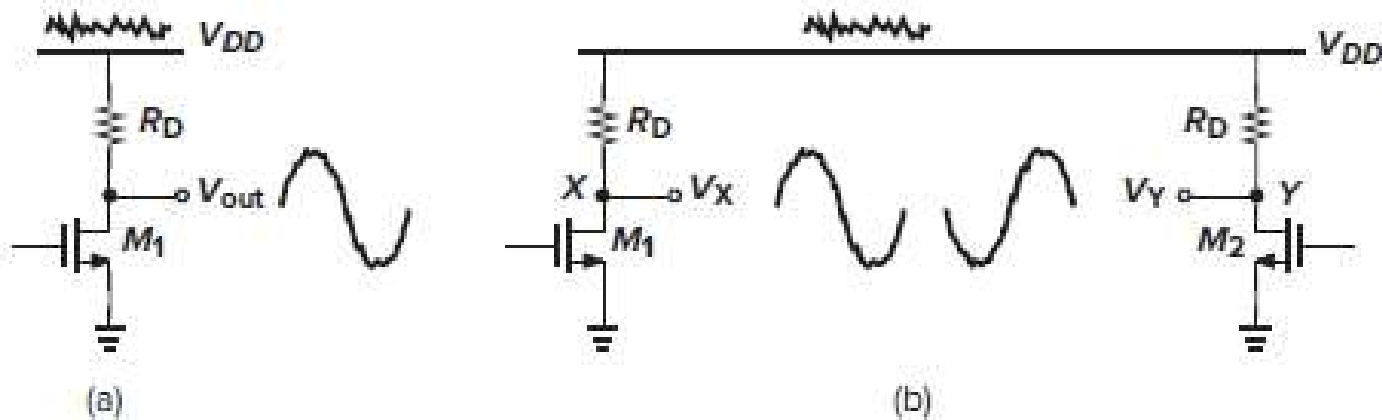


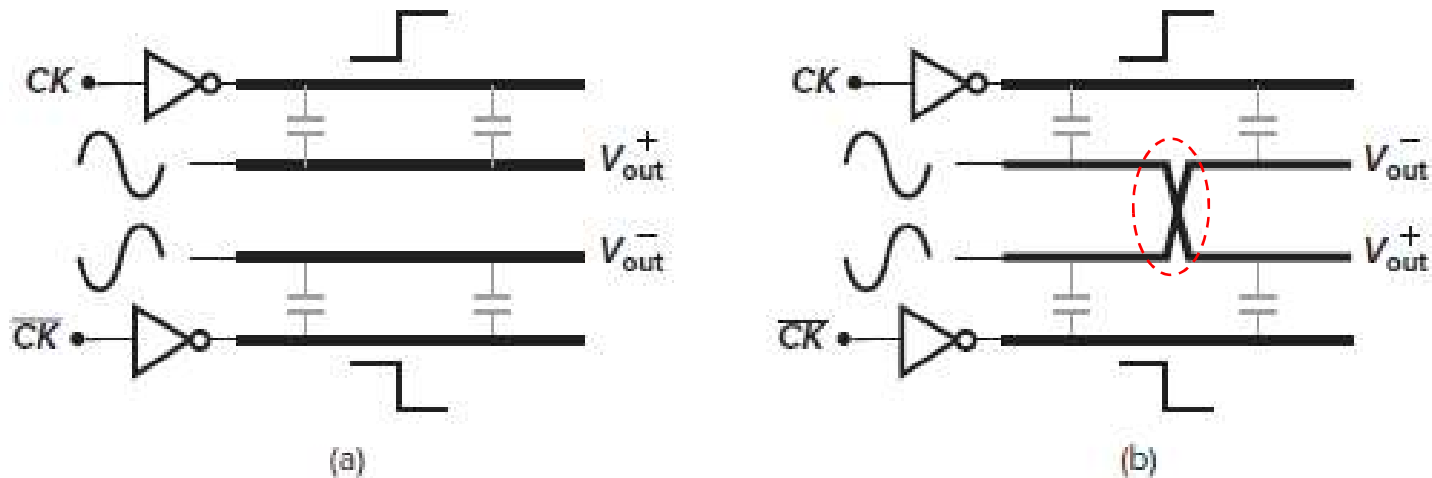
Supply gain: $A_{VD} = \Delta V_{out} / \Delta V_{DD}$




A layout trick to reduce the coupling

Differential Circuits



Pseudo-differential

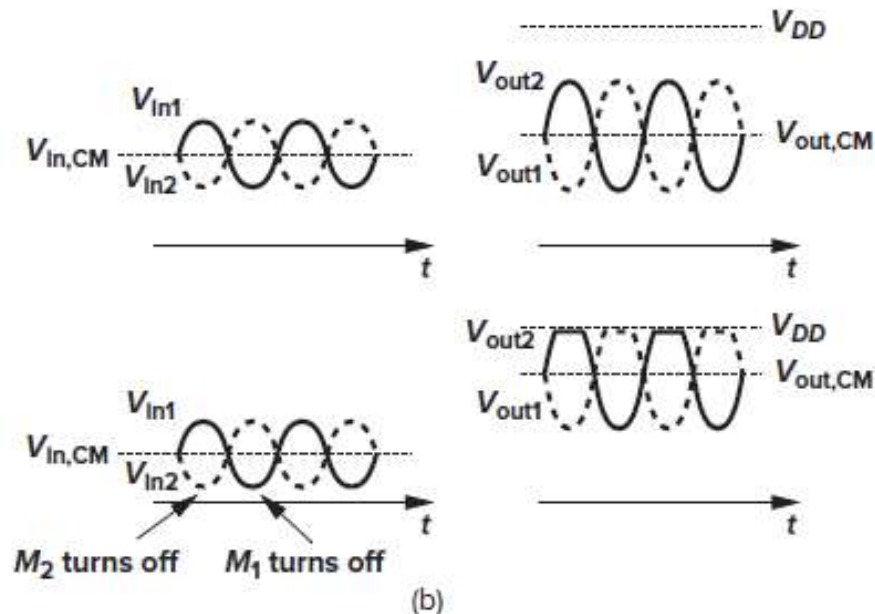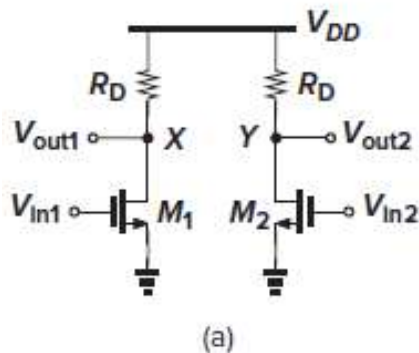




Differential pair

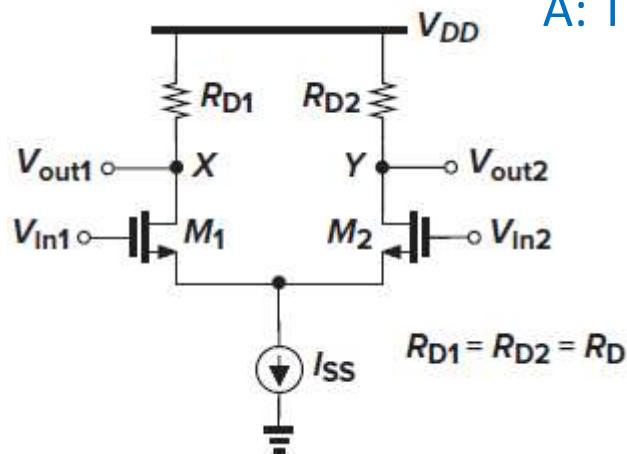

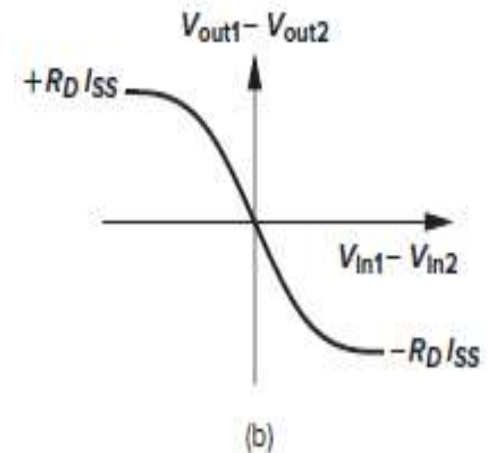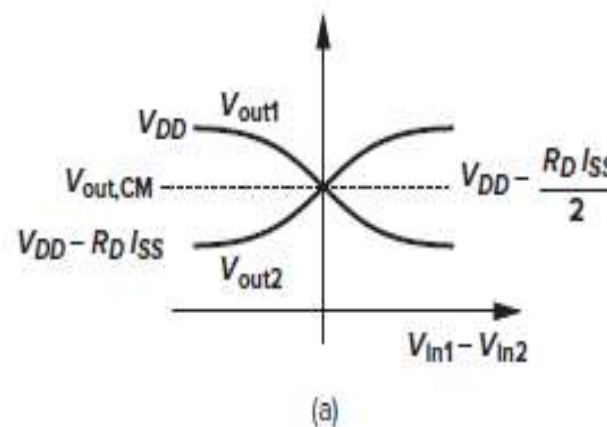Q: What's the difference between these two cases?
A: Their DC current are different!!



Differential Pair

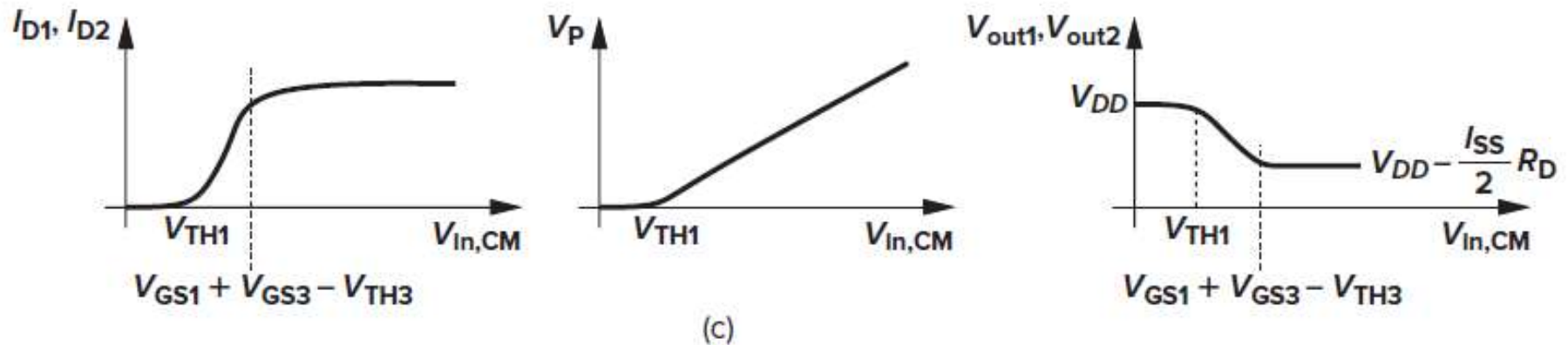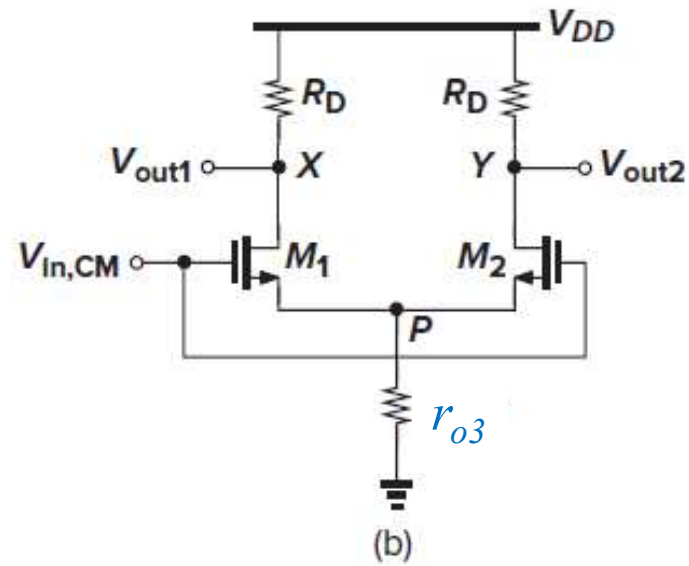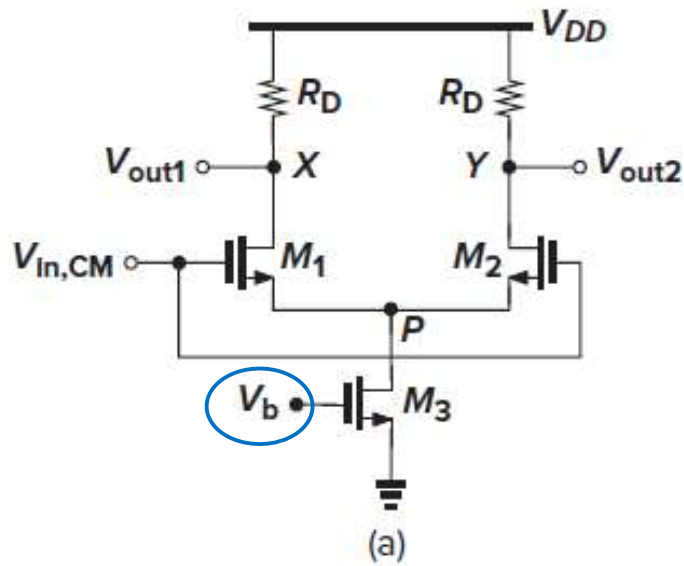

Input common-mode voltage ($V_{in,CM}$):

$$\underline{V_{GS1} + (V_{GS3} - V_{TH3})} \leq V_{in,CM} \leq \min \left[V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH}, V_{DD} \right]$$

先確認工作區!!


Differential Pair

從大訊號開始

→ 電流公式

→ g_m

→ g_m 近似式

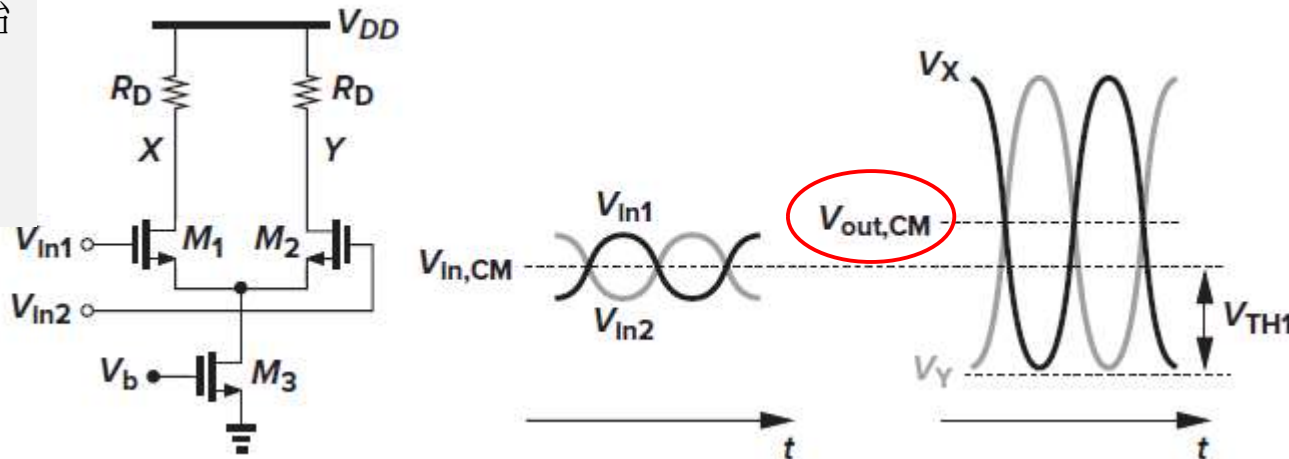

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

Actually, it is an error term for approximation

$$= \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS} (V_{in1} - V_{in2})} \sqrt{1 - \frac{\mu_n C_{ox} (W/L)}{4I_{SS}} (V_{in1} - V_{in2})^2}$$

$$(V_{in1} - V_{in2})^2 \ll 4I_{SS} / [\mu_n C_{ox} (W/L)]$$


(see next page)

$$\frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - 2\Delta V_{in}^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - \Delta V_{in}^2}}$$

$$I_{D1} - I_{D2} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} (V_{in1} - V_{in2})$$

$$|A_v| = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} R_D = g_m R_D$$

Differential Pair (Supplement)

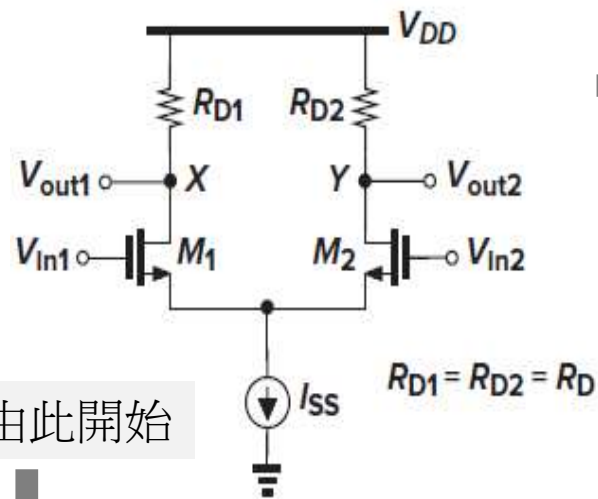

由此開始

$$(V_{GS} - V_{TH})^2 = \frac{I_D}{\frac{1}{2}\mu_n C_{ox} \frac{W}{L}}$$

$$V_{GS} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH}$$

$$V_{in1} - V_{in2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}}$$

$$\frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - I_{SS} = -2\sqrt{I_{D1}I_{D2}}$$

$$4I_{D1}I_{D2} = I_{SS}^2 - 2I_{SS}K_n\Delta V_{in}^2 + K_n^2\Delta V_{in}^4, \Delta V_{in} = V_{in1} - V_{in2}$$

$$4I_{D1}I_{D2} = (I_{D1} + I_{D2})^2 - (I_{D1} - I_{D2})^2 = I_{SS}^2 - (I_{D1} - I_{D2})^2$$

$$(I_{D1} - I_{D2})^2 = I_{SS}^2 - 4I_{D1}I_{D2}$$

$$= -K_n^2\Delta V_{in}^4 + 2I_{SS}K_n\Delta V_{in}^2$$




$$(I_{D1} - I_{D2})^2 = -\frac{1}{4}\left(\mu_n C_{ox} \frac{W}{L}\right)^2 (V_{in1} - V_{in2})^4 + I_{SS}\mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2$$

$$I_{D1} - I_{D2} = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

$$= \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} (V_{in1} - V_{in2}) \sqrt{1 - \frac{\mu_n C_{ox} (W/L)}{4I_{SS}} (V_{in1} - V_{in2})^2}$$

$$\frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - 2\Delta V_{in}^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - \Delta V_{in}^2}}$$




Differential Amplifier

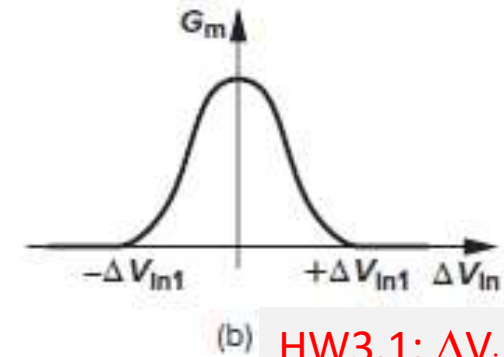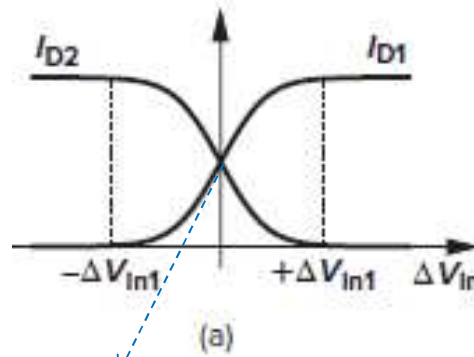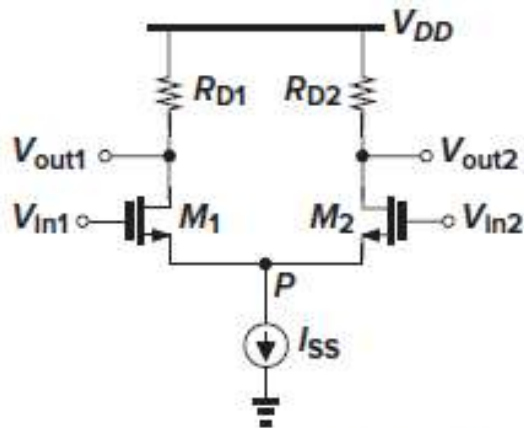




HW3.1: $\Delta V_{in1} = ?$

$$(V_{GS} - V_{TH})_{1,2} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$
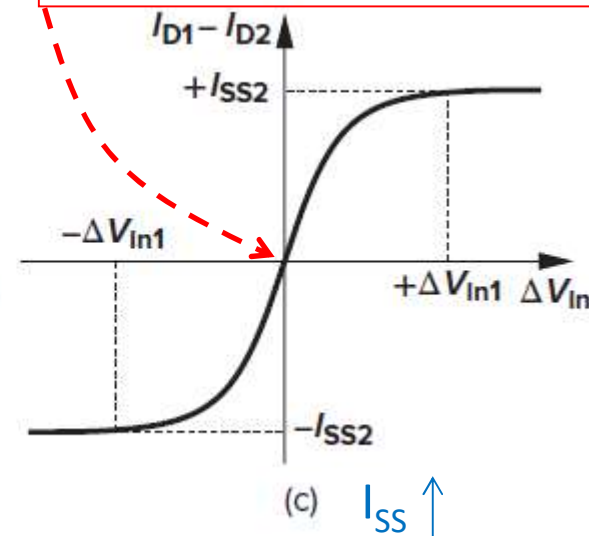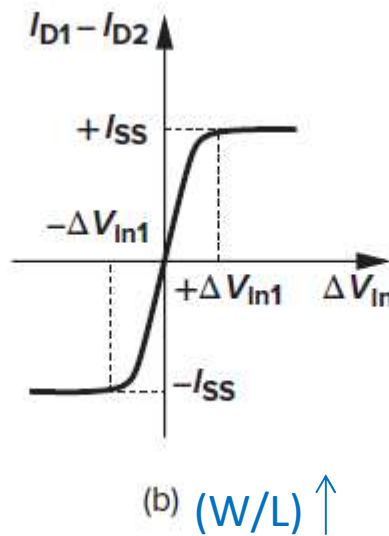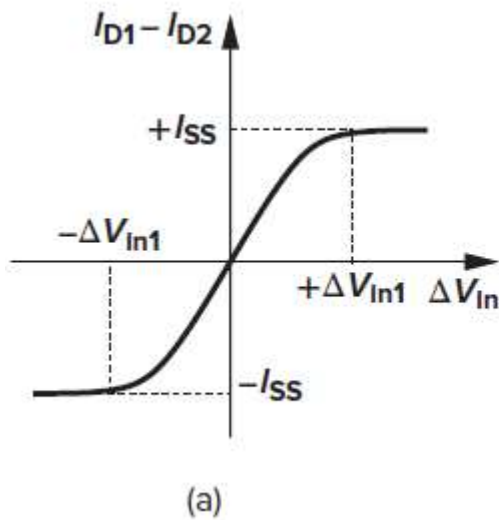
$$I_{D1} - I_{D2} = \sqrt{\mu_n C_{ox} \frac{W}{L}} I_{SS} (V_{in1} - V_{in2})$$



Small Signal Analysis

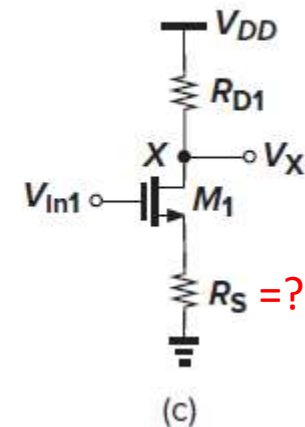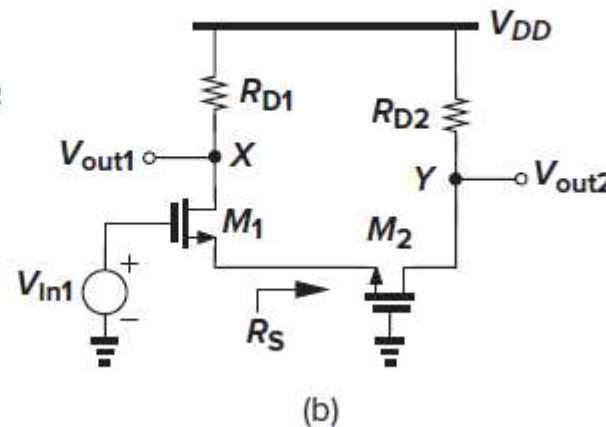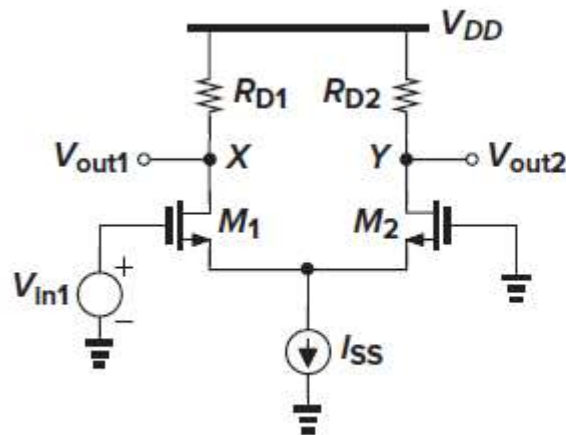

Using superposition:

Find V_{out} by V_{in1} firstly, then by V_{in2} .

Finally, add both results

$$\frac{V_X}{V_{in1}} = \frac{-R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$\frac{V_Y}{V_{in1}} = \frac{R_D}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$$


$$(V_X - V_Y)|_{\text{Due to } V_{in1}} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} V_{in1}$$

If $M_1=M_2$ and $R_{D1}=R_{D2}$


$$(V_X - V_Y)|_{\text{Due to } V_{in1}} = -g_m R_D V_{in1}$$

$$(V_X - V_Y)|_{\text{Due to } V_{in2}} = g_m R_D V_{in2}$$
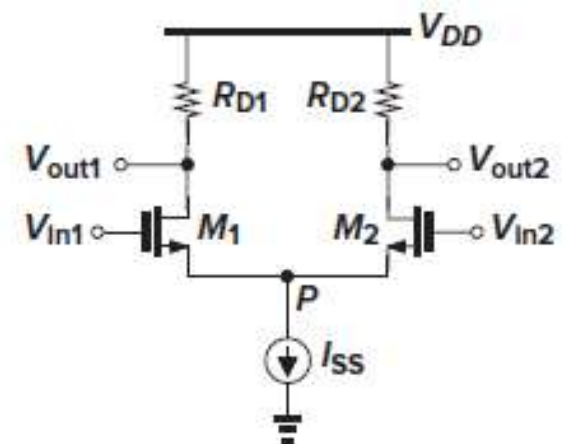
$$\frac{(V_X - V_Y)_{tot}}{V_{in1} - V_{in2}} = -g_m R_D$$





Differential Amplifier


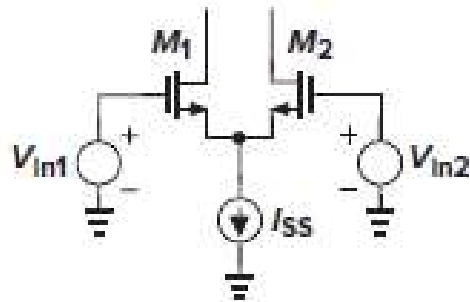


Here we introduce two kinds of input:

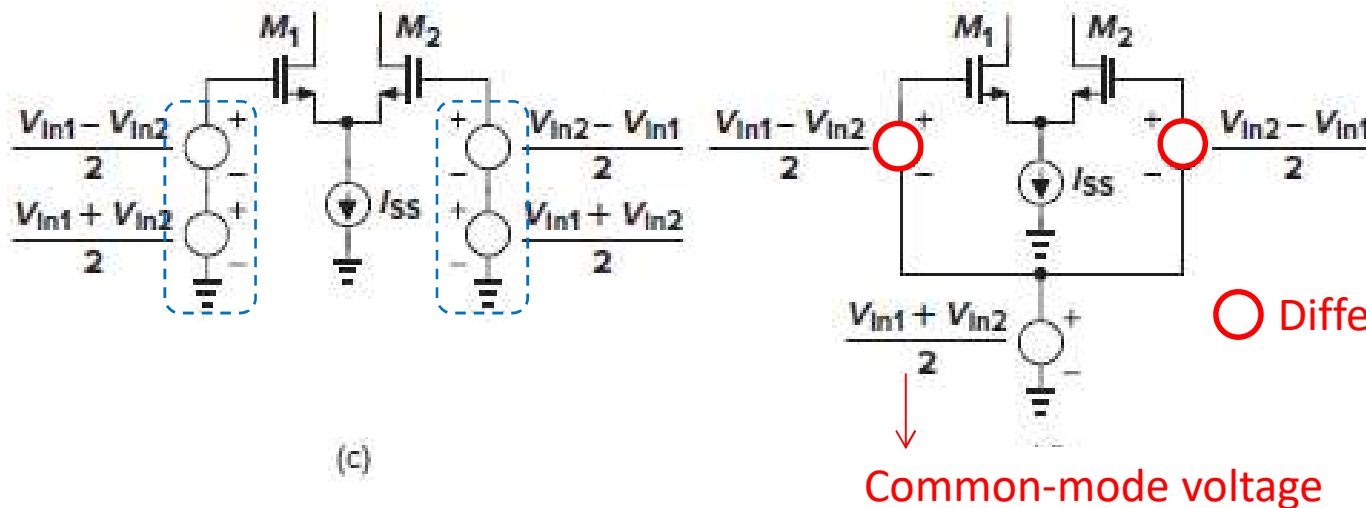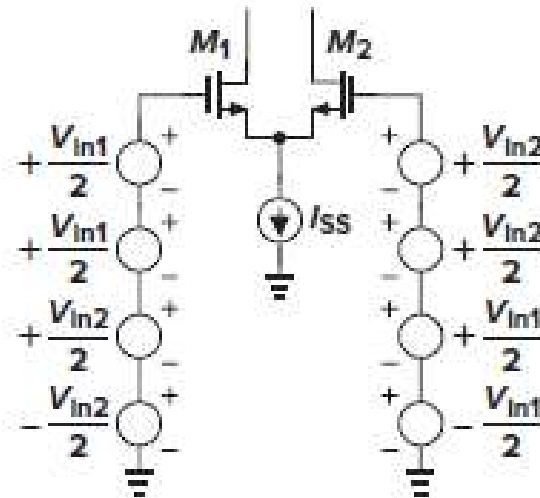1. Common-mode input (large signal)
2. Differential input (small signal)



Degenerated Differential Pair

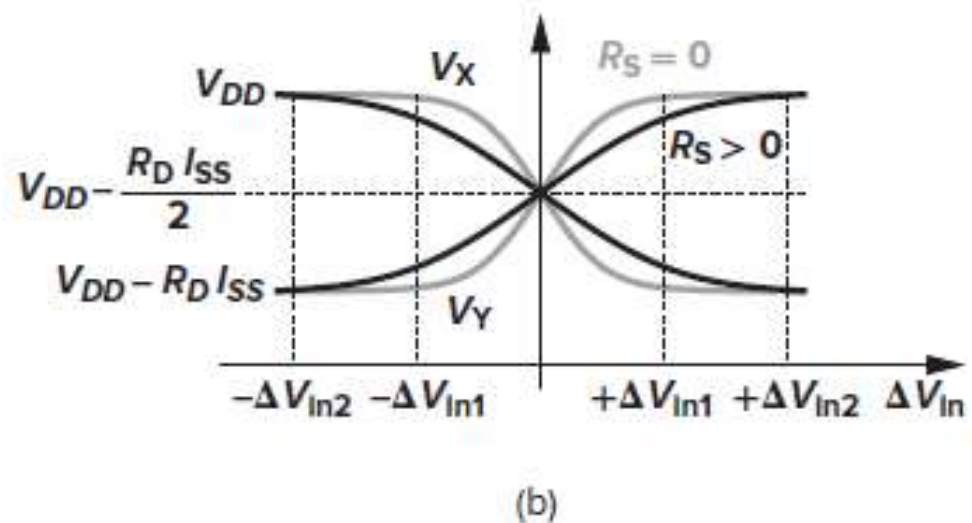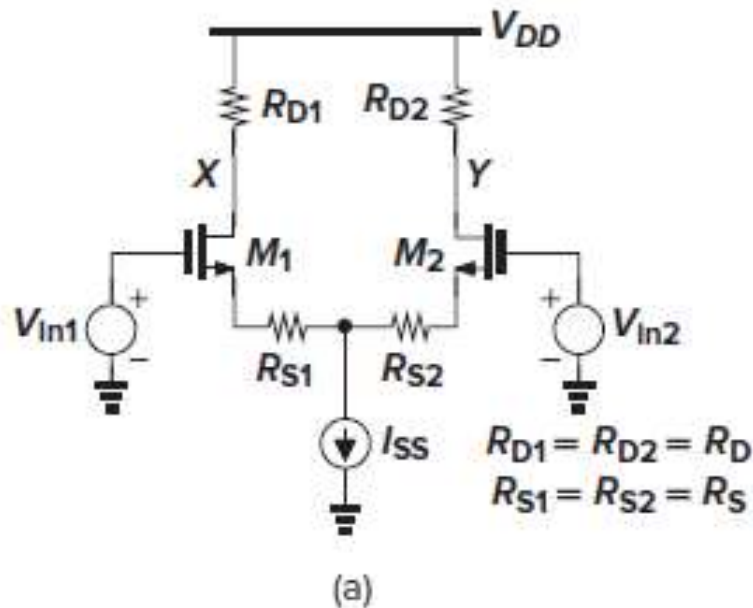


$$|A_v| = \frac{R_D}{\frac{1}{g_m} + R_S}$$

$$|A_v| = \frac{g_m}{1 + g_m R_S} R_D$$

What do we get from the degenerated differential pair?

- (1) DC Gain is reduced
- (2) Input range is increased

Differential Pair with CM Input

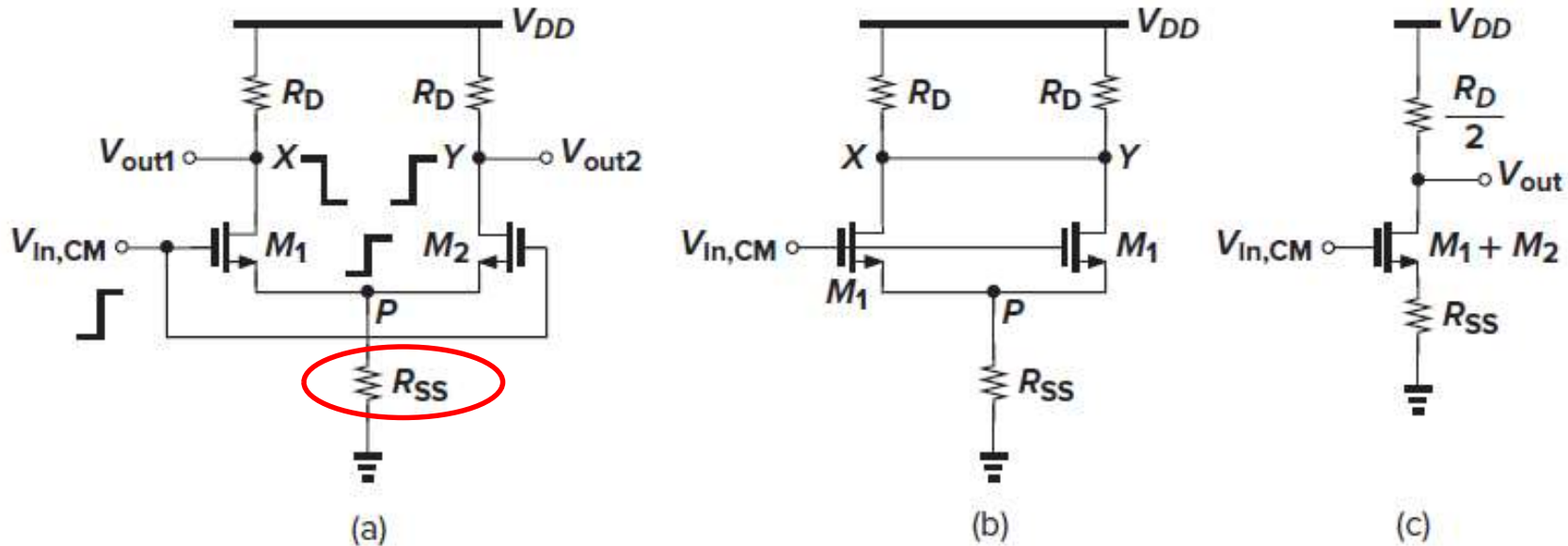


$$A_{v,CM} = \frac{V_{out,CM}}{V_{in,CM}} = -\frac{(2g_m)}{1 + (2g_m)R_{SS}} \frac{R_D}{2} = -\frac{g_m}{1 + 2g_m R_{SS}} R_D$$

$A_{v,CM}$: The gain that common-mode input variation is translated into the output common mode ($V_{i,cm} \Rightarrow V_{o,cm}$)

A_{CM-DM} : The gain that common-mode input variation is translated into the differential output ($V_{i,cm} \Rightarrow V_{o,diff}$)

CMRR (M1≠M2)

Small signal analysis

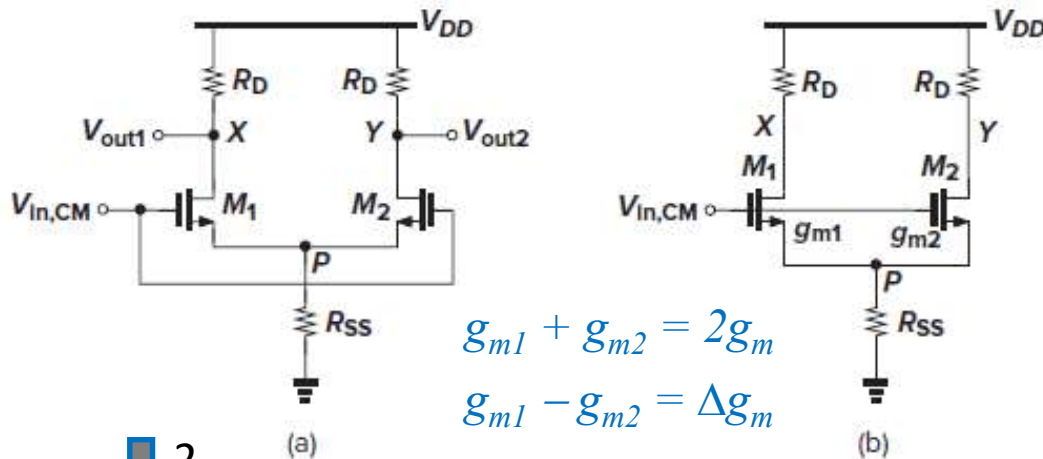

↓ 1

$$(g_{m1} + g_{m2})(V_{in,CM} - V_P)R_{SS} = V_P$$

$$V_P = \frac{(g_{m1} + g_{m2})R_{SS}}{(g_{m1} + g_{m2})R_{SS} + 1} V_{in,CM}$$

$$V_X = -g_{m1}(V_{in,CM} - V_P)R_D$$

$$= \frac{-g_{m1}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$

$$V_Y = -g_{m2}(V_{in,CM} - V_P)R_D$$

$$= \frac{-g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$

$$V_X - V_Y = -\frac{g_{m1} - g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$

$$A_{CM-DM} = -\frac{\Delta g_m R_D}{(g_{m1} + g_{m2})R_{SS} + 1}$$

↓ 2

$$|A_{DM}| = \frac{R_D}{2} \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{1 + (g_{m1} + g_{m2})R_{SS}}$$

$$\approx g_m R_D$$


$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right|$$

$$CMRR = \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{2\Delta g_m}$$

$$\approx \frac{g_m}{\Delta g_m} (1 + 2g_m R_{SS})$$

CMRR ($R_{D1} \neq R_{D2}$)

Small signal analysis

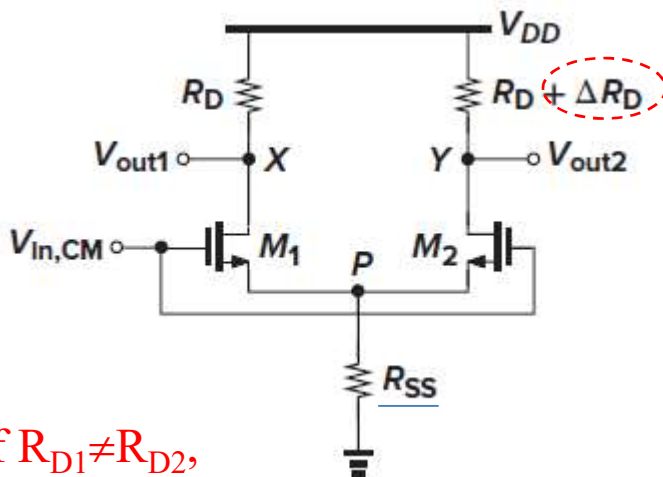

If $R_{D1} \neq R_{D2}$,


$$\Delta V_P = \frac{R_{SS}}{R_{SS} + \frac{1}{2g_m}} \Delta V_{in,CM}$$

$$\Delta V_X = -\Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} R_D$$


$$\Delta V_Y = -\Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} (R_D + \Delta R_D)$$

$$A_{CM-DM} = \frac{V_{out2} - V_{out1}}{\Delta V_{in,CM}} = -\frac{g_m \Delta R_D}{1 + 2g_m R_{SS}}$$

$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right| = \frac{R_D}{\Delta R_D} (1 + 2g_m R_{SS})$$

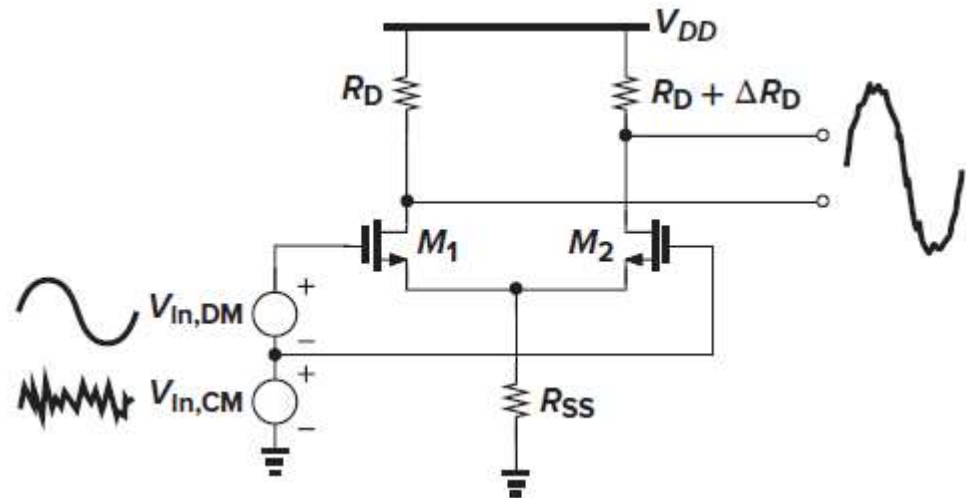


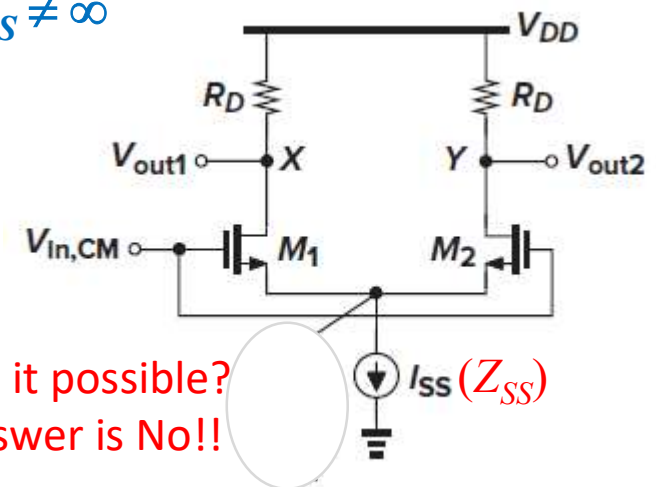If g_m or R_D has mismatch, common-mode input variation will cause diff. output change if $R_{SS} \neq \infty$



Q: $R_{SS} = \infty$, is it possible?
If Z_{SS} , the answer is No!!

CMRR by Mismatch

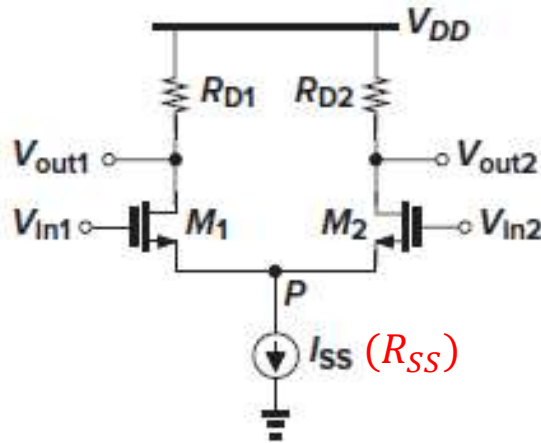

$$CMRR = \frac{A_{DM}}{A_{CM-DM}}$$

$$\underline{R_{D1} \neq R_{D2}}$$

$$CMRR = \frac{R_D}{\Delta R_D} (1 + 2g_m R_{SS})$$

$$\underline{g_{m1} \neq g_{m2}}$$



$$CMRR = \frac{g_m}{\Delta g_m} (1 + 2g_m R_{SS})$$



$$CMRR = \left(\frac{g_m}{\Delta g_m} + \frac{R_D}{\Delta R_D} \right) (1 + 2g_m R_{SS})$$

Q: How to improve CMRR?

Differential Amplifiers

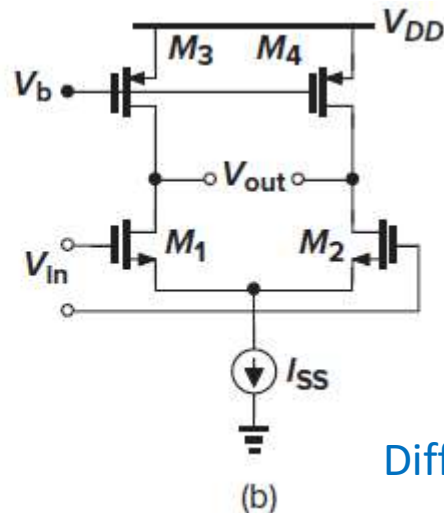
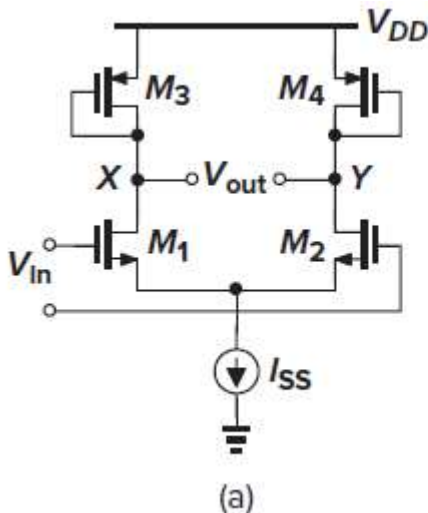


Differential DC gain:


(a)
$$A_V = \frac{V_Y - V_X}{V_{in}} \sim \frac{g_{m1,2}}{g_{m3,4}}$$

(b)
$$A_V = \frac{V_Y - V_X}{V_{in}} \sim g_{m1,2}(r_{o3,4} || r_{o1,2})$$


(c)
$$A_V = \frac{V_Y - V_X}{V_{in}} \sim g_{m1,2}(R_{1,2} || r_{o3,4} || r_{o1,2})$$

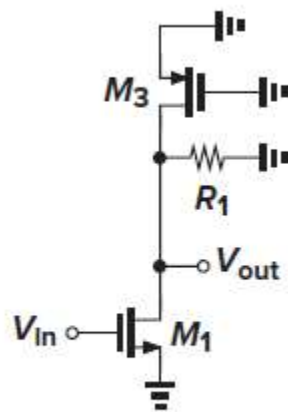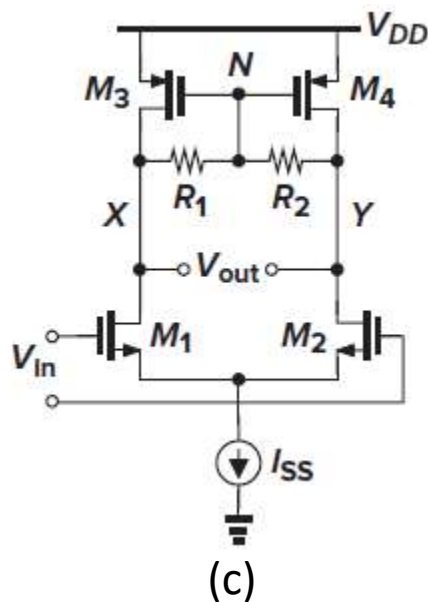


Differential Amplifiers

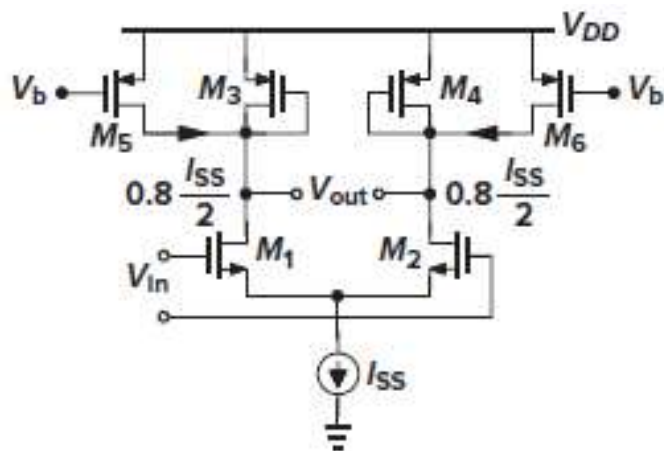

Amp (a)

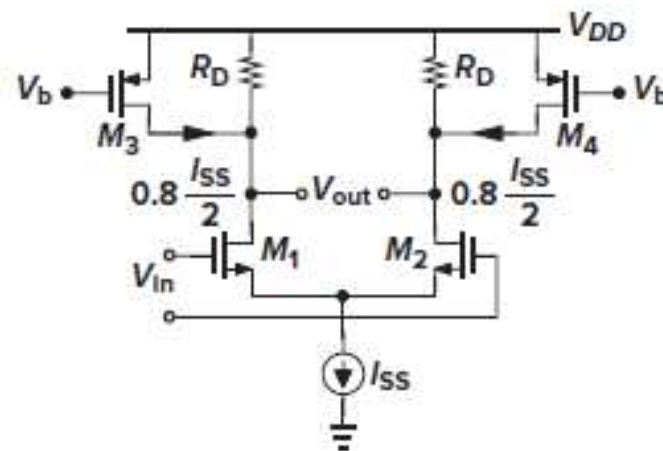

Amp (b)

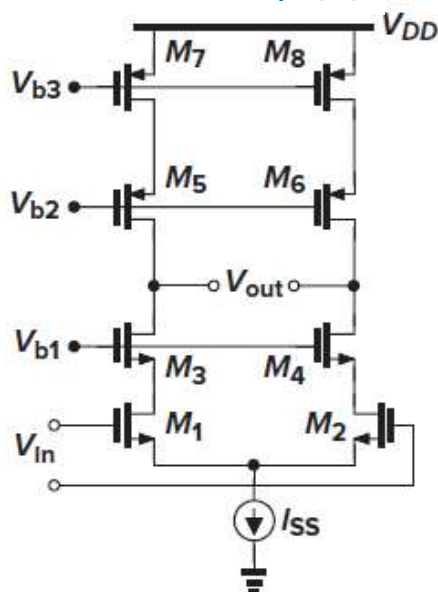

Amp (c)



Two DC design parameters:

- Differential gain
- Output resistance

Appendix:

- Voltage Gain Amplifier
- Gilbert Cell

Variable Gain Amplifier (VGA)

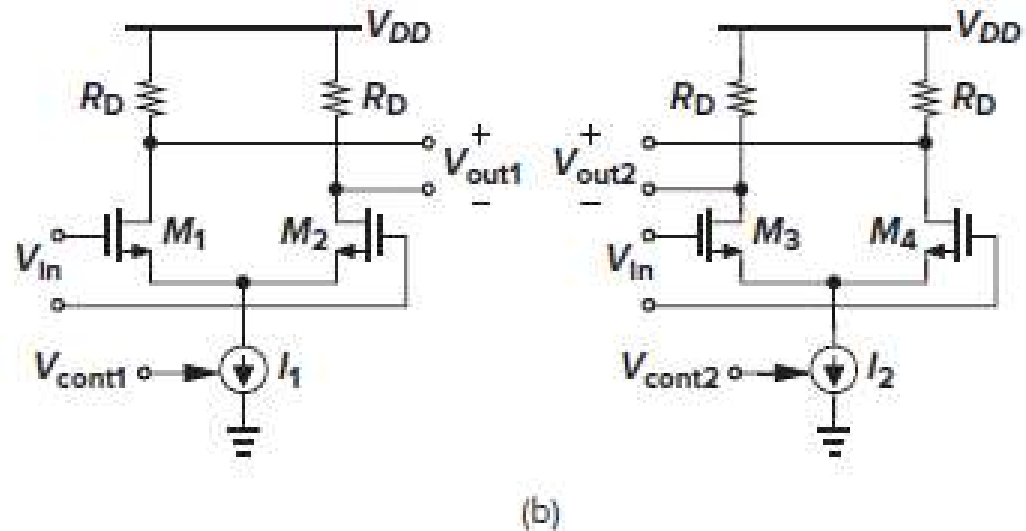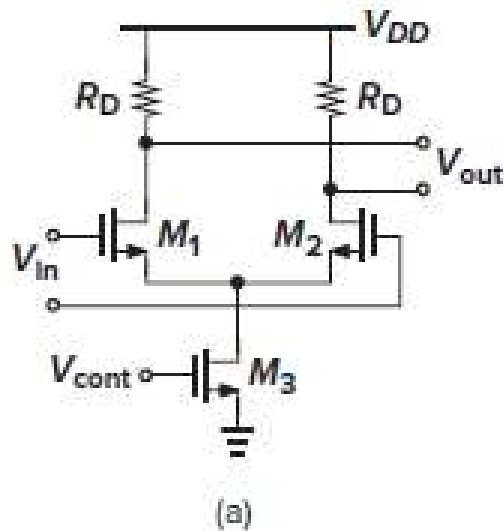

$$A_V = \frac{V_{out}}{V_{in}} \sim g_{m1,2} R_D$$

$$g_{m1,2} = \sqrt{2K_{1,2}I_{D1,2}}$$

$$I_{D1,2} = \frac{I_3}{2} = \beta_3 (V_{cont} - V_{TH3})^2$$

$$g_{m1,2} = \sqrt{2K_{1,2}\beta_3} \frac{(V_{cont} - V_{TH3})}{\Delta V_{cont}}$$

$$V_{out1} = g_{m1,2} R_D V_{in}$$


$$= R_D \sqrt{2K_{1,2}\beta_3} \Delta V_{cont1} V_{in}$$

$$\underline{V_{out1} = G \Delta V_{cont1} V_{in}}$$


Two observations:

- Gain can be adjusted
- Multiplication of two analog signals

Gilbert Cell (1)

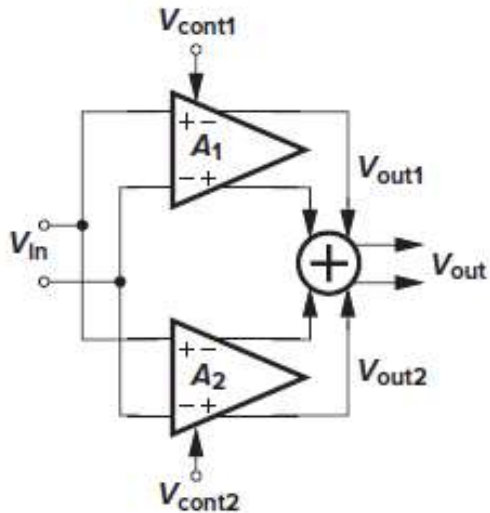


(a)

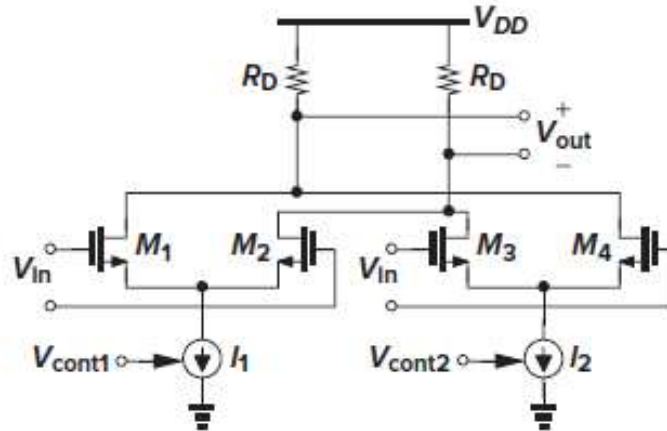


(b)

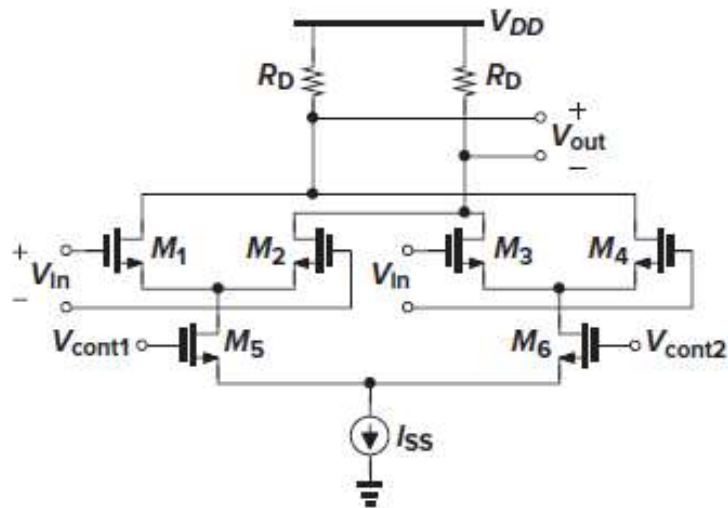
$$\Delta V_{out} = G_1 \Delta V_{cont1} \Delta V_{in} + G_2 \Delta V_{cont2} \Delta V_{in}$$







(c)

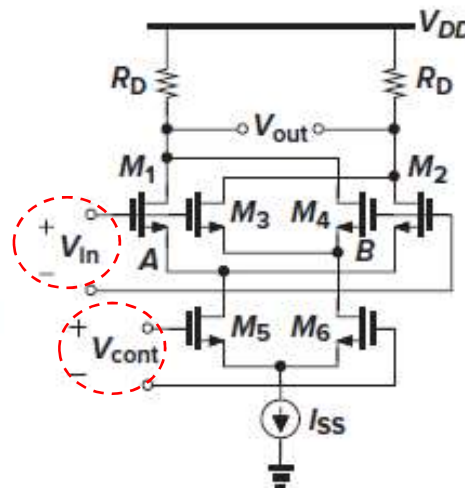

(d)

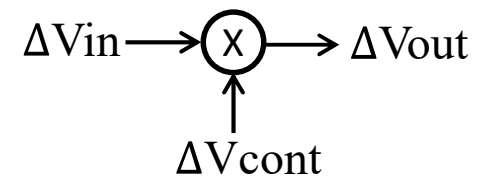

Gilbert Cell (2)

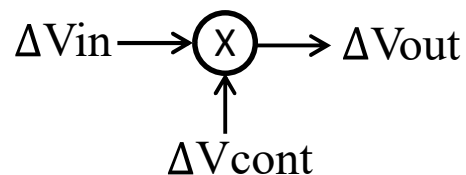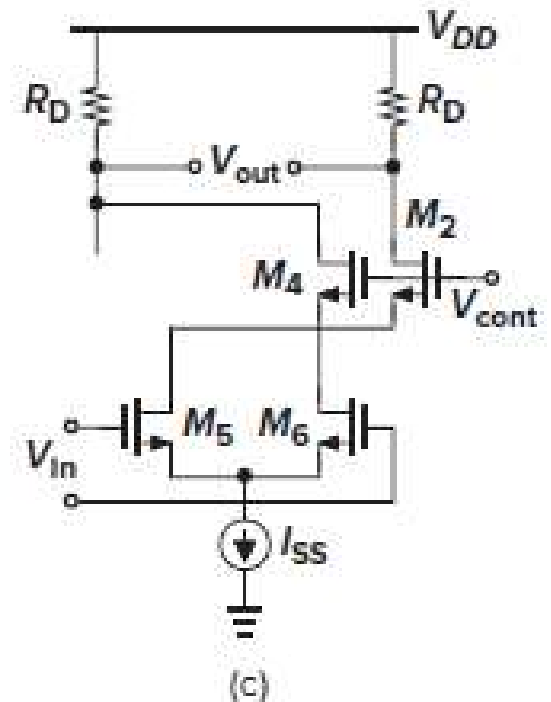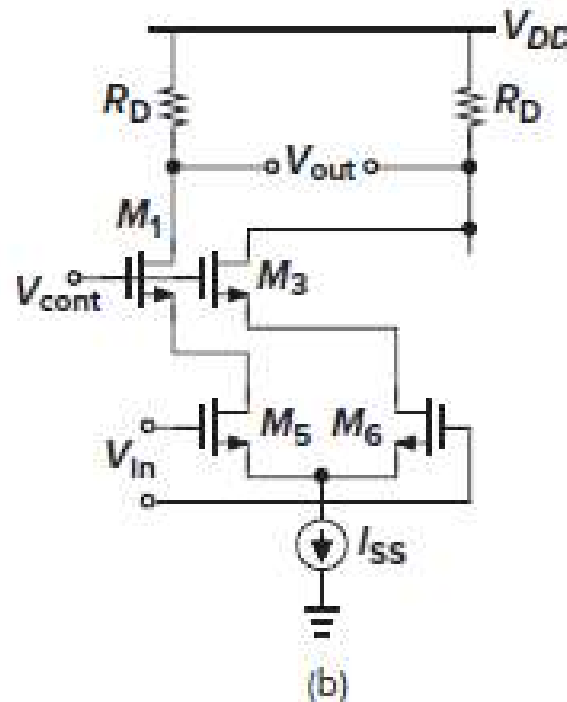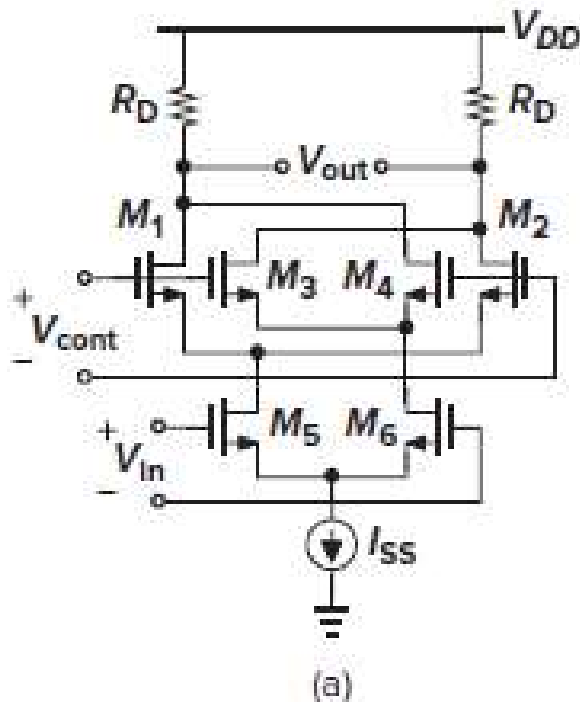

V_{cont} is much larger
 $V_{out} \sim +G V_{in}$

V_{cont} is much smaller
 $V_{out} \sim -G V_{in}$