

HW8.1 (40 points)

如圖 8.1 所示，是一個 Two-Satge Opamp 的 Miller compensation 相關電路。

- (a) 請列出在使用 Miller Capacitor (C) 做極點分離之頻率補償時，若沒有 R_Z 的問題是甚麼？請說明此問題的原因為何？
- (b) 在滿足極點—零點抵消之情況下，假設 C_E 可忽略， M_9, M_{11} ($g_m, W/L, I_d$), C_C , and C_L 皆是已知。請設計 M_{13}, M_{14}, M_{15} and I_1 。

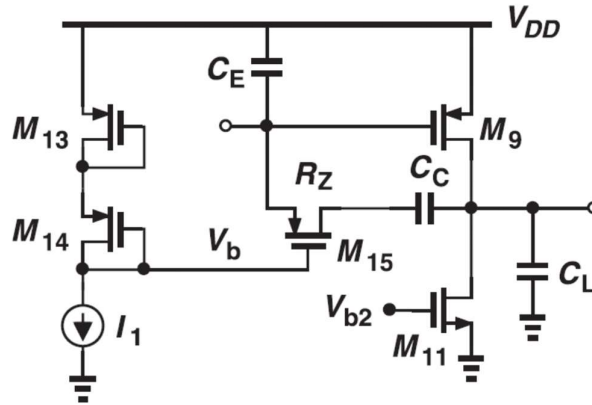


Fig. 8.1

HW8.2 (30 points)

Suppose the open-loop transfer function of a two-stage op amp is expressed as

$$H_{open}(s) = \frac{A_0 \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

- (a) 假如 $\omega_{p2} = 10A_0\omega_{p1}$ and $\omega_z = 10\omega_{p2}$ ，請劃出 $H_{open}(s)$'s bode plots for Magnitude and phase 並標示出 unit-gain frequency $\omega_u = ?$.
- (b) 承上，其 phase margin (PM) = ?
- (c) 若是 $\omega_{p2} = A_0\omega_{p1}$ and $\omega_z = 2\omega_{p2}$ ，其 phase margin (PM) = ?

HW8.3 (15 points)

The two-stage op amp of Fig. 8.3 incorporates Miller compensation to reach a phase margin of 45° . Estimate the compensation capacitor value. Using all transistors' small-signal parameters (g_m , r_o).

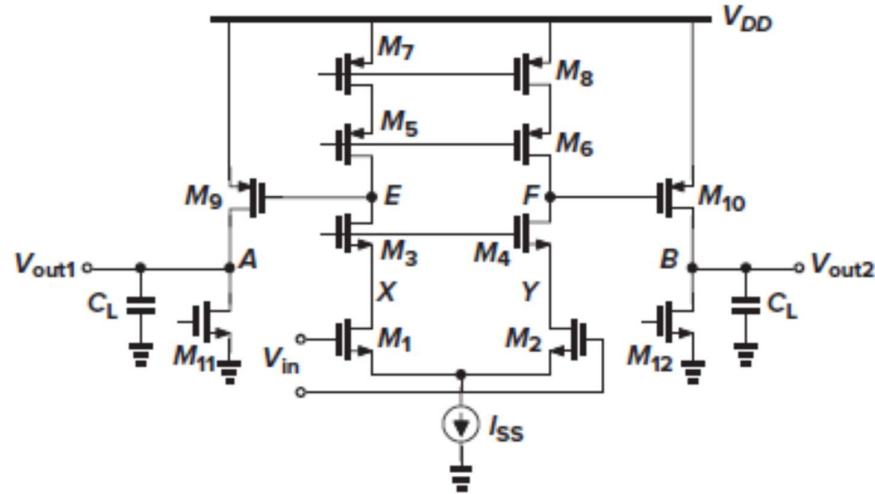


Fig. 8.3

HW8.4 (15 points)

Consider the transimpedance amplifier shown in Fig. 8.4, where $R_D = 1\text{ k}\Omega$, $R_F = 10\text{ k}\Omega$, $g_{m1} = g_{m2} = 1/(100\Omega)$, and $C_A = C_X = C_Y = 100\text{ fF}$. Neglecting all other capacitances and assuming that $\lambda = \gamma = 0$, compute the phase margin of the circuit. (Hint: break the loop at node X.)

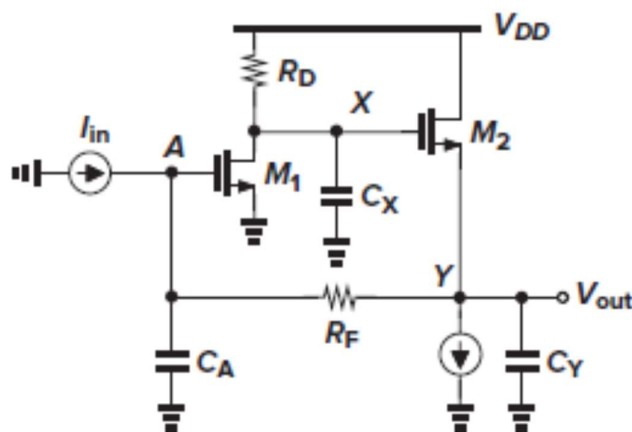


Fig. 8.4