

Homework 2 (Due date: 10/05)

HW2.1: (20 points)

Using small-signal parameters to find the voltage gain and output resistance of each amplifier in Fig 2.1 (*channel length modulation* and *body effect* cannot be ignored).

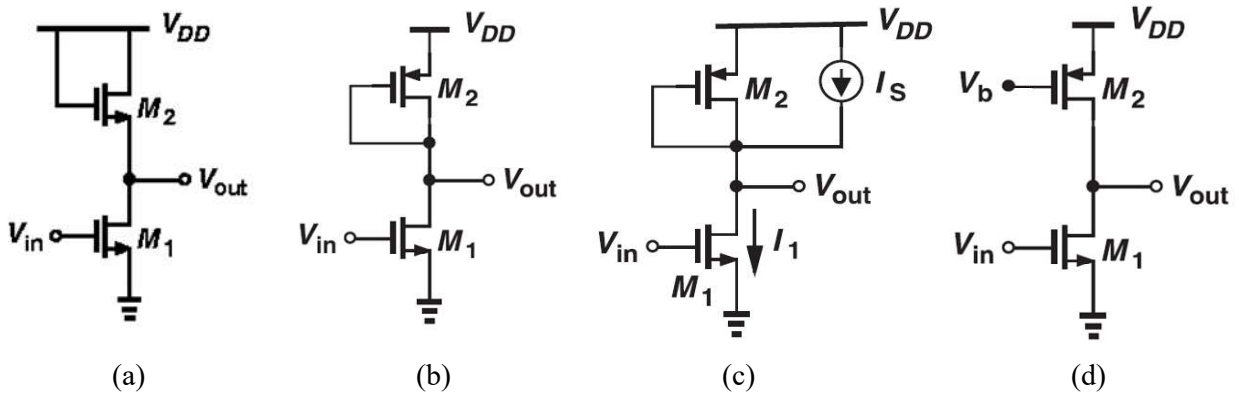


Fig. 2.1

HW2.2: (20 points)

Using small-signal parameters to derive the output resistance (R_{out}) in Fig. 2.2.

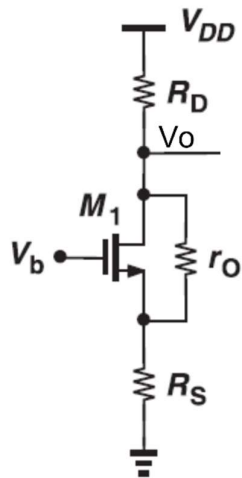


Fig. 2.2

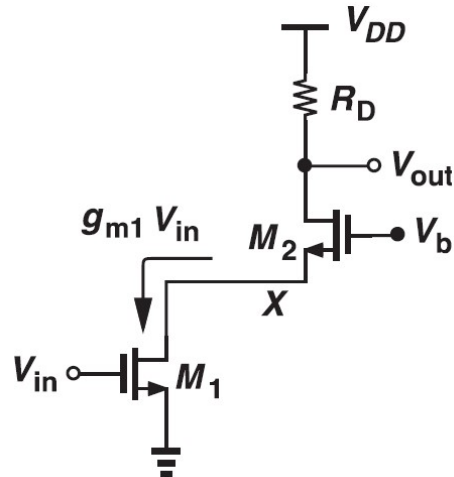


Fig. 2.3

HW2.3: (30 points)

Fig. 2.3 shows a common-gate circuit.


- If we define a minimum output voltage, $V_{out,min}$, how do you find out the valid input range of V_{in} ?
- Calculate the voltage gain and output resistance.

Homework 2 (Due date: 10/05)


HW2.4: (30 points)

Calculate the voltage gain and output resistance of circuits in Fig. 2.4.

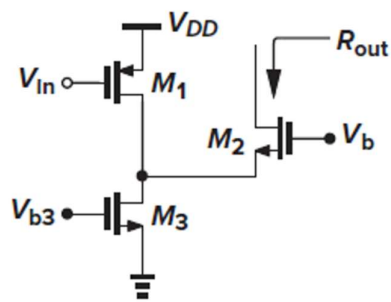Note: Fig. 2.4(a) only needs to calculate the output resistance.




(a)

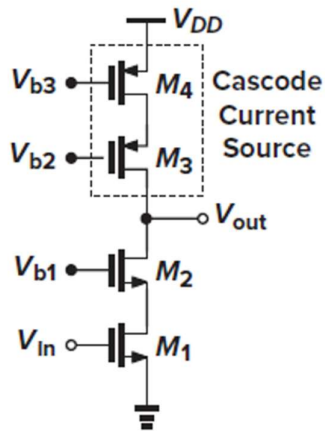

(b)

Fig. 2.4

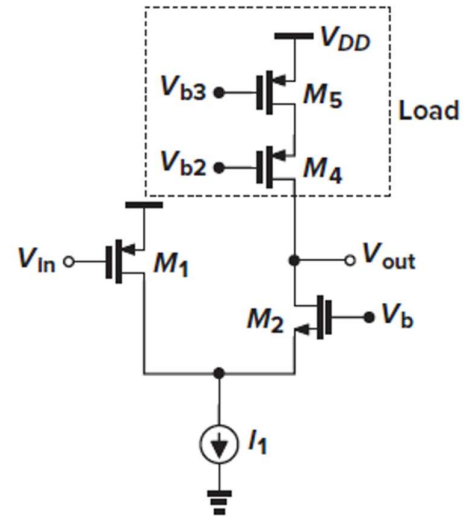

(c)