

(if not specified,  $v_d = v_1 - v_2$ ,  $v_{cm} = (v_1 + v_2)/2$  for differential amplifiers)

必須要有計算過程。

- (18%) Consider the Widlar current-source circuit with multiple output transistors shown in Figure 1. Assume  $V_{BE1(\text{on})} = 0.7 \text{ V}$ ,  $R_1 = 20 \text{ k}\Omega$ , and all base currents are negligible. (a) Find the value of  $I_{REF}$  (4%). (b) Determine values of  $R_{E2}$  such that  $I_{O2} = 20 \mu\text{A}$  (4%). (c) Determine the value of  $I_{O3}$  if  $R_{E3} = 2 \text{ k}\Omega$  (5%). (d) Assuming that  $\beta = 120$  and  $V_A = 100 \text{ V}$ , what is the output resistance of this circuit (equivalent resistance looking into the collector of transistor  $Q_3$ ) (5%)?

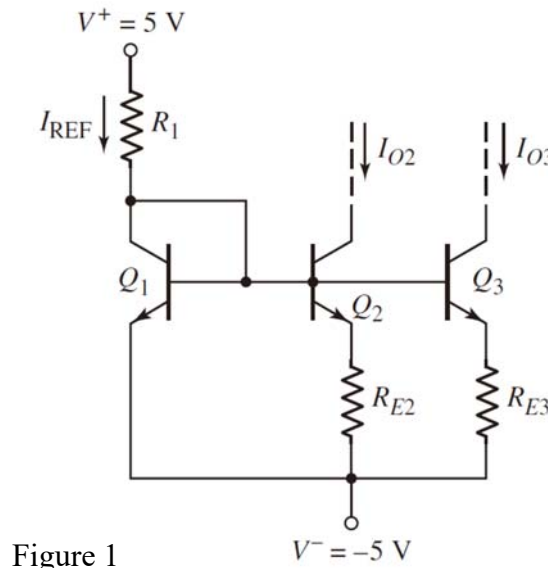


Figure 1

- (15%) The parameters of the transistors in Figure 2 are  $V_{TN} = 0.6 \text{ V}$ ,  $V_{TP} = -0.6 \text{ V}$ ,  $k'_n = 80 \mu\text{A/V}^2$ ,  $k'_p = 40 \mu\text{A/V}^2$ , and  $\lambda_n = \lambda_p = 0.02 \text{ V}^{-1}$ . The width-to-length ratios of  $M_1$  and  $M_2$  are 50, and those of all other transistors are 100. The values of  $V_{GSQ}$  is such that  $I_{DQ1} = 80 \mu\text{A}$ , and all transistors are biased in saturation region. (a) Determine the effective resistance looking into the drain of  $M_3$ . (b) Determine the small signal voltage gain  $A_v = v_o/v_i$ . (c) What is the possible highest value of the output voltage  $V_o$ .

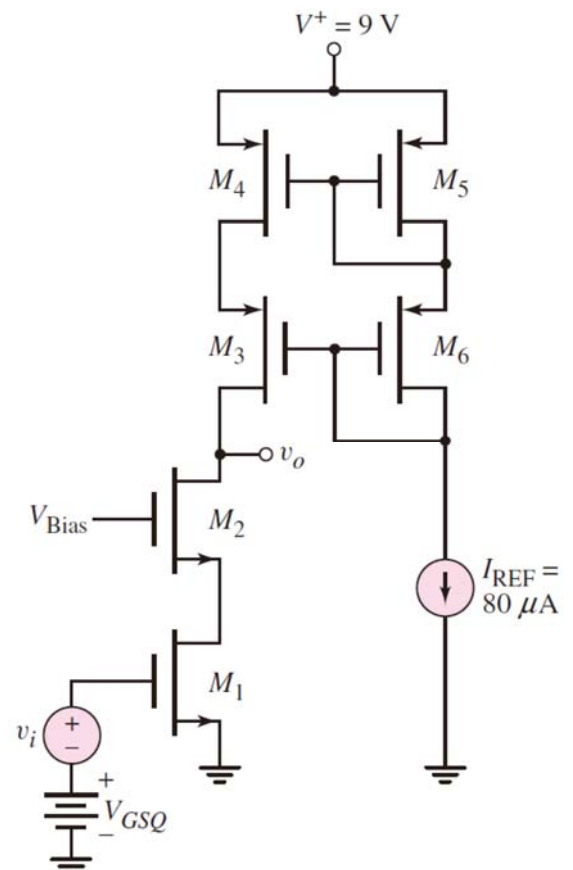


Figure 2

3. (17%) For the transistors in the circuit in Figure 3, the transistor parameters are  $K_n = 0.2 \text{ mA/V}^2$ ,  $V_{TN} = 2 \text{ V}$ , and  $\lambda = 0.02 \text{ V}^{-1}$ . (a) Determine the value of bias current  $I_Q$  (3%) and the output resistance looking into current mirror (4%). (b) Determine  $A_d = v_{o2}/v_d$  (5%). (c) Determine  $A_{cm} = v_{o2}/v_{cm}$  (5%).
4. (12%) Simplified input stage of uA741 is shown in Figure 4. (a) Use BJT small-signal parameters such as  $\beta_n$ ,  $\beta_p$ ,  $r_{\pi 1} \sim r_{\pi 4}$ ,  $g_{m1} \sim g_{m4}$  to write the equation of differential-mode input resistance  $R_{id}$  (6%). (b) If the supply voltage ( $V^+ \& V^-$ ) of uA741 is changed from  $\pm 15 \text{ V}$  to  $\pm 5 \text{ V}$ , will  $R_{id}$  become larger, smaller, or unchanged (2%)? Why (4%)?

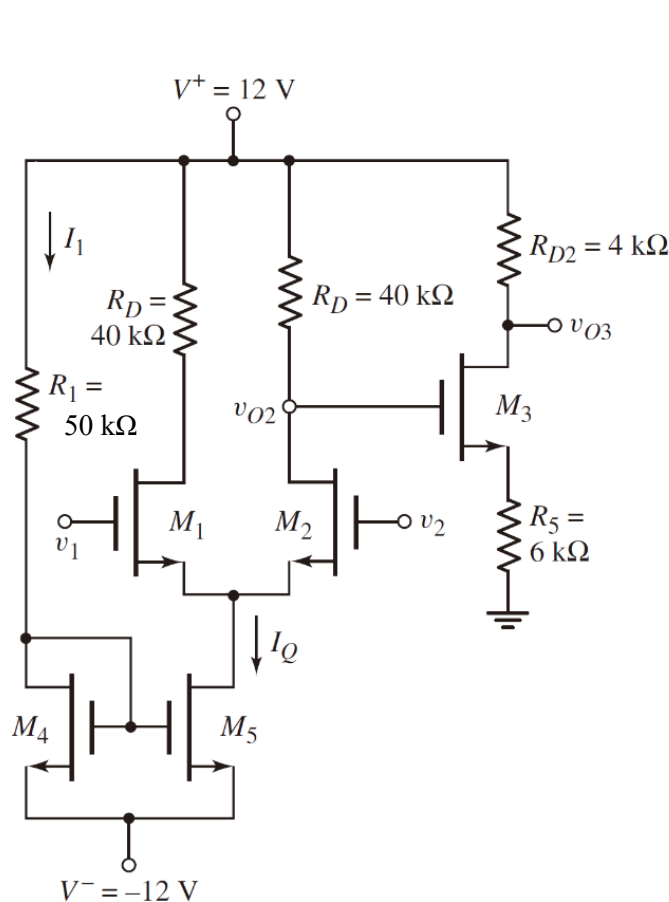


Figure 3

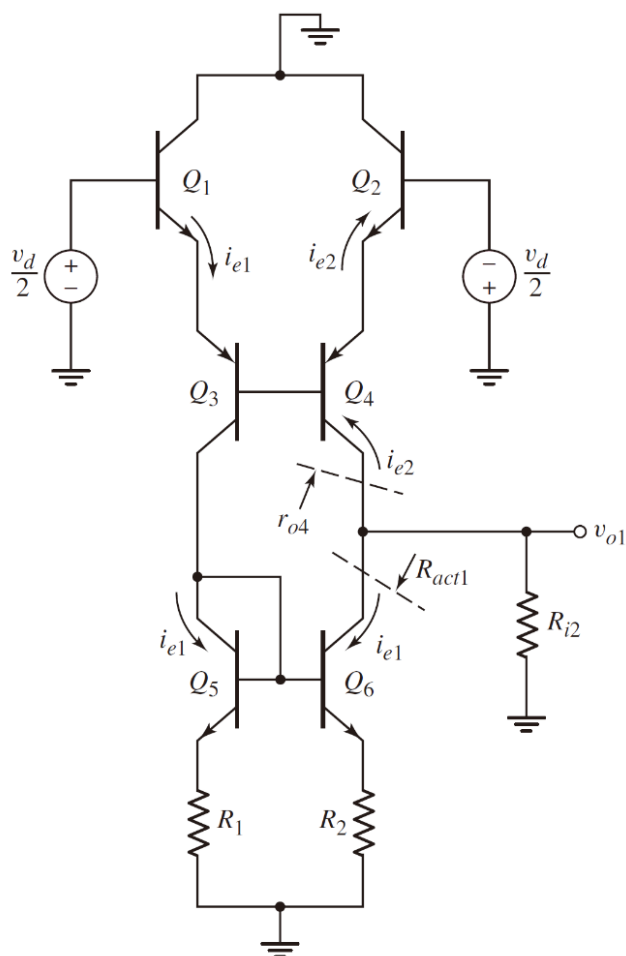


Figure 4

5. (20%) Consider the Darlington pair and output stage of the circuit in Figure 5. The parameters are  $I_{C7} = I_Q = 0.4 \text{ mA}$ ,  $I_{C8} = 2 \text{ mA}$ ,  $R_4 = 5 \text{ k}\Omega$ ,  $R_3 = 0.1 \text{ k}\Omega$ ,  $\beta = 100$  for all transistors and early voltages  $V_A = 80 \text{ V}$  for  $Q_1 \sim Q_7$  and  $Q_{11}$ . (a) Calculate the small-signal voltage gain of the differential amplifier ( $A_{v1} = v_{o2}/v_d$ ). (b) Determine the input resistance of the Darlington pair  $R_i$ . (c) Calculate the small-signal voltage gain of the Darlington pair ( $A_{v2} = v_{o3}/v_{o2}$ ). (d) Find the output resistance ( $R_o$ ).

 


Figure 5

6. (12%) Two feedback configuration are shown in Figure 6. The close-loop gain is  $A_{vf} = v_o/v_i = 20$  for both circuits. (a) Determine  $\beta_1$  and  $\beta_2$ . (b) For both circuits, estimate the percent change in the close-loop gain for both configuration if  $A_2$  is decreases by 10%.

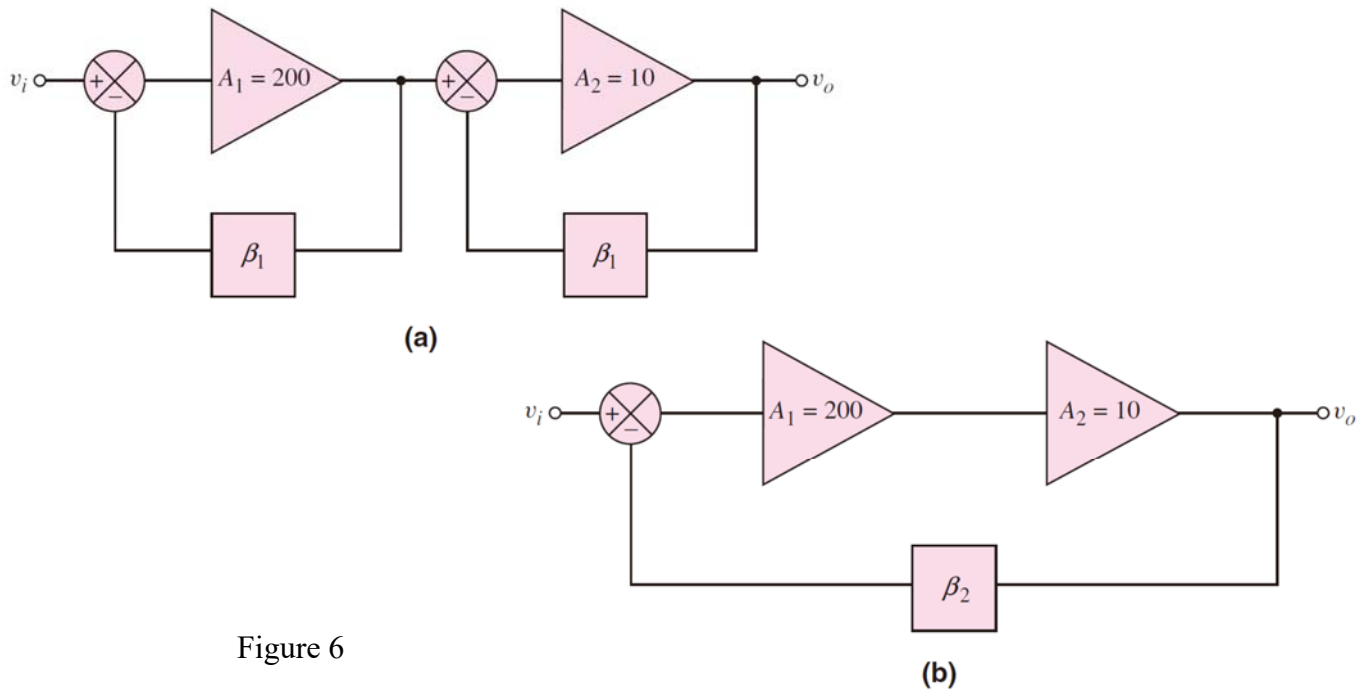


Figure 6

7. (6%) What kind of feedback configuration is this (2%)? Why (4%)?

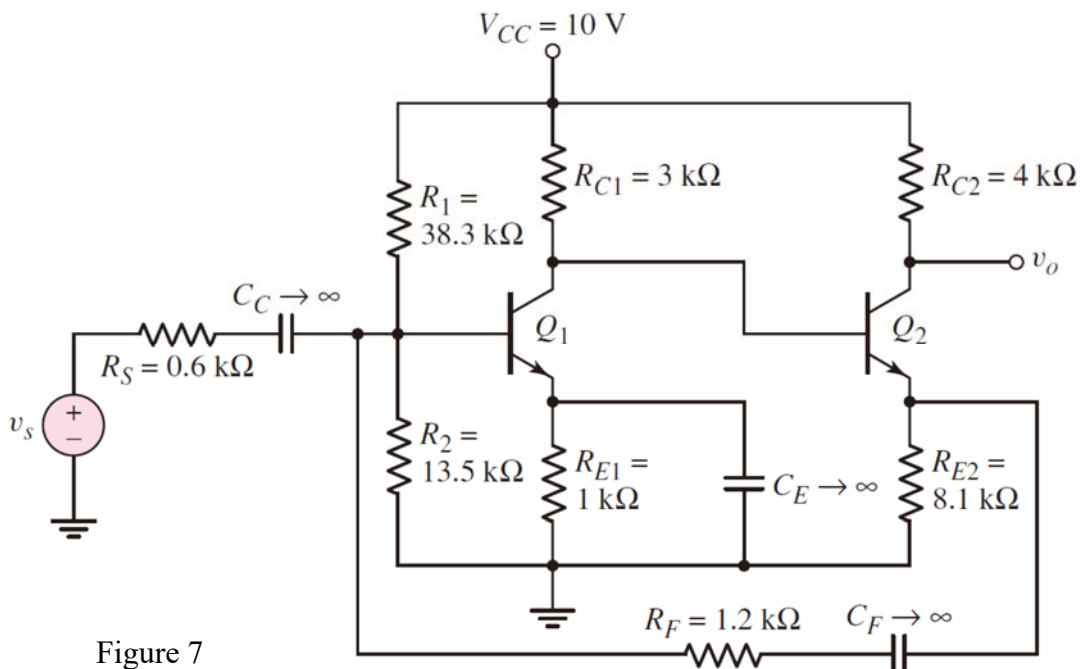


Figure 7