

Homework 5 (Due date: 11/14)

HW5.1: (20 points)

Using a long-channel model, **prove** that, in strong inversion, the transistor M_R behaves like a resistor ($R_{on,R}$) with its resistance,

$$R_{on,R} = \frac{(W/L)_C}{(W/L)_R} \frac{1}{g_{m,C}}$$

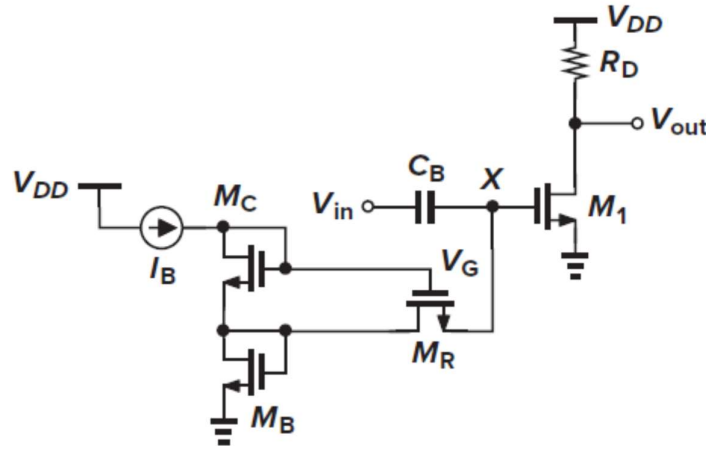


Fig. 5.1

HW5.2: (30 points)

The circuit of Fig. 5.2 is designed with $(W/L)_{1,0} = 8/2$, $(W/L)_{3,2} = 4 \cdot 8/2$, and $I_{REF} = 100 \mu A$.

Assume $\mu_n C_{ox} = 800 \mu A/V^2$, $V_{DD} = 3V$ and $\gamma = 0$. $V_{TH} = 0.5V$

- Determine V_X and the acceptable range of V_b .
- Estimate the deviation of I_{out} from $400 \mu A$ if the drain voltage of M_3 is higher than V_X by 1 V, if $\lambda = 0.1 V^{-1}$.
- How to design V_b to have a minimum drain voltage of M_3 ?

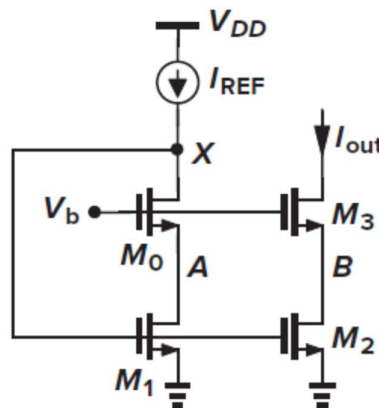


Fig. 5.2

Homework 5 (Due date: 11/14)

HW5.3 (30 points)

In the circuit shown in Fig. 5.3, a source follower using a *wide transistor* and a small bias current is inserted in series with the gate of M_3 to bias M_2 at the edge of saturation. Assuming M_0 – M_3 are identical and $\lambda \neq 0$, estimate the mismatch between I_{out} and I_{REF} if

- (a) $\gamma = 0$ (20 points), and
- (b) $\gamma \neq 0$ (10 points).

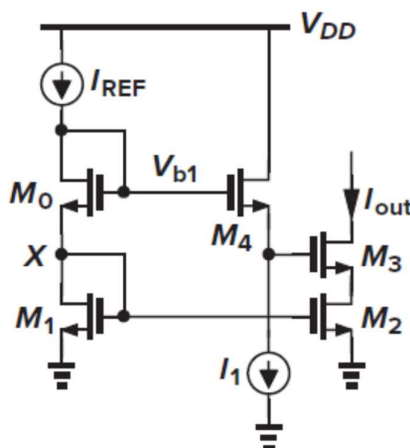


Fig. 5.3

HW5.4: (20 points)

The circuit shown in Fig. 5.4 exhibits a *negative input inductance*. Calculate the input impedance of the circuit and identify the inductive component.

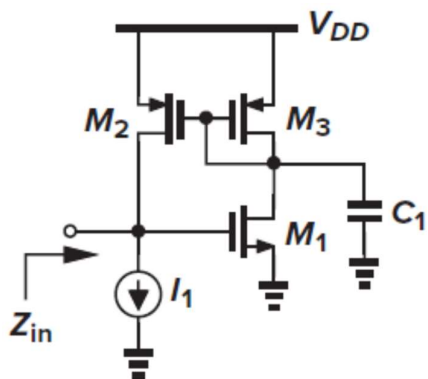


Fig. 5.4

HW5.1

由於 M_R 的 $I_D = 0$ 使得 $V_{DS} = 0$

因此 $V_{GSC} = V_{GSR} \Rightarrow V_{OVc} = V_{OVR}$

將 M_R 操作在 Deep triode Region $\Rightarrow R_{ON,R} = \frac{1}{g_{mR}}$

$$\frac{g_{mc}}{g_{mR}} = \frac{\mu_{COX}(\frac{W}{L})_C V_{OVc}}{\mu_{COX}(\frac{W}{L})_R V_{OVR}} = \frac{(\frac{W}{L})_C}{(\frac{W}{L})_R}$$

$$\Rightarrow R_{ON,R} = \frac{(\frac{W}{L})_C}{(\frac{W}{L})_R} \frac{1}{g_{mc}} \quad \#$$

HW5.2

①

Assume $\beta_2 = \mu_{COX}(\frac{W}{L})_2$

$$V_X = V_{GS1} = \sqrt{\frac{2I_{REF}}{\beta_1}} + V_{TH1} = 0.25 + 0.5 = 0.75V \quad \#$$

$$V_{OV1} + V_{GS0} \leq V_b \leq V_X + V_{TH0}$$

$$\Rightarrow 0.25 + 0.75 \leq V_b \leq 0.75 + 0.5$$

$$\Rightarrow 1V \leq V_b \leq 1.25V \quad \#$$

⑥ < 表 - >

Assume $V_b = V_{b(\min)} = 1V$

$$V_{DS1} = V_b - V_{GS0} = 0.25V$$

$$V_{DS2} = V_{DS1} + \Delta V_{DS2}$$

$$V_{DS3} = V_X - V_{DS2} = 1.5 - \Delta V_{DS2}$$

$$V_{OV3} = V_b - V_{DS2} - V_{TH3} = 0.25 - \Delta V_{DS2}$$

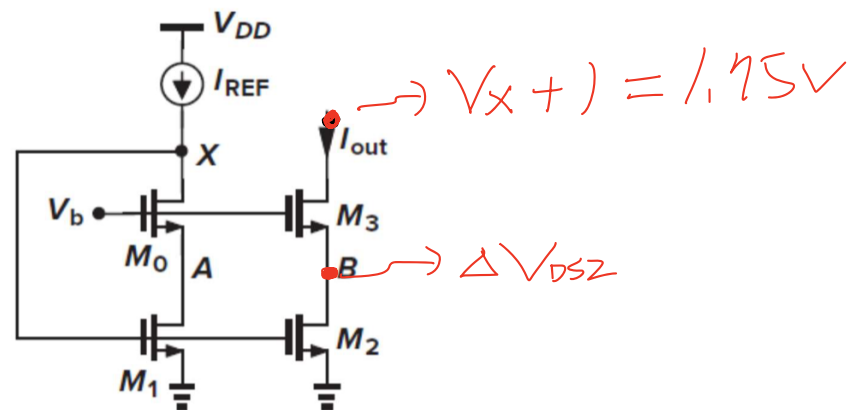


Fig. 5.2

$$I_{out} = \frac{\beta_2}{2} V_{OV2}^2 (1 + \lambda V_{DS2})$$

$$I_{out} = \frac{\beta_3}{2} V_{OV3}^2 (1 + \lambda V_{DS3})$$

$$\begin{cases} I_{out} = \frac{\beta_2}{2} \times 0.25^2 \times [1 + \lambda (0.25 + \Delta V_{DS2})] - (1) \end{cases}$$

$$\begin{cases} I_{out} = \frac{\beta_3}{2} \times (0.25 - \Delta V_{DS2})^2 [1 + \lambda (1.5 - \Delta V_{DS2})] - (2) \end{cases}$$

由 ① = ② 可得

$$\Rightarrow -0.1 \Delta V_{DS2}^3 + 1.1 \Delta V_{DS2}^2 - 0.5875 \Delta V_{DS2} + 1.8125 \mu = 0$$

$$\Rightarrow \Delta V_{DS2} = 10.437V, 0.5484V, \underline{0.01364V} \checkmark$$

$$I_{out} = 400 \mu \times \frac{1 + \lambda (V_{DS1} + \Delta V_{DS2})}{1 + \lambda V_{DS1}} \simeq 400.531 \mu A \#$$

<L2=>

$$R_{out} \simeq g_{m3} r_{o3} r_{o2}$$

$$\Delta V_{os2} = \Delta V \times \frac{r_{o2}}{R_{out}} = \frac{\Delta V}{g_{m3} r_{o3}}$$

$$I_{out} = 4 \times I_{REF} (1 + \lambda \Delta V_{os2})$$

$$g_{m3} r_{o3} = \frac{2 I_D}{V_{ov}} \times \frac{1}{\lambda I_D} = \frac{2}{\lambda V_{ov3}} \simeq \frac{2}{\lambda V_{ov0}} = 80$$

$$\Delta V_{os2} = \frac{1V}{80} = 0.0125V$$


$$\Rightarrow I_{out} = 4 \times 100 \mu A \times (1 + 0.1 \times 0.0125) \simeq 400.5 \mu A \#$$

©


設計 $V_b = 2V_{ov} + V_{TH}$ 則可得到 $V_{D3(min)}$

實際上最好保留額外的 Margin

避免因為 Body effect 使 M_2 跑進 triode

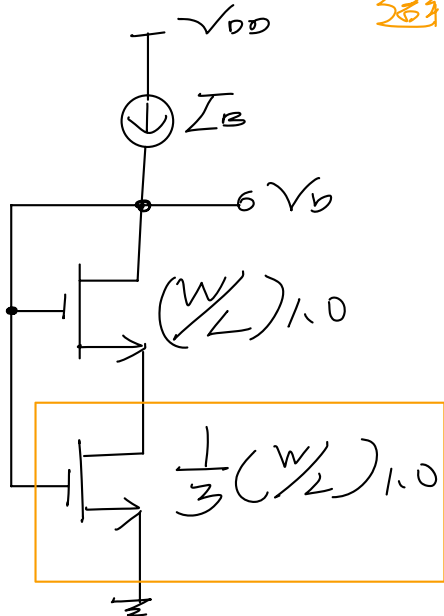

可等效為
 \Rightarrow

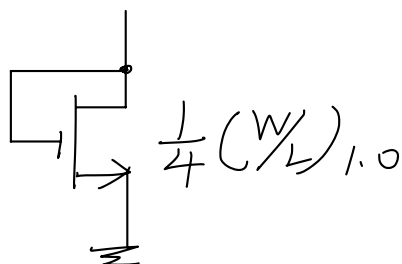

這顆的 $\frac{1}{3}(W/L)_{1,0}$ ，一樣是利用
 等效長度串聯的方式來去實現
 並且利用相同 W 與 L 的單位電晶體

HW 5.3

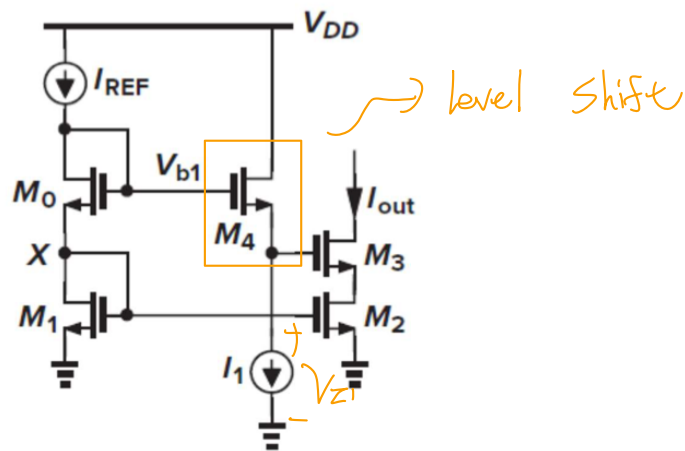


Fig. 5.3

由於 M_{0-3} size 皆相同
因此 V_{ov} 相同

①

$$\gamma = 0 \Rightarrow \text{All } V_{TH(i)} = V_{th0}$$

$$V_{b1} = V_{GS1} + V_{GS0} = 2V_{ov} + V_{TH0} + V_{TH1} = 2V_{ov} + 2V_{th0}$$

$$V_{DS2} = V_{b1} - V_{GS4} - V_{GS3}$$

M_4 using wide transistor 意味著 V_{ov} 極小

$$\text{也就是說 } V_{GS4} = V_{ov4} + V_{TH4} \approx V_{TH4} = V_{th0}$$

$$\Rightarrow V_{DS2} \approx V_{ov}$$

$$\frac{I_{out}}{I_{REF}} = \frac{1 + \lambda V_{ov}}{1 + \lambda (V_{ov} + V_{th0})} \quad \#$$

⑥ $r \neq 0$

M_0, M_3, M_4 需考慮 Body effect

$$V_{TH0} = V_{th0} + r(\sqrt{2\phi_f + V_{G0}} - \sqrt{2\phi_f})$$

$$V_{TH3} = V_{th0} + r(\sqrt{2\phi_f + V_{D02}} - \sqrt{2\phi_f})$$

$$V_{TH4} = V_{th0} + r(\sqrt{2\phi_f + V_{G1}} - \sqrt{2\phi_f})$$

$$V_{b1} = 2V_{ov} + V_{TH0} + V_{TH1}$$

$$V_{D02} \triangleq V_{b1} - V_{G03} - V_{TH4}$$

$$= 2V_{ov} + V_{TH0} + V_{TH1} - (V_{ov} + V_{TH3}) - V_{TH4}$$

$$= V_{ov} + V_{TH1} + V_{TH3} - V_{TH4}$$


$$V_{D01} = V_{ov} + V_{TH1}$$

$$\frac{I_{out}}{I_{REF}} = \frac{1 + \lambda(V_{ov} + V_{TH1} + V_{TH3} - V_{TH4})}{1 + \lambda(V_{ov} + V_{TH1})} \quad \#$$

OR

$$\frac{I_{out}}{I_{REF}} = \frac{1 + \lambda[V_{ov} + V_{th0} + r(\sqrt{2\phi_f + V_{D02}} - \sqrt{2\phi_f + V_{G1}})]}{1 + \lambda(V_{ov} + V_{th0})} \quad \#$$

HW5.4

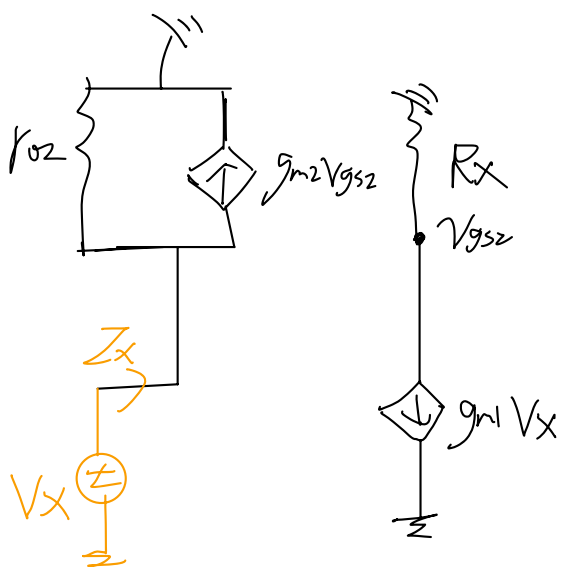

$$R_x = \frac{1}{g_{m3}} \parallel r_{o3} \parallel r_{o1} \parallel \frac{1}{sC_1}$$

$$\approx \frac{1}{g_{m3}} \parallel \frac{1}{sC_1} = \frac{1}{g_{m3} + sC_1}$$


$$V_{gs2} = -g_{m1} V_x R_x$$

$$Z_x = \frac{V_x}{I_x} + g_{m2} V_{gs2}$$

$$\Rightarrow Z_x = V_x \left(\frac{1}{r_{o2}} - g_{m1} g_{m2} R_x \right)$$

$$\Rightarrow \frac{V_x}{I_x} = r_{o2} \parallel \frac{-1}{g_{m1} g_{m2} R_x} = r_{o2} \parallel \frac{-(sC_1 + g_{m3})}{g_{m1} g_{m2}}$$
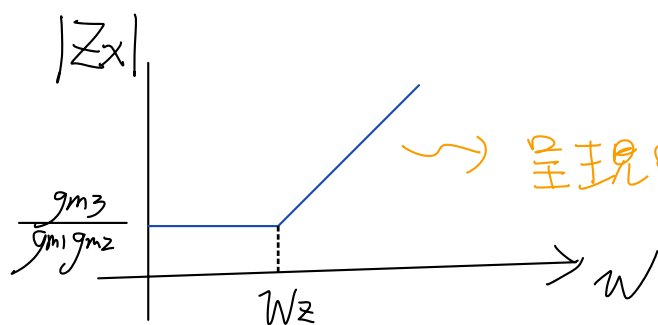
$$\Rightarrow \frac{V_x}{Z_x} = r_{o2} \parallel - \left(\frac{sC_1}{g_{m1} g_{m2}} + \frac{g_{m3}}{g_{m1} g_{m2}} \right) \approx - \left(\frac{sC_1}{g_{m1} g_{m2}} + \frac{g_{m3}}{g_{m1} g_{m2}} \right)$$



$$\omega_z = \frac{g_{m3}}{C_1}$$

→ 呈現電感性，阻抗隨 ω 上升而上升