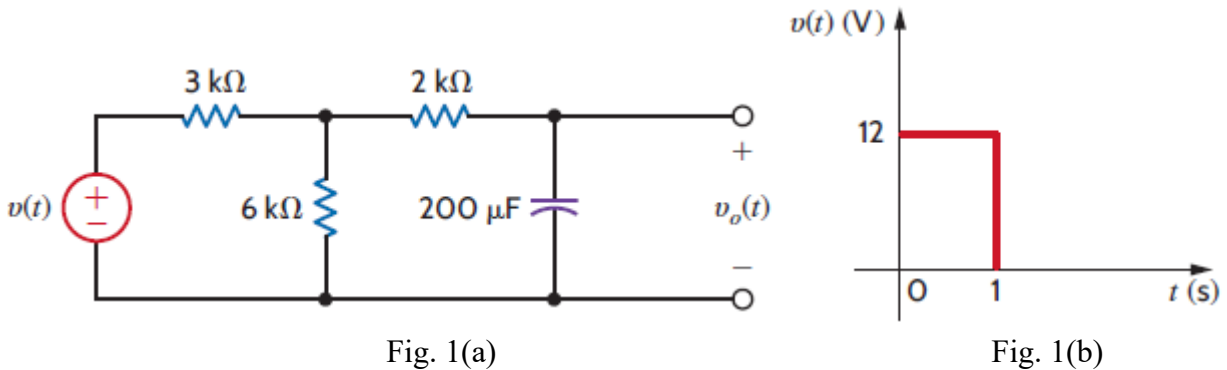


台灣科技大學一百一十學年度上學期期末考


科目名稱：電路學(一) 開課系所：電子系 ET2103301 地點：國際大樓 IB501

考試時間：111 年 12 月 29 日 上午 10:20 至 12:10 (可使用工程計算機)


1. (15%) Determine the equation for the voltage  $v_o(t)$  for  $t > 0$  in Fig. 1(a) when subjected to the input pulse shown in Fig. 1(b).



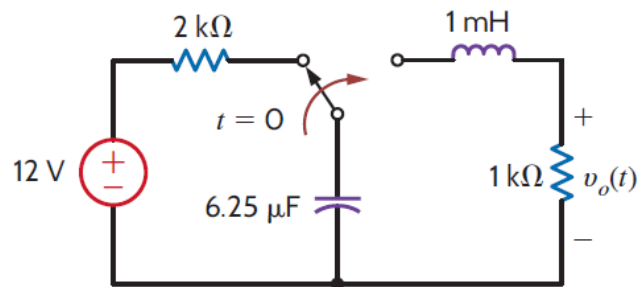
2. (15%) Please find  $v_o(t)$  for  $t > 0$ .



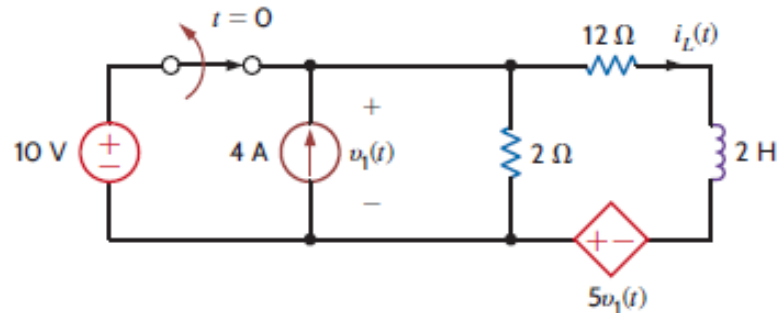3. (20%) Please find  $i_L(t)$  for  $t > 0$  in Fig. 3 using the step-by-step method.



4. (20%) Please find  $I_o$  in Fig. 4.

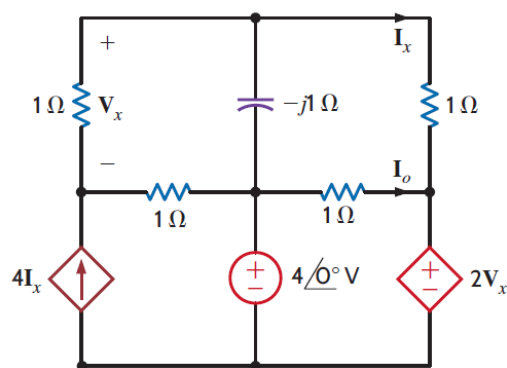

5. (15%) Please determine  $\mathbf{Z_L}$  for maximum average power transfer and the maximum average power transferred to  $\mathbf{Z_L}$  in Fig. 5.

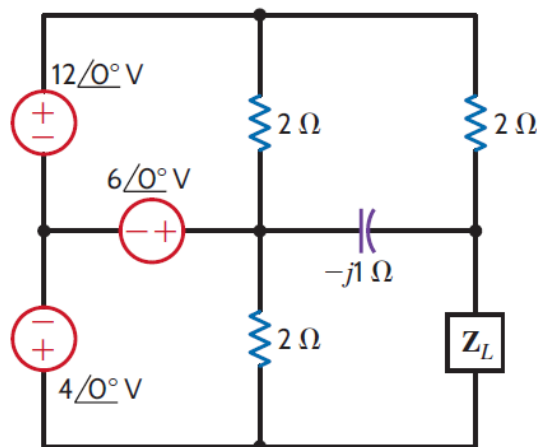


Fig. 5.

6. (12%) Two loads connected in parallel have the following parameters:

LOAD 1: 3 kW with pf = 0.8 lagging

LOAD 2: 5 kW with pf = 0.6 lagging

as shown in Fig. 6.

- Determine  $\mathbf{I}$ .
- Determine the value of the supply voltage  $\mathbf{V_s}$ .
- Determine the power factor of the source.
- Determine the complex power furnished by the source.

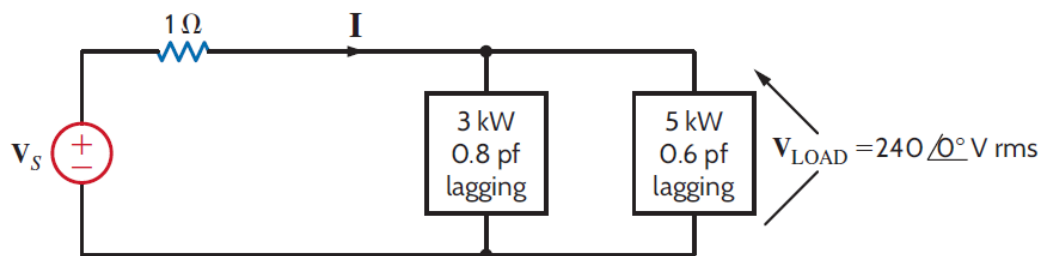


Fig. 6.

7. (13%) A bank of induction motors consumes 50 kW at a PF of 0.7 lagging from a 220 Vrms line. Determine the value of capacitance, which when placed in parallel with the load, will yield a PF of 0.9 lagging.

1.



**Solution:**

For  $0 \leq t \leq 1$  s



$t = 0^-$

$$v_C(0^-) = v_o(0^-) = 0 \text{ V}$$

$t = 0^+$

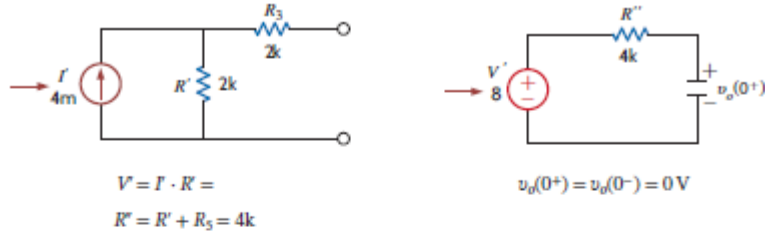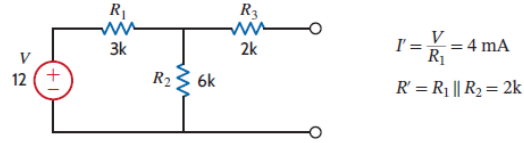

$t = \infty$

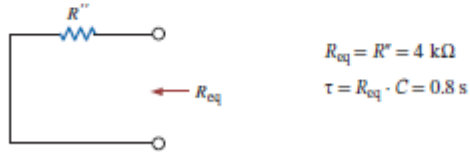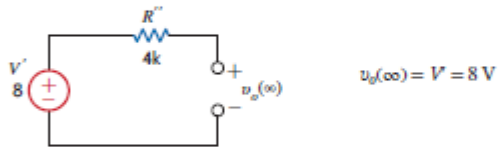

$$v_o(0^+) = 0 \text{ V} = K_1 + K_2$$

$$v_o(\infty) = 8 \text{ V} = K_1$$

$$K_2 = -8 \text{ V}$$

$$v_o(t) = 8 - 8e^{-t/0.8} \text{ V}, \quad 0 \leq t \leq 1 \text{ s}$$

$$v_o(1) = 8 - 8e^{-(1)/0.8} \text{ V} = 5.71 \text{ V}$$

For  $t \geq 1$  s ( $V = 0 \text{ V}$ )


$t' = t - 1 \text{ s}$

$t = 1^+$

$$v_o(1^-) = v_o(1^+) = 5.71 \text{ V}$$

$t = \infty$
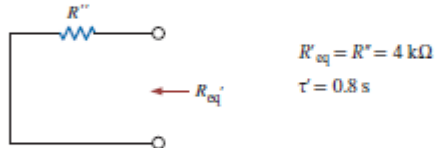
$$v_C(\infty) = v_o(\infty) = 0 \text{ V}$$



$$V_o(1^+) = 5.71 \text{ V} = K_3 + K_4$$

$$V_o(\infty) = 0 \text{ V} = K_3$$

$$K_4 = 5.71 \text{ V}$$

$$V(t) = 5.71e^{-t'/0.8} \text{ V}, \quad t > 1 \text{ s}$$

$$\therefore V(t) = \begin{cases} 8 - 8e^{-t/0.8} \text{ V}, & 0 \leq t \leq 1 \text{ s} \\ 5.71e^{-(t-1)/0.8} \text{ V}, & t > 1 \text{ s} \end{cases}$$

2.

6.3.14 Find  $v_o(t)$  for  $t > 0$  in the circuit in Fig. P6.3.14 and plot the response, including the time interval just prior to moving the switch.


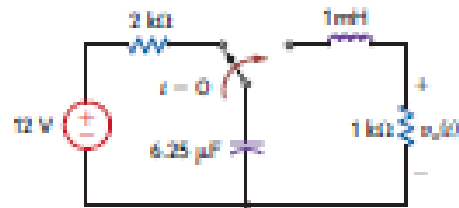


FIGURE P6.3.14

**Solution:**

$t = 0^-$

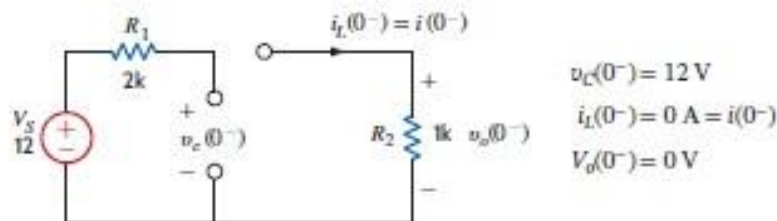

$t > 0$


$$\begin{aligned}
 \frac{d^2 i(t)}{dt^2} + \frac{R_2}{L} \cdot \frac{di(t)}{dt} + \frac{1}{LC} \cdot i(t) &= 0 \\
 S^2 + (1 \times 10^6)S + (1.6 \times 10^8) &= 0 \\
 S = \frac{-(1 \times 10^6) \pm \sqrt{(1 \times 10^6)^2 - 4(1)(1.6 \times 10^8)}}{2(1)} \\
 S = -160,000 \quad S_1 = -160,000 \quad S_2 = -999.8k \\
 i(t) = K_1 e^{-160,000t} + K_2 e^{-999.8kt} \\
 i(0^-) = i(0^+) = 0 \text{ A} = K_1 + K_2 \\
 12 = L \frac{di(0)}{dt} \\
 \frac{di(0)}{dt} = 12k \\
 \frac{di}{dt} = -160,000 \cdot K_1 e^{-160,000t} - 999.8k \cdot K_2 e^{-999.8kt} \\
 12,000 = -160,000 K_1 - 999.8k K_2 \\
 K_1 = 0.012 \quad K_2 = -0.012 \\
 i(t) = 0.012 e^{-160,000t} - 0.012 e^{-999.8kt} \text{ A, } t > 0 \\
 v_o(t) = R_2 \cdot i(t) \\
 v_o(t) = 12(e^{-160,000t} - e^{-999.8kt})
 \end{aligned}$$

3.

Solution:

$$i_L(t) = K_1 + K_2 e^{-t/\tau}$$


$$t = 0^-$$

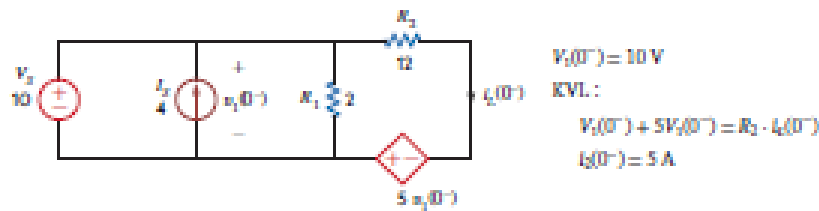

$$t = 0^+$$

$$i_L(0^+) = i_L(0^-) = 5 \text{ A}$$

$$t = \infty$$

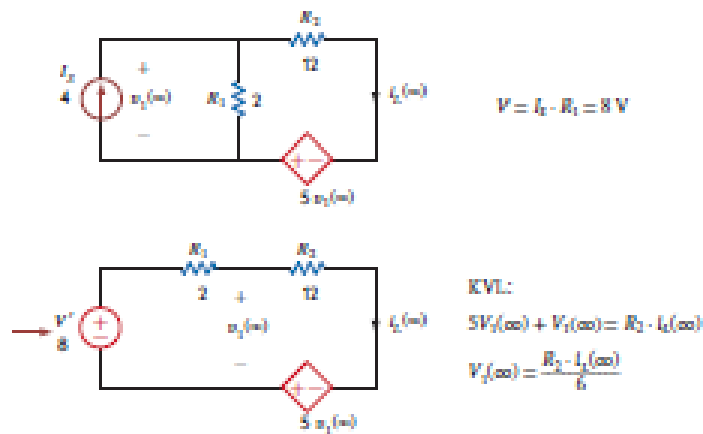

KVL:


$$5V_L(\infty) + V = (R_1 + R_2) \cdot i_L(\infty)$$

$$5\left(\frac{R_2 \cdot i_L(\infty)}{5}\right) + V = (R_1 + R_2) \cdot i_L(\infty)$$

$$i_L(\infty) = \frac{V}{\left(R_1 + \frac{1}{5}R_2\right)}$$

$$i_L(\infty) = 2 \text{ A}$$

$R_{th}$

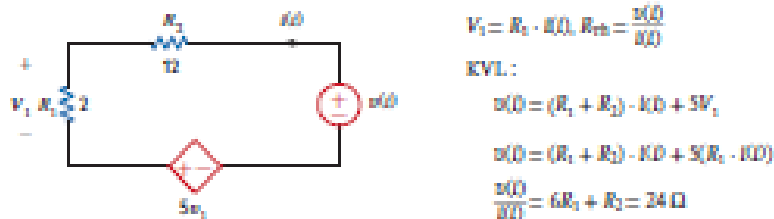

$$R_{th} = 24 \Omega$$

$$\tau = \frac{L}{R_{th}} = 83.3 \text{ ms}$$


$$i_L(0^+) = 5 \text{ A} = K_1 + K_2$$

$$i_L(\infty) = 2 \text{ A} = K_1$$

$$K_2 = 3 \text{ A}$$

$$i_L(t) = 2 + 3e^{-t/83.3 \text{ ms}} \text{ A}, \quad t > 0$$

Solution:

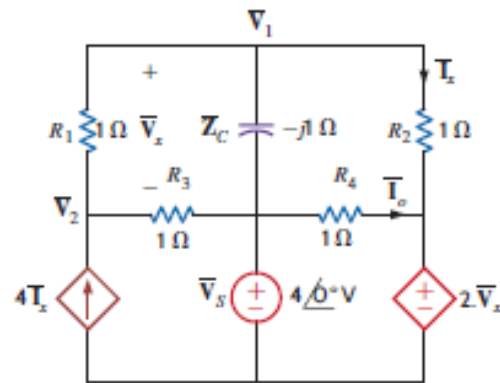

$$\mathbf{V}_x = \mathbf{V}_1 - \mathbf{V}_2$$

$$\mathbf{I}_x = \frac{\mathbf{V}_1 - 2 \cdot \mathbf{V}_x}{R_2} = \frac{-\mathbf{V}_1}{R_2} + \frac{2\mathbf{V}_2}{R_2}$$

KCL:

$$1. \frac{\mathbf{V}_1 - \mathbf{V}_2}{R_1} + \frac{\mathbf{V}_1 - \mathbf{V}_s}{Z_c} + \mathbf{I}_x = 0$$

$$\frac{\mathbf{V}_1}{R_1} - \frac{\mathbf{V}_2}{R_1} + \frac{\mathbf{V}_1}{Z_c} - \frac{\mathbf{V}_1}{R_2} + \frac{2\mathbf{V}_2}{R_2} = \frac{\mathbf{V}_s}{Z_c}$$

$$2. \frac{\mathbf{V}_2 - \mathbf{V}_1}{R_1} + \frac{\mathbf{V}_2 - \mathbf{V}_s}{R_3} - 4\mathbf{I}_x = 0$$

$$\frac{\mathbf{V}_2}{R_1} - \frac{\mathbf{V}_1}{R_1} + \frac{\mathbf{V}_2}{R_3} + \frac{4\mathbf{V}_1}{R_2} - \frac{8\mathbf{V}_2}{R_2} = \frac{\mathbf{V}_s}{R_3}$$

$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{Z_c} - \frac{1}{R_2}\right) & \left(\frac{-1}{R_1} + \frac{2}{R_2}\right) \\ \left(\frac{-1}{R_1} + \frac{4}{R_2}\right) & \left(\frac{1}{R_1} + \frac{1}{R_3} - \frac{8}{R_2}\right) \end{bmatrix} \times \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \frac{\mathbf{V}_s}{Z_c} \\ \frac{\mathbf{V}_s}{R_3} \end{bmatrix}$$

$$\mathbf{V}_1 = 3.267 \angle 17.103^\circ \text{ V}$$


$$\mathbf{V}_2 = 1.193 \angle 26.565^\circ \text{ V}$$

$$\mathbf{I}_o = \frac{\mathbf{V}_s - 2\mathbf{V}_x}{R_4}$$

$$\mathbf{I}_o = \frac{\mathbf{V}_s - 2\mathbf{V}_1 + 2\mathbf{V}_2}{R_4}$$


$$\mathbf{I}_o = 1.33 \angle -126.87^\circ \text{ A}$$

Solution:

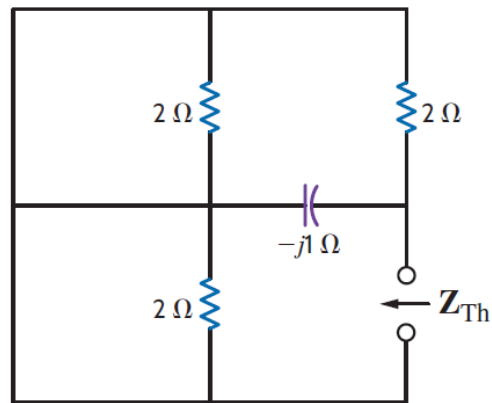

$$\bar{Z}_{Th} = 2 \parallel -j1 = 0.4 - j0.8 \Omega$$
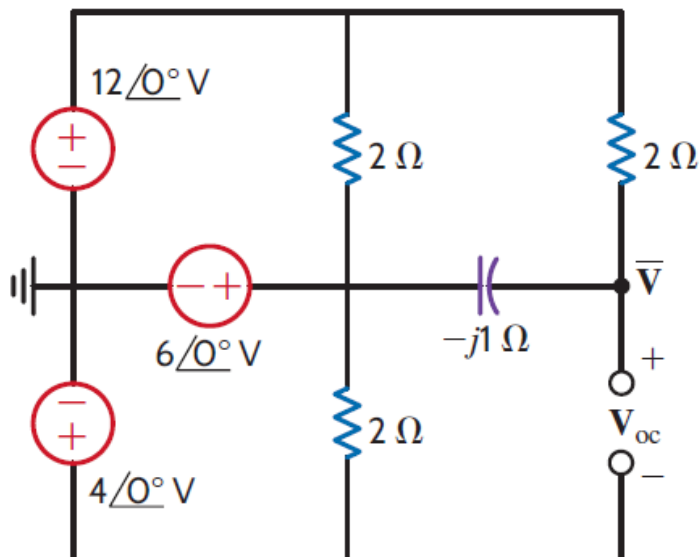
$$\bar{Z}_L = \bar{Z}_{Th}^* = 0.4 + j0.8 \Omega$$



$$\frac{\bar{V} - 6/0^\circ}{-j1} + \frac{\bar{V} - 12/0^\circ}{2} = 0$$

$$\Rightarrow \bar{V} = 7.59/-18.43^\circ \text{ V}$$

$$\bar{V}_{oc} = \bar{V} - 4/0^\circ = 4/36.87^\circ \text{ V}$$

$$P_{\max} = \frac{(V_{oc})^2}{8R_{Th}} = \frac{4^2}{8(0.4)} = 5 \text{ W}$$

**Solution:**

$$\bar{I}_1 = \frac{\left(\frac{3}{0.8}\right) \text{ kVA}}{240 \text{ V}_{\text{rms}}} \angle -\cos^{-1}(0.8) = 15.63 \angle -36.87^\circ \text{ A}_{\text{rms}}$$

$$\bar{I}_2 = \frac{\left(\frac{5}{0.6}\right) \text{ kVA}}{240 \text{ V}_{\text{rms}}} \angle -\cos^{-1}(0.6) = 34.72 \angle -53.13^\circ \text{ A}_{\text{rms}}$$

**a.**  $\bar{I} = \bar{I}_1 + \bar{I}_2 = 49.91 \angle -48.1^\circ \text{ A}_{\text{rms}}$

**b.**  $\bar{V}_S = 240 \angle 0^\circ + (\bar{I})(1) = 275.8 \angle -7.74^\circ \text{ V}_{\text{rms}}$

**c.**  $pf_S = \cos(-7.74^\circ + 48.1^\circ) = 0.762$  lagging

**d.**  $\bar{S} = \bar{V}_S \bar{I}^* = 13.77 \angle 40.36^\circ \text{ kVA}$

7.

**Solution:**

$$\theta_{\text{old}} = \cos^{-1}(0.7) = 45.57^\circ$$

$$Q_{\text{old}} = 50 \tan(\theta_{\text{old}}) = 51.01 \text{ kvar}$$

$$\theta_{\text{new}} = \cos^{-1}(0.9) = 25.84^\circ$$

$$Q_{\text{new}} = 50 \tan(\theta_{\text{new}}) = 24.22 \text{ kvar}$$

$$Q_C = Q_{\text{old}} - Q_{\text{new}} = 26.79 \text{ kvar}$$

$$C = \frac{Q_C}{2\pi(60)(220^2)} = 1.468 \text{ mF}$$