

HW8.1 (40 points)

如圖 8.1 所示，是一個 Two-Satge Opamp 的 Miller compensation 相關電路。

- (a) 請列出在使用 Miller Capacitor (C) 做極點分離之頻率補償時，若沒有 R_z 的問題是甚麼？請說明此問題的原因為何？
- (b) 在滿足極點—零點抵消之情況下，假設 C_E 可忽略， M_9, M_{11} ($g_m, W/L, I_d$), C_c , and C_L 皆是已知。請設計 M_{13}, M_{14}, M_{15} and I_1 。

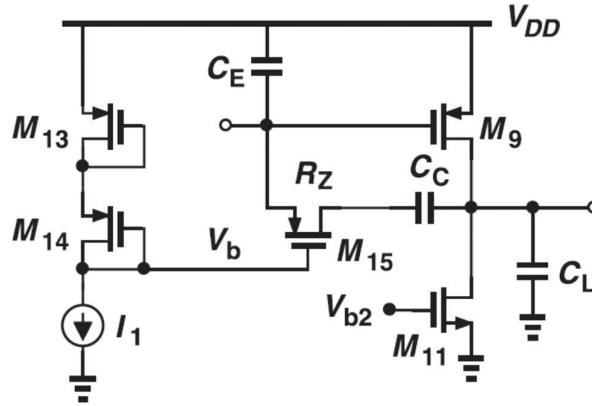


Fig. 8.1

HW8.2 (30 points)

Suppose the open-loop transfer function of a two-stage op amp is expressed as

$$H_{open}(s) = \frac{A_0 \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

- (a) 假如 $\omega_{p2} = 10A_0\omega_{p1}$ and $\omega_z = 10\omega_{p2}$ ，請劃出 $H_{open}(s)$'s bode plots for Magnitude and phase 並標示出 unit-gain frequency $\omega_u = ?$.
- (b) 承上，其 phase margin (PM) = ?
- (c) 若是 $\omega_{p2} = A_0\omega_{p1}$ and $\omega_z = 2\omega_{p2}$ ，其 phase margin (PM) = ?

HW8.3 (15 points)

The two-stage op amp of Fig. 8.3 incorporates Miller compensation to reach a phase margin of 45° . Estimate the compensation capacitor value. Using all transistors' small-signal parameters (g_m , r_o).

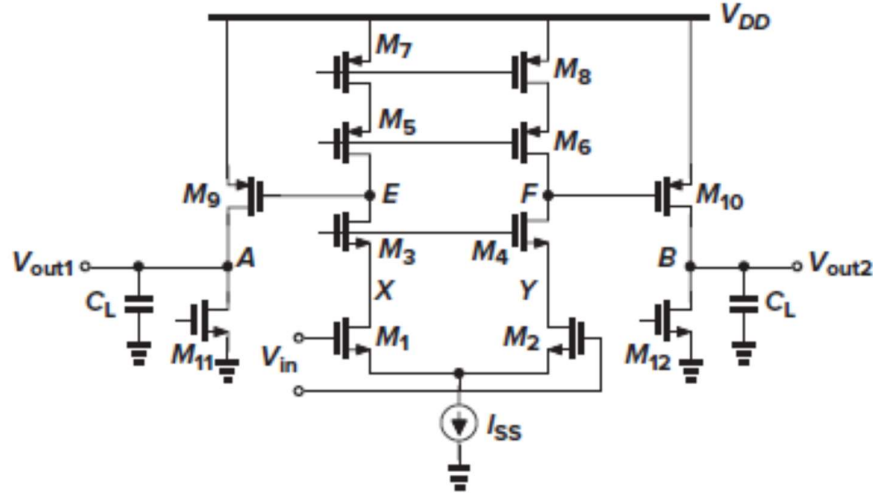


Fig. 8.3

HW8.4 (15 points)

Consider the transimpedance amplifier shown in Fig. 8.4, where $R_D = 1\text{ k}\Omega$, $R_F = 10\text{ k}\Omega$, $g_{m1} = g_{m2} = 1/(100\Omega)$, and $C_A = C_X = C_Y = 100\text{ fF}$. Neglecting all other capacitances and assuming that $\lambda = \gamma = 0$, compute the phase margin of the circuit. (Hint: break the loop at node X .)

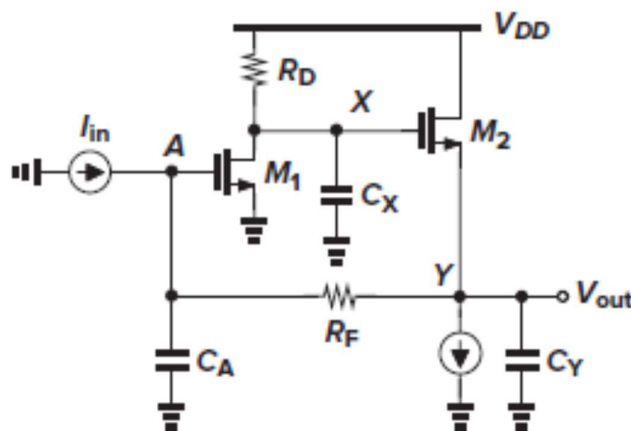


Fig. 8.4

HW 8.1

④ 若沒有使用 R_z ，將會產生 RHP 的 zero $\omega_z = \frac{g_{m9}}{C_c}$
而 RHP 的 zero，將使得 Phase 往下掉，因此當電路
接成閉迴路時，若 ω_z 與 GBW 相鄰較近時
會使得 Phase Margin 較差。

⑤ 設計使得 $p_2 = z_1$ (pole and zero cancellation) - ①

$$\Rightarrow \frac{-g_{m9}}{C_L} = \frac{1}{(g_{m9} - R_z)C_c}$$

$$\Rightarrow R_z = \frac{1}{g_{m9}} \left(1 + \frac{C_L}{C_c} \right)$$

並設計 M_9 與 M_{13} 具有相同的 γ_{ov} - ②

$$\frac{Z_1}{Z_{D9}} = \frac{\beta_{13} \gamma_{ov}^2}{\beta_9 \gamma_{ov}^2} \Rightarrow Z_1 = Z_{D9} \times \frac{(\omega_L)_{13}}{(\omega_L)_9} \quad \text{已知}$$

選擇適當的 Z_1 後，將推得 $(\omega_L)_{13}$ 為何

$$\text{由 ② 的條件可推得 } R_z = \frac{1}{g_{m14}} \frac{(\omega_L)_{14}}{(\omega_L)_{15}}$$

$$\Rightarrow \frac{1}{g_{m9}} \left(1 + \frac{C_L}{C_c} \right) = \frac{1}{g_{m14}} \frac{(\omega_L)_{14}}{(\omega_L)_{15}}$$

$$\Rightarrow (\omega_L)_{15} = \frac{g_{m9}}{g_{m14}} (\omega_L)_{14} \frac{C_c}{C_L + C_c}$$

由 $g_m = \sqrt{2\beta I_D}$ 推得

→ 選擇 $(\omega_L)_{14}$ 後
即可獲得 $(\omega_L)_{15}$

$$\Rightarrow (\omega_L)_{15} = \sqrt{(\omega_L)_9 (\omega_L)_{14}} \sqrt{\frac{Z_{D9}}{Z_1}} \frac{C_c}{C_L + C_c} \quad \text{已知}$$

HW8.2

Suppose the open-loop transfer function of a two-stage op amp is expressed as

$$H_{open}(s) = \frac{A_0 \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$



Assume ω_z 為 RHP
and $A_0 > 10$

- (a) 假如 $\omega_{p2} = 10A_0\omega_{p1}$ and $\omega_z = 10\omega_{p2}$, 請劃出 $H_{open}(s)$'s bode plots for Magnitude and phase 並標示出 unit-gain frequency $\omega_u = ?$.
 (b) 承上, 其 phase margin (PM) = ?
 (c) 若是 $\omega_{p2} = A_0\omega_{p1}$ and $\omega_z = 2\omega_{p2}$, 其 phase margin (PM) = ?

Q)

由於 $\omega_{p2} \gg \omega_{p1}$ 因此可做主極點近似
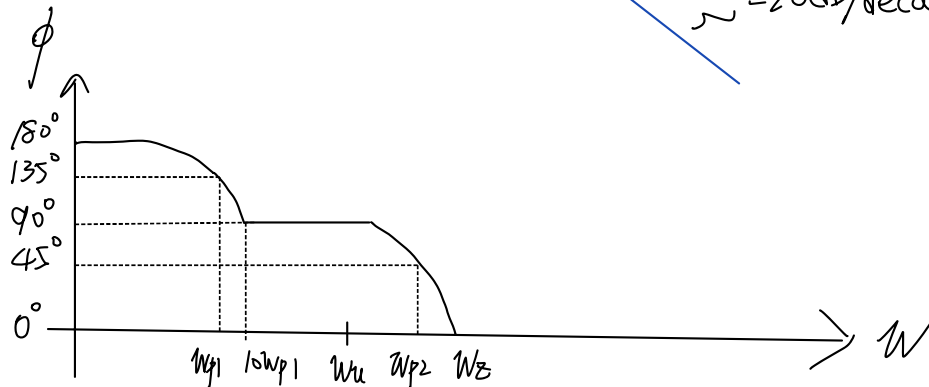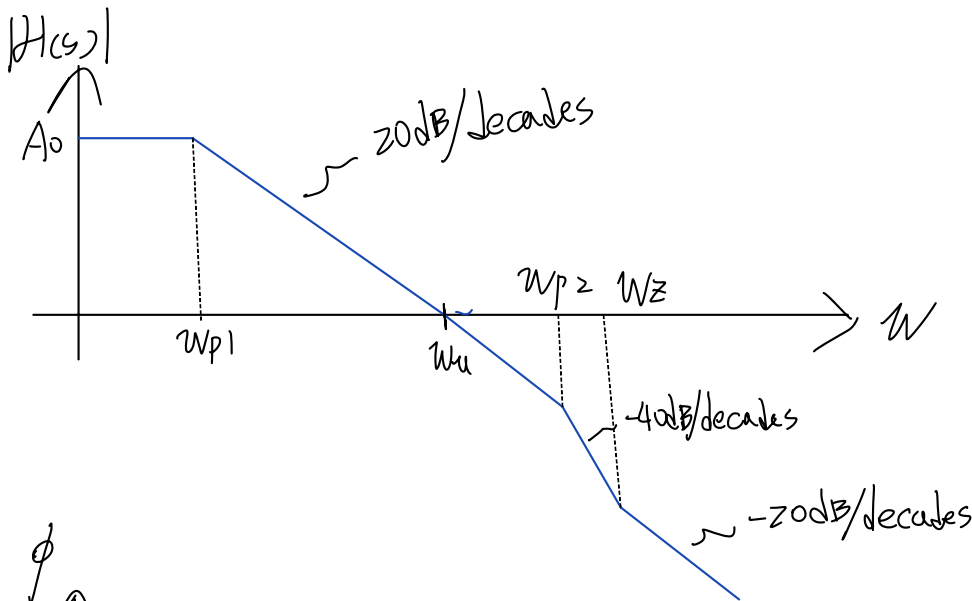
$$\omega_u \triangleq GBW = A_0 \omega_{p1}$$



#

⑥

$$\begin{aligned}
 PM &= 180^\circ - \tan^{-1}\left(\frac{w_u}{w_{p1}}\right) - \tan^{-1}\left(\frac{w_u}{w_{p2}}\right) - \tan^{-1}\left(\frac{w_u}{w_z}\right) \\
 &= 180^\circ - \tan^{-1}(10) - \tan^{-1}(0.1) - \tan^{-1}(0.01) \\
 &\approx 180^\circ - 84.28^\circ - 5.7^\circ - 0.57^\circ = 89.45^\circ \#
 \end{aligned}$$

⑦

$$\begin{aligned}
 PM &= 180^\circ - \tan^{-1}\left(\frac{w_u}{w_{p1}}\right) - \tan^{-1}\left(\frac{w_u}{w_{p2}}\right) - \tan^{-1}\left(\frac{w_u}{w_z}\right) \\
 &= 180^\circ - \tan^{-1}(10) - \tan^{-1}(1) - \tan^{-1}(0.1) \\
 &\approx 180^\circ - 84.28^\circ - 45^\circ - 5.7^\circ = 45^\circ \#
 \end{aligned}$$

HW8.3

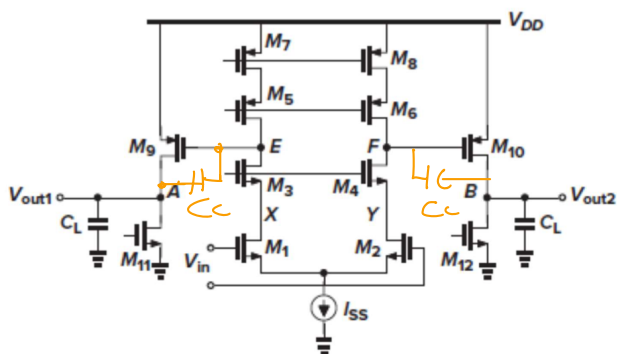


Fig. 8.3

$$R_{01} \approx g_{m3,4} r_{o3,4} r_{o1,2} \parallel g_{m5,6} r_{o5,6} r_{o7,8}$$

$$A_1 \approx g_{m1,2} R_{01} \quad A_2 \approx g_{m9,10} (r_{o9,10} \parallel r_{o11,12})$$

$$\omega_{p1} \approx \frac{-1}{R_{01} A_2 C_c} \quad \omega_{p2} \approx \frac{-g_{m9,10}}{C_L} \quad \omega_z \approx \frac{g_{m7,10}}{C_c}$$

$$\omega_u \approx A_1 \times A_2 \times \omega_{p1} = \frac{g_{m1,2}}{C_c}$$

$$\text{若設計 } \omega_u = \omega_{p2} \quad \text{且} \quad \omega_z \geq 10 \omega_u$$

$$\text{則可獲得 } PM \approx 45^\circ$$

$$\frac{g_{m1,2}}{C_c} = 10 \frac{g_{m9,10}}{C_L} \Rightarrow C_c = 0.1 C_L$$

$$\frac{g_{m1,2}}{C_c} = \frac{g_{m9,10}}{C_L} \Rightarrow \frac{g_{m1,2}}{0.1 C_L} = \frac{g_{m9,10}}{C_L} \Rightarrow g_{m1,2} = 0.1 g_{m9,10}$$

HW8.4

Consider the transimpedance amplifier shown in Fig. 8.4, where $R_D = 1 \text{ k}\Omega$, $R_F = 10 \text{ k}\Omega$, $g_{m1} = g_{m2} = 1/(100\Omega)$, and $C_A = C_X = C_Y = 100 \text{ fF}$. Neglecting all other capacitances and assuming that $\lambda = \gamma = 0$, compute the phase margin of the circuit. (Hint: break the loop at node X.)


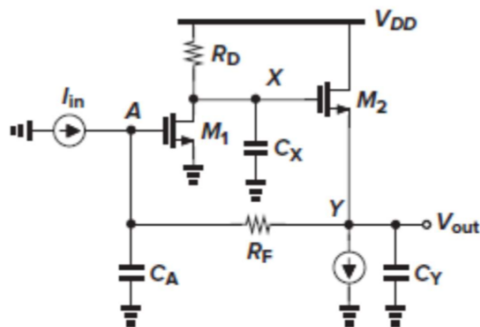


Fig. 8.4

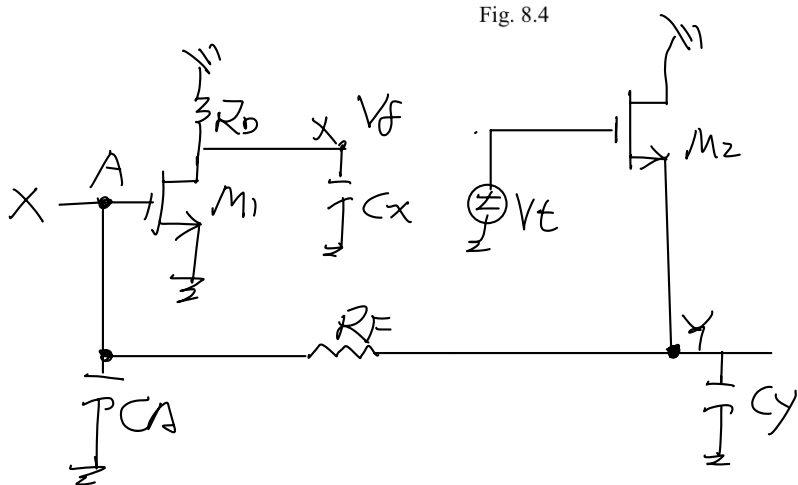

先找到 $s=0$ 下的 loop gain

$$A_0(s=0) = \frac{V_F}{V_t} = 1 \times (-g_{m1}R_D) = -g_{m1}R_D = -10$$

找出各節點上的 pole (利用 open circuit time constant Method)

實際上不能直接用來找 pole

僅能找到 $\omega_{3dB} = \frac{1}{\tau_1 + \tau_2 + \tau_3}$

但這因為了快速找到各個 pole 的趨勢

因此簡化過程!!

$$\omega_X \approx \frac{1}{R_D C_X} = 10 \text{ rad/s}$$

$$\omega_A = \frac{1}{(R_F + g_{m2}^{-1}) C_A} \approx \frac{1}{R_F C_A}$$

$$\omega_Y = -\frac{g_{m2}}{C_Y} = 100 \text{ rad/s}$$

$$H(s) = \frac{(3A_0 C = 0)}{(1 + \frac{s}{w_A})(1 + \frac{s}{w_x})(1 + \frac{s}{w_y})}$$

$$w_u = 10 w_A = w_x$$

$$\Rightarrow \phi_m = 180^\circ - \tan^{-1}\left(\frac{w_u}{w_A}\right) - \tan^{-1}\left(\frac{w_u}{w_x}\right) - \tan^{-1}\left(\frac{w_u}{w_y}\right)$$

$$= 180^\circ - 84.28^\circ - 45^\circ - 5.7^\circ = 45^\circ \neq$$