

- (12%) Assuming silicon is doped with phosphorus (P) at a concentration of  $2 \times 10^{16} \text{ cm}^{-3}$  at  $60^\circ\text{C}$ . Other parameters for the silicon sample include:  $B = 5.23 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2}$ ,  $E_g = 1.1 \text{ eV}$ ,  $\mu_n = 1250 \text{ cm}^2/\text{V} \cdot \text{s}$ ,  $\mu_p = 450 \text{ cm}^2/\text{V} \cdot \text{s}$ ,  $D_n = 35 \text{ cm}^2/\text{s}$ , and  $D_p = 10 \text{ cm}^2/\text{s}$ . (a) What are the concentrations of electrons and holes for this silicon (4%)? (b) Calculate the current density if an electric field of  $E = 50 \text{ V/cm}$  is applied to the material (4%). (c) Following (b), if this doped semiconductor material is placed at  $0^\circ\text{C}$ , will the current density be significantly increased, slightly increased, slightly decreased, or significantly decreased? (2%) and explain why (2%).
- (10%) The diode in the circuit shown in Figure 2 has a reverse-saturation current of  $I_S = 5 \times 10^{-13} \text{ A}$ . (a) Assume the cut-in voltage of the diode is  $V_f = 0.6 \text{ V}$ , determine the approximate diode voltage and current using piecewise linear model (4%). (b) Using the diode current equation and iteration method, determine the exact values of diode voltage and current (6%)?
- (12%) Let  $V_f = 0.7 \text{ V}$  for each diode in the circuit in Figure 3, and  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ . (a) For  $V_I = 10 \text{ V}$ , find  $I_{D1}$  and  $V_O$  (4%). (b) Plot  $V_O$  versus  $V_I$  for  $-10 \leq V_I \leq 10 \text{ V}$ . Indicate the breakpoints and the state of each diode in the various region of the plot (8%).

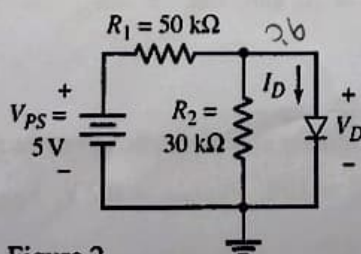


Figure 2

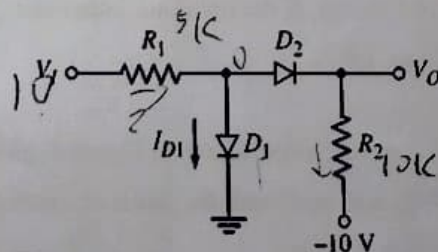


Figure 3

- (16%) Consider the rectifier circuit shown in Figure 4 with an input voltage  $v_s = 6 \sin \omega t$ , and assume the diode cut-in voltage  $V_f = 0.6 \text{ V}$ . (a) Plot the  $v_O$  versus time and indicate the maximum and minimum value of  $v_O$ . (b) Determine the fraction (percent) of time that the diode  $D_1$  is conducting. (c) What is the PIV rating of the diodes? (d) Assume a filter capacitance is connected in parallel with  $R_L = 1 \text{ k}\Omega$ , and the ripple voltage is to be limited to  $0.1 \text{ V}$ . Find the required value of the capacitor.

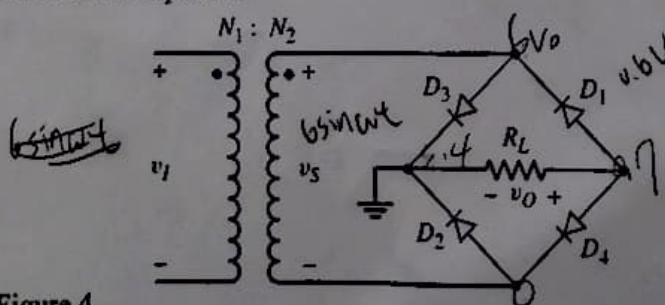


Figure 4

5. (10%) A Zener diode is connected in a voltage regulator circuit as shown in Figure 5. The Zener voltage is  $V_{Z0} = 10\text{ V}$  and the Zener resistance is assumed to be  $r_z = 0$ . The output load current varies between  $I_L = 50 \sim 500\text{ mA}$  and the input voltage varies from  $V_{PS} = 15 \sim 20\text{ V}$ . (a) Determine the value of  $R_i$  such that  $I_Z(\min) = 0.2 \cdot I_Z(\max)$ . (b) Following (a), if  $r_z = 5\ \Omega$ , determine the percent source regulation (assume minimum load current)

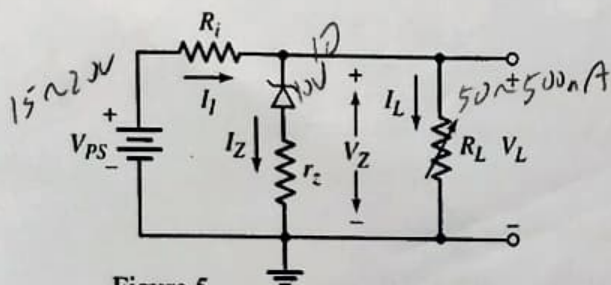


Figure 5

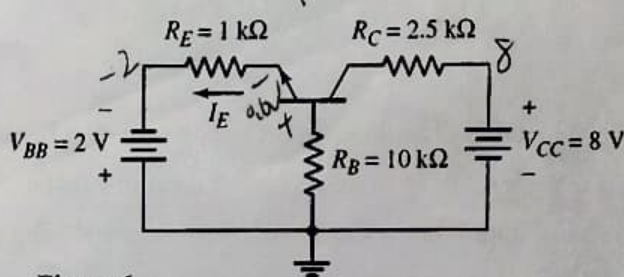


Figure 6

7. (18%) For the circuit shown in Figure 7, the transistor parameters are:  $\beta = 150$ ,  $V_{BE(on)} = 0.7\text{ V}$ ,  $V_{CE(sat)} = 0.2\text{ V}$ , and  $V_A = \infty$ . (a) sketch the load line and show the slope (3%). (b) Determine the required value of  $I_{CQ}$  such that the Q-point is in the center of the load line (3%). (c) Design  $R_1$  and  $R_2$  such that the circuit is bias-stable (6%). (d) Following (c), for the designed circuit, if the transistor parameter  $\beta$  is changed to 50, calculate the new value of  $I_{CQ}$  and  $V_{CEQ}$  (6%).
8. (14%) For the circuit shown in Figure 8, plot the voltage transfer characteristics over the range  $0 \leq V_i \leq 5\text{ V}$  and mark the status of transistor. Assume  $\beta = 100$ ,  $V_{EB(on)} = 0.7\text{ V}$ ,  $V_{EC(sat)} = 0.2\text{ V}$ , and  $V_A = \infty$ .

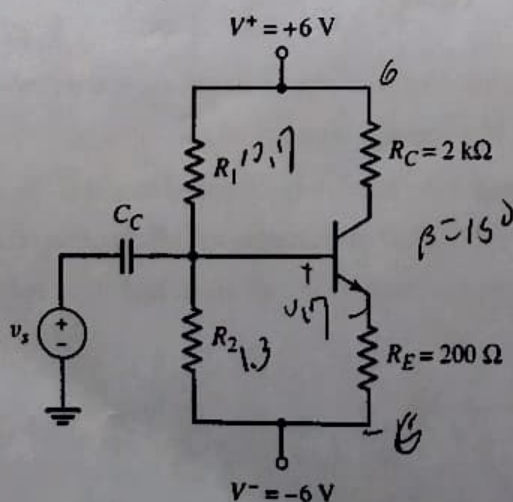


Figure 7

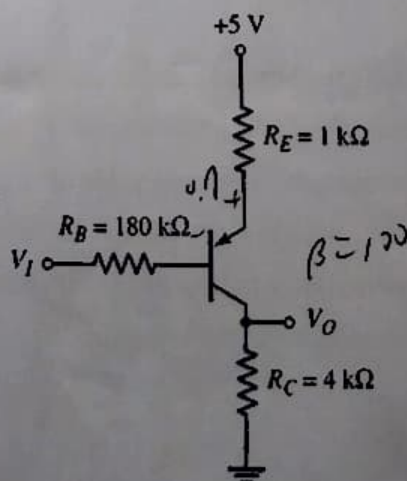


Figure 8

$$\frac{5 - 0.7 - V_i}{180k\Omega}$$