

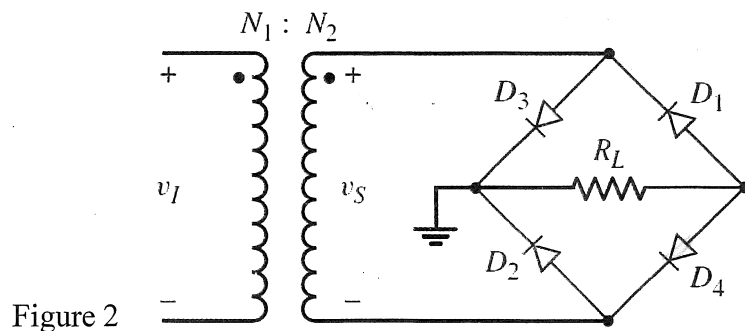
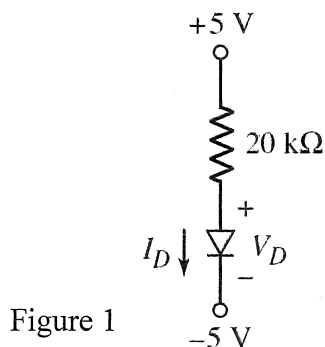




- (10%) Please explain (a) p-type semiconductor. (b) the relation of conductivity and bandgap energy.
- (10%) Consider silicon at $T=300$ K. Assume the hole concentration is given by $p = 10^{16} \cdot e^{-x/L_p} \text{ cm}^{-3}$, where $L_p = 10^{-3} \text{ cm}$. Assume $D_p = 10 \text{ cm}^2/\text{s}$. Calculate the hole diffusion current density at (a) $x = 0$ and (b) $x = 10^{-3} \text{ cm}$.
- (14%) The diode in the circuit shown in Figure 1 has a reverse-saturation current of $I_S = 10^{-13} \text{ A}$. (a) Assume the cut-in voltage of the diode is $V_\gamma = 0.7 \text{ V}$, determine the approximate diode voltage and current using piecewise linear model (5%). (b) what is the exact numbers of diode voltage and current (9%)?
- (15%) Consider the full-wave rectifier in Figure 2. Assume that turn-on voltage $V_\gamma = 0.7 \text{ V}$, the input frequency is 60 Hz, and the output resistance is $R_L = 125 \Omega$. A filter capacitor is connected in parallel with R_L . The magnitude of the peak output voltage is to be 15 V and the ripple voltage is to be 0.3 V. (a) Determine the required amplitude of v_s . (b) Determine the required filter capacitance value. (c) What is the PIV rating of the diodes?

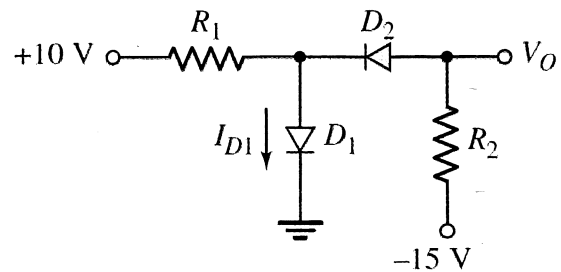

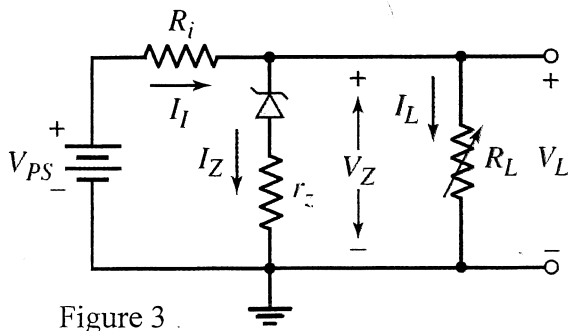5. (21%) A voltage regulator is to have nominal output voltage of 10 V. The input power supply has a nominal output of $V_{PS} = 20$ V and can vary by $\pm 25\%$. The output load current is to vary between $I_L = 0 \sim 20$ mA. (a) Ignore Zener resistance (r_Z) and consider the Zener diode as an ideal Zener diode with $V_Z = 10$ V. If the minimum Zener current is to be $I_Z = 5$ mA, determine the required R_i . (b) If the specified Zener diode has a rating of 1 W, has a 10 V voltage drop at $I_Z = 25$ mA, and has a Zener resistance of $r_Z = 5 \Omega$. Determine the maximum variation in output voltage. (c) Determine the percent source regulation (assume minimum load current).
6. (15%) Consider the circuit shown in Figure 4. Assume each diode cut-in voltage is $V_Y = 0.7$ V. (a) Determine I_{D1} , V_O and each diode status for $R_1 = 10$ k Ω , and $R_2 = 5$ k Ω . (b) Repeat part (a) for $R_1 = 5$ k Ω , and $R_2 = 10$ k Ω .



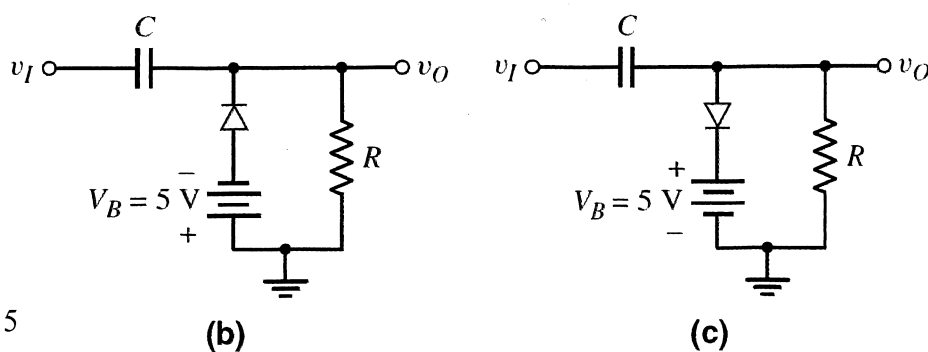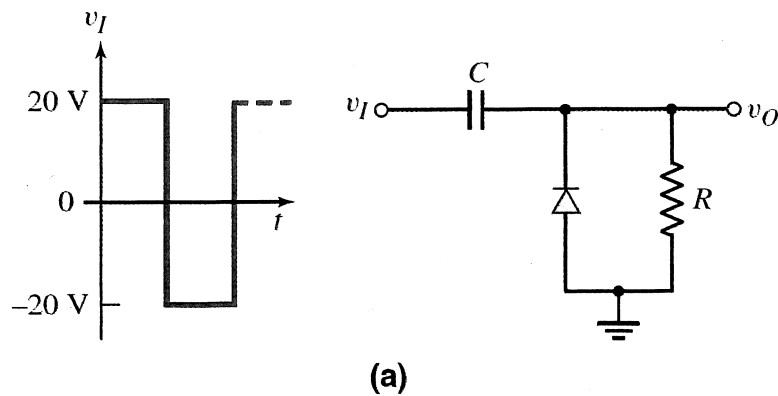7. (15%) Sketch the steady-state output voltage v_O versus time for each circuit in Figure 5 with the input voltage given. Assume $V_Y = 0$ and RC time constant is large.



1. (a) p型半導體 (b) 導電度和能隙的關係

2. $T = 300\text{K}$ $p = 10^6 e^{-x/L_p}$ where $L_p = 10^{-3}\text{cm}$ $D_p = 10\text{cm}^2/\text{s}$


(a) $x = 0$

$$J_p = -eD_p \frac{dp}{dx} = -1.6 \times 10^{-19} \times 10 \times 10^6 e^0 \times \frac{-1}{10^{-3}} = 1.6 \times 10^{-9} \text{A/cm}^2$$

(b) $x = 10^{-3}$

$$J_p = -eD_p \frac{dp}{dx} = -1.6 \times 10^{-19} \times 10 \times 10^6 e^1 \times \frac{-1}{10^{-3}} = 4.35 \times 10^{-9} \text{A/cm}^2 \quad \#$$

3.

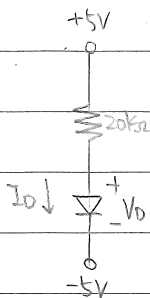

$I_s = 10^{-13}\text{A}$ $V_f = 0.7\text{V}$

(a) piecewise linear model

$$I_D = (10 - 0.6) / 20\text{k} = 0.47\text{mA}$$

$$V_D = (10 - 20\text{k} \times 0.47\text{mA}) = 0.6\text{V}$$

(b)

$$I_D = \frac{10 - V_D}{20\text{k}}, \quad I_D = I_s \left(e^{\frac{V_D}{V_f}} - 1 \right)$$

$$V_D = V_f \ln \left(\frac{I_D}{I_s} + 1 \right)$$


$$V_D = 0.5\text{V} \Rightarrow I_D = 0.475\text{mA} \Rightarrow V_D = 0.5793\text{V}$$

$$V_D = 0.5793\text{V} \Rightarrow I_D = 0.471\text{mA} \Rightarrow V_D = 0.579\text{V}$$

$$V_D = 0.579\text{V}$$

$$I_D = 0.471\text{mA} \quad \#$$

4.

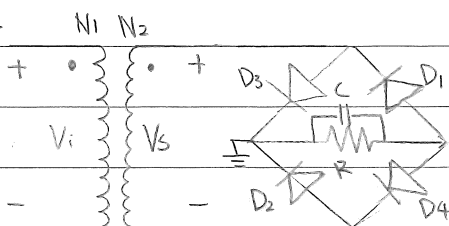

$V_f = 0.7\text{V}$ $F = 60\text{Hz}$ $R_L = 125\Omega$

$V_{op} = 15\text{V}$ $V_f = 0.3\text{V}$

(a)

$$15 = V_s - 0.7 \times 2 \Rightarrow V_s = 16.4\text{V}$$

$$V_s(t) = 16.4 \sin 377t$$


(b)

$$0.3 = \frac{15}{2 \times 60 \times 125 \times C} \Rightarrow C = \frac{15}{2 \times 60 \times 125 \times 0.3} = 3.33\text{mF}$$

(c)

$$\text{PIV} = 0.7 + 15 = 15.7\text{V} \quad \#$$

5.

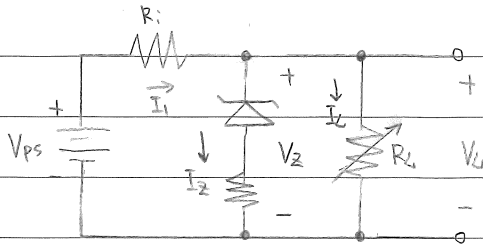

$$V_{ps} = 20V \pm 25\% (15 \sim 25)$$

$$I_L = 0 \sim 20mA$$

$$(a) V_Z = 10V \quad I_{Z(min)} = 5mA$$

$$R_i = \frac{15 - 10}{5mA + 20mA} = \frac{5}{25mA} = 0.2k\Omega$$

(b)

$$10 = V_{Z1} + 5 \times 125m$$

$$V_{Z1} = 9.875V$$

$$V_{ps} = 15V$$

$$I_Z = \frac{15 - 9.875}{240 + 5} = 20.9mA$$

$$V_Z = 9.875 + 5 \times 20.9m = 9.98V$$

$$V_{ps} = 25V$$


$$I_Z = \frac{25 - 9.875}{240 + 5} = 61.7mA$$

$$V_Z = 9.875 + 61.7m \times 5 = 10.183V$$

$$10.183 - 9.98 = 0.203V$$

(c)
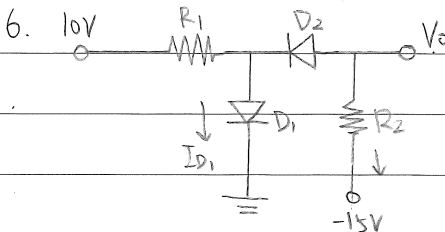
$$\text{percent source} = \frac{10 - 10.163}{24 - 16} \times 100\% = \frac{0.163}{8} \times 100\% = 2.03\% \quad \#$$



$$(a) R_1 = 10k\Omega \quad R_2 = 5k\Omega$$

設 D_1 on D_2 on

$$I_{R1} = \frac{10 - 0.7}{10k} = 0.93mA$$

$$I_{R2} = \frac{1.4 - (-15)}{5k} = 3.28mA$$

$$V_{D2} = -15 + 3.28m \times 5k - 0.7 = -2.1 \text{ (不合)}$$

$$(b) R_1 = 5k\Omega \quad R_2 = 10k\Omega$$

設 D_1 on D_2 on D_1 on D_2 off

$$I_{R1} = 1.86mA \quad I_{R2} = 1.64mA$$

$$I_{R1} = 0.93mA \quad V_{D2} = -15 - 0.7 < 0 \text{ (合)}$$

$$I_{D2} = -(1.86m - 1.64m) = -1.22mA \text{ (不合)}$$

$$V_O = -15V$$

設 D_1 on D_2 off

$$I_{R1} = 1.86mA \quad I_{R2} = 0mA$$

2. 很簡單

$$V_O = -15V \quad \#$$