

Homework 3 (Due date: 10/13)

HW3.1: (40 points)

Using small-signal parameters to find each amplifier's voltage gain and output resistance in Fig 3.1 (*channel length modulation and body effect cannot be ignored*).

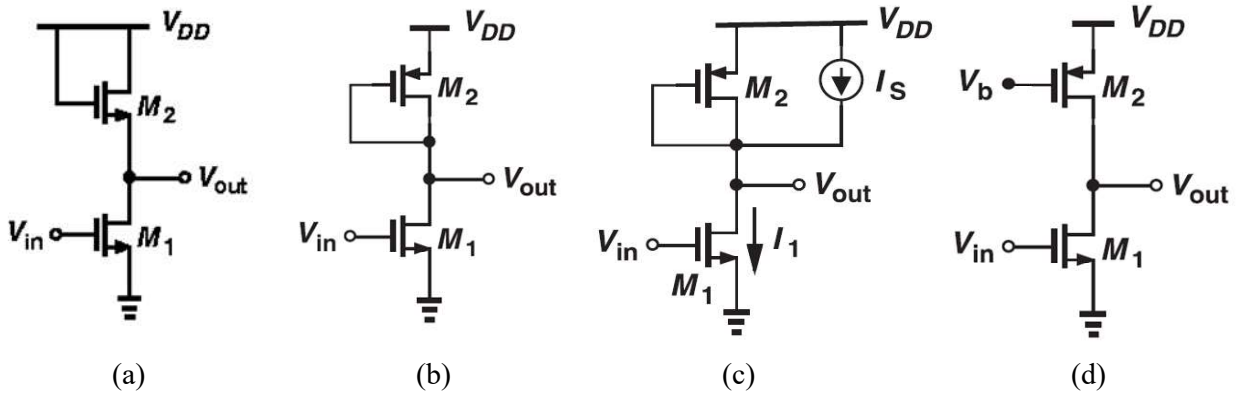


Fig. 3.1

HW3.2: (10 points)

Using small-signal parameters to derive the output resistance (R_{out}) in Fig. 3.2.

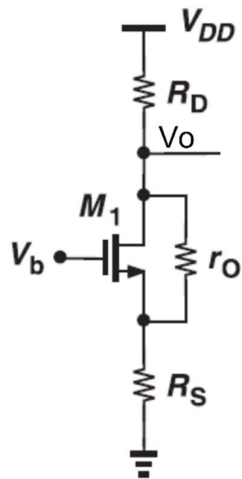


Fig. 3.2

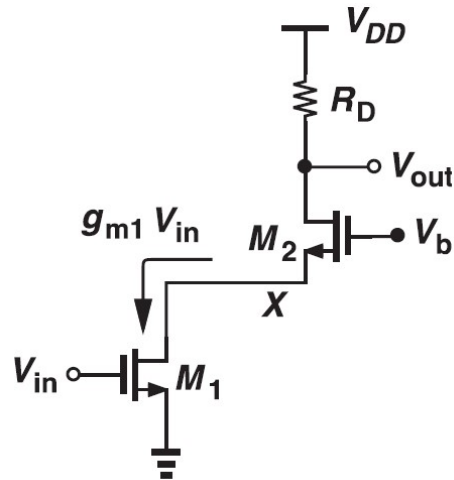


Fig. 3.3

HW3.3: (20 points)

Fig. 3.3 shows a common-gate circuit.


- If we define a minimum output voltage, $V_{out,min}$, how do you find out the valid input range of V_{in} ?
- Calculate the voltage gain and output resistance.

Homework 3 (Due date: 10/13)


HW3.4: (30 points)

Calculate the voltage gain and output resistance of circuits in Fig. 3.4.

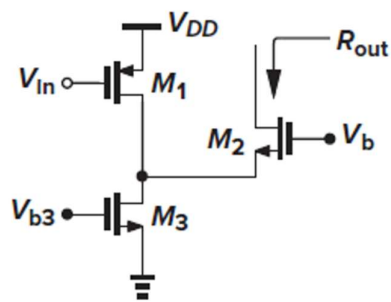Note: Fig. 3.4(a) only needs to calculate the output resistance.




(a)

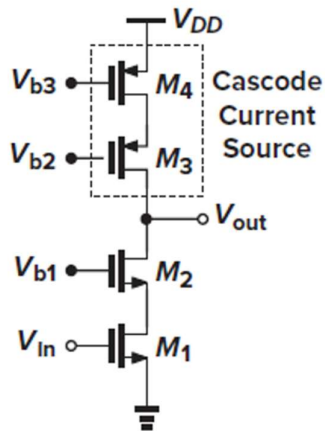

(b)


Fig. 3.4

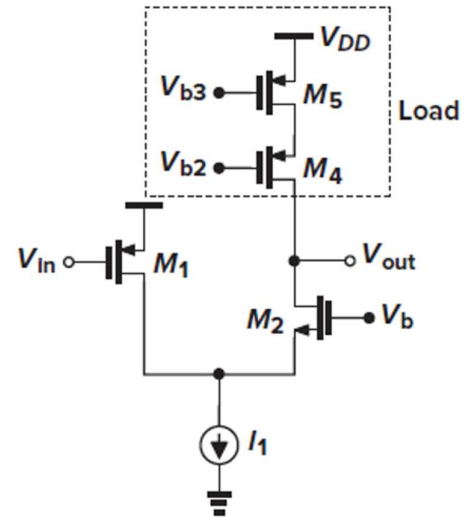

(c)

HW3.1

(a)

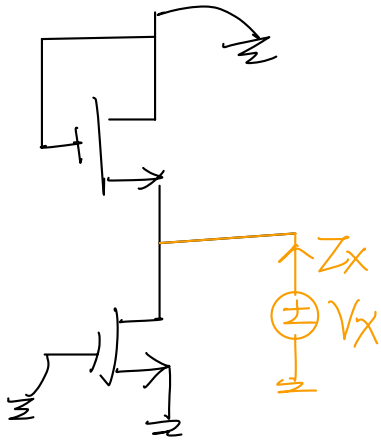


$$Z_x = (g_{m2} + g_{m2b} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}) V_x$$

$$R_{out} = \frac{V_x}{Z_x} = \frac{1}{g_{m2} + g_{m2b} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$$


$(1 + \mu)g_{m2}$
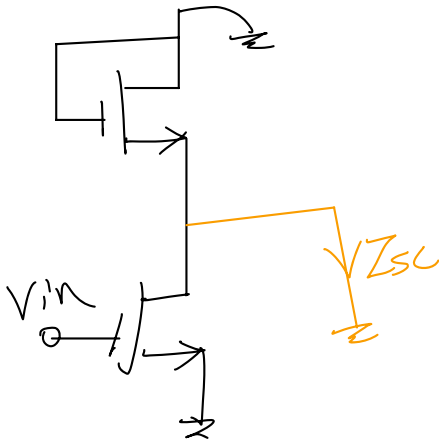
$$\text{or } R_{out} = \frac{1}{(1 + \mu)g_{m2}} \parallel r_{o1} \parallel r_{o2} \quad \#$$



$$I_{sc} = -g_{m1} V_{in}$$
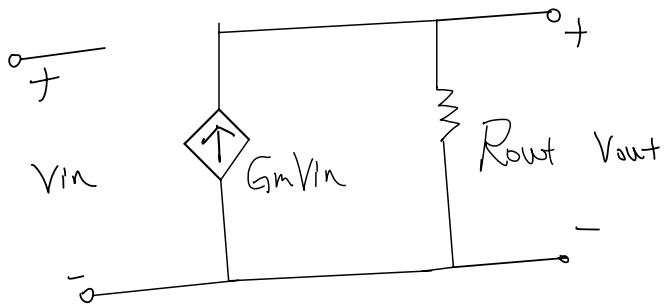
$$G_m = \frac{I_{sc}}{V_{in}} = -g_{m1}$$




$$A_v = G_m R_{out} \quad \#$$

$$A_v \approx \frac{-g_{m1}}{(1 + \mu)g_{m2}}$$

(b)

pmos $V_{SB} = 0$

No Body effect

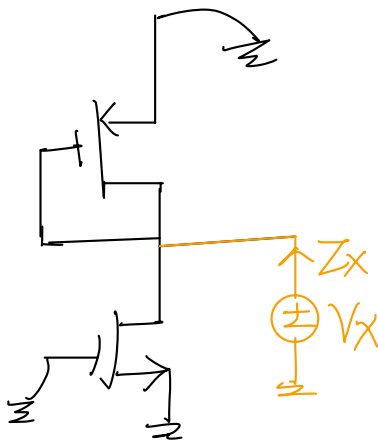


$$Z_x = (g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}) V_x$$

$$R_{out} = \frac{V_x}{Z_x} = \frac{1}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$$


$$\text{或 } R_{out} = \frac{1}{g_{m2}} \parallel r_{o1} \parallel r_{o2}$$

#

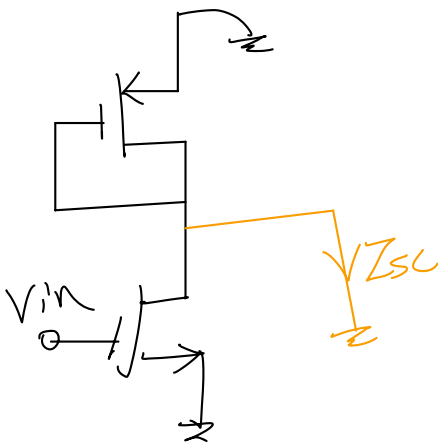

$$Z_{sc} = -g_{m1} V_{in}$$
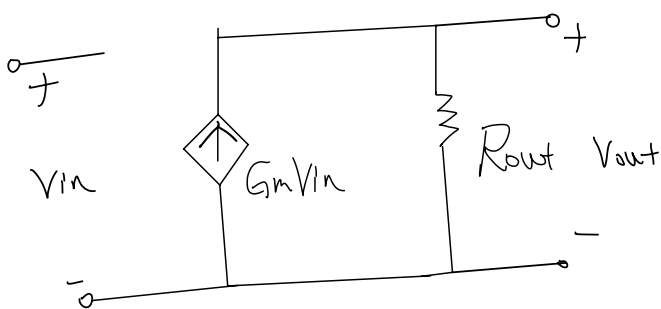
$$G_m = \frac{Z_{sc}}{V_{in}} = -g_{m1}$$



$$A_v = G_m R_{out} \quad \#$$

$$A_v \approx \frac{-g_{m1}}{g_{m2}}$$

少了 Body effect 的 factor
且在相同 (W/L) 下 pmos 的 g_{m2} 比 nmos 小
因此有比 ③ 题更大的 Gain

(c)

小訊号分析結果呈 (b) 題

但 $Z_2 = Z_1 - Z_s$ ，由 $g_m = \sqrt{2\beta_2 Z_2}$ 來看的話，會發現 g_{m2} 變小

若 $A_v \propto \frac{g_{m1}}{g_{m2}}$ 使得 A_v 變大

這題假設 $Z_s = \lambda - X$ 且 $0 < X < 1$


$$A_v \propto \frac{1}{\lambda X} \sqrt{\frac{\beta_1}{\beta_2}}$$

如果 $X = \frac{1}{4}$

$$\text{則 } A_v = \frac{\sqrt{2\beta_1 Z_1}}{\sqrt{2\beta_2 \frac{1}{4} Z_1}} = 2 \sqrt{\frac{\beta_1}{\beta_2}} \quad \text{變為原本的兩倍}$$

(D)

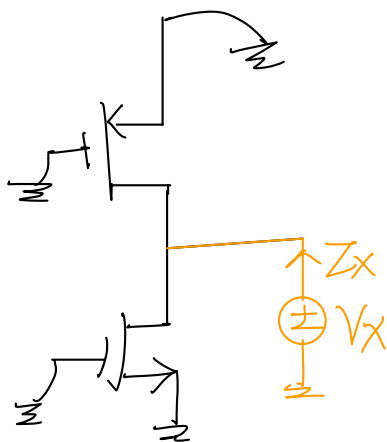$V_{gs2} = 0$ 所以 $g_{m2}V_{gs2} = 0$ 只剩下 r_o




$$Z_x = \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right)$$

$$R_{out} = \frac{V_x}{Z_x} = \frac{1}{\frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$$


或 $R_{out} = r_{o1} \parallel r_{o2}$

#

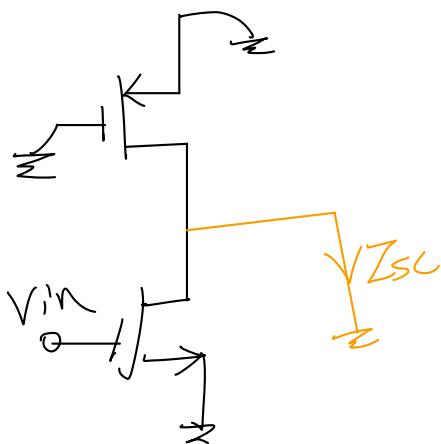

$$Z_{sc} = -g_{m1}V_{in}$$

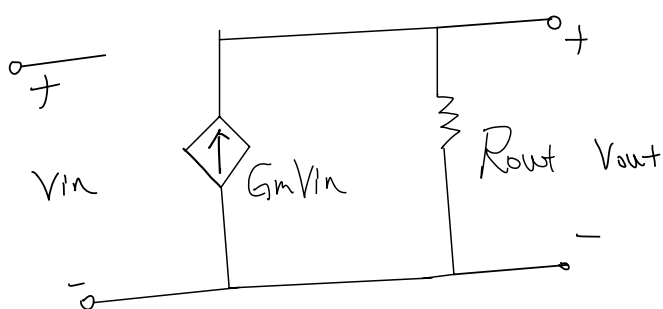
$$G_m = \frac{Z_{sc}}{V_{in}} = -g_{m1}$$




$$A_v = G_m R_{out} \quad \#$$

虽然有最大的 Gain
但 V_o 的直流单位难以被定义!!

HW3.2

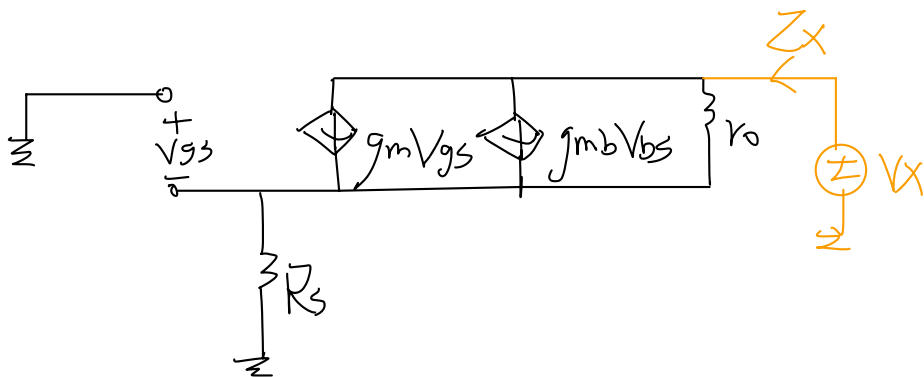
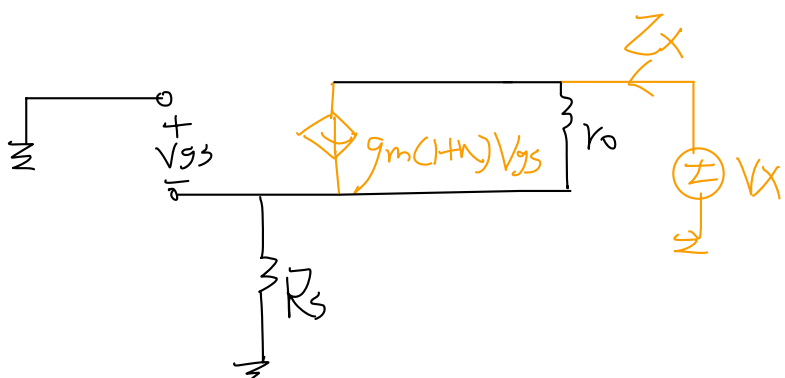
$$V_{bs} = V_{gs} \Rightarrow (g_m + g_{mb}) V_{gs} = (1 + \mu) g_m V_{gs}$$



$$V_{gs} = 0 - Z_x R_s = -Z_x R_s$$

$$V_x = Z_x R_s + Z_x [(1 + \mu) g_m R_s + 1] V_o$$

$$R_{out}' = \frac{V_x}{Z_x} = R_s + [(1 + \mu) g_m R_s + 1] V_o$$

$$\text{或 } R_{out}' = r_o + [(1 + \mu) g_m r_o + 1] R_s$$

$$R_{out} = R_o \parallel R_{out}' \quad \#$$

HW 3.3

(a)

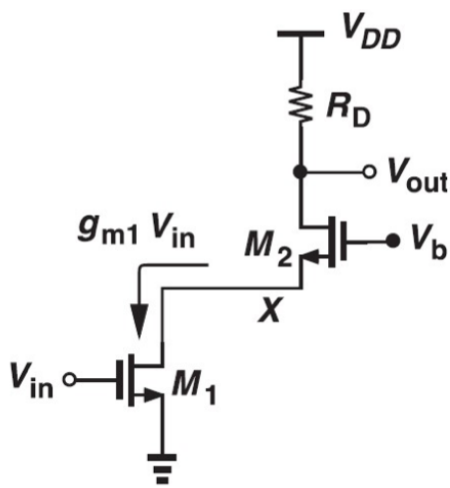


Fig. 3.3

$$V_{ZN(max)} - V_{TH1} + V_{GS2} \leq V_b \leq V_{out(min)} + V_{TH2}$$

$$V_{ZN(min)} \geq V_{TH1}$$

若 V_b 取 $V_{out(min)} + V_{TH2}$

則 $V_{ZN(max)} - V_{TH1} + V_{GS2} \leq V_{out(min)} + V_{TH2}$




$$\Rightarrow V_{ZN(max)} \leq V_{out(min)} + V_{TH1} + \cancel{V_{TH2}} - (V_{ov2} + \cancel{V_{TH2}})$$

$$\Rightarrow V_{TH1} \leq V_{ZN} \leq V_{out(min)} - V_{ov2} + V_{TH1} \quad \#$$

(b)

套用HW3.2的结果
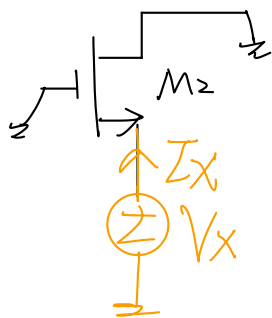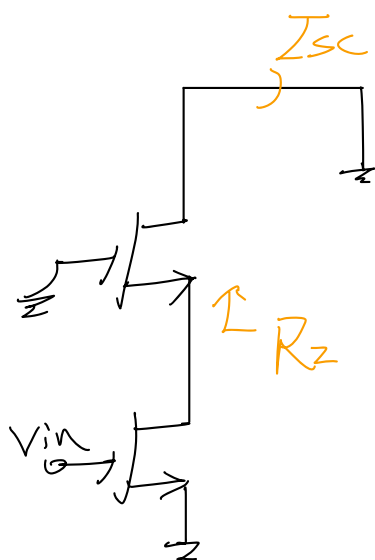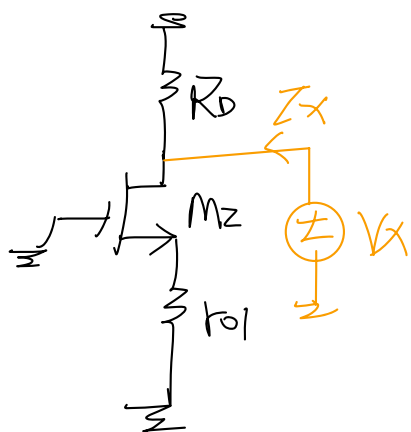
$$R_{out} = R_D \parallel \left\{ r_{o2} + [1 + (g_{m2} + g_{m2b})r_{o2}]r_{o1} \right\}$$




$$I_X = (g_{m2} + g_{m2b})V_X + \frac{V_X}{r_{o2}}$$

$$\Rightarrow R_2 = \frac{V_X}{I_X} = \frac{1}{g_{m2} + g_{m2b} + \frac{1}{r_{o2}}}$$

$$\text{或 } R_2 = \frac{r_{o2}}{1 + (g_{m2} + g_{m2b})r_{o2}}$$

$$I_{sc} = -g_{m1}V_{in} \frac{r_{o1}}{r_{o1} + R_2} = -g_{m1} \frac{r_{o1}[1 + (g_{m2} + g_{m2b})r_{o2}]}{r_{o1} + r_{o2} + (g_{m2} + g_{m2b})r_{o2}r_{o1}} V_{in}$$

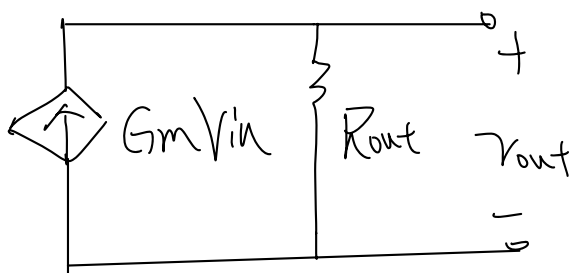
$$G_m = \frac{I_{sc}}{V_{in}} = -g_{m1} \frac{r_{o1}}{r_{o1} + R_2} = -g_{m1} \frac{r_{o1}[1 + (g_{m2} + g_{m2b})r_{o2}]}{r_{o1} + r_{o2} + (g_{m2} + g_{m2b})r_{o2}r_{o1}} \stackrel{(r_{o1} \gg R_2)}{\approx} -g_{m1}$$




$$A_v = G_m R_{out} \neq 1$$

HW 3.4

①

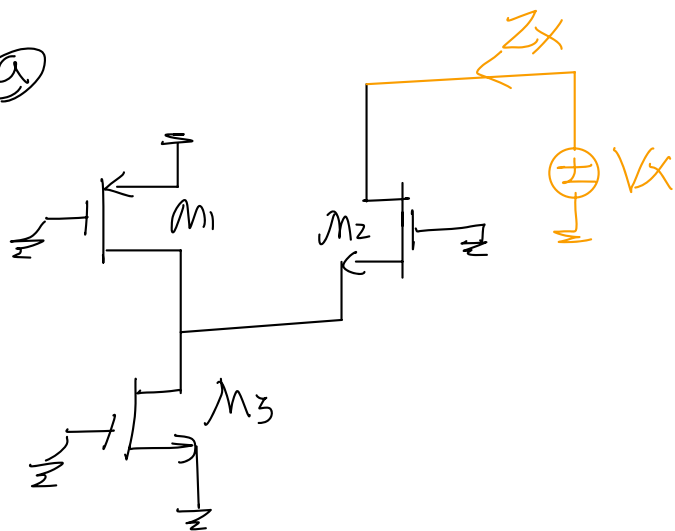


M_1 及 M_3 $g_m V_{gs} = 0$ 只剩下 r_o

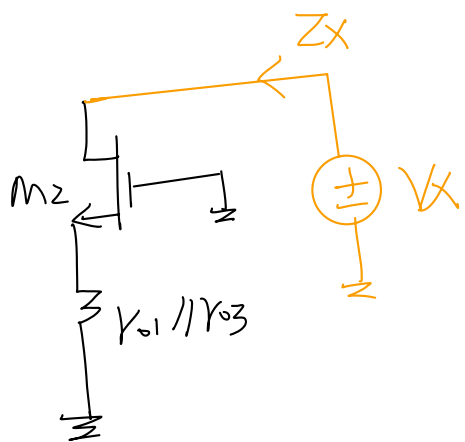



將 $r_{o1} // r_{o3}$ 當作 R_s ，即可套用 HW 3.2 的結果

$$R_{out} = r_{o2} + [1 + (g_{m2} + g_{m2b}) r_{o2}] (r_{o1} // r_{o3}) \quad \#$$

⑥

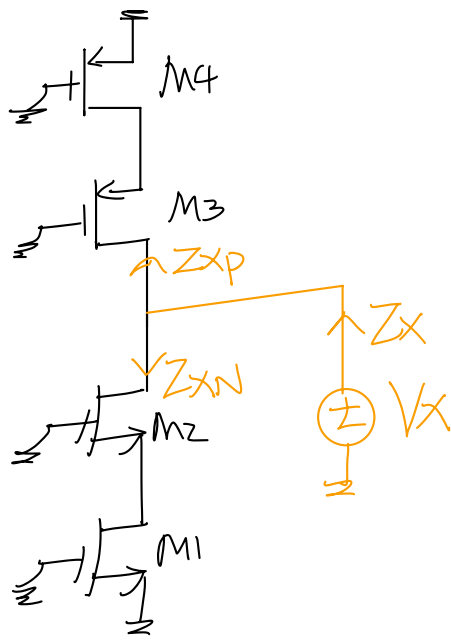

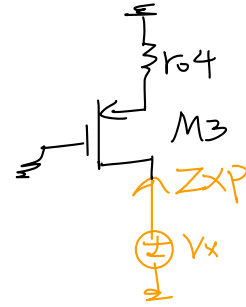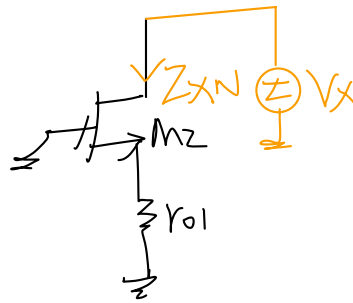
$M1, M4 \quad g_m V_{gs} = 0$ 只剩下 r_o
又可以套用 HW3.2 的结果



$$R_{oN} = \frac{V_x}{Z_{XN}} = r_{o2} + [1 + (g_{m2} + g_{m2b})r_{o2}]r_{o1}$$


$$R_{oP} = \frac{V_x}{Z_{XP}} = r_{o3} + [1 + (g_{m3} + g_{m3b})r_{o3}]r_{o4}$$
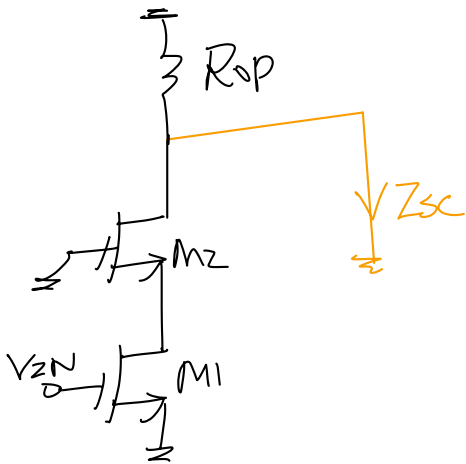
$$R_{out} = R_{oN} \parallel R_{oP} \quad \#$$



$$Z_{sc} = -g_{m1} V_{ZNX} \frac{r_{o1}}{r_{o1} + \frac{r_{o2}}{1 + (g_{m2} + g_{m2b})r_{o2}}} \approx -g_{m1} V_{ZNX}$$

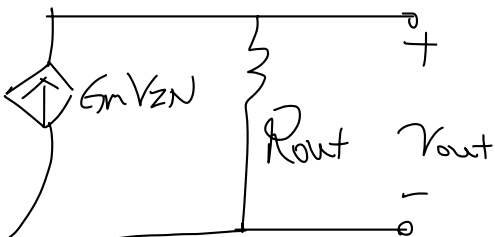
$$G_m = \frac{Z_{sc}}{V_{in}} \approx -g_{m1}$$



$$A_v = G_m R_{out} \quad \#$$

(C)

M_1 及 M_5 $g_m V_{gs} = 0$ 乘以 r_o

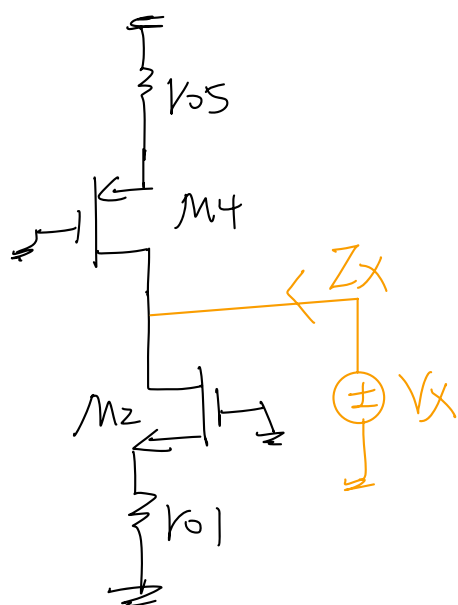


套用 HW 3.3 ⑥

$$R_{op} = r_{o4} + [1 + (g_{m4} + g_{m4b})r_{o4}]r_{o5}$$


$$R_{on} = r_{o2} + [1 + (g_{m2} + g_{m2b})r_{o2}]r_{o1}$$
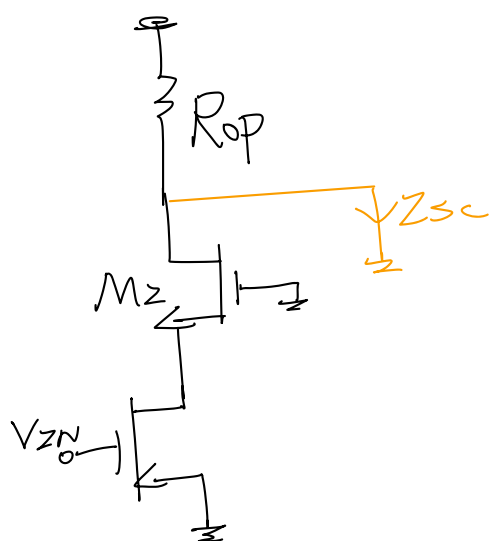
$$R_{out} = R_{on} \parallel R_{op} \quad \#$$




$$Z_{sc} = -g_{m1}V_{ZN} \times \frac{r_{o1}}{r_{o1} + \frac{r_{o2}}{1 + (g_{m2} + g_{m2b})r_{o2}}} \approx -g_{m1}V_{ZN}$$
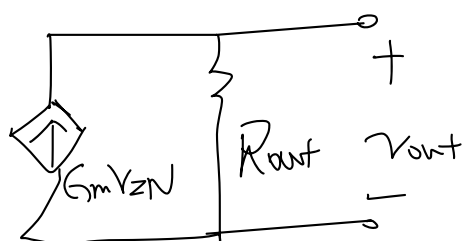
$$G_m = \frac{Z_{sc}}{V_{in}} \approx -g_{m1}$$



$$A_v = G_m R_{out}$$

〈補充〉 HW4.2

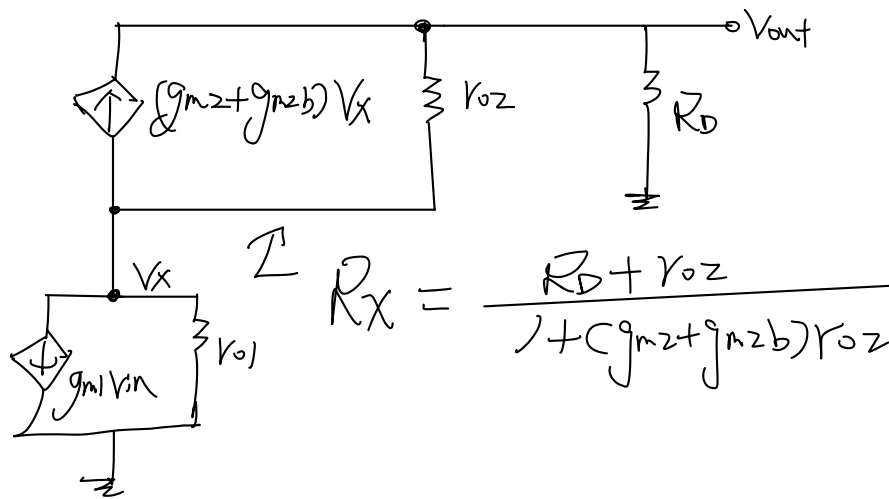

$$R_X = \frac{R_D + r_{o2}}{1 + (g_{m2} + g_{m2b})r_{o2}}$$


$$\frac{V_o}{V_{in}} = \frac{V_o}{V_X} \times \frac{V_X}{V_{in}}$$

$$\frac{V_X}{V_{in}} = -g_{m1}r_{o1} \quad (X)$$

這是錯的!!


要考慮 r_{o1} 與 R_X 的分流!!

這是HW3.3 有多位同學犯的錯誤，下次不要再寫錯了！

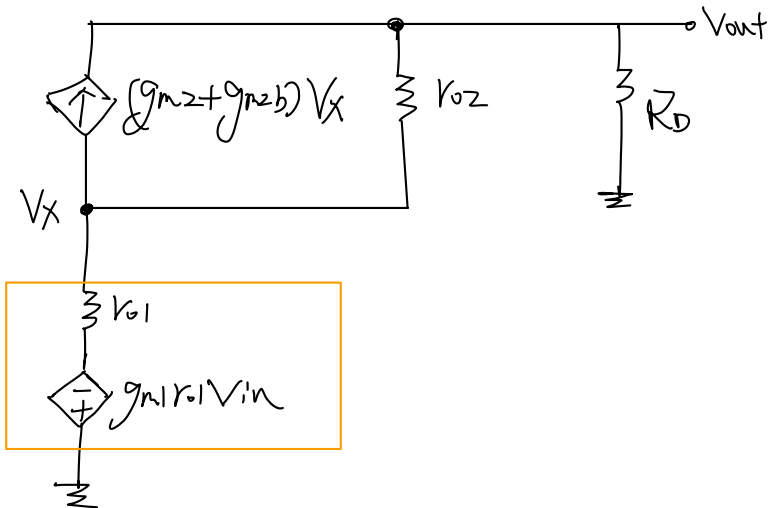

可将 M_1 换作等效电压源，不就变回单纯的CG放大器

利用电压放大器模型做等效!!

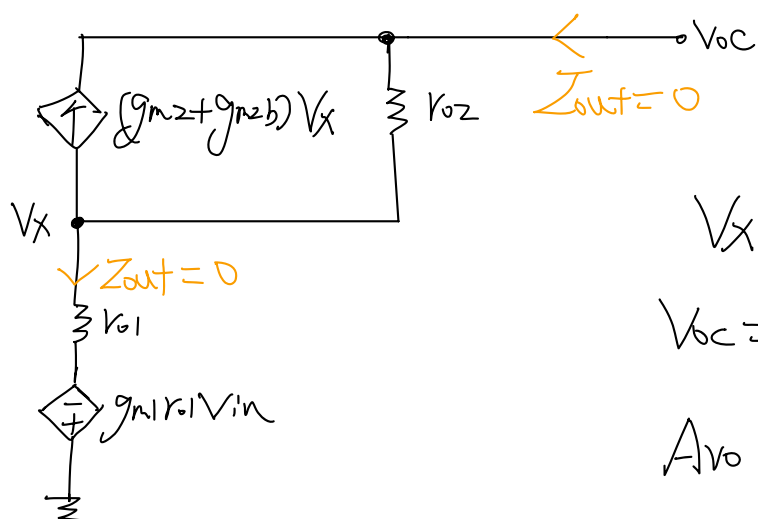


$$V_X = -g_{m1}r_{o1}V_{in}$$

$$V_{oc} = -g_{m1}r_{o1}V_{in} - (g_{m2}+g_{m2b})r_{o2}V_X$$

$$A_{vo} = \frac{V_{oc}}{V_{in}} = -g_{m1}r_{o1}[(g_{m2}+g_{m2b})r_{o2} + 1]$$
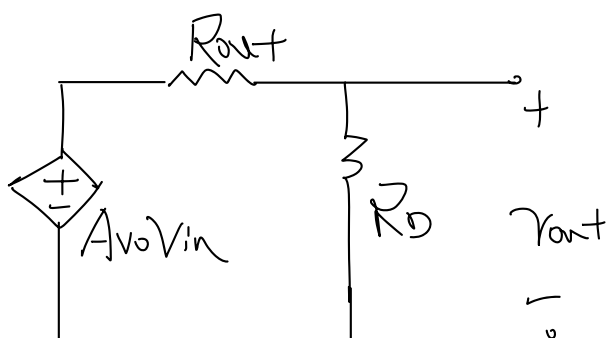
$$R_{out} = r_{o1} + r_{o2} + (g_{m2}+g_{m2b})r_{o2}r_{o1}$$



$$\frac{V_{out}}{V_{in}} = A_{vo} \frac{R_D}{R_{out} + R_D} \quad \#$$

補充〈轉導法〉

Lemma In a linear circuit, the voltage gain is equal to $-G_m R_{out}$, where G_m denotes the transconductance of the circuit when the output is shorted to ground [Fig. 3.32(b)] and R_{out} represents the output resistance of the circuit when the input voltage is set to zero [Fig. 3.32(c)].

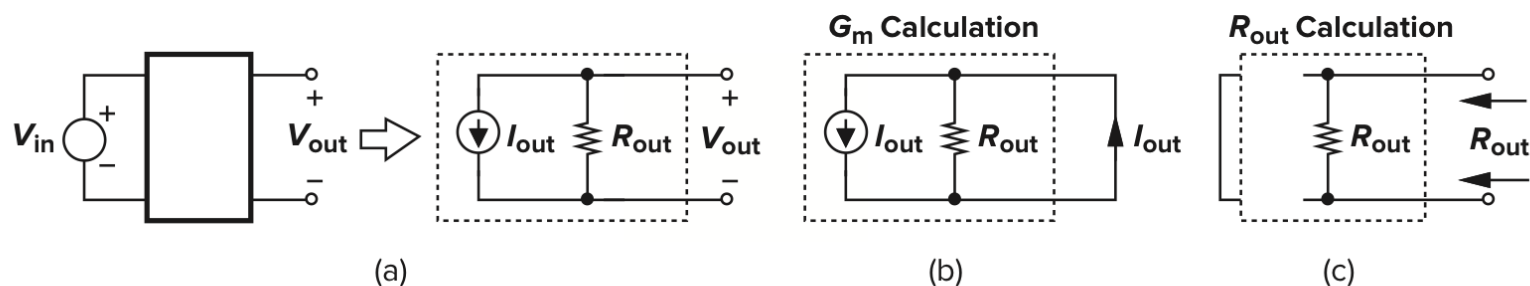


Figure 3.32 (a) Norton equivalent of a linear circuit; (b) G_m calculation; and (c) R_{out} calculation.

The lemma can be proved by noting that the output voltage in Fig. 3.32(a) is equal to $-I_{out} R_{out}$, and I_{out} can be obtained by measuring the short-circuit current at the output. Defining $G_m = I_{out} / V_{in}$, we have $V_{out} = -G_m V_{in} R_{out}$. This lemma proves useful if G_m and R_{out} can be determined by inspection. Note the direction of I_{out} .


使用轉導法可以將較為複雜的電路，簡化的比較容易分析，是一種還不錯的電路分析方式，至少我自己是蠻喜歡用的，但也不一定要使用轉導放大器模型，其他四種放大器的模型也可以拿來做等效哦。
同學們可以自己練習看看，如何使用轉導法來做分析！！

CS:

$$G_m = \frac{g_m r_o}{R_s + [1 + (g_m + g_{mb}) R_s] r_o}$$

$$R_{out} = R_s + [1 + (g_m + g_{mb}) R_s] r_o$$

$$A_v = -G_m (R_{out} \parallel R_D)$$

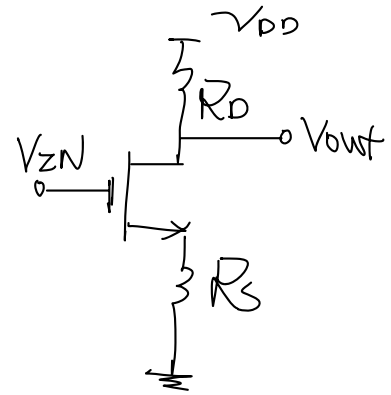


CD:

$$G_m = g_m \frac{r_o}{R_D + r_o}$$

$$R_{out} = \frac{R_D + r_o}{1 + (g_m + g_{mb}) r_o}$$

$$A_v = G_m (R_{out} \parallel R_s)$$

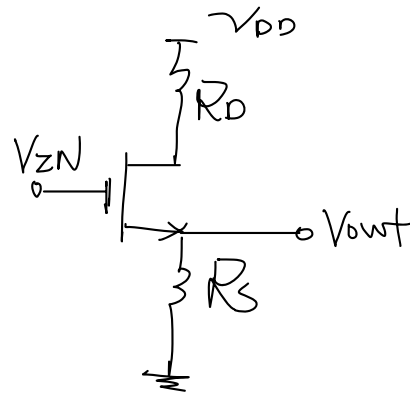

CG:

$$G_m = \frac{1 + (g_m + g_{mb}) r_o}{R_s + [1 + (g_m + g_{mb}) R_s] r_o}$$

$$R_{out} = R_s + [1 + (g_m + g_{mb}) R_s] r_o$$

$$A_v = G_m (R_D \parallel R_{out})$$

