

國立臺灣科技大學答案卷



National Taiwan University of Science and Technology Answer Sheet

姓名/Name 張恒豪 學號/Student ID B11002110 班級/Class 四電子二乙
科目/Course title 電子學 日期/Date 112.3.29

評分 Score	教師簽章 Signature of Lecturer
	85

記分欄 從此處開始寫起。試卷用紙務須節用，非經主試認可不得續用其他紙張作答。/Please write from here.

1.

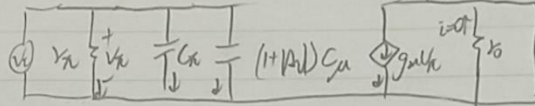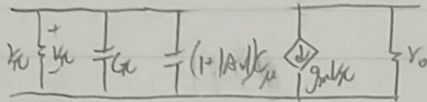

求使 $\frac{v_o}{v_x} = 0$ 的頻率 \Rightarrow 等同於輸出端短路

$$|A_v| = |g_m v_o|$$

$$f_B = \frac{1}{2\pi} \cdot \frac{1}{(C_{p\mu} + C_{\mu})}$$

$$C_{p\mu} = Y_{\mu} C_{\mu}$$

$$C_{p\mu} = Y_{\mu} (1 + g_m v_o) C_{\mu}$$

$$= \frac{1}{2\pi Y_{\mu} [C_{\mu} + (1 + g_m v_o) C_{\mu}]} \text{ Hz} \quad \#1$$

$$g_m v_x + \frac{v_x}{2\pi f_1 (1 + |A_v|) C_{\mu}} + \frac{v_x}{2\pi f_1 C_{\mu}} + \frac{v_x}{r_n} = 0$$

$$g_m + 2\pi f_1 [(1 + |A_v|) C_{\mu} + C_{\mu}] + \frac{1}{r_n} = 0$$

$$\Rightarrow 2\pi f_1 [(1 + |A_v|) C_{\mu} + C_{\mu}] = -\frac{1}{r_n} - g_m$$


$$\Rightarrow f_1 = \frac{-\frac{1}{r_n} - g_m}{2\pi [(1 + |A_v|) C_{\mu} + C_{\mu}]} \quad \#1$$

$$\Rightarrow |f_1| = \frac{g_m + \frac{1}{r_n}}{2\pi [(1 + g_m v_o) C_{\mu} + C_{\mu}]} \text{ Hz} \quad \#1$$

-10

訂正在 P.3

2.

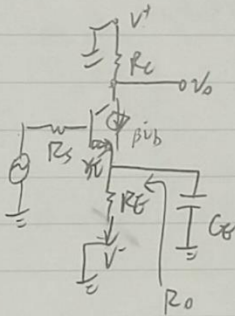

$|A_v|$: C_E 為開路

$$\frac{v_o}{v_i} = \frac{Y_{\mu} + (1 + \beta) i_B}{R_s + Y_{\mu} + (1 + \beta) R_E} \cdot \frac{1}{Y_{\mu} + (1 + \beta) R_E} \cdot \beta (R_L) = \frac{-\beta R_L}{R_s + Y_{\mu} + (1 + \beta) R_E} \cdot \frac{1}{Y_{\mu} + (1 + \beta) R_E} \quad \#2$$

$|A_v|$: C_E 為短路:

$$\frac{v_o}{v_i} = \frac{Y_{\mu}}{R_s + Y_{\mu}} \cdot \frac{1}{Y_{\mu}} \cdot \beta (R_L) = \frac{-\beta R_L}{R_s + Y_{\mu}} \cdot \frac{1}{Y_{\mu}} \quad \#2$$

$|f_1|$: 當變晶體 E 極等效為開路:

$$|R_E| = \frac{1}{2\pi f_1 C_E} \Rightarrow 2\pi |f_1| = \frac{1}{R_E C_E} \Rightarrow |f_1| = \frac{1}{2\pi R_E C_E} \text{ Hz} \quad \#2$$

$|f_2|$: C_E 被短路的頻率:


$$|f_2| = \frac{1}{2\pi \tau}$$

$$\tau = C_E (R_o) = C_E (R_E // \frac{Y_{\mu} + R_s}{1 + \beta})$$

$$\Rightarrow |f_2| = \frac{1}{2\pi C_E (R_E // \frac{Y_{\mu} + R_s}{1 + \beta})} \text{ Hz} \quad \#2$$

可轉頁再寫

3

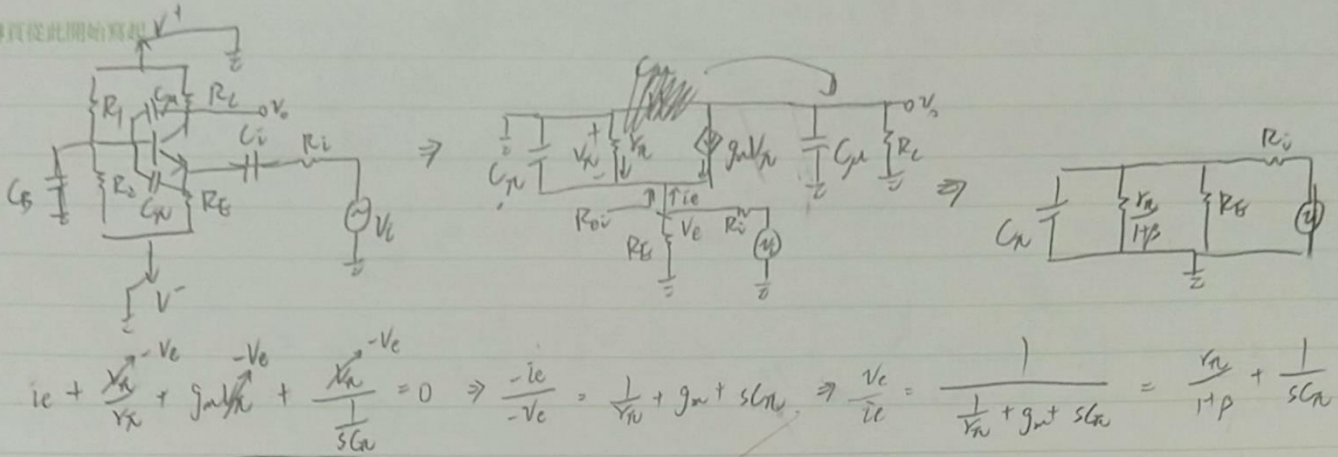


$$i_c + \frac{v_o}{R_C} + \frac{v_o}{R_L} = 0 \Rightarrow \frac{-i_c}{-v_o} = \frac{1}{R_C} + \frac{1}{R_L} \Rightarrow \frac{v_o}{i_c} = \frac{1}{\frac{1}{R_C} + \frac{1}{R_L}} = \frac{R_C R_L}{R_C + R_L}$$

$$f_{Hn} = \frac{1}{2\pi \tau_{pn}} = \frac{1}{2\pi C_n \left(\frac{R_C R_L}{R_C + R_L} \right)} \text{ Hz}$$

$$f_{H\mu} = \frac{1}{2\pi \tau_{p\mu}} = \frac{1}{2\pi C_{\mu} R_C} \text{ Hz}$$

4.

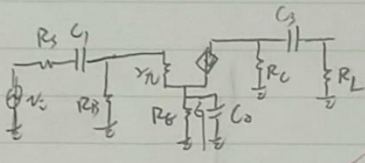求 τ_1 : C_1, C_2 短路

$$\tau_1 = C_1 (R_1 + R_2 // R_E)$$

求 τ_2 : C_1, C_3 短路


$$\tau_2 = C_2 \left(R_E // \left(\frac{R_1 + R_2 // R_E}{1 + \beta} \right) \right)$$

求 τ_3 : C_1, C_3 短路

$$\tau_3 = C_3 (R_C + R_L)$$

$$\Rightarrow \omega_L = \frac{1}{\tau_1} + \frac{1}{\tau_2} + \frac{1}{\tau_3}$$
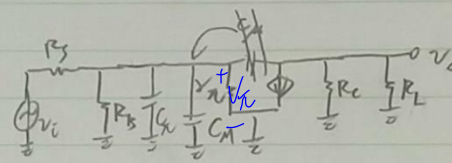
$$= \frac{1}{C_1 (R_1 + R_2 // R_E)} + \frac{1}{C_2 \left(R_E // \left(\frac{R_1 + R_2 // R_E}{1 + \beta} \right) \right)} + \frac{1}{C_3 (R_C + R_L)} \text{ rad/s}$$






$$\tau_p = (R_1 // R_2 // R_E) (C_1 + (1 + \beta) C_{\mu})$$

$$|A_v| = \frac{R_1 // R_2}{R_1 + R_2 // R_E} \cdot \frac{1}{1 + \beta} \cdot \frac{R_C // R_L}{R_E}$$

$$|A_v| = \left| \frac{v_o}{v_i} \right| = \frac{R_C // R_L}{R_E} \cdot \beta \cdot \frac{R_1 // R_2}{R_1 + R_2 // R_E}$$

$$\Rightarrow \omega_H = \frac{1}{\tau_p} = \frac{1}{(R_1 // R_2 // R_E) \left[C_1 + \left(1 + \beta \cdot \frac{R_C // R_L}{R_E} \right) C_{\mu} \right]} \text{ rad/s}$$

5.

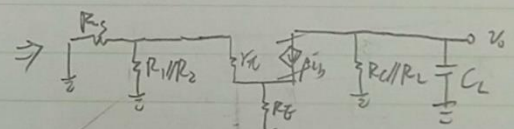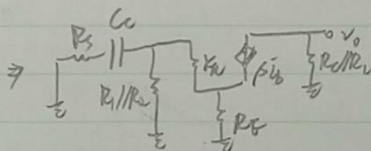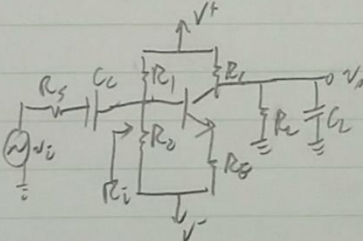


$$|A_v| = \frac{R_i}{R_s + R_i} \cdot \frac{1}{\beta} \cdot \frac{R_C // R_L}{R_E}$$

$$R_i = R_1 // R_2 // (R_E + (1 + \beta) R_E)$$


$$= \frac{R_1 // R_2 // (R_E + (1 + \beta) R_E)}{R_s + R_1 // R_2 // (R_E + (1 + \beta) R_E)} \cdot \frac{\beta \cdot R_C // R_L}{R_E + (1 + \beta) R_E} \text{ V/V}$$

$$f_L = \frac{1}{2\pi C_1 \left[R_s + \left(\frac{R_1 // R_2 // (R_E + (1 + \beta) R_E)}{\beta} + R_E \right) \right]} \text{ Hz}$$
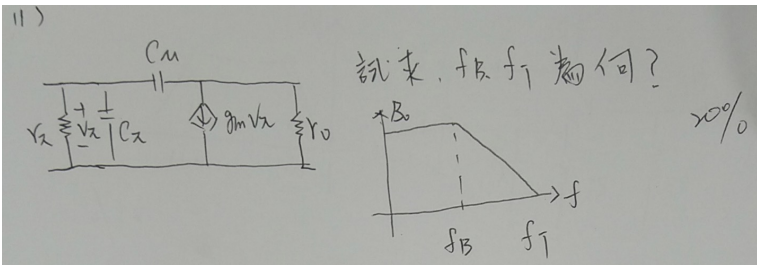
$$f_H = \frac{1}{2\pi C_2 \left(\frac{R_C // R_L}{\beta} \right)} \text{ Hz}$$



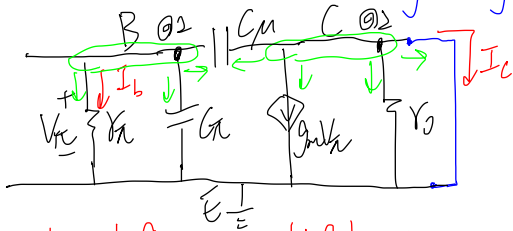Connect the collector to the signal ground to determine the high frequency effect to the BJT:



By the definition, $|h_{fe}| = 1$ at $f = f_T$.

$$h_{fe} = \frac{I_c}{I_b}$$

By KCL:

$$\textcircled{1}: I_b + \frac{v_x}{\frac{1}{sC_\pi}} + \frac{v_x}{\frac{1}{sC_\mu}} = 0 \Rightarrow I_b = -v_x(sC_\pi + sC_\mu)$$

$$\textcircled{2}: -\frac{v_x}{\frac{1}{sC_\mu}} + g_m v_x + I_c = 0 \Rightarrow I_c = v_x(sC_\mu - g_m)$$

$$= -\frac{sC_\mu - g_m}{sC_\pi + sC_\mu} = -\frac{C_\mu}{C_\pi + C_\mu} + \frac{g_m}{s(C_\pi + C_\mu)}$$

$j\omega = j2\pi f$

$$\Rightarrow |h_{fe}| = \sqrt{\left(-\frac{C_\mu}{C_\pi + C_\mu}\right)^2 + \left(\frac{g_m}{2\pi f(C_\pi + C_\mu)}\right)^2} \approx \frac{g_m}{2\pi f(C_\pi + C_\mu)}$$

$C_\pi \ll C_\mu, A \ll 1$
 $B \approx \left(\frac{10^3}{10^6}\right)^2 \gg 1$

\Rightarrow When $|h_{fe}| = 1$, $f = f_T$:

$$|h_{fe}| = 1 = \frac{g_m}{2\pi f_T(C_\pi + C_\mu)} \Rightarrow f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} \quad \#1$$