

### HW6.1 (20 points)

Calculate the close-loop input and output resistance ( $R_{in,CL}$  and  $R_{out,CL}$ ) using small-signal parameters.

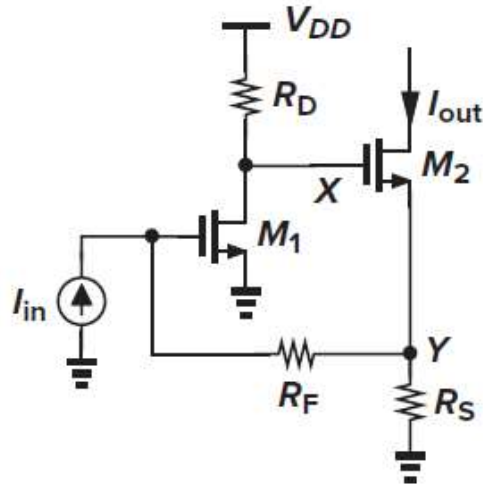


Fig. 6.1

### HW6.2 (20 points)

As shown in Fig. 6.2(a), please prove that the loop gain,  $I_F/I_t$  (shown in Fig. 6.2(c)), is the same as that using  $V_F/V_t$  (shown in Fig. 6.2(b)).

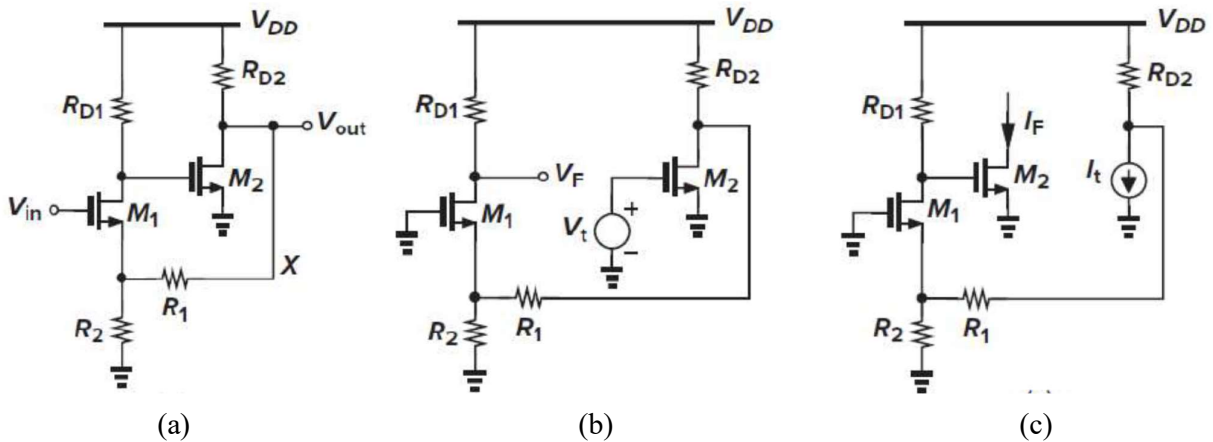


Fig. 6.2

### HW6.3 (40 points)

Using feedback techniques, calculate the input and output impedance and voltage gain of each circuit in Fig. 6.3. Using small-signal parameters to represent your solutions.

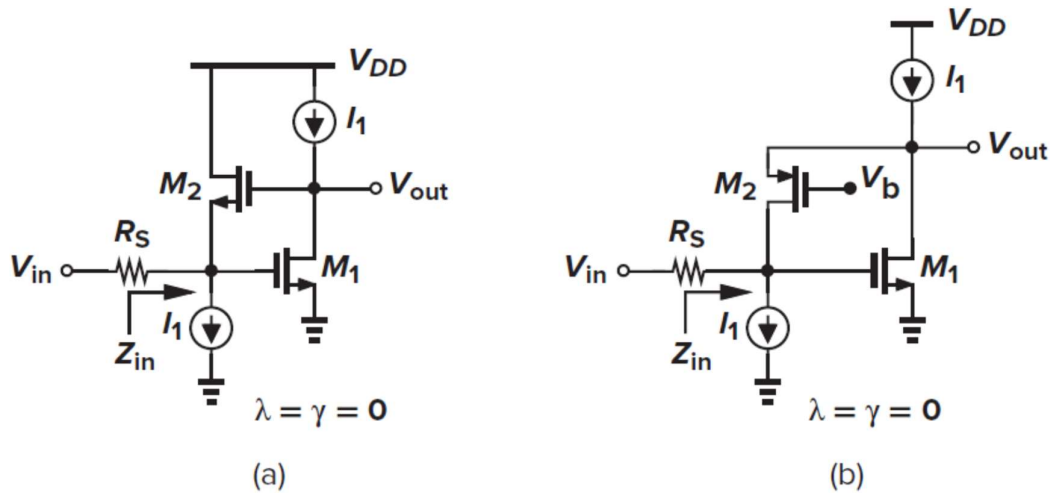


Fig. 6.3

### HW6.4 (20 points)

In the circuit of Fig. 6.4, assuming that  $\lambda = \gamma = 0$ , calculate the closed-loop gain and output impedance. Using small-signal parameters to represent your solutions.

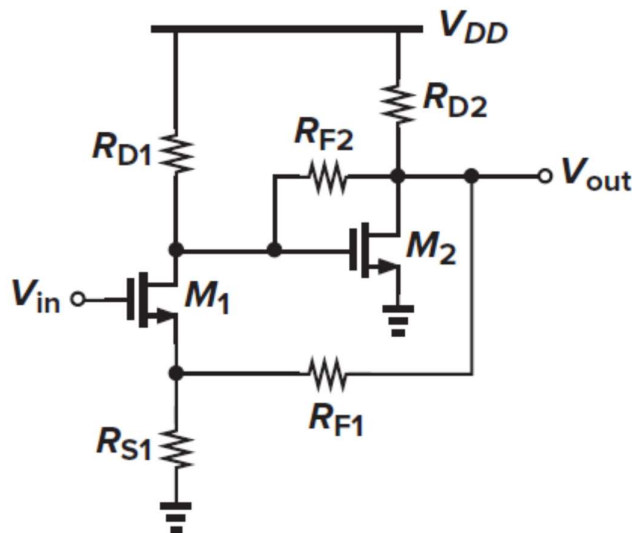


Fig. 6.4