

陳子成

B10702131

台灣科技大學一百零八學年度下學期期末考

科目名稱：電路學(二) 開課系所：電子系 ET2104301 地點：國際大樓 IB306

考試時間：109 年 6 月 4 日 下午 13:20 至 15:10 (可使用工程計算機)

1. (10%) Please sketch the magnitude characteristic of the Bode plot, labeling all critical slopes and points for the following function:

$$G(j\omega) = \frac{0.2(j\omega + 1)}{j\omega[(j\omega/12)^2 + (j\omega/36) + (1/144)]}$$

1st zero +
2nd zero = 36

2. (10%) Please find I_o in the network in Fig. 1.

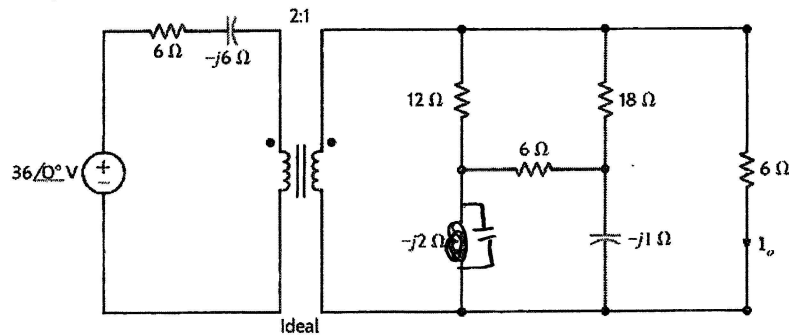


Fig. 1

3. (20%) The circuit in Fig. 2 is operated at steady state before the switch open.
 (a) Please use the Laplace transforms to calculate the current $i(t)$ for $t > 0$. (10%)
 (b) Please determine the transfer function of V_o/V_i for $t > 0$. (10%)

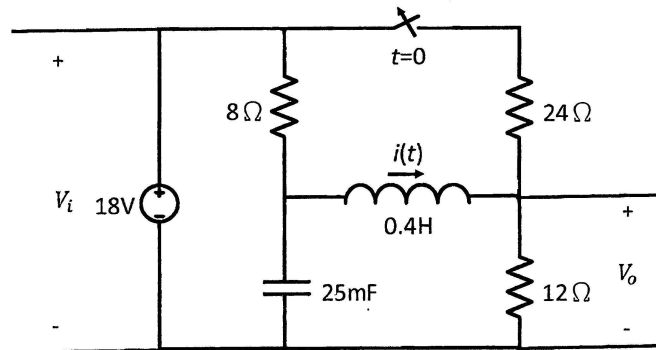


Fig. 2

4. (15%) Please use the Laplace transforms to calculate the current $i_L(t)$ in Fig. 3.

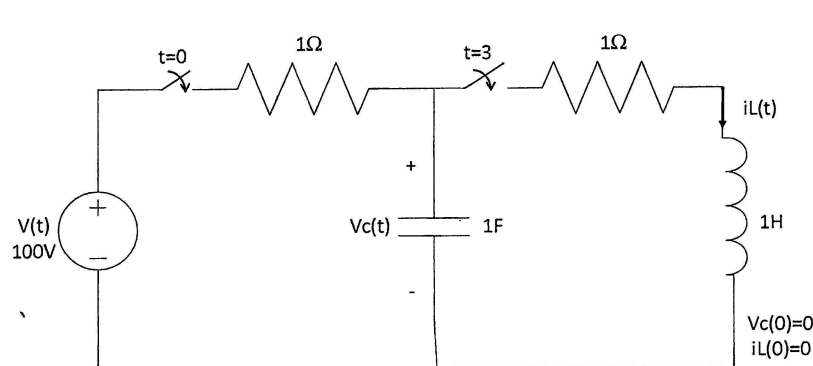


Fig. 3

$$f(t-3) = e^{-3s}$$

5. (10%) Please find Z parameters for the two-port network shown in Fig. 4 and determine the voltage gain of the entire circuit with a $4\text{k}\Omega$ load attached to the output.

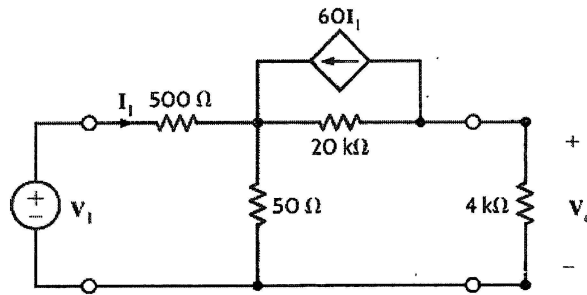


Fig. 4.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

6. (15%) Please modify the circuit in Fig. 5 to form a high-pass notch filter, and then determine the transfer function from the input voltage to the output voltage (V_o/V_{in}), plot the magnitude of the transfer function v.s. angular frequency, and analyze the frequency responses including the notch frequency ω_n , resonant frequency ω_o , low-frequency gain and high-frequency gain.

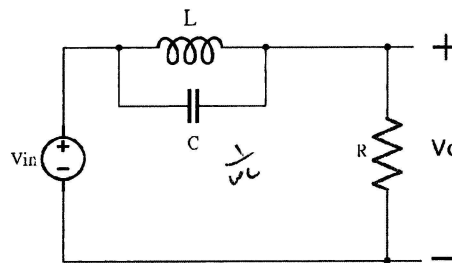


Fig. 5.

$$\omega_n \times \omega_o = \omega_o^2 \quad R = L \cdot C$$

$$\frac{1}{R} \cdot \omega_o L = \frac{1}{\omega_o R C} R = Q_s$$

$$B_V = \frac{\omega_o}{Q_s}$$

有2個極值點 一個是 ω_o
一個是 Notch

7. (10%) A balanced Y-connected load and a balanced Δ -connected load are supplied by a three-phase 480-Vrms 50Hz generator. The branch impedances of the Y and Δ loads are $26\angle 35^\circ \Omega$ and $34\angle -50^\circ \Omega$, respectively.

(a) Please determine the active and reactive powers drawn by Y and Δ -connected loads. (5%)

(b) Please determine the phasor voltage and phasor current for any one branch of each three-phase load, and substitute into the power equation for balanced three-phase loads. Given that the phase angle for Y system V_{AN} is 30° and the phase angle for Δ system V_{BA} is 180° . (5%)

8. (10%) Given the circuit in Fig. 6, please find the complex power supplied by the source, and the source power factor. If $f = 50\text{Hz}$, please find $V_s(t)$.

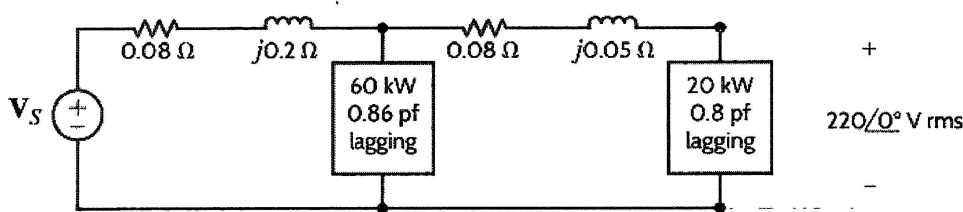


Fig. 6

$$\text{pf} \text{ and } V_s(t)$$

$$220\angle 0^\circ \text{ V rms}$$