

台灣科技大學一百零八學年度下學期作業（二）

科目名稱：電路學(二) 開課系所：電子系 ET2104301

繳交期限：即日起至 109.5.17

- (15%) The switch in Fig. 1 has been closed for a long time and is opened at $t = 0$. Please use Laplace transform to find $i(t)$ for $t > 0$.

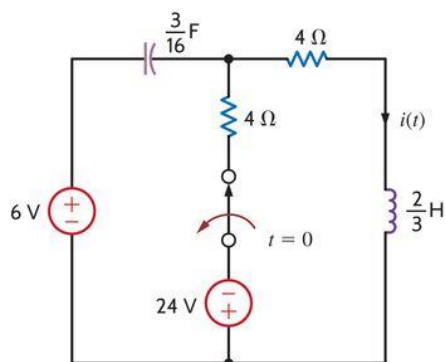


Fig. 1.

- (15%) Please use loop analysis to find $v_o(t)$ for $t > 0$ in Fig. 2.

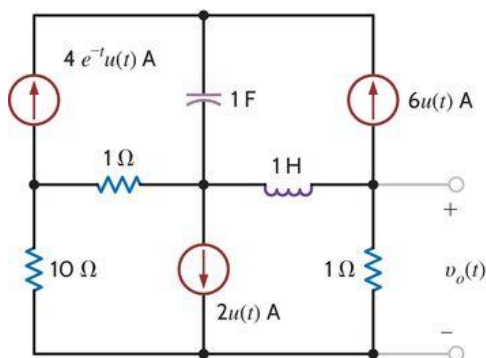


Fig. 2.

- (15%) The switch shown in Fig. 3 moves from position 1 to position 2 at $t = 0$. Please use Laplace transforms to find $v(t)$ for $t > 0$

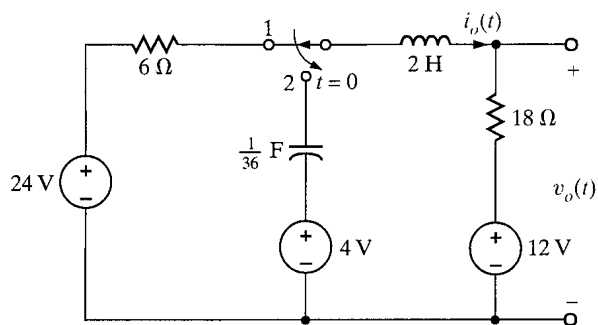


Fig. 3.

4. (15%) In Fig. 4, the switch moves from the position 1 to the position 2 at $t = 0$. Please use Laplace transform to find $v(t)$ for $t > 0$.

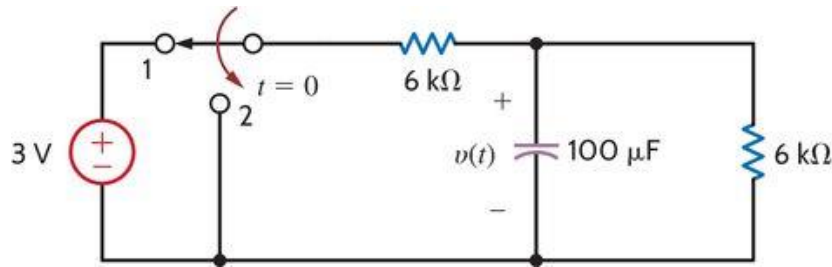


Fig. 4.

5. (20%) Please sketch the magnitude characteristic of the Bode plot(10%) and use Matlab to prove(10%), labeling all critical slopes and points for the function below:

$$G(j\omega) = \frac{10^4(j\omega + 2)}{(j\omega + 10)(j\omega + 100)}$$

6. (20%) Please find $f(t)$ by given the following functions $F(s)$.

(a) (5%) $F(s) = \frac{(s^2 + 5s + 4)}{(s + 2)(s + 4)(s + 8)}$

(b) (5%) $F(s) = \frac{s(s + 6)}{(s + 3)(s^2 + 6s + 18)}$

(c) (5%) $F(s) = \frac{(s + 4)(s + 8)}{s(s^2 + 8s + 32)}$

(d) (5%) $F(s) = e^{-3s} \frac{(95s + 100)}{s(s^2 + 2s + 2)}$