

Lab1 MOSFET

Department of Electronic and Computer Engineering
National Taiwan University of Science and Technology
MSIC Lab

Professor : 鍾勇輝


TA : 郭駿浩、郭哲原

2024/03/06




**Analog Integrated Circuit
Design and Applications**

 
- Lab1_1：利用Virtuoso了解MOSFET的特性。
- 實驗步驟：試著利用Virtuoso將圖一的電路描述出來，讓Length = 0.18um，Width = 1um， $V_{DS} = 1.8$ V。試著將 V_{GS} 從0 V到1.8 V每次增加0.01 V，觀察 I_{DS} 。即為模擬 $I_{DS} - V_{GS}$ Characteristic Curve。



$$\frac{W}{L} = \frac{1\mu m}{0.18\mu m}$$

 


MOSFET I-V Curve

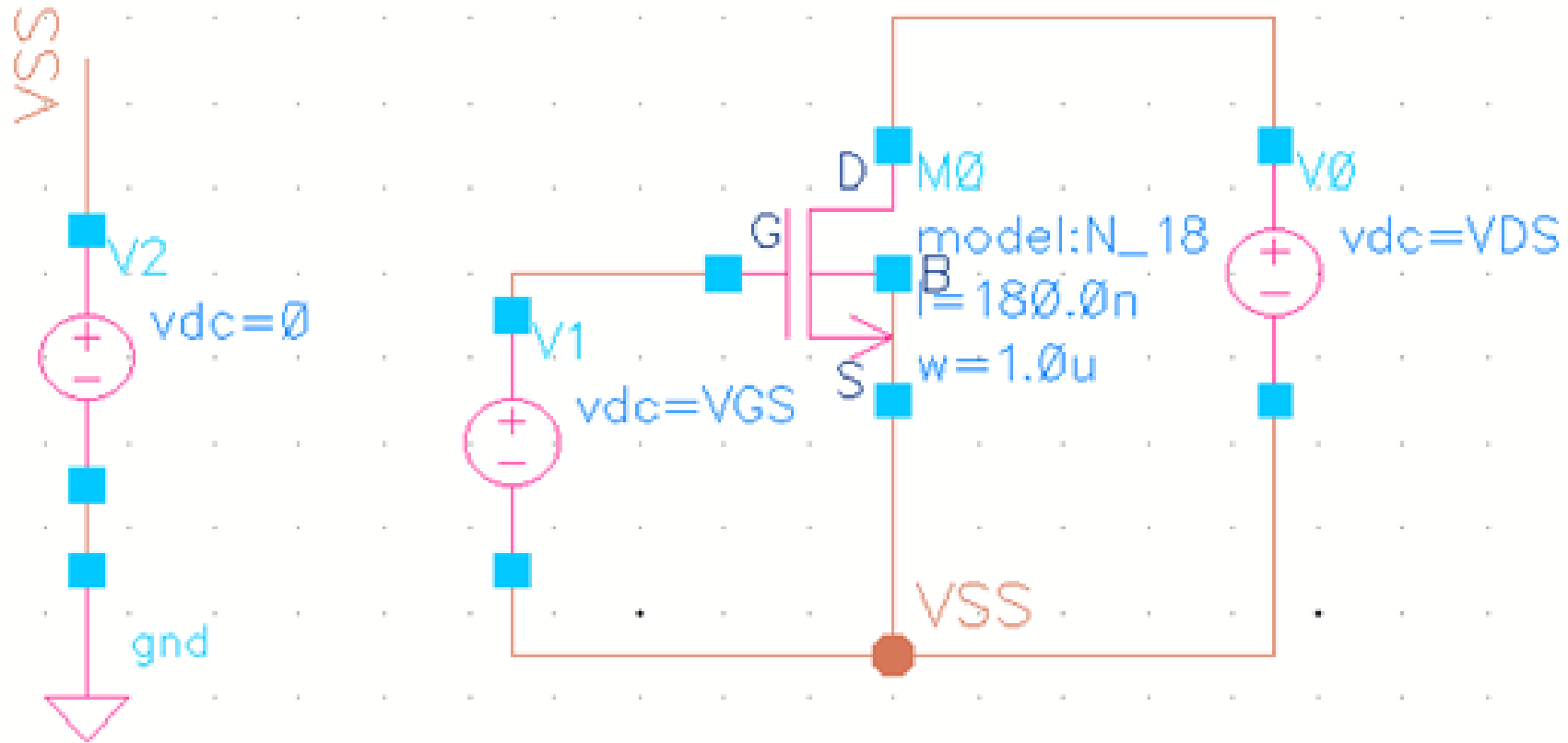


MOSFET I-V Curve

1.

 



2.


 


3.選擇cic018.l這個檔案


(路徑: /home/學號/cic18/CIC_PDK/model/New_Folder)

MOSFET I-V Curve

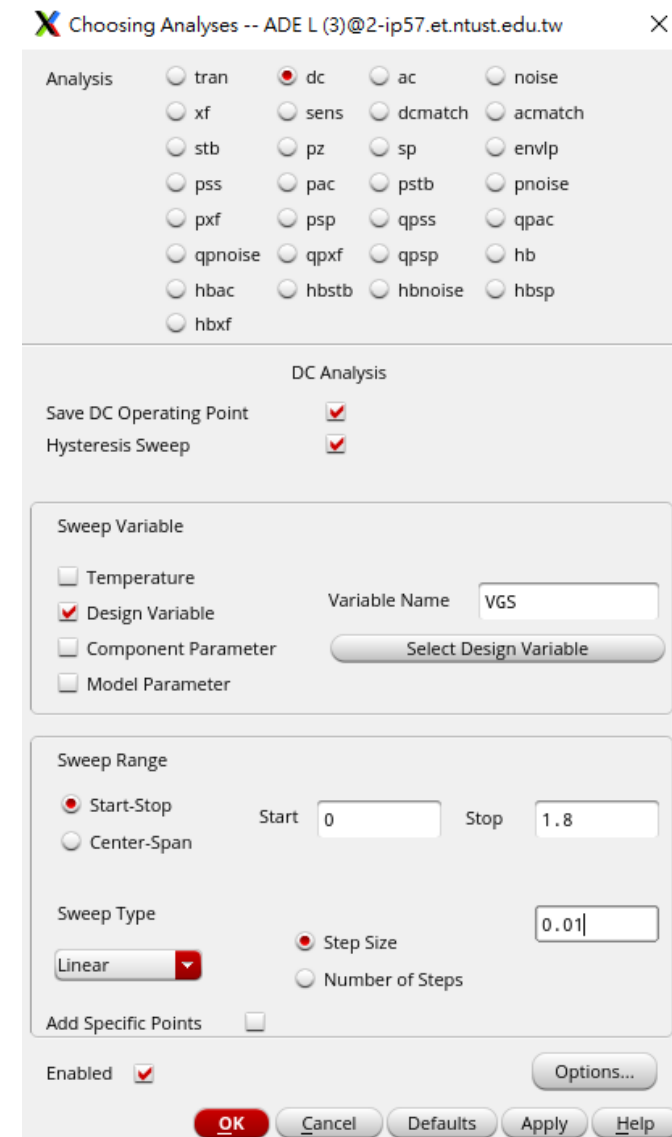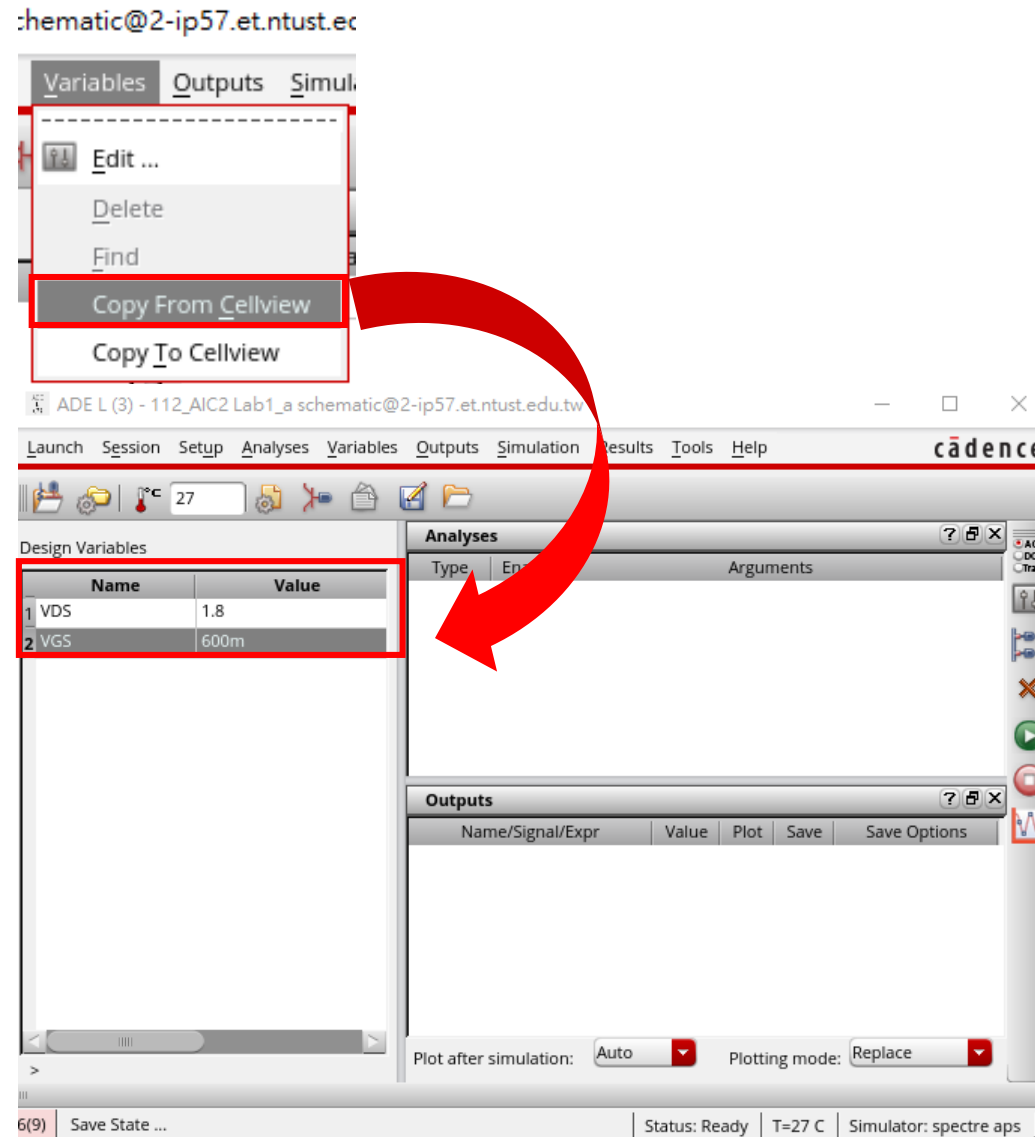


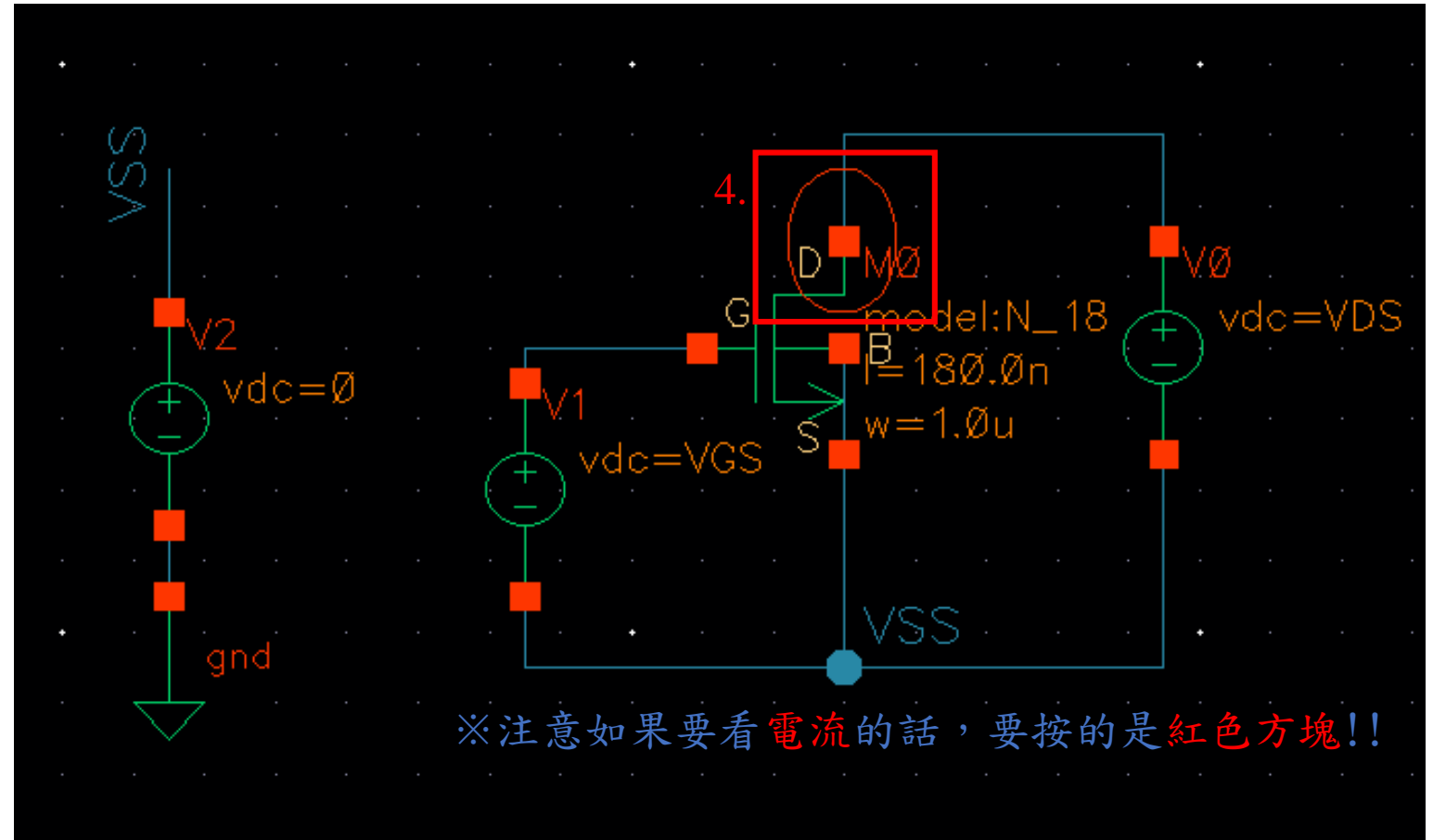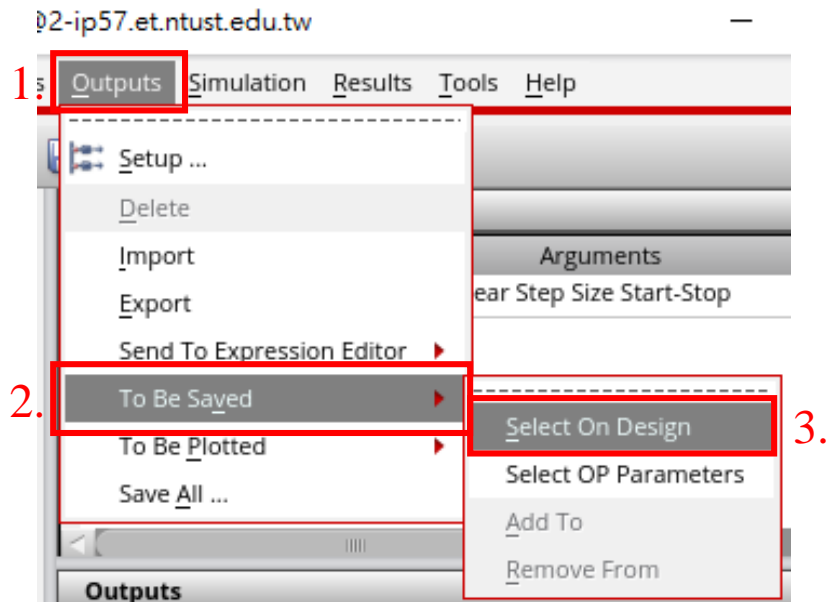

MOSFET I-V Curve

 

 
- Lab1_2：改變NMOS的Width，例如把Width放大兩倍，放大三倍，模擬 $I_{DS} - V_{GS}$ Characteristic Curve觀察 I_D 的變化。
- 實驗步驟：試著利用Hspice將圖一的電路描述出來，讓 Length = 0.18um，Width = 1um/ 2um / 3um， $V_{DS} = 1.8$ V。試著將 V_{GS} 從0 V到1.8 V每次增加0.01 V，觀察 I_{DS} 。即為模擬 $I_{DS} - V_{GS}$ Characteristic Curve。




$$\frac{W}{L} = \frac{1\mu m}{0.18\mu m}$$



$$\frac{W}{L} = \frac{2\mu m}{0.18\mu m}$$

$$\frac{W}{L} = \frac{3\mu m}{0.18\mu m}$$

 


MOSFET I-V Curve

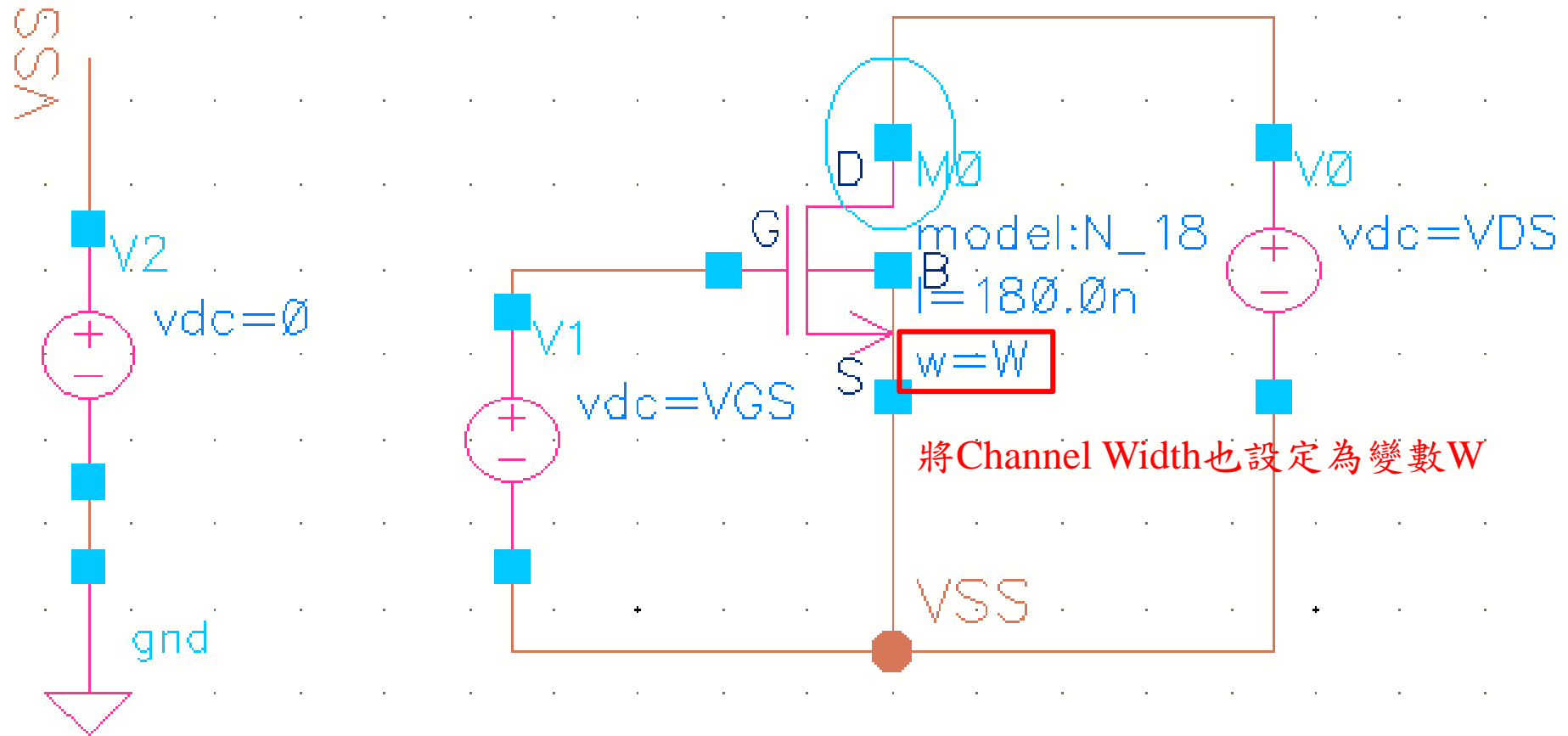

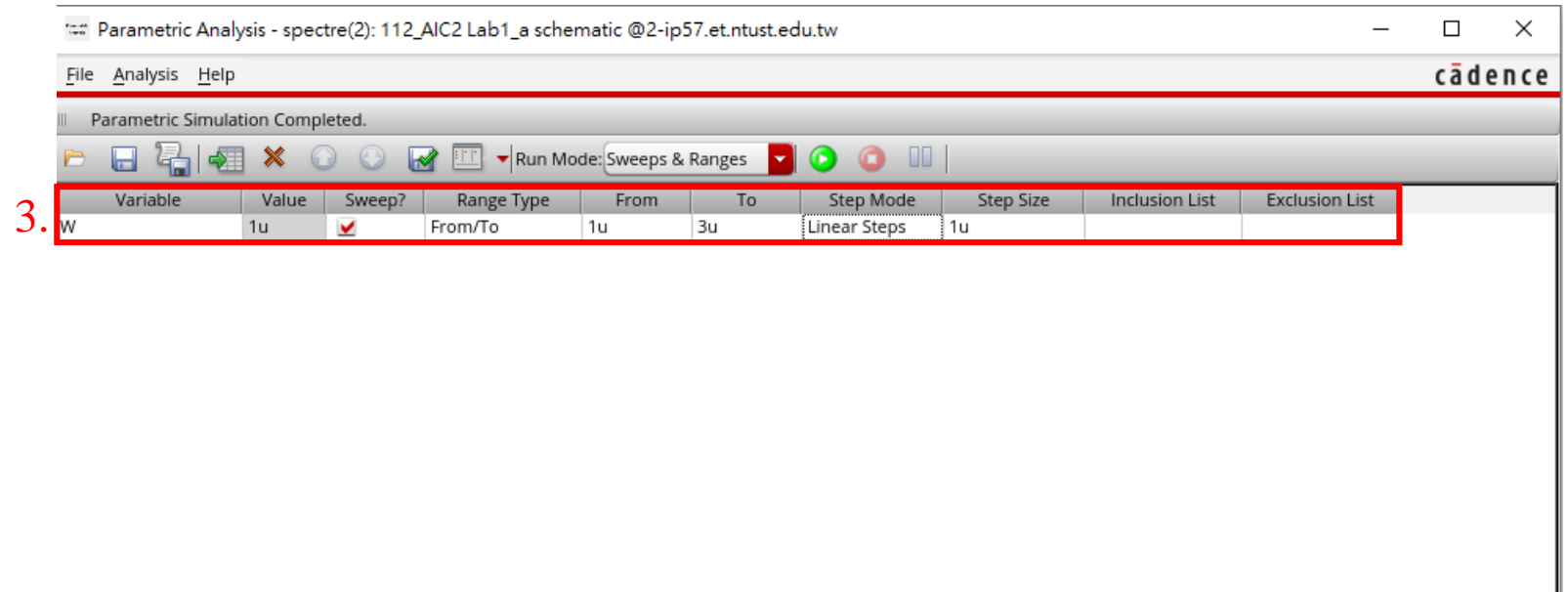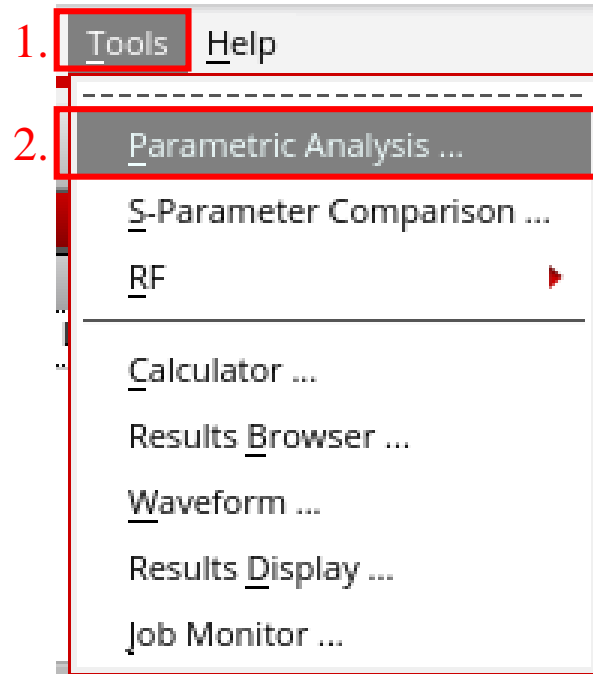


MOSFET I-V Curve


Tue Feb 20 12:39:44

 

 - Lab1_3：由Gate端輸入偏壓 $V_{GS} = 1.8\text{ V}$ ，接著將 V_{DS} 從0 V到1.8 V每次增加0.01 V，觀察 $I_{DS} - V_{DS}$ Characteristic Curve。



 
$$\frac{W}{L} = \frac{1\mu m}{0.18\mu m}$$




- 改變Gate端的偏壓 $V_{GS} = 1.5\text{ V}$ 、 $V_{GS} = 1.2\text{ V}$ 、 $V_{GS} = 0.9\text{ V}$ 、 $V_{GS} = 0.6\text{ V}$ 、 $V_{GS} = 0.3\text{ V}$ 、 $V_{GS} = 0\text{ V}$ ，看 $I_{DS} - V_{DS}$ Characteristic Curve，因為MOS在飽和區時， $I_{DS} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$ 由模擬可知，在只有改變 V_{GS} 值的情況下，可以証明得知 I_{DS} 與 V_{GS} 的平方成正比。
- 使 $V_{GS} = 1.8\text{ V}$ ， $V_{DS} = 1.8\text{ V}$ 改變NMOS元件Channel Width，讓Width = 1.2um，Width = 1.8um，Width = 2.4um，模擬 $I_{DS} - V_{DS}$ Characteristic Curve， $I_{DS} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$ ，由模擬可知道， I_{DS} 與Width成正比，而模擬出來的結果確實也成線性關係。

 
- 用 .dc 看 NMOS 特性曲線
 1. I_D 對 V_{GS}
($V_{DS} = 0 \sim 1.8 \text{ V}$; $V_{DS} = 0.9 \text{ V}$)
 2. I_D 對 V_{DS}
($V_{DS} = 0 \sim 1.8 \text{ V}$; Sweep $V_{GS} = 0.6 \text{ V}$ 、 0.7 V 、 0.8 V)



 - 用 .dc 看 PMOS 特性曲線
 1. I_D 對 V_{SG}
($V_{SD} = 0 \sim 1.8 \text{ V}$; $V_{SD} = 0.9 \text{ V}$)
 2. I_D 對 V_{SD}
($V_{SD} = 0 \sim 1.8 \text{ V}$; Sweep $V_{SG} = 0.6 \text{ V}$ 、 0.7 V 、 0.8 V)
 3. V_{TH} 對 V_{BS}
($V_{BS} = 0 \sim 1.8 \text{ V}$; $V_{SG} = 0.7 \text{ V}$; $V_{SD} = 0.9 \text{ V}$)



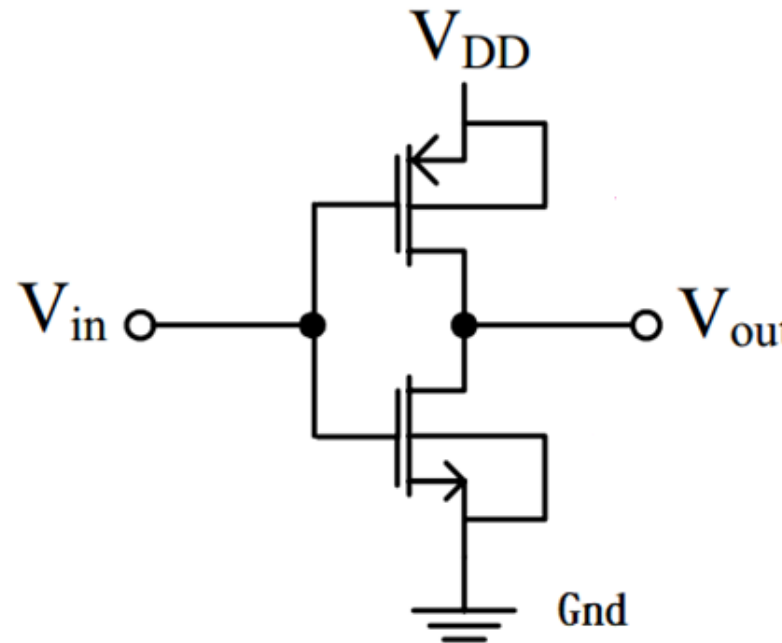- 利用Virtuoso模擬Inverter電路，使用.tran看輸入和輸出的時序圖
- V_{out} 's loading cap is 50fF
- Design (W/L) to meet
 - L-H and H-L delays less than 100ps
 - Both rise and fall time of V_{out} are less than 100ps



Edit Object Properties@2-ip57.et.ntust.edu.tw

Apply To:

Show: ☐ system ☒ user ☒ CDF

Property	Value	Display
Library Name	analogLib	off
Cell Name	vpu1se	off
View Name	symbol	off
Instance Name	V0	off

User Property	Master Value	Local Value	Display
lvignore	TRUE		off

CDF Parameter	Value	Display
Frequency name for 1/period		off
Noise file name		off
Number of noise/freq pairs	0	off
DC voltage		off
AC magnitude		off
AC phase		off
XF magnitude		off
PAC magnitude		off
PAC phase		off
Voltage 1	0 V	off
Voltage 2	1.8 V	off
Period	1u s	off
Delay time	10n s	off
Rise time	50p s	off
Fall time	50p s	off
Pulse width		off
Temperature coefficient 1		off
Temperature coefficient 2		off
Nominal temperature		off

- 檔名：Lab1_學號.pdf
- 請勿抄襲，抄襲者0分
- 評分標準：
 - 規定時間內繳交，逾時者會扣分(如有其他原因導致未繳交請與助教聯絡)
 - 符合題目要求規格
 - 完整的設計流程(考慮的原因詳細分析，設計參數如何決定)
 - 模擬結果與分析
 - 面積越小分數越高

Thank You For Your Attention