

B10702131 陳瑞鳳

台灣科技大學一百零八學年度下學期平時考 (一)

科目名稱：電路學(二) 開課系所：電子系 ET2104301 地點：國際大樓 IB306

考試時間：109 年 3 月 26 日 下午 13:20 至 15:10 (可使用工程計算機)

1. (15%) Please find I_o in Fig. 1.

檢付電路。

計算題組

把式子寫出來，用克拉克斯！

寫法用對

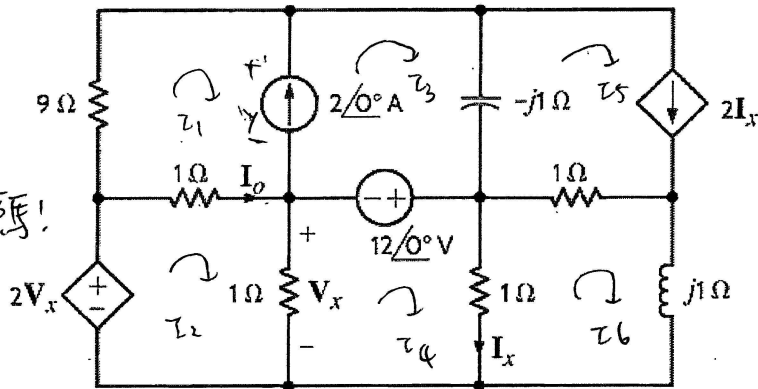


Fig. 1.

2. (15%) Please use nodal analysis to find I_o in Fig. 2.

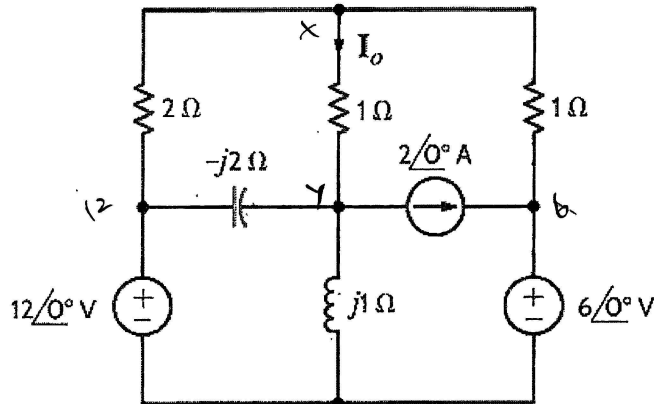


Fig. 2.

3. (20%) If Z_L has unity power factor feature, please find Z_L for maximum power transfer and the maximum power that can be transferred to the load Z_L in Fig. 3.

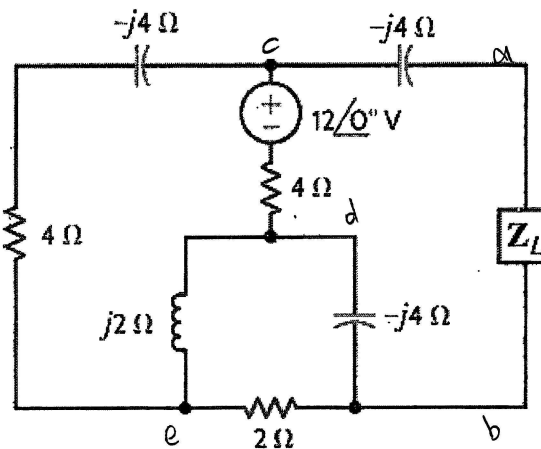


Fig. 3.

同相电压源 功率. $v_s = v_m \sin(377t + \theta_v)$

4. (15%) Given the circuit in Fig. 4, please find the complex power supplied by the source, and the source power factor. If $f = 60\text{Hz}$, please find V_s .

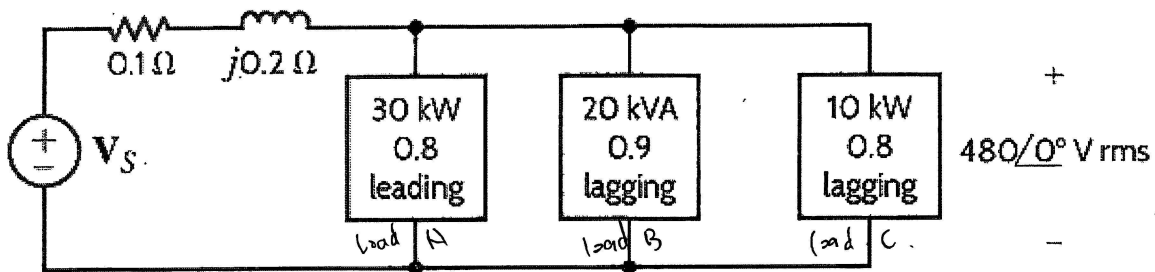


Fig. 4.

5. (15%) In a balanced three-phase wye-wye system, the source is an abc-sequence set of voltages and $V_{an} = 120\angle 40^\circ \text{ V rms}$. If the a-phase line current and line impedance are known to be $7.1\angle -10.28^\circ \text{ A rms}$ and $0.8 + j1\Omega$ respectively, find the load impedance.

6. (10%) An abc-phase-sequence three-phase balanced Y-connected source supplies power to a balanced Δ -connected load. The impedance per-phase in the load is $20 + j14\Omega$. If the source voltage for the a phase is $V_{an} = 120\angle 70^\circ \text{ V rms}$ and the line impedance is zero, please find the phase currents in the Y-connected source. α 相电流是多少

7. (10%) A balanced three-phase source supplies power to three loads: The loads are

Load 1: 30 kVA at 0.8 pf lagging

Load 2: 24 kW at 0.6 pf leading

Load 3: unknown

$$S = V I^* !!$$

功率因数 leading 和 lagging

If the line voltage and total complex power at the load are 208 Vrms and $120\angle 0^\circ \text{ kVA}$, respectively, please find the complex power and the power factor of the unknown load.

$$20 \text{ kVA}$$