

1. (15%) Please find the output voltage $V_o(t)$ in Fig. 1(a) for $t > 0$ when the input source $v(t)$ is given in Fig. 1(b). The initial current in the $4H$ inductor is one and the others are zero.

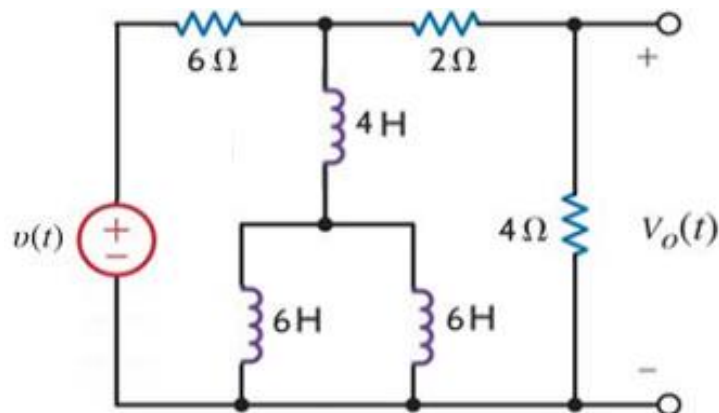


Fig. 1(a).

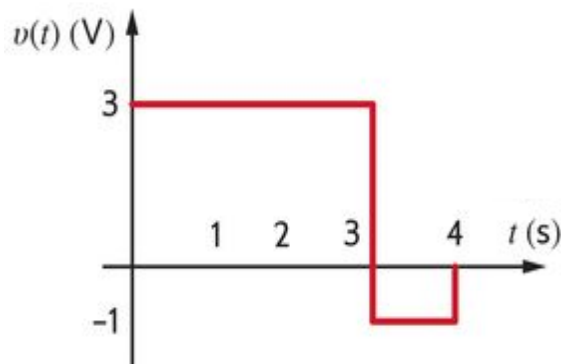


Fig. 1(b).

2. (15%) Assume the circuit is operated at the steady state initially, please find $i(0^+)$ in Fig. 2.

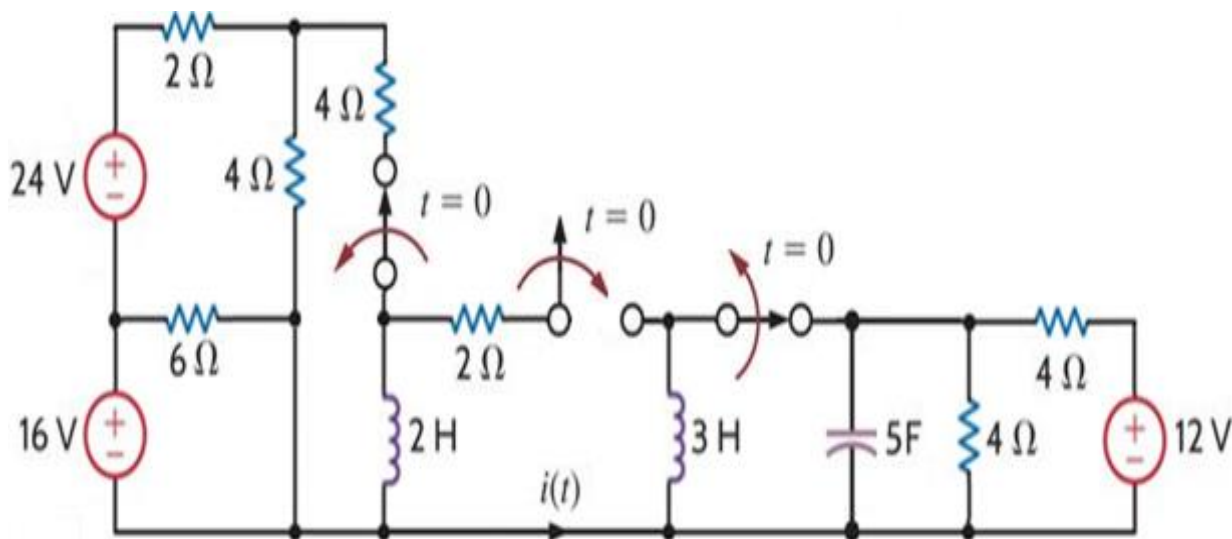


Fig. 2.

3. (15%) Please find the output voltage $v_o(t)$ in Fig. 3 if the initial voltage in the capacitor is zero.

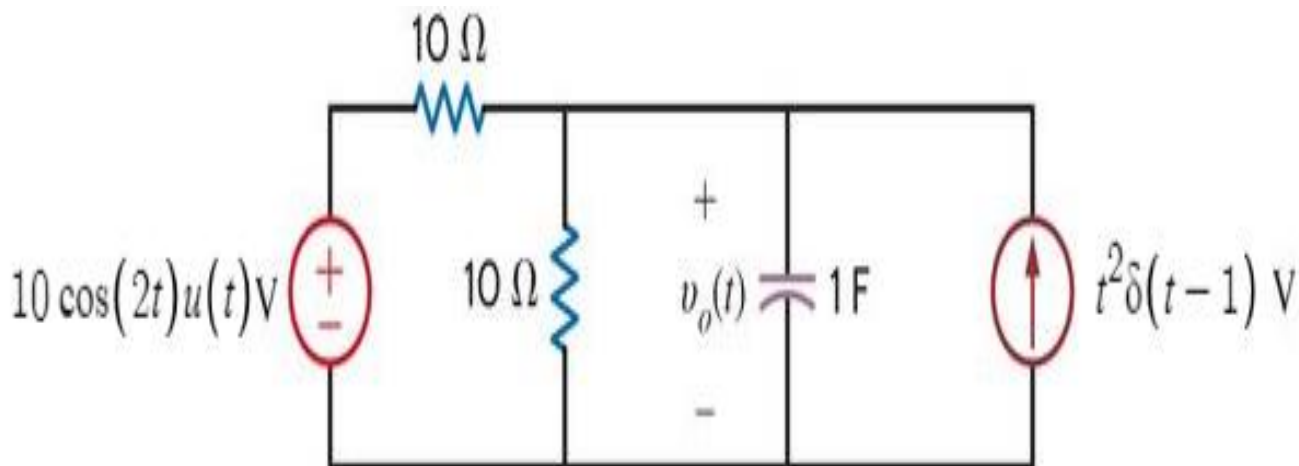


Fig. 3.

4. (10%) The magnitude characteristic of the Bode plot is depicted in Fig. 4. Please determine the transfer function of $G(j\omega)$.

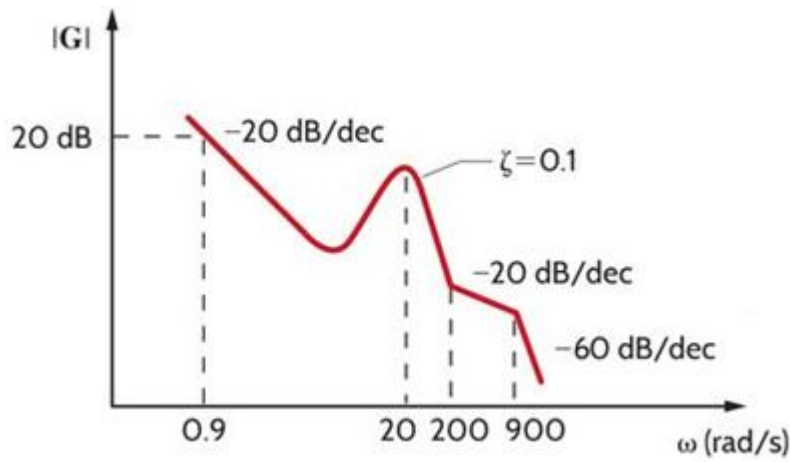


Fig. 4.

5. (15%) There is a critical-damping RLC parallel resonant circuit with $C=0.25\mu\text{F}$ and $L=4\text{H}$, please answer the following questions:
- (5%) (a) Please determine the value of R for this critically-damped system.
- (10%) (b) What is the resonant angular frequency ω_0 , quality factor Q , bandwidth B_w , and half-power angular frequency ω_H and ω_L of this system?

6. (15%) The circuit is operated at the steady state initially, please find $v_o(t)$ for $t > 0$ in Fig. 5.

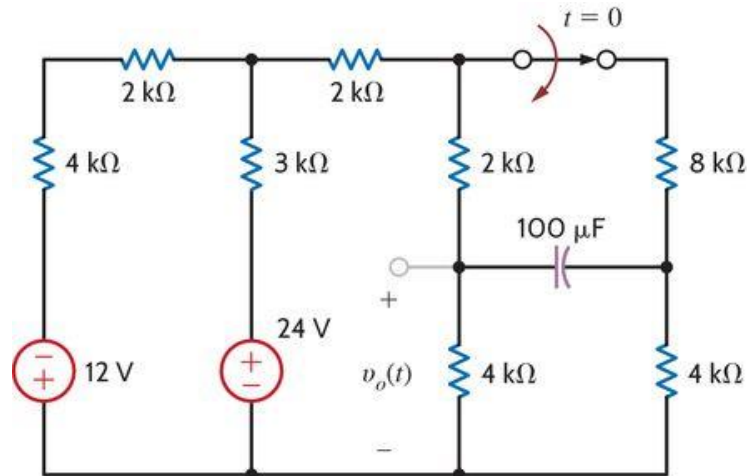


Fig. 5.

7. (15%) Please sketch the magnitude characteristic of the Bode plot for the following transfer function.

$$\mathbf{H}_{(j\omega)} = \frac{5(j\omega + 10)}{j\omega(j\omega + 100)}$$