

# 國立臺灣科技大學答案卷


National Taiwan University of Science and Technology Answer Sheet

姓名/Name \_\_\_\_\_ 學號/Student ID \_\_\_\_\_ 班級/Class \_\_\_\_\_

科目/Course title \_\_\_\_\_ 日期/Date \_\_\_\_\_

評分 Score	教師簽章 Signature of Lecturer

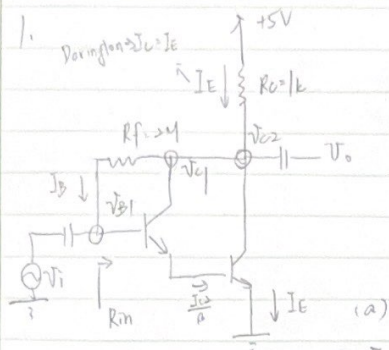記分欄 從此處開始寫起。試卷用紙務須節用，非經主試認可不得續用其他紙張作答。/Please write from here



⇒ 這盞頓電路 有或一個大的 BJT

$$\beta_{\text{對置}} = \beta^2 = 100^2 = 10000$$


$$V_{C1} = V_{C2} = 5 - R_{C1} \cdot I_E$$

$$V_{B1} = 5 - R_{C1} \cdot I_E - R_f \cdot I_B = 5 - 1k \cdot I_E - 2M \cdot \frac{I_E}{\beta^2} = 5 - I_E (1k + \frac{2M}{10000})$$

$$\text{又 } V_{B1} = 0.7 + 0.7 = 1.4V$$

$$\therefore I_E = \frac{5 - 1.4}{1.2k} = \frac{3.6}{1.2k} = 3mA \approx I_{C2} \quad \#$$
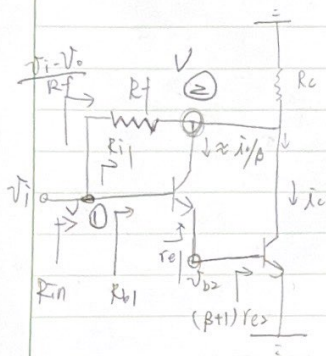
$$I_{B1} = \frac{3mA}{\beta^2} = 3 \cdot 10^{-7} A \quad \text{又 } I_{C1} = \beta \cdot 3 \cdot 10^{-7} = 3 \cdot 10^{-5} A \approx I_{E1} = I_{B2} \quad \#$$



$$V_{B2} = V_i \frac{(\beta+1)R_{E2}}{(\beta+1)R_{E2} + R_{E1}}$$

$$R_{E2} = \frac{V_T}{I_{E2}} = \frac{25m}{3mA} = 8.33 \dots$$

$$R_{E1} = \frac{V_T}{I_{C1}} \approx \frac{25m}{3 \cdot 10^{-5}} = 833.33 \dots$$

$$V_{B2} = V_i \frac{101 \cdot 8.33}{101 \cdot 8.33 + 833} \approx 0.5 V_i$$

$$i_{C1} = g_{m2} V_{B2} = g_{m2} \cdot 0.5 V_i$$

$$\text{又 } g_{m2} = \frac{I_{C2}}{V_T} = \frac{3mA}{25m} = 0.12 \text{ } \#$$

$$\therefore i_{C1} = 0.12 \cdot 0.5 V_i = 0.06 V_i$$

$$\text{node equation: } \downarrow \text{代入}$$

$$\frac{V_o - V_i}{R_C} + i_{C1} + \frac{V_o - V_i}{R_f} + \frac{i_{C1}}{\beta} = 0$$

$$V_o \left( \frac{1}{1k} + \frac{1}{2M} \right) = -V_i \left[ \left( 1 + \frac{1}{100} \right) \cdot 60m - \frac{1}{2M} \right]$$

$$A_v = \frac{V_o}{V_i} = - \frac{\frac{101}{100} \times 60 - \frac{1}{2000}}{1 + \frac{1}{2000}} \approx -60.5 \quad \#$$

For dc analysis, open-circuit the two coupling capacitors. Then replace the 9-V source and the two 20-k $\Omega$  resistors by their Thévenin equivalent, namely, a 4.5-V source and a 10-k $\Omega$  series resistance. The latter can be added to the 10-k $\Omega$  resistor that is connected to the base. The result is the circuit shown in Fig. 1, which can be used to calculate  $I_E$ .

$$(a) I_E = \frac{4.5 - 0.7}{2 + \frac{20}{\beta + 1}} = \frac{3.8}{2 + \frac{20}{101}} = 1.73 \text{ mA}$$

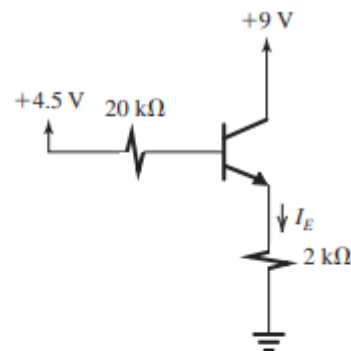


Figure 1

$$I_C = \alpha I_E = 0.99 \times 1.73 \text{ mA}$$

$$= 1.71 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = 68.4 \text{ mA/V}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{1.73 \text{ mA}} = 14.5 \Omega$$

$$= 0.0145 \text{ k}\Omega$$

$$r_\pi = (\beta + 1)r_e = 101 \times 0.0145$$

$$= 1.46 \text{ k}\Omega$$

(b) Replacing the BJT with its  $T$  model (without  $r_o$ ) and replacing the capacitors with short circuits results in the equivalent-circuit model shown in Fig. 2.

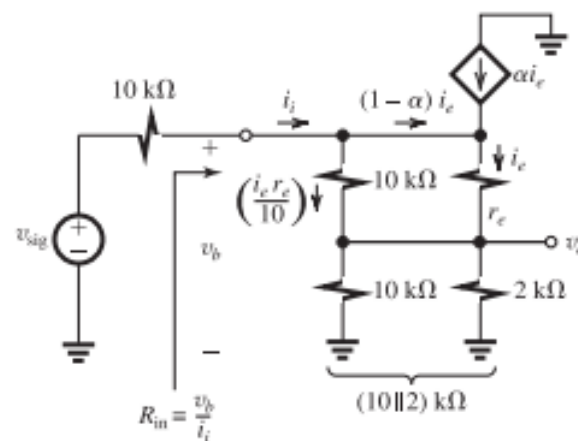


Figure 2

From Fig. 2 we see that

$$v_e = \left( i_e + i_e \frac{r_e}{10} \right) (10 \parallel 2)$$

$$v_b = v_e + i_e r_e = i_e (10 \parallel 2) \left( 1 + \frac{r_e}{10} \right) + i_e r_e$$

$$i_i = (1 - \alpha)i_e + i_e \frac{r_e}{10}$$

$$= \frac{i_e}{\beta + 1} + i_e \frac{r_e}{10}$$

We can now obtain  $R_{in}$  from

$$\begin{aligned} R_{in} &\equiv \frac{v_b}{i_i} = \frac{(10 \parallel 2) \left( 1 + \frac{r_e}{10} \right) + r_e}{\frac{1}{\beta + 1} + \frac{r_e}{10}} \\ &= \frac{(\beta + 1)(10 \parallel 2) \left( 1 + \frac{r_e}{10} \right) + (\beta + 1)r_e}{1 + (\beta + 1) \frac{r_e}{10}} \\ &= \frac{101 \times (10 \parallel 2) \times (1 + 0.00145) + 101 \times 0.0145}{1 + 101 \times 0.00145} \\ &= \frac{168.577 + 1.4645}{1 + 0.14645} = 148.3 \text{ k}\Omega \end{aligned}$$

$$\frac{v_b}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{148.3}{148.3 + 10} = 0.937$$

$$\begin{aligned} \frac{v_o}{v_b} &= \frac{v_e}{v_b} = \frac{i_e \left( 1 + \frac{r_e}{10} \right) (10 \parallel 2)}{i_e \left( 1 + \frac{r_e}{10} \right) (10 \parallel 2) + i_e r_e} \\ &= \frac{1.00145 \times (10 \parallel 2)}{1.00145 \times (10 \parallel 2) + 0.0145} \\ &= 0.991 \text{ V/V} \end{aligned}$$

$$G_v \equiv \frac{v_o}{v_{sig}} = 0.937 \times 0.991 = 0.93 \text{ V/V}$$

(3)

$$300 \times \frac{3.5}{26.5 + 3.5} = 30 \frac{3.5}{5} = 3.5 \text{ (V}_q\text{)}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = I_{DSS} \left(1 - \frac{V_q - V_s}{V_P}\right)^2$$

$$= \sqrt{S/2K}$$

$$= 12 \text{ m} \left(1 + \frac{3.5 - V_s}{5}\right)^2 = \frac{V_s}{2K}$$

$$= 3.12 \left(1 + \frac{3.5 - V_s}{5}\right)^2 = V_s$$

$$= 36 (1.7 - 0.2V_s)^2 = V_s$$

$$36 \cdot (2.89 - 0.68V_s + 0.04V_s^2) = V_s$$

$$104.04 - 24.48V_s + 1.44V_s^2 = V_s$$

$$1.44V_s^2 - 25.48V_s + 104.04 = 0$$

$$V_s = \frac{25.48 \pm \sqrt{25.48^2 - 4 \cdot 1.44 \cdot 104.04}}{2 \cdot 1.44} = \frac{25.48 \pm \sqrt{49.96}}{2.88}$$

$$= 11.7 \text{ or } \underline{6.393} \checkmark$$

$$V_{GS} = 3.5 - 6.14 = 2.9 \text{ (V)} \#$$

$$3.5 - 11.7 = 7.8 \text{ (utoff)} \times$$

$$3.5 - 6.4$$

$$I_D = 12 \text{ m} \cdot \left(1 + \frac{-2.9}{5}\right)$$



$$= 3.04 \text{ mA} \#$$

$$r_o = \frac{300}{5.04 \text{ m}} \Rightarrow \frac{r_o}{r_i} = -g_m (R_D \parallel R_L \parallel r_o)$$

$$g_m \Rightarrow -\frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$\Rightarrow -\frac{24 \text{ m}}{5} \left(1 - \frac{-2.9}{-5}\right)$$
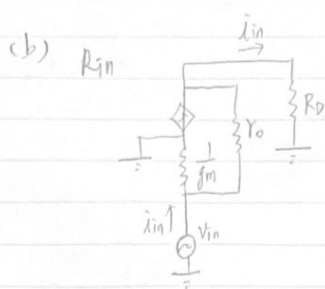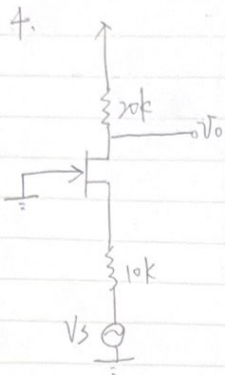
$$\begin{aligned} & -g_m (R_D \parallel R_L \parallel r_o) \\ &= -\frac{24 \text{ m}}{5} \cdot 0.42 \cdot (1.5 \text{ k} \parallel 59.5 \text{ k}) \\ &= -2.95 \end{aligned}$$




$$(i_{in} - g_m v_{in}) r_o + i_{in} R_D = v_{in}$$

$$i_{in} (r_o + R_D) = v_{in} (1 + g_m r_o)$$

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{r_o + R_D}{1 + g_m r_o} = \frac{100k + 20k}{1 + 2m \cdot 100k}$$

$$= \frac{120k}{201}$$

$$\approx 600 \Omega$$

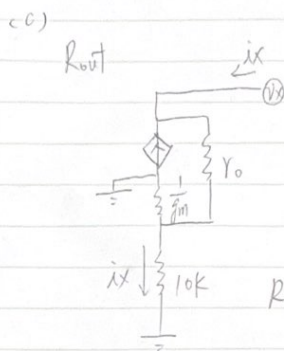

$$(i_x + g_m i_x \cdot 10k) r_o + i_x \cdot 10k = v_x$$


$$i_x (1 + g_m 10k) r_o + i_x \cdot 10k = v_x$$

$$R_{out} = \frac{v_x}{i_x} = (1 + g_m 10k) r_o + 10k$$

$$= 100k + 2m \cdot 10k \cdot 100k + 10k$$

$$= 100k + 2000k + 10k$$

$$= 2110k$$

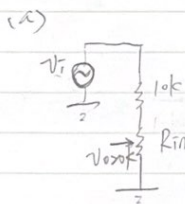

$$\frac{v_o}{v_i} = \frac{20k}{10k + R_{in}} = \frac{20k}{10k + 600} \approx 1.89$$

$$\frac{g_m r_o + 1}{r_o + g_m r_o \cdot 10k + 20k} \cdot 20k$$

$$= \frac{200 + 1}{100k + 2000k + 20k} \cdot 20k$$

$$= \frac{201}{2120} \times 20 \approx 1.89$$



# 國立臺灣科技大學答案卷

National Taiwan University of Science and Technology Answer Sheet

姓名/Name \_\_\_\_\_ 學號/Student ID \_\_\_\_\_ 班級/Class \_\_\_\_\_

科目/Course title \_\_\_\_\_ 日期/Date \_\_\_\_\_

評 分 Score	教 師 簽 章 Signature of Lecturer

記分欄

從此處開始寫起。試卷用紙務須節用，非經主試認可不得續用其他紙張作答。/Please write from here.

(5)

$$5 \times \frac{54.6}{95.4 + 150 + 54.6} = 5 \times \frac{54.6}{300} = 0.91 \quad (Q_1 \text{ 的 } V_{gs})$$

$$I_D \cdot R_S = 0.4 \text{ mA} \times 10 \text{ k} = 4 \Rightarrow Q_1 \text{ 的 } V_S = -5 + 4 = -1$$

$$\begin{aligned} \text{驗證: } k_n (V_{gs} - V_t)^2 &= 0.8 (0.91 - (-1) - 1.2)^2 \\ &= 0.8 \times (0.71)^2 \\ &= 0.4 \text{ (mA)} \quad \text{sat} \end{aligned}$$

$$\text{由於 } \lambda = 0 \therefore r_o = \infty$$

$$\frac{v_o}{v_i} = -g_m (R_D \parallel r_o) \quad \because r_o = \infty \therefore \frac{v_o}{v_i} = -g_m R_D$$

$$= -g_m R_D$$

$$= -2 \cdot k_n (V_{gs} - V_t) \cdot R_D$$

$$= -2 \cdot 0.8 \text{ mA} \cdot 0.71 \cdot 2.5 \text{ k}$$

$$= -2.84 \quad \#$$

$$\begin{aligned} g_m &= 2 k_n V_{ov} \\ &= \frac{2 I_D}{V_{ov}} \\ &= 2 \sqrt{k_n I_D} \end{aligned}$$

三種算出來差不多